

### Problem 1

The scheme in the left figure is a PT100 RTD signal conditioner. Component values are  $R_1 = 11 \text{ k}\Omega$ ,  $R_2 = 11.8 \text{ k}\Omega$ ,  $R_3 = 105 \text{ k}\Omega$ ,  $R_4 = 12.4 \text{ k}\Omega$ ,  $R_5 = 3.01 \text{ k}\Omega$ . The precision CMOS OA has  $A_o = 110 \text{ dB}$  and  $GBWP = 2 \text{ MHz}$ . Consider the behavior at  $T = 0^\circ\text{C}$ .

1. Find the expression of the output voltage. What is the function of  $R_1$ ?
2. Compute the loop gain and find the minimum value of  $R_2$  that ensures stability. Consider then a (differential) input capacitance  $C_i = 10 \text{ pF}$  and evaluate the phase margin.
3. Compute the output rms noise voltage considering the equivalent noise source of the OA  $\sqrt{S_V} = 14 \text{ nV}/\sqrt{\text{Hz}}$  and the resistors noise ( $4k_B T \approx 1.646 \times 10^{-20} \text{ J}$ ).
4. The RTD resistance is not perfectly linear with temperature:  $R_T = 60.26, 100, 138.5$  and  $175.84 \text{ }\Omega$  for  $T = -100, 0, 100$  and  $200^\circ\text{C}$ . Explain the function of resistor  $R_2$  (hint: just evaluate the output. Please, be *quantitative* in your answer).

### Problem 2

A charge-based sensor outputs delta-like signals  $Q\delta(t)$  onto a capacitor  $C$ . The signal is affected by high-frequency noise (with triangular autocorrelation) as well as by a slow baseline. To eliminate the latter, a time-variant filter with a weighting function  $w(t, \tau)$  is then applied.

1. The filter subtracts two samples, one with the baseline and one with signal + baseline. Consider the voltage noise only and compute the output  $S/N$ .
2. Evaluate the output noise due to  $S_I$  (consider for simplicity white current noise and a rectangular approximation of the integral in the frequency domain).
3. The negative delta function is now replaced by a (unit area) gated integrator. Compute the weighting function in the time domain for the input (current) signal.
4. Compute the (exact!) total output noise of the new filter.

For a correct evaluation, you are asked to write your answers in a readable way; thank you

Do a good job!

# Solution

## Problem 1

### 1.1

The voltage at the inputs of the OA is

$$V^- = V^+ = V_o \frac{R_4}{R_3 + R_4} = kV_o,$$

that is also the voltage at the node before  $R_1$ , into which no current flows. Via simple superposition we get:

$$kV_o = V_r \frac{R_2 \parallel R_T}{R_2 \parallel R_T + R_5} + V_o \frac{R_5 \parallel R_T}{R_5 \parallel R_T + R_2},$$

from which we obtain

$$V_o = V_r \frac{\frac{R_2 \parallel R_T}{R_2 \parallel R_T + R_5}}{k - \frac{R_5 \parallel R_T}{R_5 \parallel R_T + R_2}} = V_r \frac{R_2 R_T}{k(R_2 R_5 + R_2 R_T + R_5 R_T) - R_5 R_T} = V_r \frac{R_2 R_T (R_3 + R_4)}{R_2 R_4 R_T + R_2 R_4 R_5 - R_3 R_5 R_T}$$

$R_1$  is obviously needed for bias current compensation. In fact, resistances seen from the OA inputs are  $R_4 \parallel R_3$  and  $R_1 + R_T$ , both equal to approximately 11.1 k $\Omega$ .

### 1.2

The loop gain is easily computed:

$$G_{loop} = -A(s) \left( k - \frac{R_5 \parallel R_T}{R_5 \parallel R_T + R_2} \right) \approx -0.1A(s)$$

and remains negative if

$$k > \frac{R_5 \parallel R_T}{R_5 \parallel R_T + R_2} \Rightarrow R_2 > (R_5 \parallel R_T) \left( \frac{1}{k} - 1 \right) = (R_5 \parallel R_T) \frac{R_3}{R_4} \approx R_T \frac{R_3}{R_4} = 847 \Omega,$$

largely satisfied in our case. To consider the effect of  $C_i$ , it is wise to just compute the position of the pole it generates, that is

$$f_p = \frac{1}{2\pi C_i (R_1 + R_T + R_3 \parallel R_4)} \approx 717 \text{ kHz},$$

larger than the 0dB frequency  $f_0$  ( $= 200 \text{ kHz}$ ), so stability is not affected. The phase margin is now:

$$\phi_m = 90^\circ - \arctan \left( \frac{f_0}{f_p} \right) \approx 74^\circ.$$

### 1.3

We use current sources for resistor noise and group them into two sources at the OA inputs, having values

$$S_{I_n}^+ = \frac{4k_B T}{R_2} + \frac{4k_B T}{R_T} + \frac{4k_B T}{R_5} \approx 1.66 \times 10^{-22} \text{ A}^2/\text{Hz};$$

$$S_{I_n}^- = \frac{4k_B T}{R_3} + \frac{4k_B T}{R_4} \approx 1.48 \times 10^{-24} \text{ A}^2/\text{Hz},$$

while the voltage noise of  $R_1$  is in series with the OA one ( $S_{V_n} = S_V + 4k_B T R_1 \approx 3.77 \times 10^{-16} \text{ V}^2/\text{Hz}$ ), as shown in Fig. 1 (left), where we considered  $R_5 \parallel R_T \approx R_T$ . The output PSD becomes then

$$S_{V_o} = \frac{S_{I_n}^+ (R_T \parallel R_2)^2 + S_{I_n}^- (R_3 \parallel R_4)^2 + S_{V_n}}{(k - R_T/(R_T + R_2))^2} = 1.76 \times 10^{-16} + 1.93 \times 10^{-14} + 3.99 \times 10^{-14} \approx \left( 244 \text{ nV}/\sqrt{\text{Hz}} \right)^2,$$

which, considering a closed-loop bandwidth of 200 kHz, translates into an rms output noise:

$$\sqrt{V_o^2} = 244 \times 10^{-9} \sqrt{\frac{\pi}{2} 2 \times 10^5} \approx 137 \mu\text{V}.$$

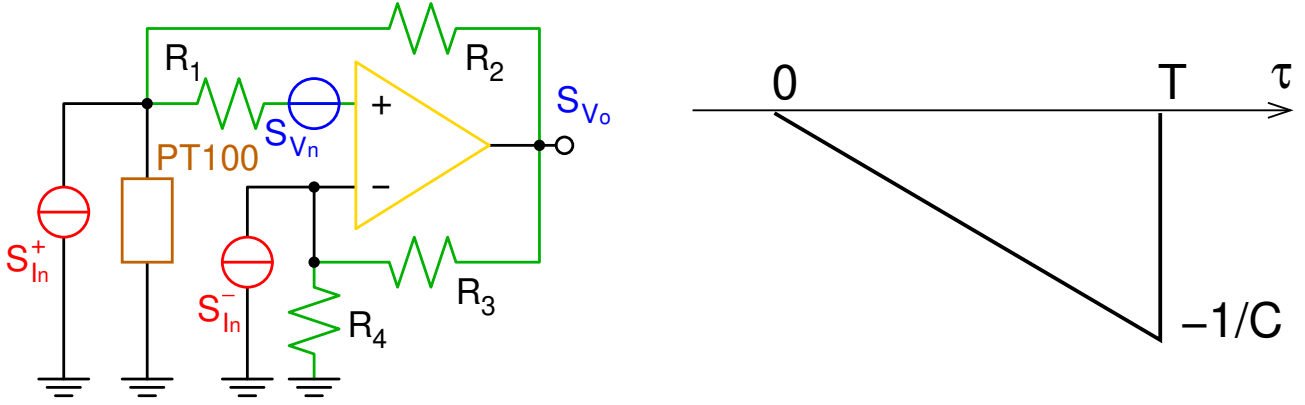


Figure 1: Left = Scheme for noise calculation. Right = Weighting function for the current signal.

## 1.4

Let's compute the output voltage with and without  $R_2$  for the different temperatures:

$T$	$V_o/V_r$ (no $R_2$ )	$V_o/V_r$ (with $R_2$ )
$-100^\circ\text{C}$	0.1858	0.1940
$0^\circ\text{C}$	0.3044	0.3272
$100^\circ\text{C}$	0.4165	0.4602
$200^\circ\text{C}$	0.5226	0.5933

From these data we can extract the variation in  $V_o$  for a  $100^\circ\text{C}$  temperature difference:

$T$ range	$\Delta V_o/V_r$ (no $R_2$ )	$\Delta V_o/V_r$ (with $R_2$ )
$-100 - 0^\circ\text{C}$	0.1186	0.1332
$0 - 100^\circ\text{C}$	0.1121	0.1330
$100 - 200^\circ\text{C}$	0.1061	0.1331

We can see that the scheme with  $R_2$  is much more linear! This happens because  $R_2$  introduces a small positive feedback that provides a slightly higher output for high values of  $R_T$ , compensating its nonlinearity.

## Problem 2

### 2.1

The delta-like signal pulse is integrated by the capacitor, resulting in a step voltage that is sampled and gives an output signal

$$V_o = \frac{Q}{C}.$$

while the output noise is obviously two times the input voltage noise, leading to

$$\frac{S}{N} = \frac{Q/C}{\sqrt{2n_V^2}} = \frac{Q}{C} \sqrt{\frac{T_n}{S_V}},$$

where we remember that in a triangular autocorrelation model  $\overline{n_V^2} = S_V/2T_n$ , as  $S_V$  is a unilateral PSD.

### 2.2

In the frequency domain, the current transfer would be

$$V_o = I_n \frac{1}{sC} W(t, s) \Rightarrow S_{V_o} = \frac{S_I}{C^2} \left| \frac{W(t, f)}{2\pi f} \right|^2,$$

where

$$W = 1 - e^{j2\pi fT} \Rightarrow |W|^2 = 2(1 - \cos(2\pi fT)).$$

We must then compute

$$\overline{V_o^2} = \frac{2S_I}{C^2} \int_0^\infty \frac{1 - \cos(2\pi fT)}{(2\pi f)^2} df = S_I \frac{T}{\pi C^2} \int_0^\infty \frac{1 - \cos x}{x^2} dx = S_I \frac{T}{2C^2},$$

where we have taken as equivalent bandwidth of the function one half of its first zero, i.e.,  $\pi$ . The result in this case is exact, but please do not take this as a general rule.

### 2.3

We begin with remembering that  $w(t, \tau)$  is the response in  $t$  to a (current)  $\delta$  function applied in  $\tau$ . However, the current is integrated by the capacitor  $C$  (see the Laplace transform of the weighting function computed in 2.2,  $W(t, s)/sC$ ), meaning that we have a step voltage at the input of the time-variant filter. The output can easily be computed and results in the triangular weighting function depicted in Fig. 1 (right). Please note that the new weighting function  $w'(t, \tau)$  is the integral (up to  $t = 0$ ) of  $w(t, \tau)$ , as apparent from the Laplace analysis.

Note also that this approach can be easily applied to the case in 2.2, resulting in a rectangular weighting function of amplitude  $1/C$ , which returns the previous result.

### 2.4

The current noise contribution can easily be computed from

$$\overline{V_o^2} = \frac{S_I}{2} \int w'^2(t, \tau) d\tau = \frac{S_I}{2} \int_0^T \left(\frac{\tau}{T}\right)^2 d\tau = \frac{S_I}{2} \frac{T}{3}.$$

The weighting function for the voltage noise contains a delta function, meaning that the entire input noise is found at the output, and  $\overline{V_o^2} = \overline{n_V^2}$ . To make this point clear, we can start from

$$\overline{V_o^2} = \int R_{VV}(\gamma) k_{wt}(\gamma) d\gamma,$$

and note that  $k$  must contain a delta at  $\gamma = 0$ . The rest of the integral will give a result dependent on  $T_n$ , much lower than the mean square value. Calculations are left to the reader; the final result for the voltage noise is

$$\overline{V_o^2} = \overline{n_V^2} + \overline{n_V^2} \frac{T_n^2}{3T^2} = \overline{n_V^2} + S_V \frac{T_n}{6T^2}.$$