

### Problem 1

The scheme in the left figure is a current source. Parameter values are  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ . The OA has  $GBWP = 1 \text{ MHz}$  and  $A_0 = 100 \text{ dB}$ .

1. Find the expression of the closed-loop (ideal) gain.
2. The input current source has a parallel capacitance  $C_s = 30 \text{ pF}$ . Discuss the stability of the circuit and compensate if necessary (consider for simplicity the case  $|Z_L| \ll R_2$ ).
3. Compute the output rms noise current considering the equivalent noise sources of the amplifier,  $\sqrt{S_V} = 10 \text{ nV}/\sqrt{\text{Hz}}$  and  $\sqrt{S_I} = 1 \text{ pA}/\sqrt{\text{Hz}}$ , and resistors ( $4k_B T \approx 1.646 \times 10^{-20} \text{ J}$ ). Consider for simplicity the circuit in #1.1 (i.e., without capacitor  $C_s$ ).
4. With reference to #1.2, consider the case in which  $Z_L = R_L \leq R_2$  and compensate the stage.

### Problem 2

In ultrasonic sensing, a train of pulses is sent to a target, and the reflected signal (assumed equal to the transmitted one, for simplicity) is measured to extract the delay and the distance of the target. Consider a signal made up of a series of  $N$  rectangular pulses, as in the right figure, with amplitude  $A$  and pulse width  $T_P$ . A white noise having bilateral PSD  $\lambda$  is also present at the signal recovery stage.

1. A gated integrator is used as a filter. Compute the resulting  $S/N$ .
2. What is the best filter that can be used to detect the signal? Sketch the output signal and compute the resulting  $S/N$ .
3. Consider an input noise with exponential autocorrelation  $R_{xx}(\tau) = \overline{n_x^2} e^{-|\tau|/T_n}$  and estimate the output noise (consider the filter in #1.2 and assume large value of  $N$  and long correlation time  $T_n$ ).
4. There is a large low-frequency noise at the input. Is it possible to modify the pulse shape in order to reduce its effect (while still using the best filter option)?

Useful expressions: 
$$\sum_k k \alpha^k = \frac{\alpha}{(1 - \alpha)^2}$$

For a correct evaluation, you are asked to write your answers in a readable way; thank you

Do a good job!

Results will be posted by September 16<sup>th</sup>

Mark registration: by Friday, Sept. 18<sup>th</sup>

# Solution

## Problem 1

### 1.1

As the input pins of the OA must stay at the same potential, the voltage drops across  $R_1$  and  $R_2$  must be equal, which means:

$$I_i R_1 = I_o R_2 \Rightarrow I_o = I_i \frac{R_1}{R_2}.$$

### 1.2

Breaking the loop at the OA output, we can obtain the following expression for  $G_{loop}$ :

$$G_{loop} = -A(s) \left( \frac{1}{1 + sC_s R_1} - \frac{Z_L}{Z_L + R_2} \right) \approx -A(s) \frac{1}{1 + sC_s R_1},$$

where we assumed  $|Z_L| \ll R_2$ . The additional pole introduced by  $C_s$  is located at  $f_p = 1/(2\pi C_s R_1) \approx 530$  kHz, and reduces the phase margin below  $45^\circ$ . To compensate the stage, we can simply put a capacitor  $C_c$  in parallel to  $R_1$ , as shown in Fig. 1 (left), obtaining:

$$G_{loop} = -A(s) \frac{1 + sC_c R_1}{1 + s(C_c + C_s)R_1}.$$

Note that in this case there is no specific requirement on the phase margin, so we can follow two approaches. First, let's set a phase margin of  $45^\circ$ , meaning that we must place the frequency of the zero at  $f_{0dB}$ , i.e.

$$f_{0dB} = \sqrt{\frac{GBWP}{2\pi(C_c + C_s)R_1}} = f_z = \frac{1}{2\pi C_c R_1} \Rightarrow C_c^2 - KC_c - KC_s = 0,$$

where  $K = 1/(2\pi R_1 GBWP) = 15.9$  pF. This equation leads to  $C_c \approx 31$  pF and to  $f_p = 261$  kHz,  $f_z = 513$  kHz. Due to the pole-zero proximity, the actual phase margin is  $\phi_m = 90 - \arctan(513/261) + 45 \approx 72^\circ$ . A more rough-and-ready approach can be as follows: we set the zero at the original pole position, which in this case means  $C_c = C_s$ . The pole now goes at 265 kHz, where  $|G_{loop}| = 1000/265 = 3.77$ . The new  $f_{0dB}$  is then  $265\sqrt{3.77} \approx 515$  kHz, and the phase margin is  $\phi_m = 90 - \arctan(515/265) + \arctan(515/530) \approx 71^\circ$ .

### 1.3

The noise transfers are easily computed and result in

$$\begin{aligned} S_{I_o} &= \left( S_I^- + \frac{4k_B T}{R_1} \right) \left( \frac{R_1}{R_2} \right)^2 + S_I^+ + \frac{4k_B T}{R_2} + S_V \frac{1}{R_2^2} = \\ &= (10^{-24} + 1.646 \times 10^{-24})100 + 10^{-24} + 1.646 \times 10^{-23} + 10^{-22} = 3.8 \times 10^{-22} \text{ A}^2/\text{Hz}, \end{aligned}$$

leading to

$$\overline{I_o^2} \approx S_{I_o} \frac{\pi}{2} GBWP \approx (24 \text{ nA})^2,$$

where we have again considered  $|Z_L| \ll R_2$  for simplicity. If we consider  $Z_L = R_L = R_2$ , we get  $f_{0dB} \approx GBWP/2$  and  $\sqrt{\overline{I_o^2}} \approx 17$  nA.

### 1.4

The solution for the case  $R_L = 0$  has been already discussed in #1.2, so we are left with the other extreme, i.e.,  $R_L = R_2$ . If we retain the previous compensation scheme,  $G_{loop}$  becomes now

$$G_{loop} = -A(s) \left( \frac{1 + sC_c R_1}{1 + s(C_c + C_s)R_1} - \frac{1}{2} \right) = -\frac{A(s)}{2} \frac{1 + s(C_c - C_s)R_1}{1 + s(C_c + C_s)R_1},$$

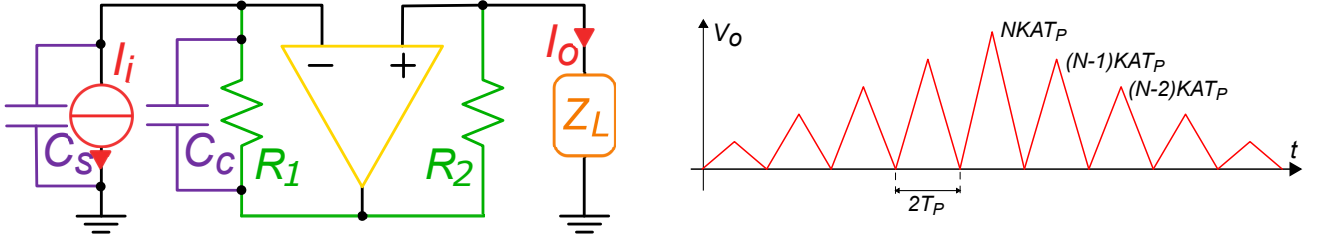


Figure 1: Left = Compensation scheme. Right = Output signal for the case  $N = 5$ .

where we can see that the position of the zero has changed. In particular, it is a good idea to pick  $C_c > C_s$ , so that the zero remains in the LHP. In fact, it is quite obvious that any choice of  $C_c \gg C_s$  would be fine, as it would lead to a pole-zero cancellation.

Just for the sake of it, we can repeat the calculations in #1.2, leading to

$$C_c^2 - C_c(K + 2C_s) + C_c^2 - KC_s = 0 \Rightarrow C_c \approx 92 \text{ pF}$$

and to  $f_p = 130 \text{ kHz}$ ,  $f_z = 253 \text{ kHz}$ . Again, the close proximity of the pole-zero couplet increases the actual phase margin to  $135 - \arctan(253/130) = 72^\circ$ .

## Problem 2

### 2.1

The GI should work over the entire signal duration, which is  $(2N - 1)T_P$ . The resulting  $S/N$  is then

$$\frac{S}{N} = \frac{KANT_P}{\sqrt{K^2\lambda(2N-1)T_P}} = A\sqrt{\frac{N^2T_P}{(2N-1)\lambda}} \approx A\sqrt{\frac{NT_P}{2\lambda}},$$

where  $K$  is the gain of the GI.

### 2.2

The best option is to use a matched filter, with a weighting function equal to the signal. The output signal is reported in Fig. 1 (right), where  $K$  is the amplitude of the weighting function, and we have set  $t = 0$  as the pulse arrival time. The output rms noise can be easily computed as that of a GI working over  $NT_P$  (remember that this only works if the input noise is white!), and  $S/N$  is given by

$$\frac{S}{N} = \frac{KANT_P}{\sqrt{K^2\lambda NT_P}} = A\sqrt{\frac{NT_P}{\lambda}},$$

with an improvement of a factor  $\sqrt{2}$  with respect to the previous case.

### 2.3

To compute the output noise, we need the time correlation of the weighting function that, however, has already been computed: it is in fact equal to the output signal, provided that we set  $A = K$  and that the maximum is centered in zero. If we approximate as usual each triangular function with a delta function having the same area, we obtain

$$\overline{n_o^2} \approx \overline{n_x^2}(KT_P)^2 \left( N + 2(N-1)e^{-2T_P/T_n} + 2(N-2)e^{-4T_P/T_n} + \dots \right).$$

We can break the part into parenthesis into two terms, one with the  $N$  terms, the other with the remaining. The first one becomes (let  $\alpha = e^{-2T_P/T_n}$ )

$$N + 2N\alpha + 2N\alpha^2 + \dots = N \left( 2 \sum_k \alpha^k - 1 \right) = N \frac{1 + \alpha}{1 - \alpha}.$$

The second term is instead (apart from the minus sign):

$$2\alpha + 4\alpha^2 + 6\alpha^3 + \dots = 2 \sum_k k\alpha^k = \frac{2\alpha}{(1-\alpha)^2}.$$

The total noise becomes then

$$\overline{n_o^2} \approx \overline{n_x^2} (KT_p)^2 \frac{N(1-\alpha^2) - 2\alpha}{(1-\alpha)^2}.$$

## 2.4

To reduce the LF noise, we need a weighting function with a zero in  $f = 0$  (in the frequency domain, of course). In the time domain, this means that the integral of  $w(t, \tau)$  must be zero. However, because of the matched filter,  $w(t, \tau)$  is equal to the pulse shape, so it suffices to send a pulse with zero average value. In our case, we can simply shift the pulses by a factor equal to  $A/2$ .