

For a correct evaluation, please write your answers in a readable way; thank you!

Problem 1

The scheme in the left figure is a non-inverting amplifier. The OA has low-frequency gain of 100 dB and $GBWP = 1$ MHz. Consider $R_2 = 200$ k Ω and $R_3 = 2$ k Ω .

1. Find the expression of the ideal gain and the range of variation of R_1 in order to change the gain in the range 1 – 100.
2. Consider the OA input capacitance C_i and find its maximum value that can grant a phase margin of 45° for the whole range of gain.
3. Compute the output rms noise voltage considering the equivalent noise sources of the amplifier $\sqrt{S_V} = 10$ nV/ $\sqrt{\text{Hz}}$, $\sqrt{S_I} = 10$ pA/ $\sqrt{\text{Hz}}$ and resistors ($4k_B T \approx 1.646 \times 10^{-20}$ J). Consider unity gain for simplicity.
4. We want to double the ideal gain. Propose a modification of the circuit (do not add resistors in series/parallel to R_1 or R_2 nor add an additional gain stage). An approximated solution is also fine (if discussed properly).

Problem 2

A sensor outputs exponential pulses Ae^{-t/T_F} , plagued by a white noise with bilateral PSD λ , as shown in the figure on the right. After a large-bandwidth preamplifier, an LTI optimum filter is applied, that must process the pulse within a time T .

1. Draw the optimum weighting function and compute S/N .
2. Compute the signal at the output of the optimum filter.
3. We want the output signal to go to zero as soon as possible after $t = T$ (without reducing S/N), so that multiple pulses may be processed without pile-up issues. Propose a new weighting function (approximations are also fine).
4. The white noise is non-stationary and with PSD proportional to the signal. Find the new optimum S/N .

Do a good job!

Solution

Problem 1

1.1

A voltage equal to $V_i/2$ is obviously present at the OA inputs. The KCL at the inverting input node leads to:

$$\frac{V_i}{2R_1} = \frac{V_i}{2R_2} + \frac{V_o - V_i/2}{R_2} \Rightarrow V_o = V_i \frac{R_2}{2R_1}.$$

The circuit is a non-inverting amplifier with a gain expression similar to what is obtained from an inverting scheme (i.e., without the “1+” term). The range of values for R_1 is then 1 – 100 k Ω . R_3 is a biasing resistor and does not affect the gain.

1.2

The input capacitor adds a pole to the loop gain, whose time constant is $C_i R_{eq}$. The resistance seen by the capacitor is

$$R_{eq} = \frac{R_3}{2} + R_1 \parallel \frac{R_2}{2} = \frac{R_3}{2} + \frac{R_1 R_2}{2R_1 + R_2} = \frac{R_3}{2} + \frac{R_2}{2(1+G)},$$

where $G = R_2/2R_1$ is the ideal gain. The second term ranges from 2 (at $G = 100$) to 51 k Ω (at $G = 1$). The loop gain without C_i is instead:

$$G_{loop} = -A(s) \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_2} = -A(s) \frac{1}{2(1+G)} \Rightarrow f_{0dB} = \frac{GBWP}{2(1+G)}.$$

To achieve a phase margin higher than 45° we then set

$$\frac{1}{2\pi C_i R_{eq}} \geq f_{0dB} \Rightarrow C_i \leq \frac{1+G}{\pi R_{eq} GBWP} \leq \frac{2}{\pi 5.1 \times 10^{10}} \approx 12 \text{ pF},$$

where the last inequality stems from the fact that the lowest value is achieved for $G = 1$ and $R_{eq} = 51$ k Ω . Note that a higher values of R_3 could be desired in some cases. Then, a bypass capacitor should be added.

1.3

The circuit for noise calculations is reported in Fig. 1 (left). From it, we can easily derive:

$$S_{V_o} = \left(S_V + S_I^+ \frac{R_3^2}{4} + 2k_B T R_3 \right) \left(1 + \frac{R_2}{R_1 \parallel R_2} \right)^2 + \left(S_I^- + \frac{4k_B T}{R_2} + \frac{4k_B T}{R_1 \parallel R_2} \right) R_2^2 \approx 4.18 \times 10^{-12} \frac{\text{V}^2}{\text{Hz}},$$

dominated by the $S_I^- R_2^2$ term. Since in this case we have $f_{0dB} = GBWP/4 = 250$ kHz (see #1.2), we get

$$\sqrt{V_0^2} = \sqrt{S_{V_o} \frac{\pi}{2} f_{0dB}} \approx 1.3 \text{ mV}.$$

1.4

If we look at the solution in #1.1, we can see that replacing V_o with $V_o/2$ in the current balance equation would do the job:

$$\frac{V_i}{2R_1} = \frac{V_i}{2R_2} + \frac{V_o/2 - V_i/2}{R_2} \Rightarrow V_o = V_i \frac{R_2}{R_1}.$$

Another way of reaching this conclusion is the following: if we want to multiply the gain by a factor of 2, we can simply *divide* by the same factor the feedback transfer F , as $G_{id} = 1/F$.

In any case, a simple voltage divider is all we need. The scheme is reported in Fig. 1 (right). However, please note that this is an *approximate* solution, working when $R_4 \ll R_2$, so that the voltage divider midpoint is close to $V_o/2$. Working out the exact transfer is left to the reader; the result is

$$\frac{V_o}{V_i} = \frac{R_2}{R_1} + \frac{R_4(R_2 - R_1)}{2R_1 R_2}.$$

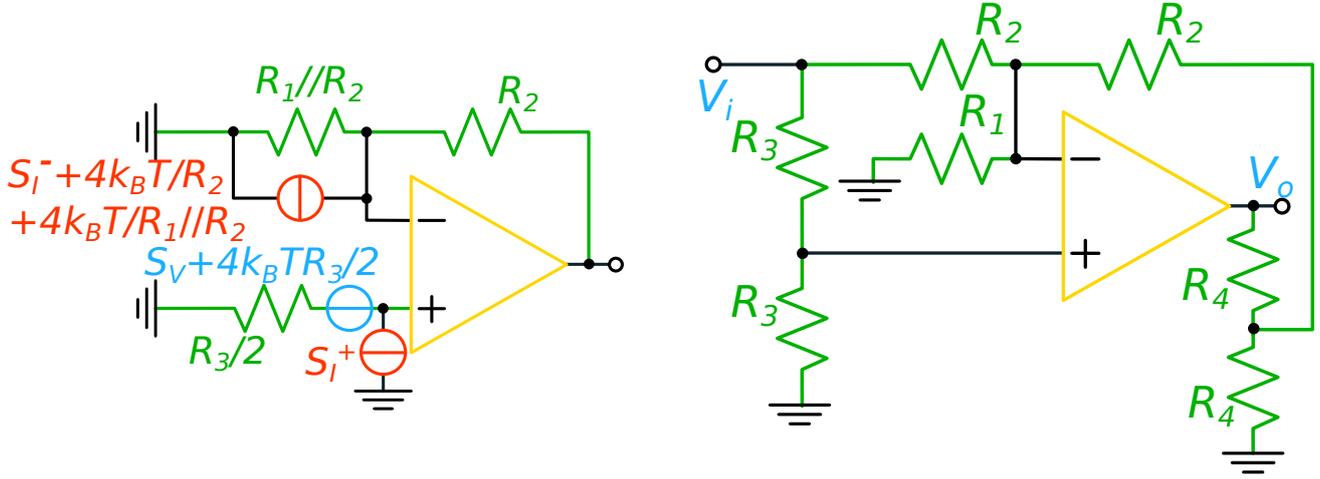


Figure 1: Left = Scheme for noise calculation. Right = Possible scheme for achieving double gain (with $R_4 \ll R_2$).

For example, picking $R_1 = 2 \text{ k}\Omega$ ($G = 100$) results in $G = 100.495$ if $R_4 = 20 \text{ k}\Omega$. If the values of R_1 and R_2 are fixed, an exact solution can be found by tailoring the resistors in the divider to achieve the desired attenuation.

Problem 2

2.1

Since only the signal from $t = 0$ to $t = T$ can be used to provide the output, the optimum weighting function matches the signal only in this time interval. Hence, it is an exponential signal truncated after an interval T , as shown in Fig. 2 (left).

The maximum output is obviously achieved for $t = T$, where we have

$$y(T) = \int x(\tau)w(T, \tau)d\tau = AK \int_0^T x^2(\tau)d\tau = AK \frac{T_F}{2} (1 - e^{-2T/T_F}),$$

while the output mean square noise is

$$\overline{n_y^2} = \lambda K^2 \int_0^T x^2(t)dt = \lambda K^2 \int_0^T e^{-2t/T_F} dt = \lambda K^2 \frac{T_F}{2} (1 - e^{-2T/T_F}).$$

We have therefore

$$\left(\frac{S}{N}\right)_T = A \sqrt{\frac{T_F}{2\lambda}} \sqrt{1 - e^{-2T/T_F}} = \left(\frac{S}{N}\right)_{opt} \sqrt{1 - e^{-2T/T_F}}.$$

Note that the prefactor is the optimum value of S/N , achieved when $T \rightarrow \infty$. For example, with $T = 0.83T_F$ we already get 90% of the optimum value.

2.2

The output signal is

$$y(t) = A \int x(\tau)w(t, \tau)d\tau.$$

For $t \leq T$ this results in

$$y(t) = AK \int_0^t e^{-\tau/T_F} e^{-(\tau-t+T)/T_F} d\tau = AK \frac{T_F}{2} e^{(t-T)/T_F} (1 - e^{-2t/T_F}) = AK T_F e^{-T/T_F} \sinh\left(\frac{t}{T_F}\right).$$

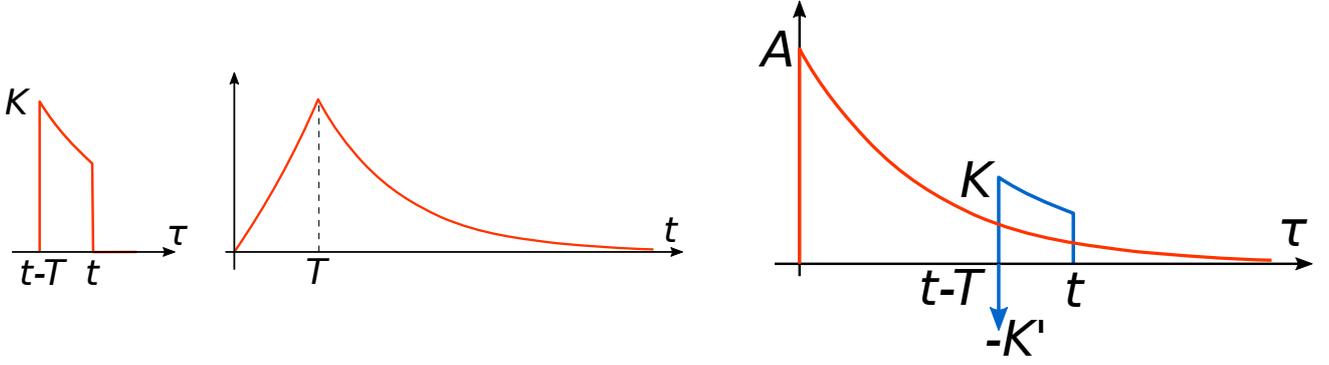


Figure 2: Left = Weighting function and output signal of the optimum filter. Right = Modified weighting function (blue) and input signal (red).

For $t > T$ we obviously have an exponential decay of the signal:

$$y(t) = y(T)e^{-(t-T)/T_F} = AKT_F \sinh\left(\frac{T}{T_F}\right) e^{-t/T_F}.$$

The output signal is also shown in Fig. 2 (left).

2.3

To reduce the output signal, we need to add a negative part to the weighting function. This part must come after the exponential one, so not to affect the optimum S/N . The simpler solution is placing a negative delta function with area $-K'$, as depicted in Fig. 2 (right). For $t > T$ we can exploit the previous results and write

$$y(t) = y(T)e^{-(t-T)/T_F} - K' A e^{-(t-T)/T_F}.$$

Setting $y(t) = 0$ we obtain

$$K' = \frac{y(T)}{A} = K \frac{T_F}{2} \left(1 - e^{-2T/T_F}\right).$$

2.4

We know that in this case the optimum weighting function is constant: $w(t, \tau) = K$ in the interval $0 - T$. If we label $\lambda(t) = \lambda_0 x(t)$ we have:

$$y(T) = K \int_0^T Ax(\tau) d\tau = KAT_F \left(1 - e^{-T/T_F}\right)$$

while the output mean square value of the noise is

$$\overline{n_y^2}(T) = \int_0^T \lambda(\tau) w^2(T, \tau) d\tau = \lambda_0 K^2 T_F \left(1 - e^{-T/T_F}\right),$$

from which

$$\left(\frac{S}{N}\right)_T = A \sqrt{\frac{T_F}{\lambda_0}} \sqrt{1 - e^{-T/T_F}}.$$