

For a correct evaluation, please write your answers in a readable way; thank you!

### Problem 1

The scheme in the left figure is an amplifier for a capacitive sensor having  $C_s = 33$  pF. Other parameters are  $R_1 = 10$  M $\Omega$ ,  $R_2 = 100$  k $\Omega$ ,  $R_3 = 1$  k $\Omega$ ,  $C = 1$   $\mu$ F. The OA has low-frequency gain of 100 dB and  $GBWP = 100$  kHz. Consider initially the circuit without  $C$  and  $R_2$  (both assumed to be of infinite value).

1. Find the (ideal) output voltage vs. time when the sensor outputs delta-like pulses.
2. From now on, add capacitor  $C$ . Compute the loop gain and evaluate the phase margin.
3. Compute the output rms noise voltage considering the equivalent voltage noise source of the amplifier ( $\sqrt{S_V} = 15$  nV/ $\sqrt{\text{Hz}}$ ) and resistors ( $4k_B T \approx 1.646 \times 10^{-20}$  J).
4. Consider the OA bias currents and discuss the purpose of  $R_2$ .

### Problem 2

A sensor outputs a rectangular current pulse of width  $T$  and small amplitude  $I_s \approx 100$  fA. The signal is affected by shot noise and is amplified by a transimpedance stage, followed by an LPF.

1. Find a suitable value for  $T$  that grants  $S/N = 10$ , and the value of  $R$  that allows to neglect its thermal noise.
2. Remove the LPF and replace  $R$  with a capacitor  $C$  (and a switch). Evaluate the new value of  $T$ .
3. The current signal is now  $I_s = I_0 e^{-t/T}$  with  $I_0 \approx 100$  fA, still affected by shot noise. The current noise source of the CMOS OA is  $\sqrt{S_{OA}} = 0.3$  fA/ $\sqrt{\text{Hz}}$ . What is the optimum weighting function (remove the LPF)?
4. Compute  $S/N$  in the optimum case. Remember that  $\int \frac{e^{-2x}}{e^{-x} + a} dx = a \ln(e^{-x} + a) - e^{-x}$  (for  $a \geq 0$ ).

Do a good job!

# Solution

## Problem 1

### 1.1

Without resistor  $R_2$  there is no current flowing in the feedback path, meaning that the input current flows into the capacitor  $C_s$ , providing a step output voltage:

$$V_o = \frac{Q}{C_s} u(t).$$

### 1.2

We disconnect the current source and open both loops at the OA output, applying a test signal  $V_s$ . We easily get

$$V^+ = V_s \frac{1/sC_s}{R_1 + R_3 + 1/sC + 1/sC_s} \approx V_s \frac{C}{C + C_s + sCC_sR_1},$$

which leads to

$$G_{loop} = -A(s) \left( 1 - \frac{C}{C + C_s + sCC_sR_1} \right) = -A(s) \frac{C_s}{C + C_s} \frac{1 + sCR_1}{1 + sC_tR_1},$$

where  $C_t = CC_s/(C + C_s) \approx C_s$  is the series capacitance. The pole and zero are now  $f_p = 1/(2\pi R_1 C_t) \approx 482$  Hz,  $f_z = 1/(2\pi R_1 C) \approx 16$  mHz. At higher frequencies  $G_{loop} = -A(s)$  and the phase margin is  $90^\circ$ . The loop gain is plotted in Fig. 1 (left).

### 1.3

The scheme for noise calculation is depicted in Fig. 1 (right), where  $V_n$  and  $V_R$  are the noise sources associated to the OA and resistor  $R_1 + R_3$ . Current  $I$  can be written as

$$I = \frac{V_n - V_R}{R_1 + R_3 + 1/sC} \approx (V_n - V_R) \frac{sC}{1 + sCR_1},$$

and flows into the capacitor  $C_s$ , leading to:

$$V_o - V_n = I \frac{1}{sC_s} = (V_n - V_R) \frac{C/C_s}{1 + sCR_1} \Rightarrow V_o = V_R \frac{C/C_s}{1 + sCR_1} + V_n \frac{C}{C_t} \frac{1 + sC_tR_1}{1 + sCR_1}.$$

Note that the second transfer has a pole and a zero, beyond which the gain is 1. The output mean square noise is then

$$\begin{aligned} \overline{V_o^2} &= S_R \left( \frac{C}{C_s} \right)^2 \frac{1}{4CR_1} + S_V \left[ \left( \frac{C}{C_t} \right)^2 \frac{1}{4CR_1} + \frac{\pi}{2} (f_{0dB} - f_z) \right] \\ &\approx 2.3 \times 10^7 S_R + (2.3 \times 10^7 + 1.57 \times 10^5) S_V = 5.2 \times 10^{-9} + 3.8 \times 10^{-6} \approx (2 \text{ mV})^2. \end{aligned}$$

Note that the noise is dominated by the low-frequency terms, controlled by the ratio  $C/C_s$ . A smaller value of  $C$  could then be employed, but this scheme has other problems: for example, if the OA current noise contribution were computed, the result would be  $V_o = I_n/sC_s$ , i.e., a divergence at low frequency.

### 1.4

The main purpose of resistor  $R_2$  is to provide a DC path for the OA bias currents. In its absence,  $I_B^+$  would charge the capacitor  $C_s$  leading to saturation of the output. It is also nice to note that this resistor reduces the noise DC gains, that become 1 for  $V_n$  and zero for  $V_R$ , removing also the singularity for the current noise. As a bonus comment,  $R_2$  also decouples the two capacitors, that now give rise to two poles (and two zeroes) in the loop, and the system remains stable. However, the closed-loop transfer has complex poles, which is not desirable. A better design is achieved by increasing the value of  $C$ , to counteract the reduction in resistance seen with the addition of  $R_2$ .

If you wish to solve the circuit, the full transfer function becomes

$$\frac{V_o}{I_s} = \frac{R_1 + R_2 + sC(R_1R_2 + R_1R_3 + R_2R_3)}{1 + s(CR_3 + C_s(R_1 + R_2)) + s^2CC_s(R_1R_2 + R_1R_3 + R_2R_3)} \approx \frac{R_1(1 + sCR_2)}{1 + s(CR_3 + C_sR_1) + s^2CC_sR_1R_2}.$$

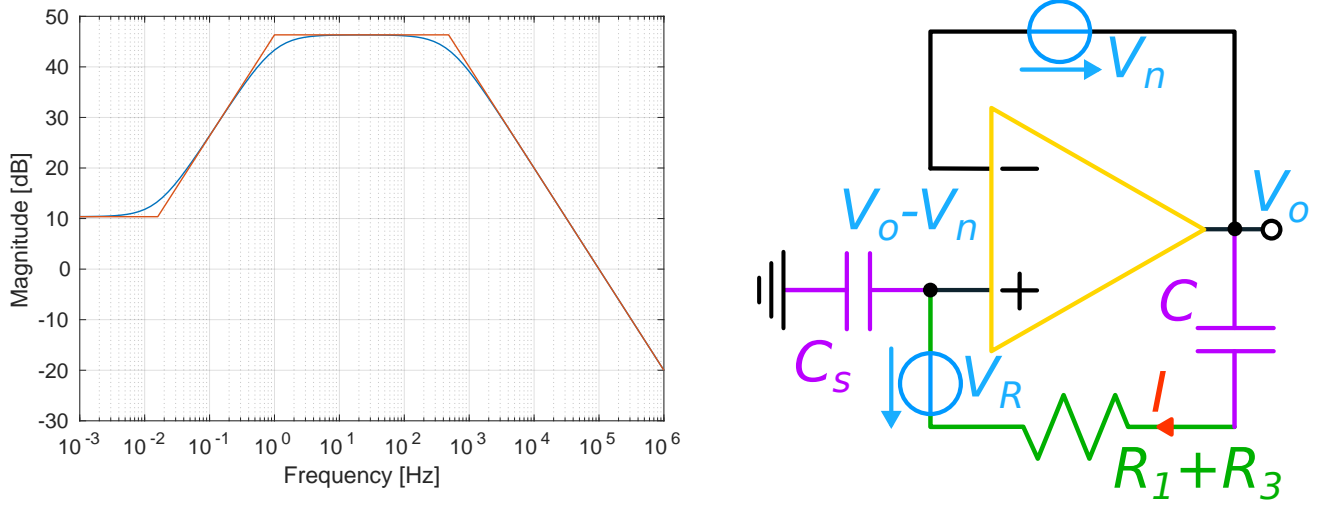


Figure 1: Left = Bode plot of the loop gain (blue) and its asymptotic approximation (red). Right = Scheme for noise calculation.

## Problem 2

### 2.1

We begin with the LPF. The unilateral shot noise PSD associated to a current  $I_s$  is  $S_I = 2qI_s$ . The  $S/N$  ratio at the output of the LPF is then

$$\frac{S}{N} = \frac{I_s R}{\sqrt{2qI_s R^2 BW_n}} = \sqrt{\frac{I_s}{2qBW_n}} = 10 \Rightarrow BW_n = \frac{I_s}{200q} \approx 3.1 \text{ kHz}.$$

If we are using a single-pole LPF, its bandwidth will be about 2 kHz, i.e., a time constant of about 80  $\mu$ s. The signal will reach the steady state after about  $5 \times 80 = 400 \mu$ s, that is the (minimum) value for  $T$ . Resistor  $R$  must be such that

$$\frac{4k_b T}{R} \ll 2qI_s \Rightarrow R \gg \frac{2k_B T}{qI_s} = 5.1 \times 10^{11} \Omega.$$

This requirement is very tight, and a better solution is always used (see next point).

### 2.2

The OA now works as a gated integrator. Signal and noise are then (GI with a gain of  $1/C$ ):

$$V_0 = \frac{I_s}{C} T \quad \overline{V_o^2} = \frac{S_I}{2} \frac{1}{C^2} T,$$

leading to:

$$\frac{S}{N} = \frac{I_s T}{\sqrt{qI_s T}} = \sqrt{\frac{I_s T}{q}} = 10 \Rightarrow T = \frac{100q}{I_s} = 160 \mu\text{s}.$$

Note that this is the optimum filter for this case.

### 2.3

For the case of non-stationary white noise with PSD  $\lambda(t)$ , we have

$$V_o(t) = \int I_s(\tau) w(t, \tau) d\tau \quad \overline{V_o^2(t)} = \int \lambda(\tau) w^2(t, \tau) d\tau,$$

where the input current noise bilateral PSD is  $\lambda(t) = qI_s(t) + \frac{S_{OA}}{2}$ , leading to the optimum choice

$$w(t, \tau) \propto \frac{I_s(\tau)}{\lambda(\tau)} = \frac{I_0 e^{-t/T}}{qI_0 e^{-t/T} + S_{OA}/2} \propto \frac{e^{-t/T}}{e^{-t/T} + S_{OA}/2qI_0} = \frac{e^{-t/T}}{e^{-t/T} + a},$$

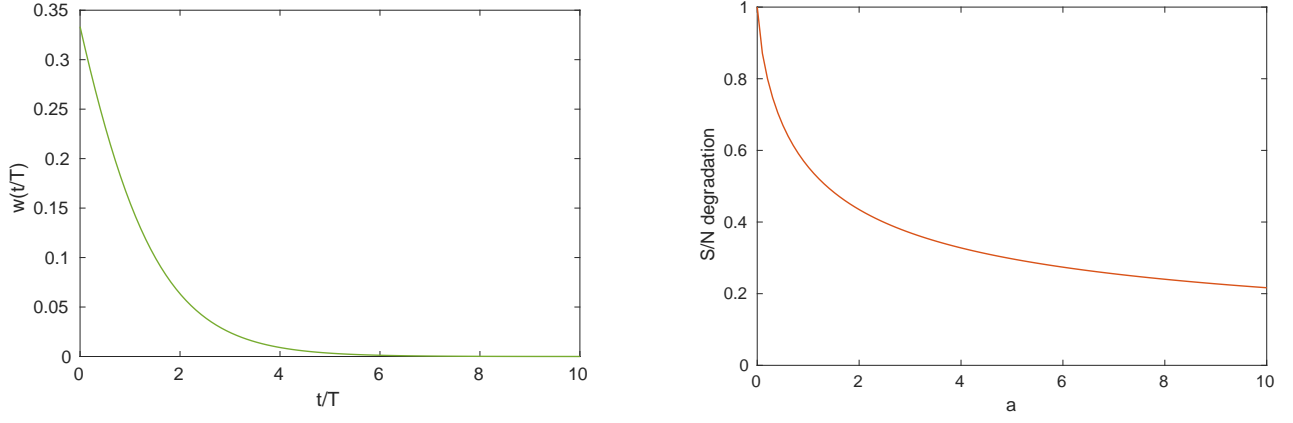


Figure 2: Left = Optimum weighting function. Right =  $S/N$  degradation due to the OA current noise.

where  $a = S_{OA}/2qI_0 = 2.8$ . The weighting function is reported in Fig. 2 (left).

## 2.4

The output signal and noise are

$$\begin{aligned}
 V_o &= K \int_0^\infty I_0 e^{-t/T} \frac{e^{-t/T}}{e^{-t/T} + a} dt = KT I_0 \int_0^\infty \frac{e^{-2x}}{e^{-x} + a} dx = KT I_0 (a \ln a - a \ln(1+a) + 1) \\
 \overline{V_o^2(t)} &= K^2 T \int_0^\infty \left( q I_0 e^{-x} + \frac{S_{OA}}{2} \right) \left( \frac{e^{-x}}{e^{-x} + a} \right)^2 dx = q I_0 K^2 T \int_0^\infty \frac{e^{-2x}}{e^{-x} + a} dx = \\
 &= q I_0 K^2 T (a \ln a - a \ln(1+a) + 1),
 \end{aligned}$$

from which

$$\frac{S}{N} = \sqrt{\frac{I_0 T}{q}} \sqrt{a \ln a - a \ln(1+a) + 1}.$$

For  $a = 2.8$  the second term is about 0.38. The degradation factor due to the OA noise is shown in Fig. 2 (right) as a function of  $a$ .