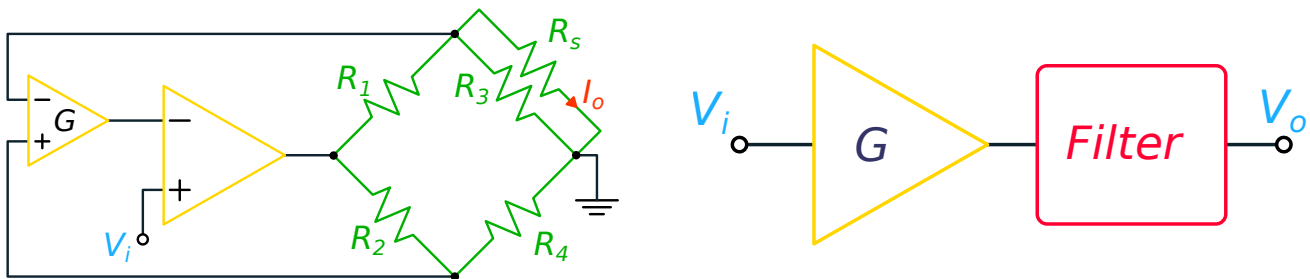


For a correct evaluation, please write your answers in a readable way; thank you



Solving six points correctly gives you 30/30

### Problem 1

The scheme in the left figure is a  $V - I$  converter. OA parameters are  $A_0 = 120$  dB and poles at 10 Hz and 1 MHz. Consider  $G = 1$  and balanced bridge condition  $R_1 R_4 = R_2 R_3$ .

1. Evaluate the (ideal) gain  $I_o/V_i$ .
2. Evaluate the loop gain and discuss the stability for  $R_s \rightarrow 0$ .
3. Compute the output noise current PSD due to the equivalent voltage and current noise sources of the OA.
4. Propose a compensation scheme for  $R_s \rightarrow 0$ , considering equal bridge resistors for simplicity. If possible, do not change the ideal gain.

### Problem 2

A sensor outputs sinusoidal signals  $V_i = A \cos 2\pi f_r t$ , with  $f_r = 80$  Hz and  $A \approx 5 \mu\text{V}$ . The signal feeds an amplifier with gain  $G$  and equivalent input white noise  $\sqrt{S_I} = 50 \text{ pA}/\sqrt{\text{Hz}}$ ,  $\sqrt{S_V} = 100 \text{ nV}/\sqrt{\text{Hz}}$  and noise corner frequency of 3 kHz.

1. A band-pass filter is placed at the output. What is the bandwidth needed to measure  $A$  with  $S/N = 10$ ?
2. An LIA with square-wave reference at  $f_r$  is used to recover the signal. What is the new value of the LPF bandwidth?
3. Two square-wave interferences with frequencies of 1.2 and 1.5 kHz are present at the amplifier input. What is their output signals?
4. The frequency of the signal  $V_i$  is not constant but switches between 70 and 90 Hz every 100 ms, while the mixer reference frequency  $f_r$  remains at 80 Hz. What is the output signal? Find then a better value for  $f_r$  and estimate the new output signal.

Allowed time: 2 hours 45 minutes – Do a good job!

# Solution

## Problem 1

### 1.1

As the differential input voltage of the OA is zero, the  $G$  stage output is  $V_i$ . But  $G = 1$ , so its differential input voltage is also  $V_i$ . The midpoint between  $R_1$  and  $R_3$  is at bias  $I_o R_s$ , leading to the condition in Fig. 1 (left), from which we can easily express the currents flowing in  $R_1$  and  $R_2$  as

$$I_1 = I_o + I_o \frac{R_s}{R_3} \quad I_2 = \frac{I_o R_s + V_i}{R_4}.$$

The KVL between ground and the OA output becomes then

$$I_o R_s + I_1 R_1 = I_o R_s + V_i + I_2 R_2 \Rightarrow I_o = V_i \frac{R_2 + R_4}{R_1 R_4} = V_i \frac{R_1 + R_3}{R_1 R_3},$$

where the balancing condition  $R_1/R_3 = R_2/R_4$  has been used.

### 1.2

We break the loop at the OA output and apply a test voltage  $V_T$ , obtaining the input voltages of the  $G$  stage:

$$V^+ = V_T \frac{R_4}{R_2 + R_4} \quad V^- = V_T \frac{R_p}{R_1 + R_p},$$

where  $R_p = R_3 \parallel R_s$ . The inverting input of the OA is then  $V^+ - V^-$  ( $G = 1$ ), and the loop gain becomes

$$G_{loop} = -A(s) \left( \frac{R_4}{R_2 + R_4} - \frac{R_p}{R_1 + R_p} \right) = -A(s) \frac{R_2}{R_2 + R_4} \frac{R_3 - R_p}{R_1 + R_p}.$$

For large values of  $R_s$ ,  $R_p \rightarrow R_3$  and  $|G_{loop}| \rightarrow 0$ ; this is obviously undesirable, but does not affect the stability, that remains good with phase margin of  $90^\circ$ .

For  $R_s \rightarrow 0$ , instead,  $R_p \rightarrow R_s \ll R_1, R_3$  and

$$G_{loop} = -A(s) \frac{R_4}{R_2 + R_4}.$$

The HF pole of  $A(s)$  falls at 1 MHz, where  $|A(s)| = 10$ . To ensure stability for any  $R_s$  we must then have

$$\frac{R_4}{R_2 + R_4} < \frac{1}{10} \Rightarrow \frac{R_2}{R_4} = \frac{R_1}{R_3} > 9.$$

### 1.3

The voltage noise source is subjected to the same transfer as the input signal. Current noise sources are instead short-circuited by the input and the  $G$  stage and give no contribution. It is then

$$S_{I_o} = S_V \left| \frac{R_1 + R_3}{R_1 R_3} \right|^2.$$

### 1.4

The worst case is  $R_s \rightarrow 0$ , where we have

$$G_{loop} = -A(s) \frac{R_4}{R_2 + R_4} = -\frac{A(s)}{2},$$

with phase margin of  $90 - \arctan(\sqrt{5}) \approx 24^\circ$ . If we want to not change the ideal gain, we cannot place any compensation element across the bridge (otherwise, a capacitor in parallel to  $R_2$  could work). The same can

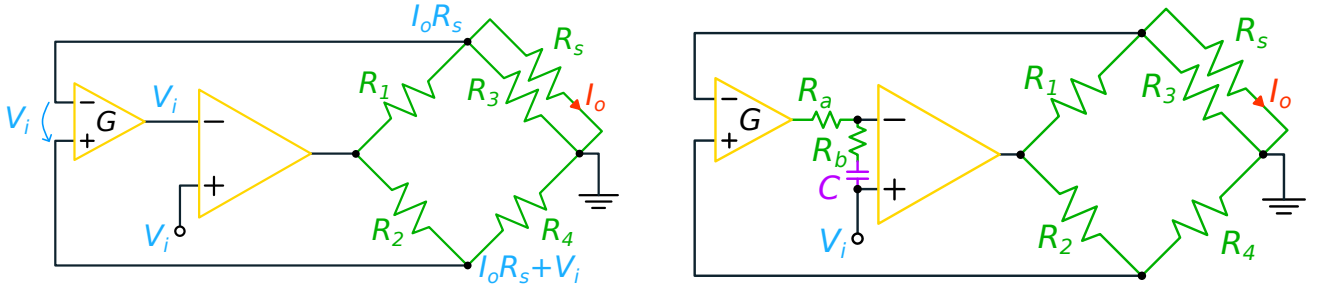


Figure 1: Left = Scheme for gain calculation. Right = possible compensation scheme.

be said for an  $R - C$  series network across the  $G$  input pins. So, it is better to move such a network across the input pins of the OA. But, since this is driven by the output voltage source of  $G$ , an extra resistor is needed, as shown in Fig. 1 (right). We have then a lag network whose zero could be placed before the OA second pole, say at  $f_z = 100$  kHz, and the pole to a frequency  $f_p$  that gives  $|G_{loop}(f_z)| = 0\text{dB}$ . We have then

$$\begin{cases} G_0 f_{p0} = G_1 f_{p1} \\ G_1 f_{p1}^2 = f_z^2 \end{cases} \Rightarrow f_p = \frac{f_z^2}{G_0 f_{p0}} = 2 \text{ kHz}.$$

The resulting diagram is reported in Fig. 2 (left). Please note that in this case, even a simple voltage divider (*i.e.*, without the capacitor  $C$ ) that lowers the loop gain by a factor of 5 would work, giving a larger bandwidth. Usually such a solution is not recommended, but here the reduction is small and can be accepted. Finally, the pole and zero values are given by

$$f_z = \frac{1}{2\pi C R_b} \quad f_{p1} = \frac{1}{2\pi C (R_a + R_b)}.$$

## Problem 2

### 2.1

If the BP filter is centered at  $f_r$ , the output signal amplitude is obviously  $V_o = AG$ . Moreover, since  $f_r \ll f_{nc}$ , the flicker noise is dominant and the noise PSD to consider is actually

$$S_{V_i}(f_r) = S_V \frac{f_{nc}}{f_r} = 3.75 \times 10^{-13} \text{ V}^2/\text{Hz},$$

where we have neglected  $S_I$  assuming a low-impedance input.  $S/N$  then becomes:

$$\frac{S}{N} = \frac{A}{\sqrt{S_{V_i}(f_r) BW_n}} = 10 \Rightarrow BW_n = \frac{A^2}{100 S_{V_i}(f_r)} = 0.67 \text{ Hz},$$

*i.e.*, a filter  $BW = 0.42$  Hz and a quality factor (see Drill #1)  $Q = f_r/BW \approx 188$ . Such a filter is well beyond the limit of what can be achieved with OAs!

### 2.2

The output signal is due to the product of the sinusoidal input signal and the harmonic at  $f_r$  of the reference square wave (of amplitude  $B$ ), while the noise is collected by all the harmonics:

$$V_o = GA \frac{2B}{\pi} \quad \overline{n_o^2} = 2BW_n G^2 \left( \frac{2B}{\pi} \right)^2 \sum_k \frac{S_{V_i}((2k+1)f_r)}{(2k+1)^2},$$

where the factor 2 in the noise expression stems from the fact that  $S_{V_i}$  is unilateral. As the noise corner frequency is much larger than  $f_r$ , we can consider a pure flicker noise condition, that leads to (see class notes)

$$\left( \frac{S}{N} \right) = \frac{A}{\sqrt{2BW_n S_{V_i}(f_r)}} \frac{1}{1.0256} = 10 \Rightarrow BW_n \approx \frac{A^2}{210 S_{V_i}(f_r)} = 0.31 \text{ Hz} \Rightarrow BW = \frac{2}{\pi} BW_n \approx 0.2 \text{ Hz},$$

which means a filter time constant  $T_F \approx 0.8$  s.

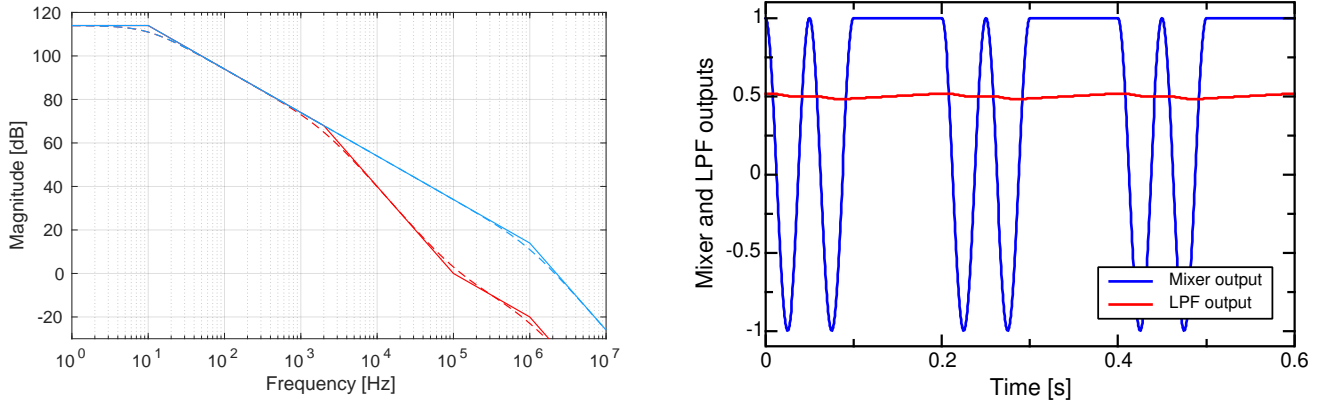


Figure 2: Left = Bode plots of the original and compensated loop gains. Right = mixer and output signal when the frequency is switched as in #2.4.

### 2.3

The 1.5 kHz interference does not give any output, as none of its harmonics fall within the transmission window of the LIA. In reality, issues such as the saturation of the amplifier and/or of the LIA limit the maximum tolerable amplitude of the interference. These are quantified by the dynamic reserve of the LIA and are not considered here.

The fundamental harmonic of the 1.2 kHz interference, instead, falls right on the 15<sup>th</sup> harmonic of the 80 Hz reference, resulting in an output signal of

$$V_{int} = G \frac{2B}{15\pi} \frac{4A_i}{\pi},$$

where  $A_i$  is the interference amplitude. Please note that in reality we should also consider the higher harmonics (*e.g.*, the third harmonics at 3.6 kHz corresponds to the 45<sup>th</sup> one of the reference), but the result does not change. Even if not required, we can now set a condition to achieve a small output error:

$$V_{int} \ll GA \frac{2B}{\pi} \Rightarrow A_i \ll \frac{15}{4} \pi A \approx 59 \mu V.$$

### 2.4

The LF component at the mixer output is a sinusoidal signal with the difference in frequency between the two input signals (we consider the first harmonic of the square wave), i.e.

$$V_M = GA \frac{2B}{\pi} \cos((f_r - f_s)t).$$

If we consider just the cosine term, we see that in our case,  $\Delta f = f_r - f_s$  is  $\pm 10$  Hz, which does *not* affect it (cosine is an even function). We then get a sinusoidal output signal that is filtered by the LPF, leading to  $V_o = 0$ .

A better solution is to move the reference frequency to 70 or 90 Hz, in order to have  $\Delta f = 0$  (i.e.,  $\cos(\Delta f t) = 1$ ) for half of the time. In the other half,  $\Delta f = 20$  Hz, and the cosine term is averaged to zero by the LPF. So, the LPF output signal will be one half the previous one. Fig. 2 (left) shows the  $\cos(\Delta f t)$  term and the (normalized) LPF output.