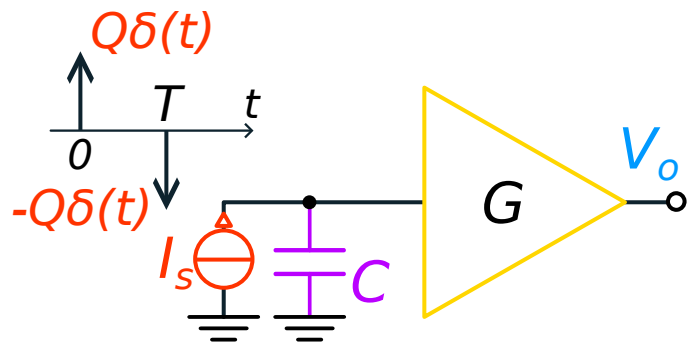
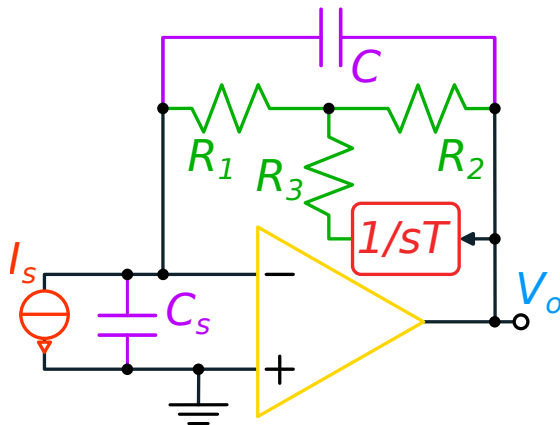


For a correct evaluation, please write your answers in a readable way; thank you



Solving six points correctly gives you 30/30

### Problem 1

The scheme in the left figure is a preamplifier for an accelerometer, schematized by a current source and its capacitance  $C_s = 1.2 \text{ nF}$ . Parameters are  $R_1 = 100 \text{ M}\Omega$ ,  $R_2 = 17 \text{ k}\Omega$ ,  $R_3 = 2 \text{ k}\Omega$ ,  $C = 1.25 \text{ nF}$ ,  $T = 40 \text{ s}$ . The OA has  $A_0 = 120 \text{ dB}$  and  $GBWP = 4 \text{ MHz}$ .

1. Neglect the integrator block and  $R_3$  (for this point only) and evaluate the ideal gain.
2. Repeat the previous point for the full circuit (consider  $R_1 \gg R_2, R_3$ ). What is the purpose of the integrator block?
3. Compute the high-frequency output noise voltage PSD and rms value considering the equivalent voltage noise source of the OA  $\sqrt{S_V} = 20 \text{ nV}/\sqrt{\text{Hz}}$ .
4. Suggest a realization for the integrator block in the above scheme using only one OA. *Hint: think of the standard integrator and tweak its input.*

### Problem 2

A sensor outputs a current signal made of two delta pulses with charge  $Q \approx 5 \text{ fC}$  separated by  $T = 80 \text{ ms}$ . The sensor, with a capacitance of  $C = 500 \text{ pF}$  is connected to a voltage amplifier with gain  $G = 10$  and equivalent input noise  $\sqrt{S_I} = 1 \text{ pA}/\sqrt{\text{Hz}}$ ,  $\sqrt{S_V} = 4 \text{ nV}/\sqrt{\text{Hz}}$ .

1. Compute the output signal and noise PSD.
2. Compute the weighting function of the optimum filter.
3. Compute the optimum  $S/N$ .
4.  $S_V$  and  $S_I$  have a flicker component with the same noise corner frequency  $f_{nc}$ . What is the maximum value of  $f_{nc}$  that allows to neglect the flicker noise (in the previous optimum filter case)? *Hint: consider the noise sources after the whitening filters and find a suitable approximation for  $|W(f)|^2$  in the FN case.*

Allowed time: 2 hours 45 minutes – Do a good job!

Results will be posted by July 24<sup>th</sup>

Mark registration: Friday, July 26<sup>th</sup>

# Solution

## Problem 1

### 1.1

Without the integrator block and  $R_3$ , the feedback network is the parallel of  $C$  and  $R_1 + R_2$ . The output voltage is then

$$\frac{V_o}{I_s} = \frac{R_1 + R_2}{1 + sC(R_1 + R_2)} \approx \frac{R_1}{1 + sCR_1}.$$

### 1.2

We label  $V_m$  the node between  $R_1$  and  $R_2$  and write the KCL:

$$\frac{V_m}{R_1} + \frac{V_m - V_o}{R_2} + \frac{V_m - \frac{V_o}{sT}}{R_3} = 0 \Rightarrow V_o \left( \frac{1}{R_2} + \frac{1}{sTR_3} \right) = V_m \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \approx V_m \left( \frac{1}{R_2} + \frac{1}{R_3} \right),$$

from which

$$V_m = V_o \frac{sTR_3 + R_2}{sT(R_2 + R_3)}.$$

The KCL at the input node of the OA gives then

$$I_s = sCV_o + \frac{V_m}{R_1} \Rightarrow \frac{V_o}{I_s} = \frac{sTR_1(R_2 + R_3)}{s^2TCR_1(R_2 + R_3) + sTR_3 + R_2}.$$

We now have a zero in the origin and two coincident poles (the quality factor is 0.5023) at 67 mHz, beyond which the gain follows the result in #1.1. A Bode plot of the gain is reported in Fig. 1 (left). The zero in the origin cancels any effect related to offset and bias currents of the OA.

### 1.3

At HF, the impedances of the capacitors is small and the feedback network is dominated by  $C$  (note that the output of the integrator is almost zero). We have then a partition between  $C_s$  and  $C$ , i.e.,

$$V_o = V_n \frac{C + C_s}{C} \Rightarrow S_{V_o} = S_V \frac{(C + C_s)^2}{C^2} \approx \left( 39 \text{ nV}/\sqrt{\text{Hz}} \right)^2$$

and

$$G_{loop} = -A(s) \frac{\frac{1}{sC_s}}{\frac{1}{sC_s} + \frac{1}{sC}} = -A(s) \frac{C}{C + C_s},$$

i.e.,  $f_{0dB} = GBWP \ C/(C + C_s) \approx 2 \text{ MHz}$ , leading to

$$\overline{V_o^2} \approx S_V \frac{(C + C_s)^2}{C^2} \frac{\pi}{2} f_{0dB} \approx (69 \text{ } \mu\text{V})^2.$$

Full calculation (still considering  $R_1 \gg R_2, R_3$ ) leads to

$$V_o = V_n \frac{sT(R_2 + R_3)(1 + s(C + C_s)R_1)}{s^2TCR_1(R_2 + R_3) + sTR_3 + R_2},$$

from where the HF limit can be recovered.

### 1.4

The standard integrator is obviously inverting, so to achieve the desired result we should apply the input at the NI input of the OA. But this result in

$$\frac{V_o}{V_i} = 1 + \frac{1}{sCR} = \frac{1 + sCR}{sCR},$$

which is good apart from the zero. To cancel it, we can apply an LPF at the input, resulting in the scheme of Fig. 1 (right), that gives the desired result.

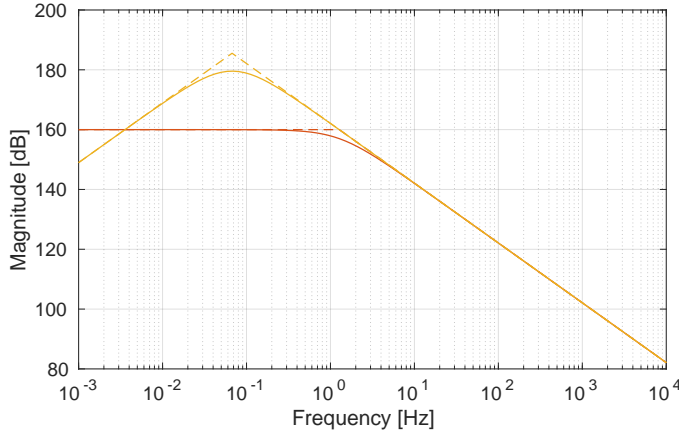


Figure 1: Left = Circuit gain with (yellow) and without (red) the integrator stage. Right = scheme for a NI integrator.

## Problem 2

### 2.1

The current signal is integrated by the capacitor  $C$ , resulting in a rectangular signal at the amplifier output:

$$V_o = I_s \frac{1}{sC} G \Rightarrow V_o(t) = \frac{QG}{C} \int (\delta(t) - \delta(t - T)) dt = \frac{QG}{C} \text{rect}(0, T),$$

where  $\text{rect}$  is the unit-amplitude rectangular function. The output noise is instead

$$V_o = \left( V_n + \frac{I_n}{sC} \right) \Rightarrow S_{V_o} = G^2 \left( S_V + \frac{S_I}{(\omega C)^2} \right) = G^2 S_V \frac{1 + \omega^2 C^2 \frac{S_V}{S_I}}{\omega^2 C^2 \frac{S_V}{S_I}} = G^2 S_V \frac{1 + \omega^2 T_n^2}{\omega^2 T_n^2},$$

where  $T_n = C \sqrt{S_V / S_I} \approx 2 \mu\text{s}$ .

### 2.2

As the noise PSD is not white, a whitening filter is needed, whose TF  $H_w$  is given by

$$S_{V_o} |H_w|^2 = \text{const} \Rightarrow |H_w| \propto \frac{1}{\sqrt{S_{V_o}}} = K \frac{\omega T_n}{\sqrt{1 + (\omega T_n)^2}} \Rightarrow H_w(s) = \frac{s T_n}{1 + s T_n},$$

i.e., an LTI HPF. This filter obviously affects the signal as well, that now becomes (remember the step response of the HPF):

$$V_w(s) = V_o(s) H_w(s) = \frac{QG}{sC} (1 - e^{-sT}) \frac{s T_n}{1 + s T_n} \Leftrightarrow V_w(t) = \frac{QG}{C} \left( e^{-t/T_n} u(t) - e^{-(t-T)/T_n} u(t - T) \right).$$

The second stage  $W_2$  of the optimum filter is now a matched filter with weighting function proportional to  $V_w(t)$ . In the frequency domain, we have then

$$W_2(T, f) = \frac{1 - e^{-j\omega T}}{1 + \omega T_n} \quad |W(T, f)| \propto |H_w(f)| |W_2(T, f)| = (1 - e^{-j\omega T}) \frac{\omega T_n}{1 + (\omega T_n)^2}.$$

Note that the expression of  $W$  is equal to  $V_o(f) |H_w(f)|^2$ , and could have been obtained as  $V_o(f) / S_{V_o}(f)$ .

### 2.3

To compute  $S/N$ , we can look at the whitening filter output and remember that

$$\left( \frac{S}{N} \right)_{\text{opt}} = \frac{Q}{C \sqrt{S_V/2}} \sqrt{2 \int_0^\infty e^{-2t/T_n} dt} = \frac{Q}{C} \sqrt{\frac{2T_n}{S_V}} = 5,$$

where the factor of 2 before the integral accounts for the two equal exponential signals that do not overlap. Of course, the same result can be obtained from

$$\left(\frac{S}{N}\right)_{opt} = \frac{Q}{C} \sqrt{\int \frac{|X(f)|^2}{S_V(f)/2} df},$$

considering again only the first delta function (and multiplying by two), obtaining

$$\left(\frac{S}{N}\right)_{opt} = \frac{Q}{C} \sqrt{2 \int \frac{\left|\frac{1}{\omega}\right|^2}{\frac{S_V}{2} \frac{1 + (\omega T_n)^2}{(\omega T_n)^2}} \frac{d\omega}{2\pi}} = \frac{Q}{C} \sqrt{\frac{2T_n}{\pi S_V} \int \frac{d\omega T_n}{1 + (\omega T_n)^2}} = \frac{Q}{C} \sqrt{\frac{2T_n}{S_V}}.$$

## 2.4

Beyond the whitening filter, the noise PSD is equal to  $G^2 S_V(f)$ , that now contains both white and flicker components. The WN contribution is then

$$\overline{n_{WN}^2} = G^2 S_V \int w_2^2(t, \tau) d\tau = 2G^2 S_V \frac{1}{4T_n} = G^2 \frac{S_V}{2T_n},$$

where we have considered the matched filter amplitude  $1/T_n$ . For FN we need to switch to the frequency domain, where the input noise is  $S_V f_{nc}/f$  and

$$\overline{n_{FN}^2} = G^2 S_V f_{nc} \int_0^\infty \frac{|W_2^2(t, f)|^2}{f} df = G^2 S_V f_{nc} \int_0^\infty \frac{|1 - e^{-j\omega T}|^2}{|1 + j\omega T_n|^2} \frac{d\omega}{\omega} = 2G^2 S_V f_{nc} \int_0^\infty \frac{1 - \cos \omega T}{1 + (\omega T_n)^2} \frac{d\omega}{\omega}.$$

The HF limit is set by  $f_H = 1/(2\pi T_n)$ . At low frequencies, where the denominator equals 1, the numerator goes to zero as  $f \rightarrow 0$  and then oscillates between 0 and 2, with average value equal to one, behaving like an HPF. A nice guess for  $f_L$  could be as follows: at low frequencies we have

$$1 - \cos \omega T \approx \frac{(\omega T)^2}{2},$$

while an HPF with time constant  $T_L$  has a square modulus of the transfer function equal to  $(\omega T_L)^2$ . Equalling the terms, we get

$$T_L = \frac{T}{\sqrt{2}} \Rightarrow f_L = \frac{1}{2\pi T_L} = \frac{1}{\sqrt{2}\pi T} \approx \frac{1}{4.4 T}$$

from which we get

$$\overline{n_{FN}^2} \approx 2G^2 S_V f_{nc} \log\left(\frac{f_H}{f_L}\right) \approx 2G^2 S_V f_{nc} \log\left(\frac{2.2 T}{\pi T_n}\right) \approx 20.5 G^2 S_V f_{nc}.$$

To get equal contributions, we must have

$$20.5 G^2 S_V f_{nc} = G^2 \frac{S_V}{2T_n} \Rightarrow f_{nc} = \frac{1}{41T_n} = 12.2 \text{ kHz}.$$

This value is quite high, meaning that our filter is effective in reducing LF noise. Please note that a simpler estimate of  $f_L$  based on

$$1 - \cos \omega T = 1 \Rightarrow \omega_L T = \frac{\pi}{2} \Rightarrow f_L = \frac{1}{4T}$$

returns a very similar value (12.5 kHz) for  $f_{nc}$ .