



## Active filters

Alessandro Spinelli

Phone: (02 2399) 4001

[alessandro.spinelli@polimi.it](mailto:alessandro.spinelli@polimi.it)

[home.deib.polimi.it/spinelli](http://home.deib.polimi.it/spinelli)



Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes




# Active filters

- Filter networks made with active elements
- No need to use inductors or large resistors
- Easier to implement high-order filters
- Improved performance




# Transfer function (LP case)

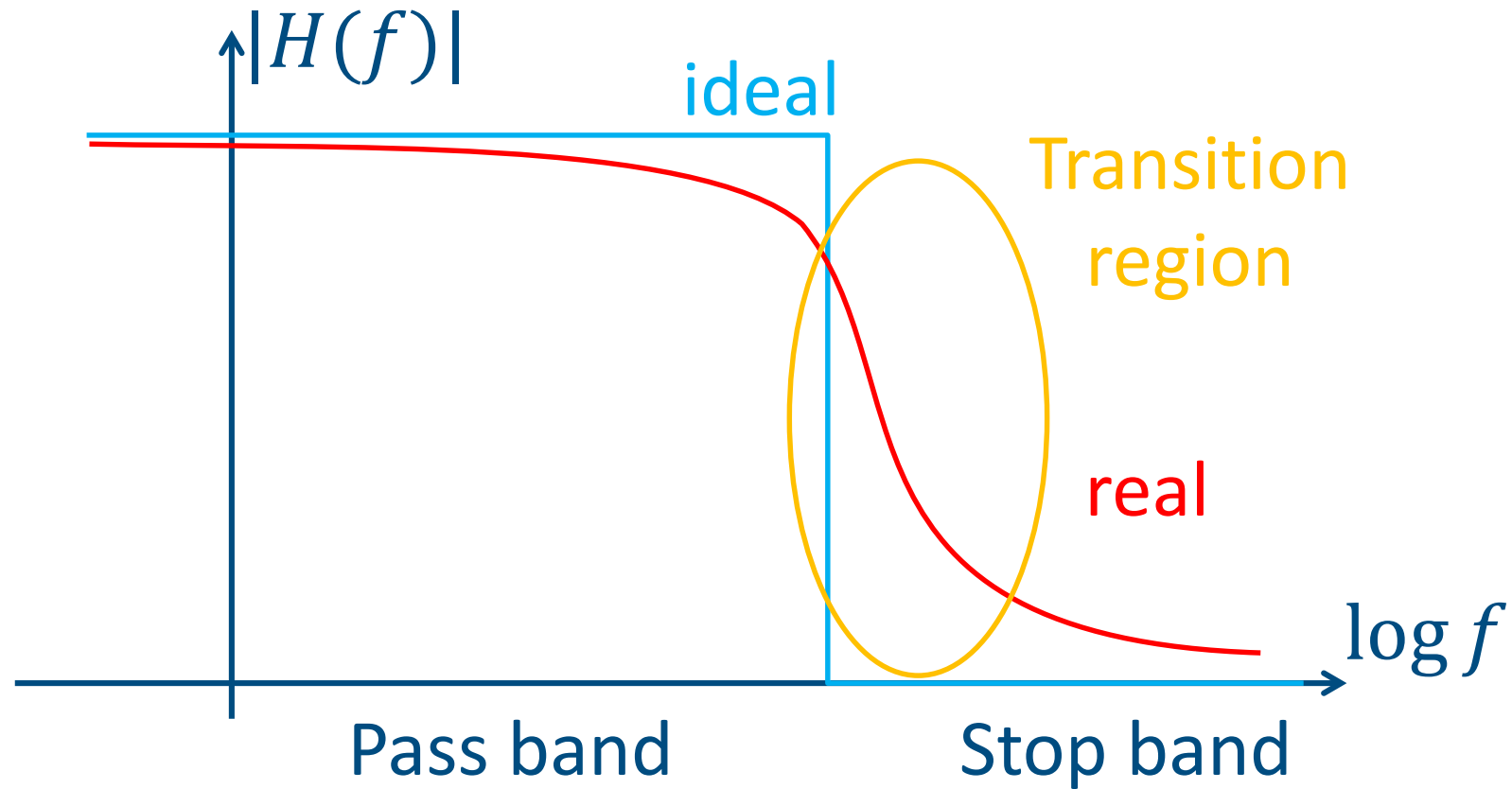



# Typical design parameters

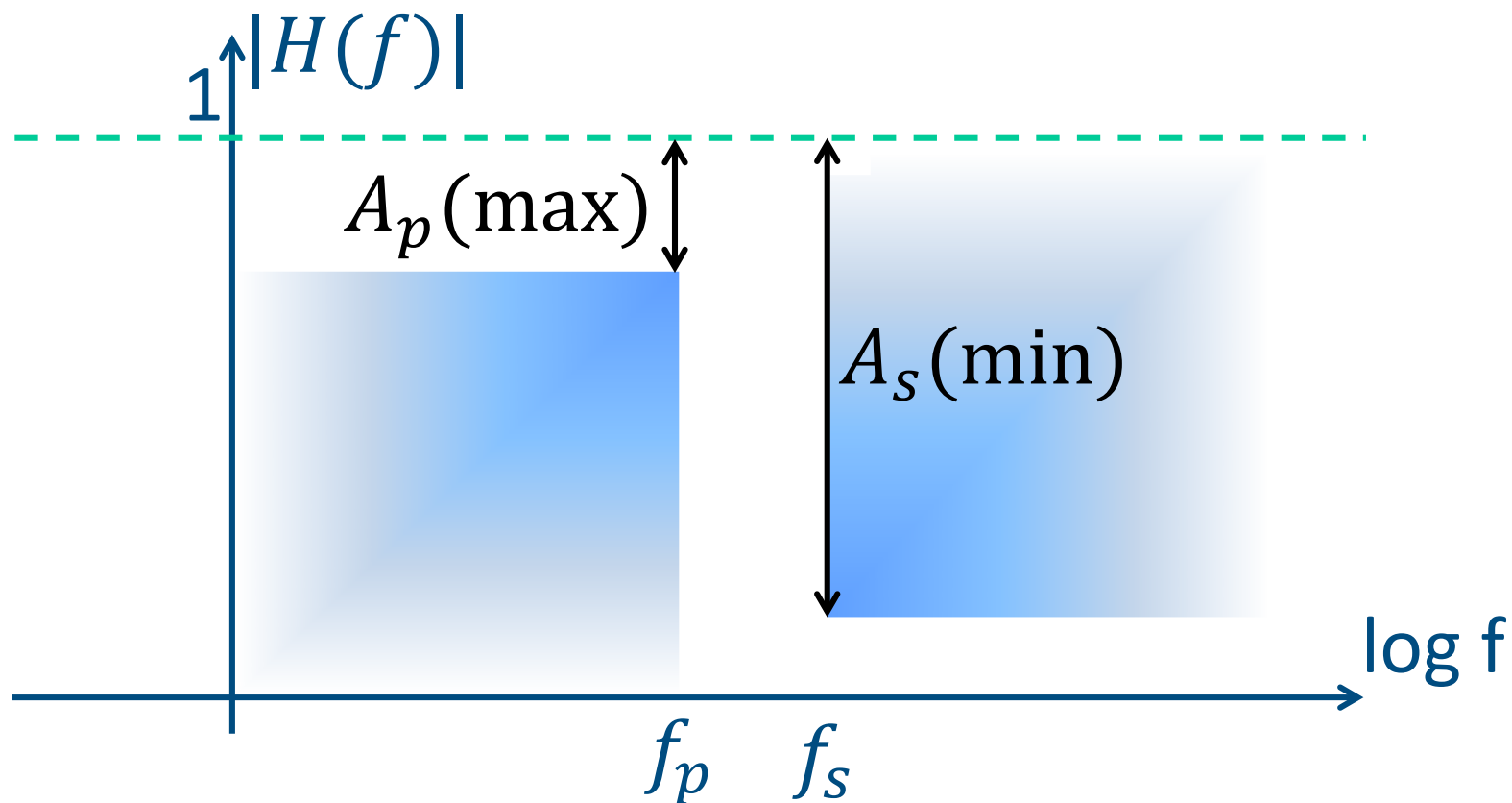



# Butterworth LP filters (1930)

- Single-pole filter:

$$H = \frac{1}{1 + s\tau} \Rightarrow |H| = \frac{1}{\sqrt{1 + (s\tau)^2}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}}$$

- Extension to  $n$  poles:

$$|H| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_0}\right)^{2n}}}$$



# Poles and zeroes

$$1 + \left( \frac{\omega}{\omega_0} \right)^{2n} = 0$$

$$\omega = -js \Rightarrow s^{2n} = -1^{n-1} \omega_0^{2n} = \rho^{2n} e^{jn\theta}$$


$$\rho = \omega_0$$

$$\theta = \frac{\pi}{2} + \frac{2k-1}{2n} \pi$$


where  $k = 1, \dots, n$ . The remaining  $n$  poles are in RHP and solution only of the  $|\cdot|^2$



# Butterworth LP filters (1930)

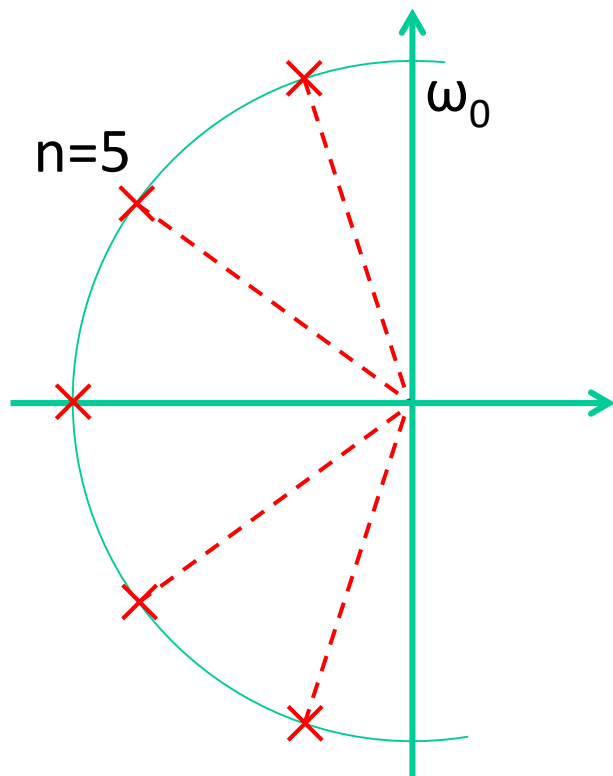
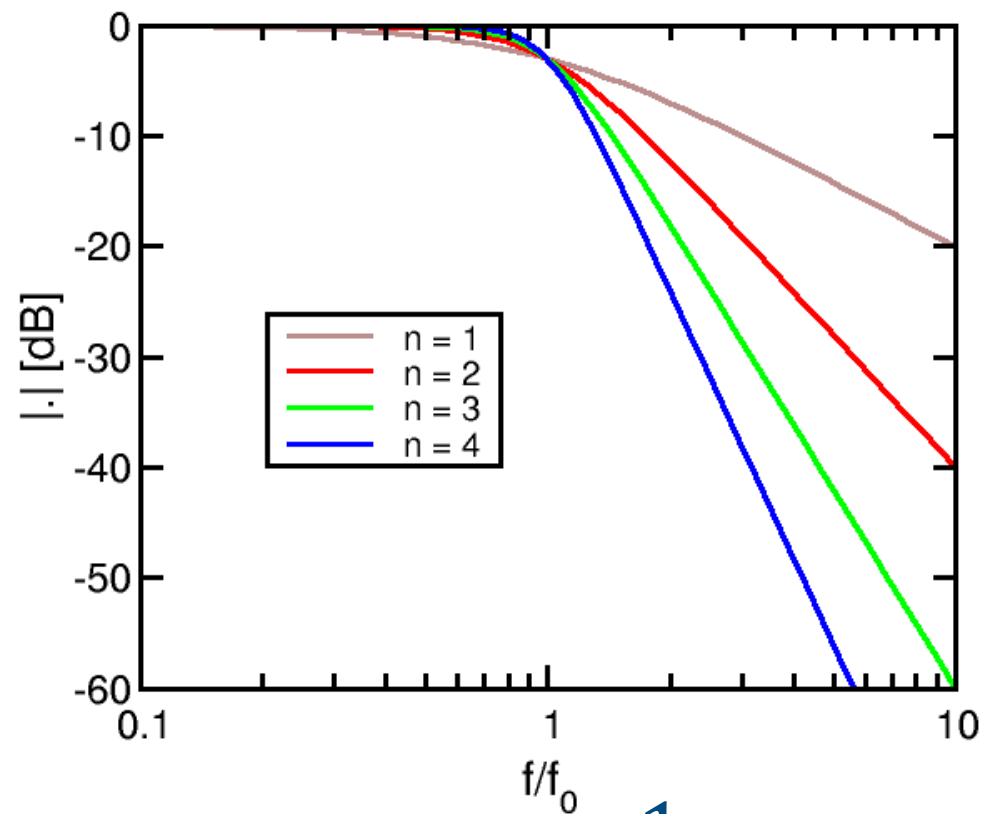
$$\theta = \frac{\pi}{2} + \frac{2k-1}{2n}\pi$$




$$|H| = \frac{1}{\sqrt{1 + (f/f_0)^{2n}}}$$



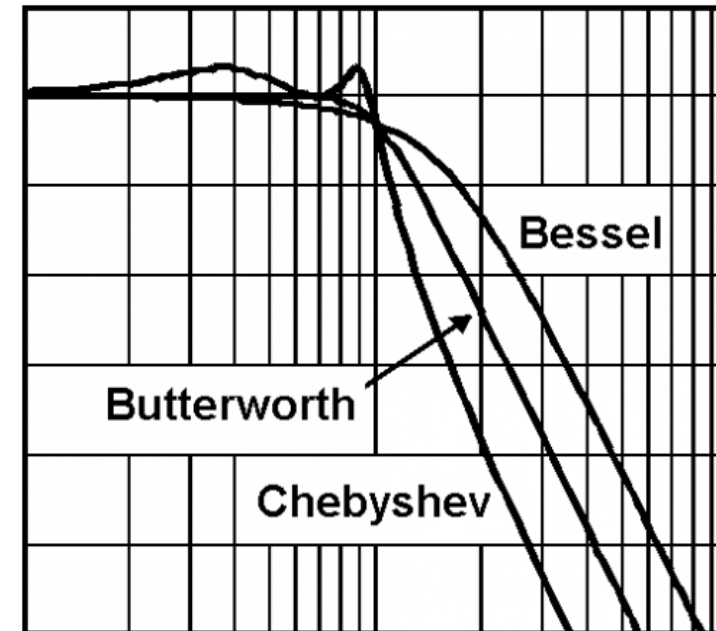
# Notes

- Butterworth filters correspond to a «maximally flat» approximation, with no ripples in the frequency response
- Attenuation at  $f_0$  is 3 dB, independent of  $n$
- Other solutions exist, that optimize attenuation or phase response





# Sallen-Key LP filter (1955)

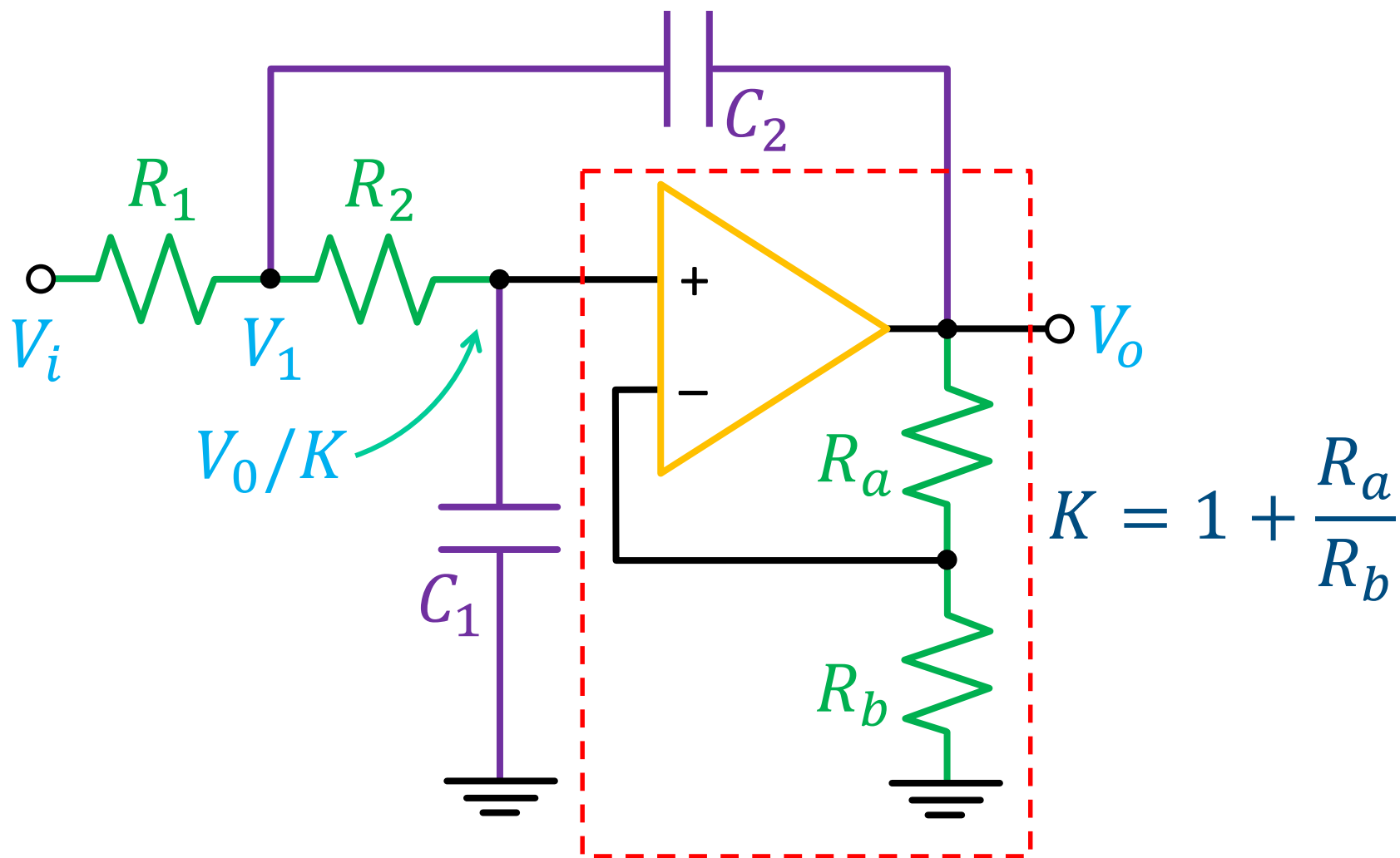



# Transfer function

$$\begin{cases} sC_2(V_o - V_1) + \frac{V_i - V_1}{R_1} = V_1 \frac{sC_1}{1 + sC_1 R_2} \\ \frac{V_1}{1 + sC_1 R_2} = \frac{V_o}{K} \end{cases} \quad \begin{aligned} R_1 &= R_2 = R \\ C_1 &= C_2 = C \end{aligned}$$


$$\frac{V_o}{V_i} = \frac{K}{(sRC)^2 + sRC(3 - K) + 1} = \frac{K/(RC)^2}{s^2 + s \frac{3 - K}{RC} + \left(\frac{1}{RC}\right)^2}$$


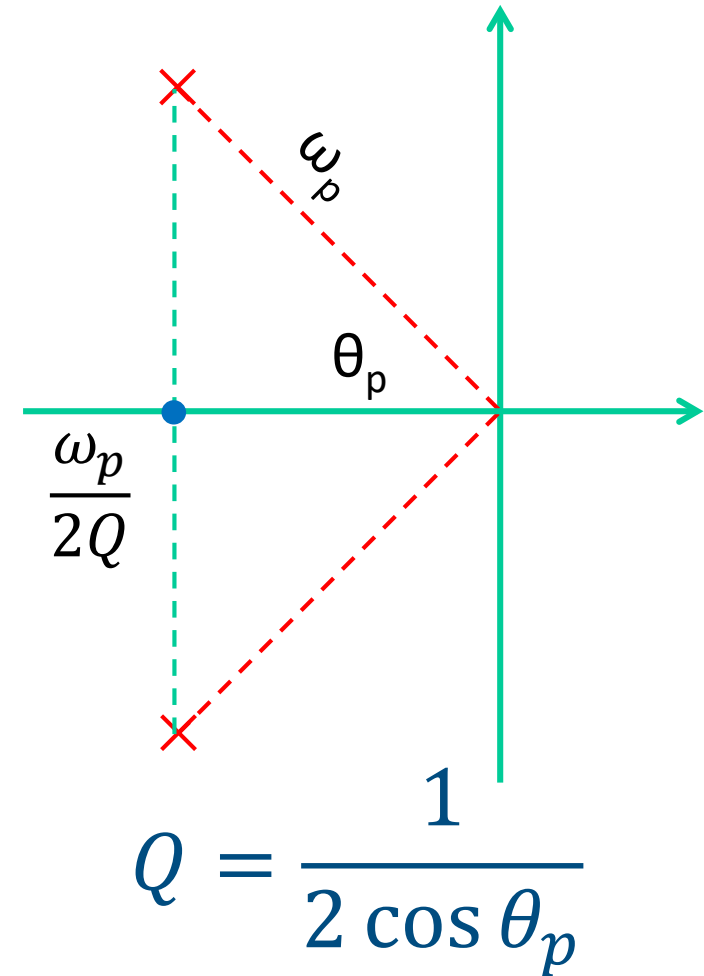
# Filter design

$$RC = \frac{1}{\omega_p}; \quad K = 3 - \frac{1}{Q}$$

- Since  $K \geq 1$ ,  $Q \geq 0.5 \Rightarrow$  poles are always complex (or real coincident)
- $K$  must be less than 3 to avoid instability






# Comments

- SK cells can be cascaded for high-order filters
- Use OA with  $GBWP \approx 10 - 30 f_p$  for not affecting the filter response
- Also check the slew rate at  $f_p$
- $R_o$  will limit the attenuation in the stop band



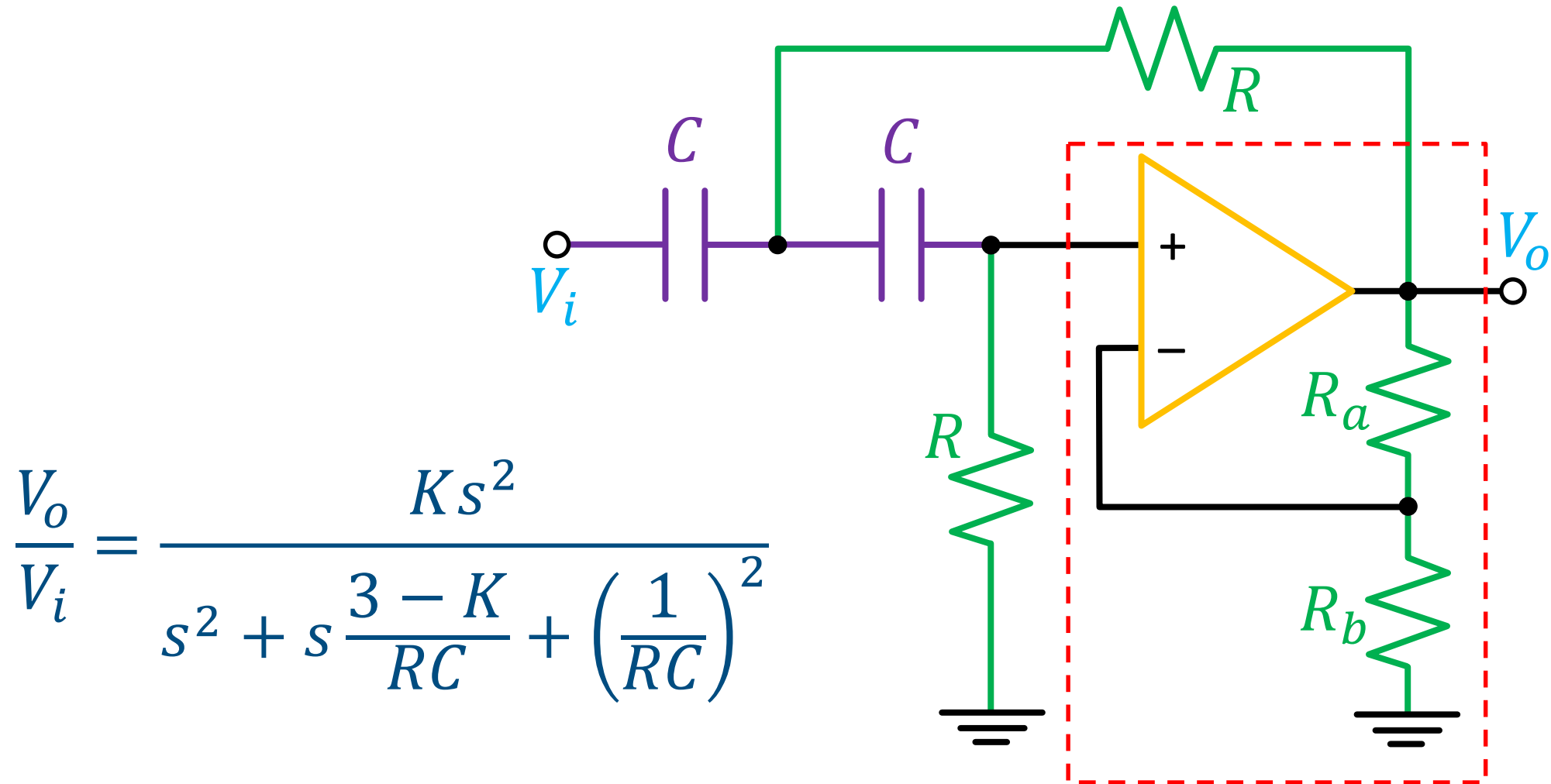
# High-pass SK filter ( $R \leftrightarrow C$ )



$$\frac{V_o}{V_i} = \frac{Ks^2}{s^2 + s\frac{3-K}{RC} + \left(\frac{1}{RC}\right)^2}$$



# Band-pass filters

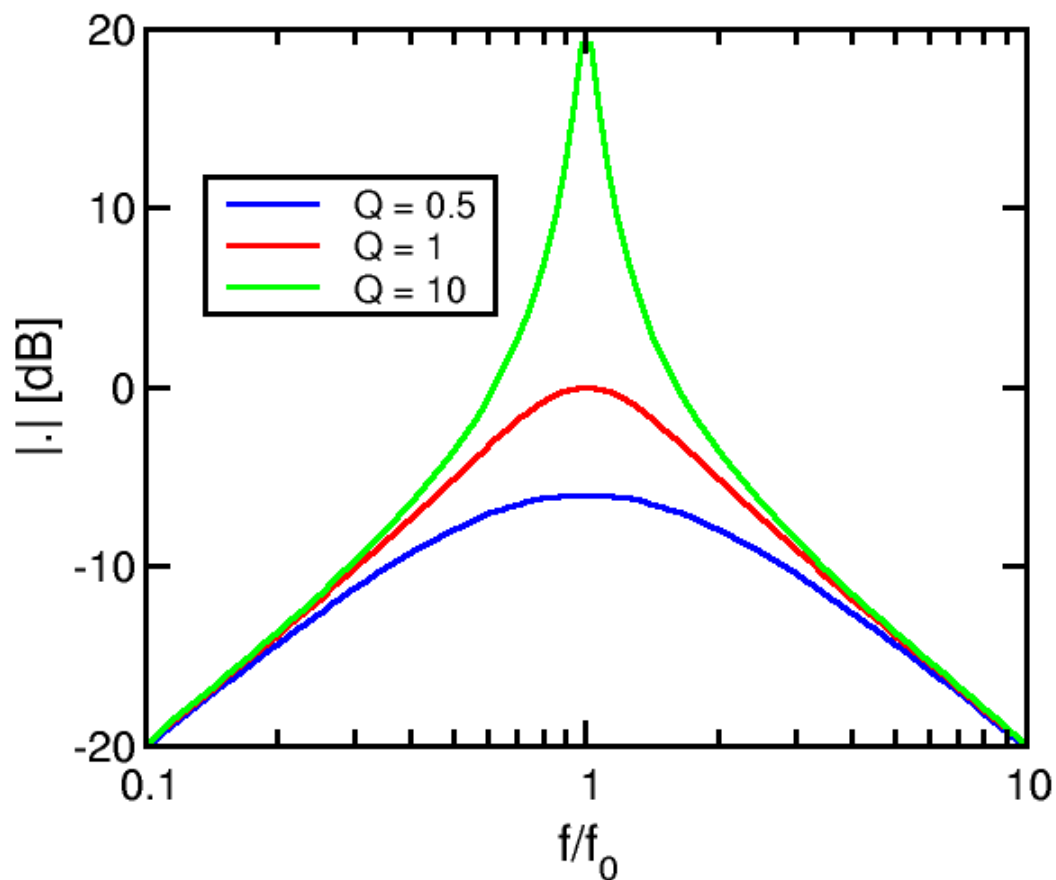

$$f_0 = \sqrt{f_H f_L}$$

$$Q = \frac{f_0}{BW} = \frac{f_0}{f_H - f_L}$$



# Band-pass SK filter

$$f_0 = \frac{1}{2\pi RC}$$

$$Q = \frac{1}{3 - k}$$

$$G_0 = \frac{k}{3 - k}$$

