

# Reflections on transmission lines

Alessandro Spinelli


Phone: (02 2399) 4001

[alessandro.spinelli@polimi.it](mailto:alessandro.spinelli@polimi.it)


[home.deib.polimi.it/spinelli](http://home.deib.polimi.it/spinelli)

Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes

# Transmission-line model

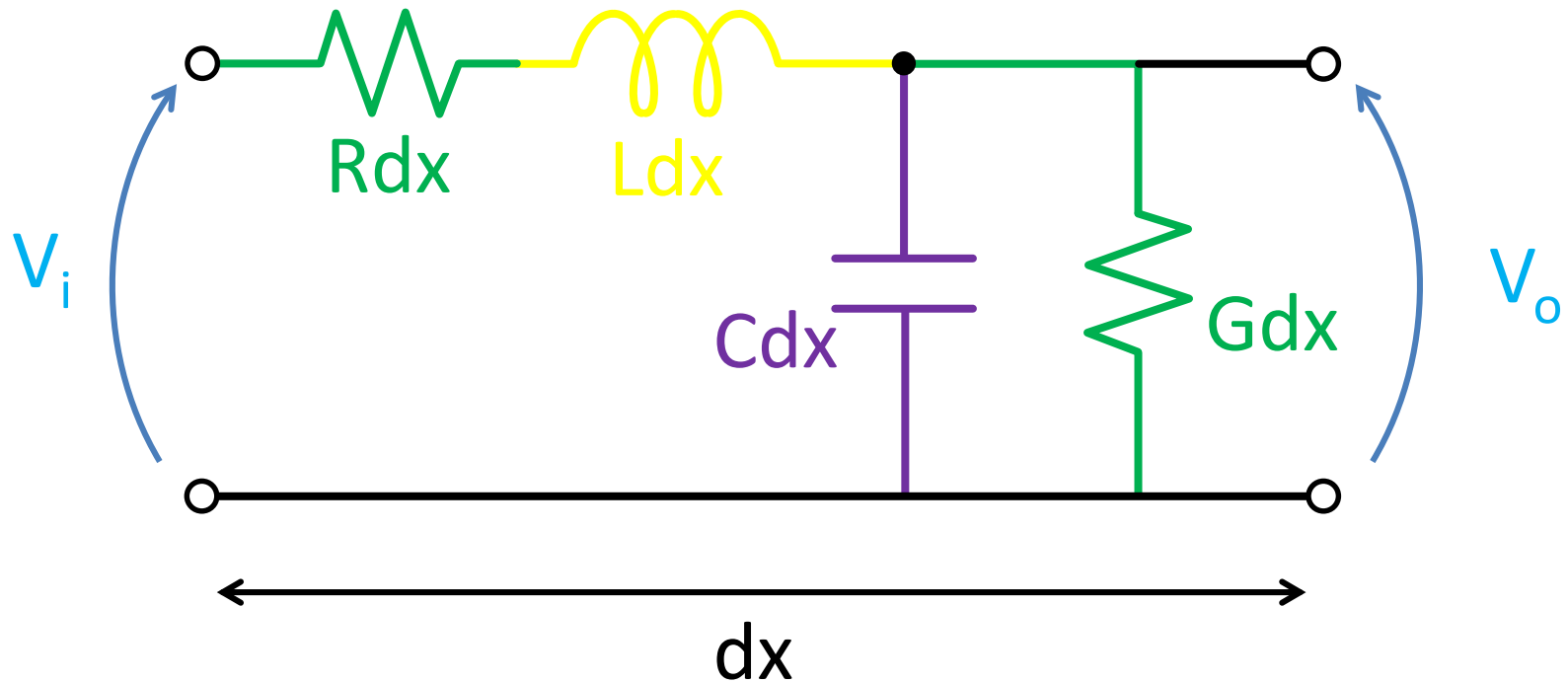

# Characteristic impedance

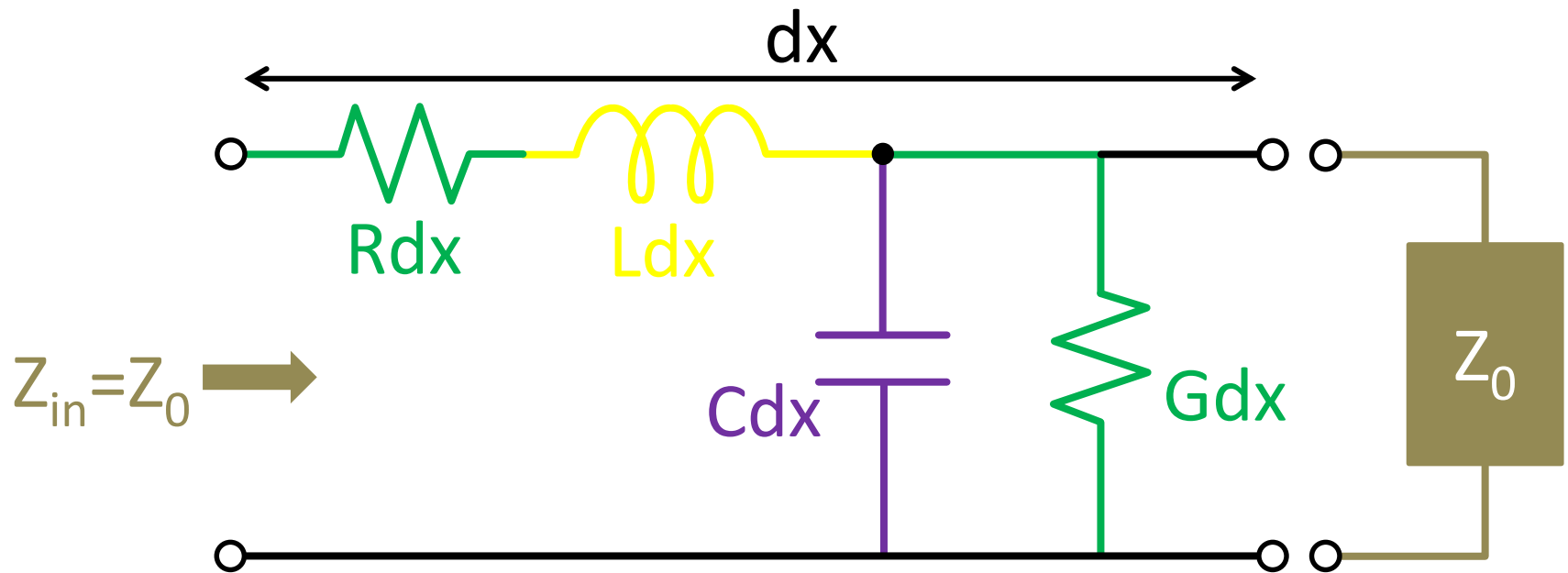


$$Z_0 = Rdx + j\omega Ldx + Z_0 \parallel \left( \frac{1}{Gdx + j\omega Cdx} \right)$$

# Calculations...


$$Z_0 = (R + j\omega L)dx + \frac{Z_0}{1 + Z_0(G + j\omega C)dx}$$

$$\cancel{Z_0} + Z_0^2(G + j\omega C)dx = (R + j\omega L)dx + Z_0(R + j\omega L)(G + j\omega C)dx^2 + \cancel{Z_0}$$

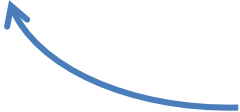 neglected

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$


# Typical results

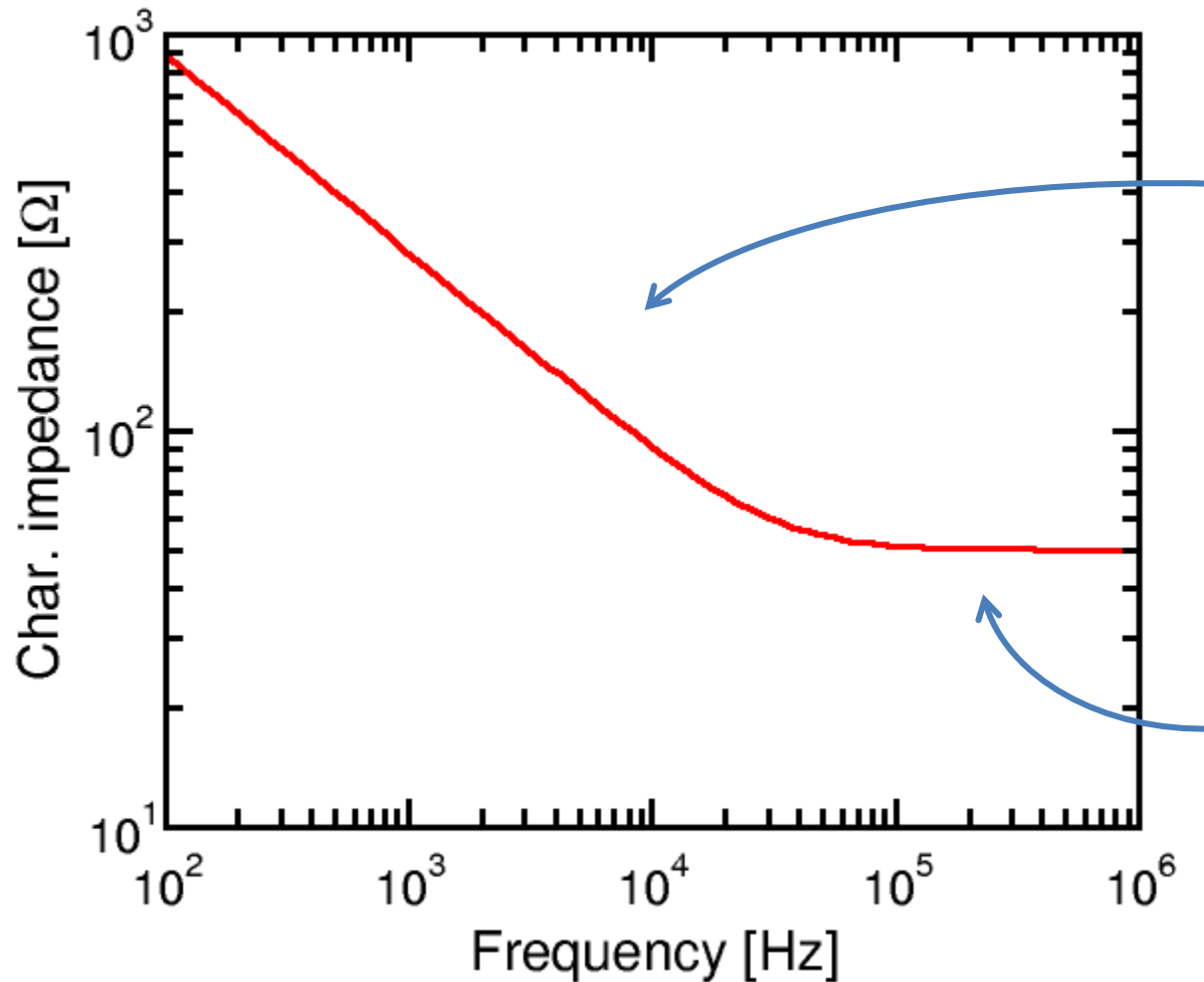

$$Z_0 = \sqrt{\frac{R}{j\omega C}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

# Non-dissipative line (R=G=0)

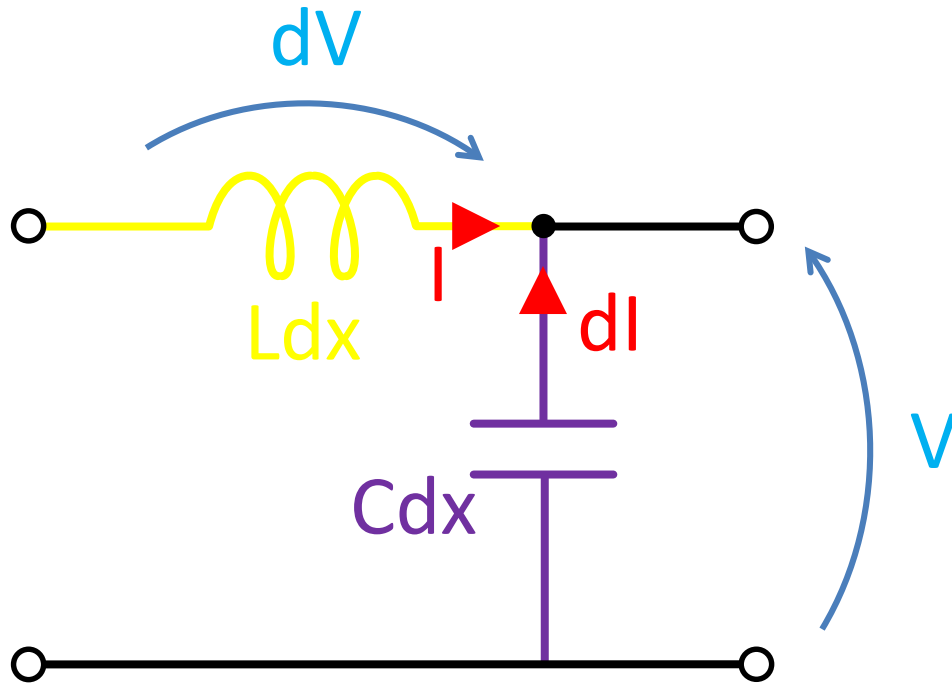

$$dV = -Ldx \frac{dI}{dt}$$

$$dI = -Cdx \frac{dV}{dt}$$

$$\frac{d^2V}{dx^2} = LC \frac{d^2V}{dt^2}$$


$$\frac{d^2I}{dx^2} = LC \frac{d^2I}{dt^2}$$

# Travelling-wave equations


$$V(x, t) = V^+ \left( t - \frac{x}{u} \right) + V^- \left( t + \frac{x}{u} \right)$$

$$I(x, t) = I^+ \left( t - \frac{x}{u} \right) + I^- \left( t + \frac{x}{u} \right)$$

forward

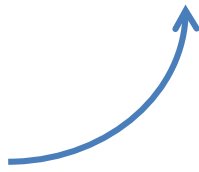

backward

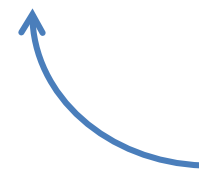

$$u = \frac{1}{\sqrt{LC}} = \text{propagation speed}$$

# $Z_0$ revisited – 1

We consider the forward wave. From

$$\frac{dV^+(t - x/u)}{dx} = -L \frac{dI^+(t - x/u)}{dt}$$

we take  $z = t - x/u$ , i.e.

$$\begin{aligned} \frac{dV^+ \left( t - \frac{x}{u} \right)}{dx} &= \frac{dV^+(z)}{dz} \frac{dz}{dx} = -\frac{1}{u} \frac{dV^+(z)}{dz} \\ \frac{dI^+ \left( t - \frac{x}{u} \right)}{dt} &= \frac{dI^+(z)}{dz} \frac{dz}{dt} = \frac{dI^+(z)}{dz} \end{aligned}$$

## $Z_0$ revisited – 2


- Replacing, we get

$$\frac{dV^+}{dz} \sqrt{LC} = L \frac{dI^+}{dz} \rightarrow V^+ = Z_0 I^+$$

and analogously  $V^- = -Z_0 I^-$

which is the result already obtained

# Example: coaxial cables

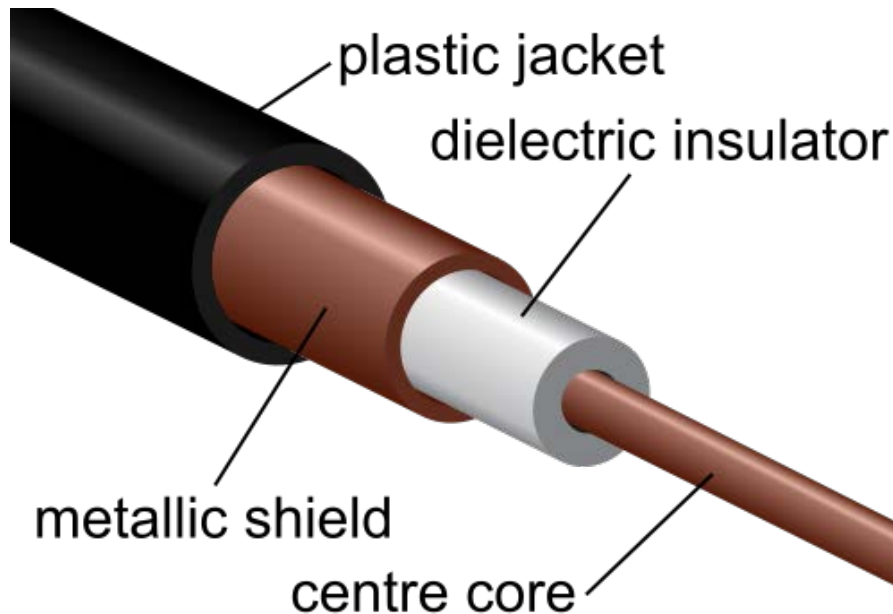

$$C = \frac{2\pi\epsilon}{\ln(D/d)}$$


$$L = \frac{\mu}{2\pi} \ln(D/d)$$

$$Z_0 = \sqrt{\frac{L}{C}} = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \ln\left(\frac{D}{d}\right) = \frac{138}{\sqrt{\epsilon_r}} \ln\left(\frac{D}{d}\right) [\Omega]$$

# 50 $\Omega$ cables

- Chosen as compromise between power-handling capabilities (maximum at around 30  $\Omega$ ) and attenuation (minimum around 60-70  $\Omega$ )
- Diameters of inner and outer conductors have «good» values and are easy to manufacture
- Other values can be used in special applications (e.g. 93  $\Omega$  for digital transmission, 25  $\Omega$  for RF,...)

# Loaded line

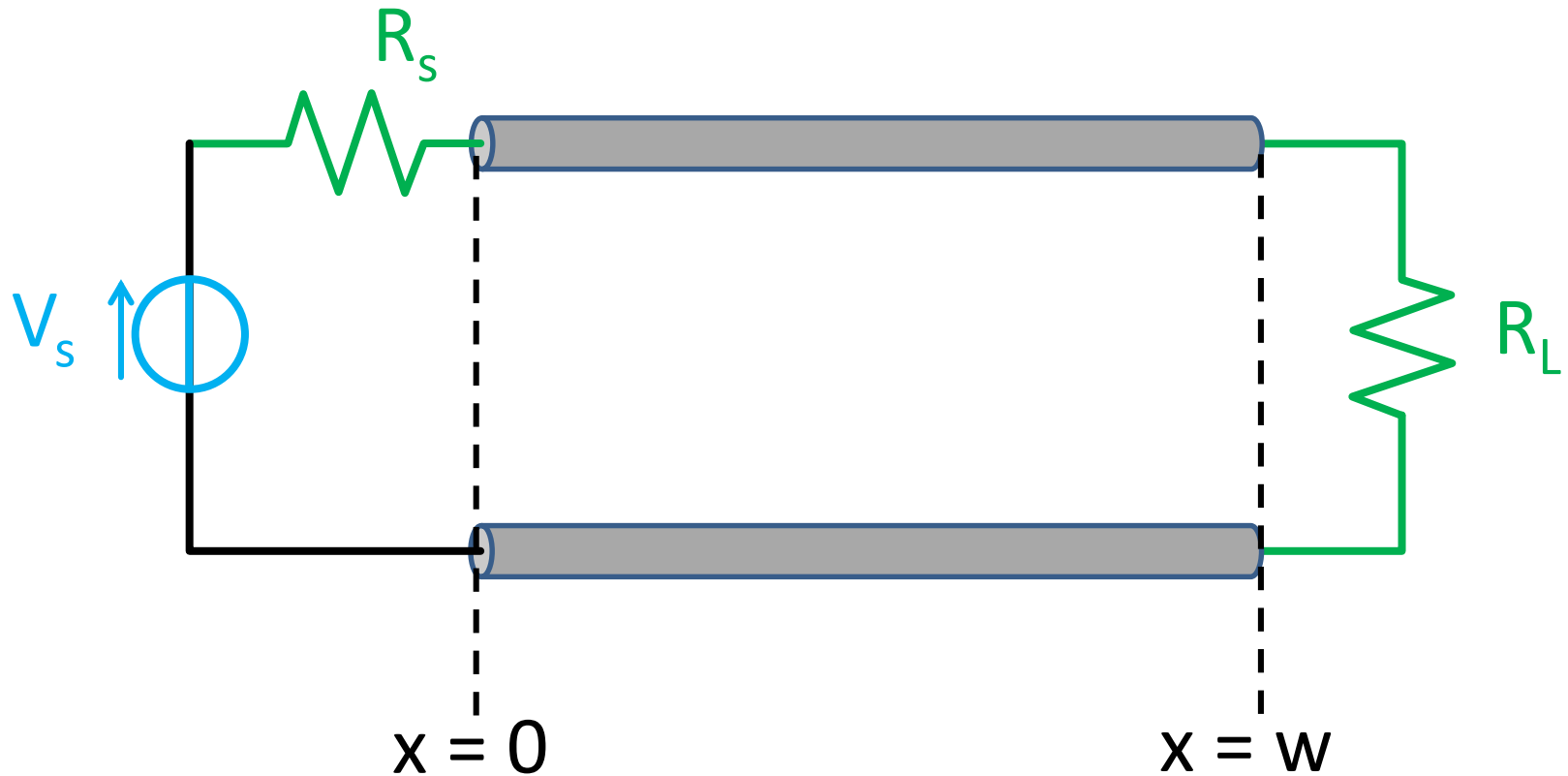

# Boundary condition

- Load resistor forces

$$V(w, t) = R_L I(w, t)$$

where  $V = V^+ + V^-$  and  $I = I^+ + I^-$

- Recalling that  $I^\pm = \pm V^\pm / Z_0$ , we get

$$V^+ + V^- = \frac{R_L}{Z_0} (V^+ - V^-)$$

# Matched line ( $R_L = Z_0$ )

$$V^+ + V^- = V^+ - V^- \Rightarrow V^- = 0$$

- No backward wave
- The line behaves as of infinite length (recall the calculation of  $Z_0$ )

# The case of $R_L \neq Z_0$

- Waves are partially reflected from the mismatch at the load:  $V^- \neq 0$
- We define a voltage reflection coefficient at the load,  $\Gamma_w$ , as

$$\Gamma_w = \frac{V^- \left( t + \frac{w}{u} \right)}{V^+ \left( t - \frac{w}{u} \right)}$$
$$V^+ (1 + \Gamma_w) = \frac{R_L}{Z_0} V^+ (1 - \Gamma_w)$$

# Reflection coefficient

$$\frac{R_L}{Z_0} = \frac{1 + \Gamma_w}{1 - \Gamma_w}$$

$$\Gamma_w = \frac{R_L - Z_0}{R_L + Z_0}$$


$$-1 \leq \Gamma_w \leq 1$$

$$R_L = 0$$

$$R_L = \infty$$
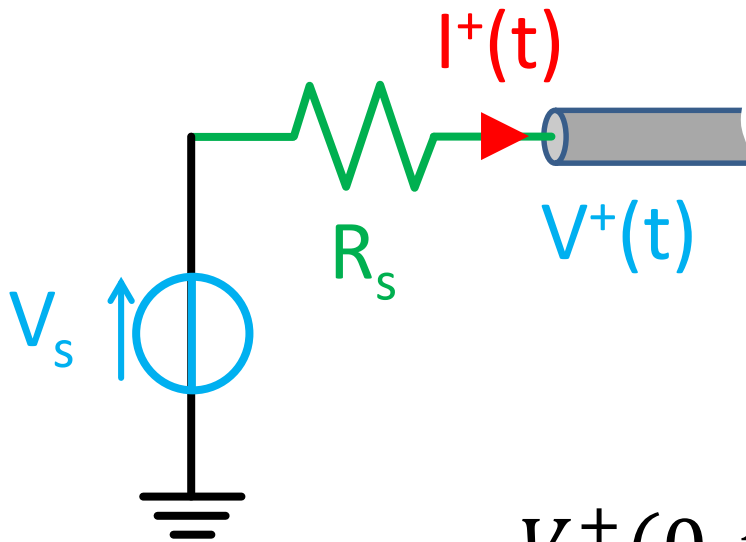
# Reflection at the source


$$\Gamma_0 = \frac{V^+(t)}{V^-(t)} = \frac{R_s - Z_0}{R_s + Z_0} \Rightarrow \frac{R_s}{Z_0} = \frac{1 + \Gamma_0}{1 - \Gamma_0}$$




$$\begin{aligned} V_s &= V^+ + I^+ R_s \\ &= V^+ \left( 1 + \frac{R_s}{Z_0} \right) \end{aligned}$$

$$V^+(0, t) = V_s \frac{Z_0}{Z_0 + R_s} = V_s \frac{1 - \Gamma_0}{2}$$


# Line matched at load side

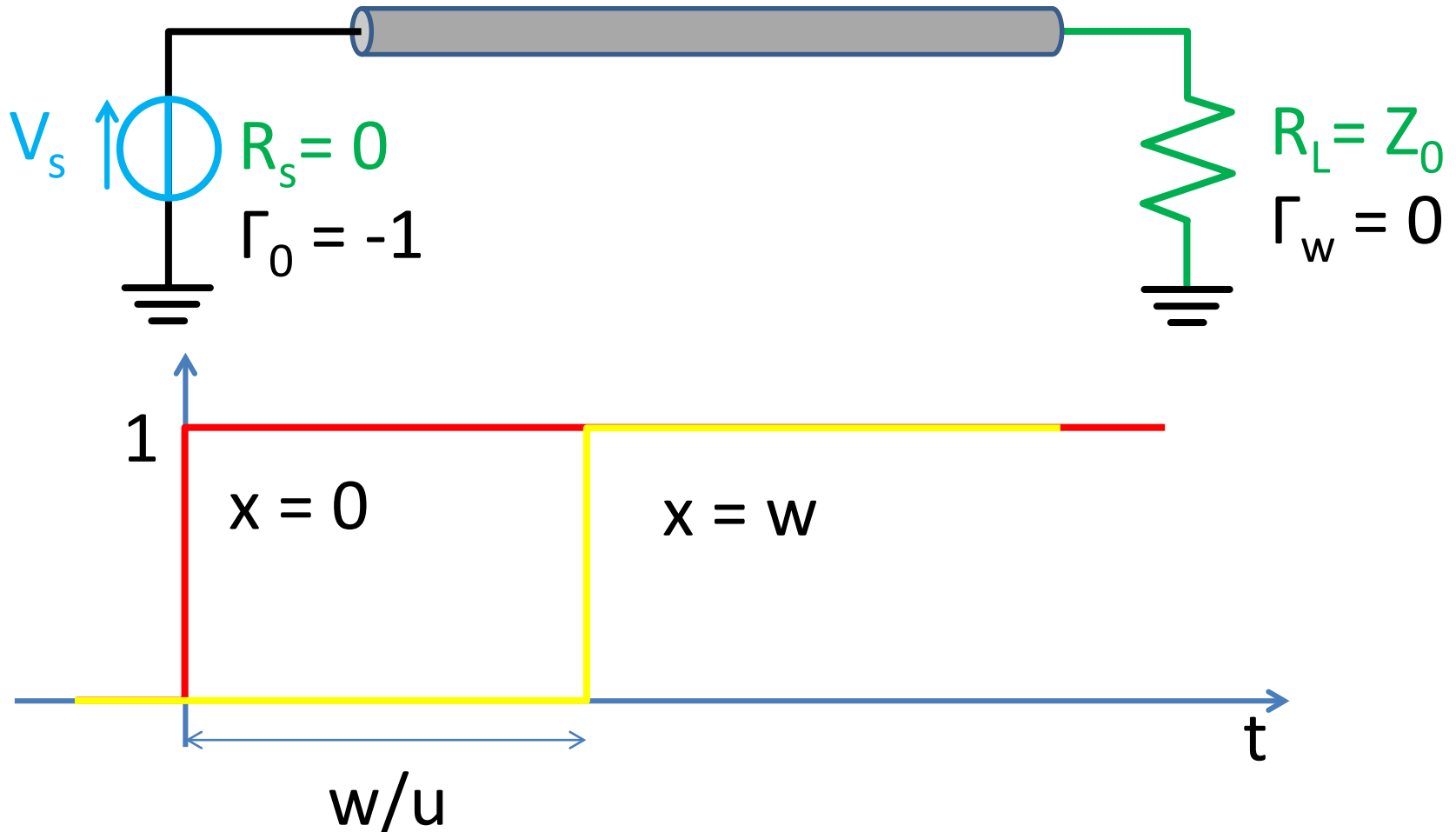


# Line matched at both sides

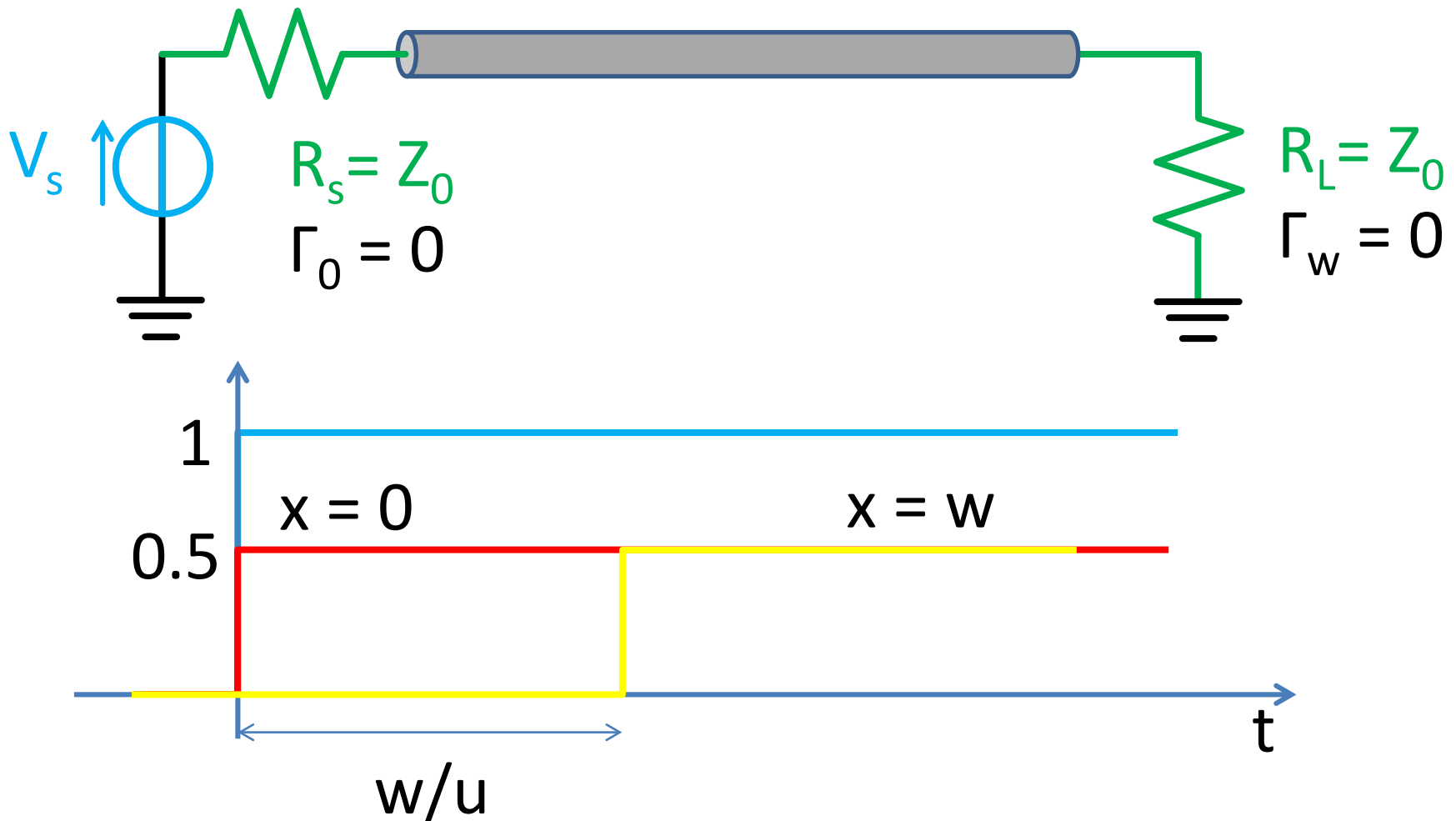

# Line open-circuited at load

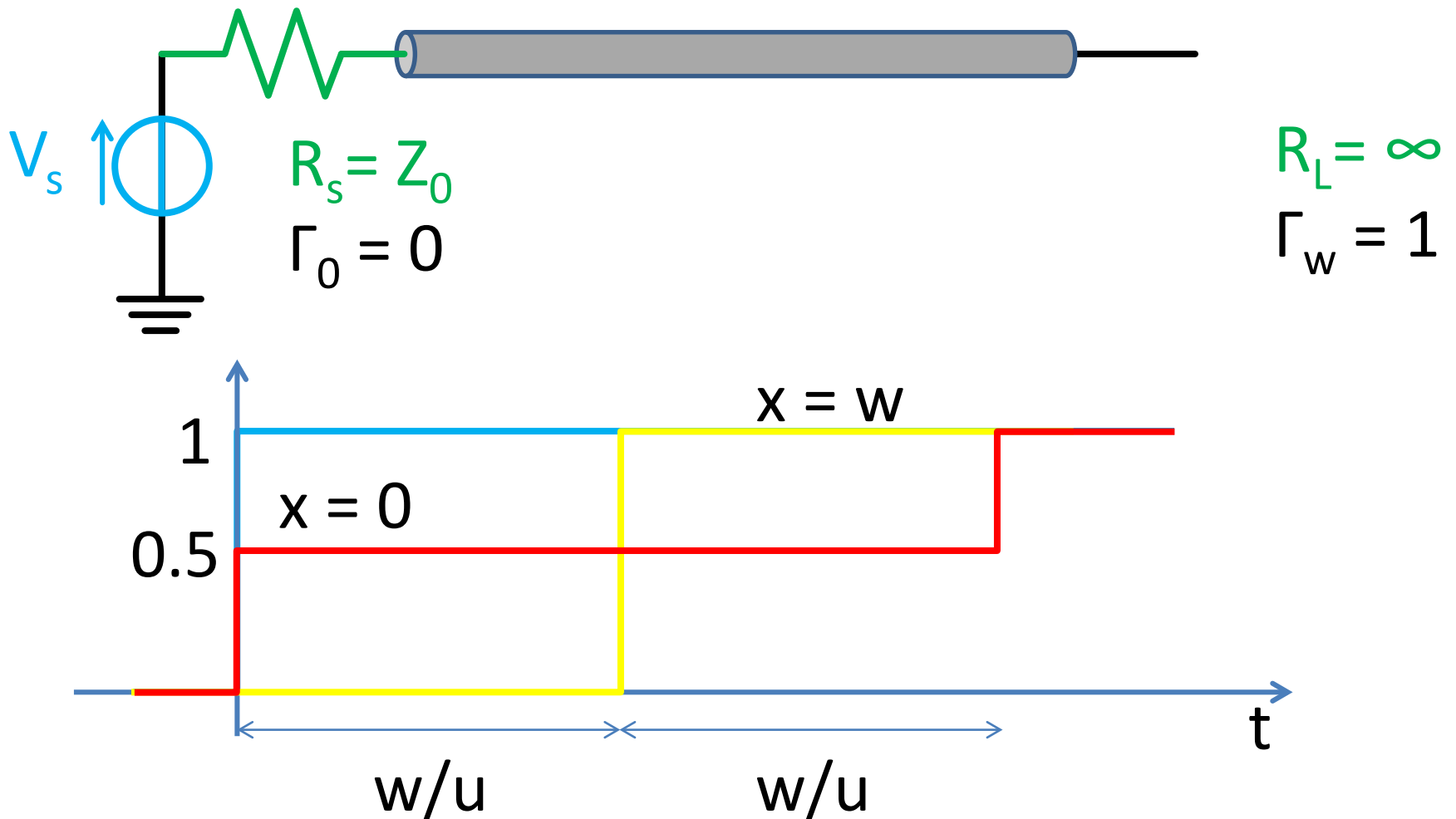


# Line short-circuited at load

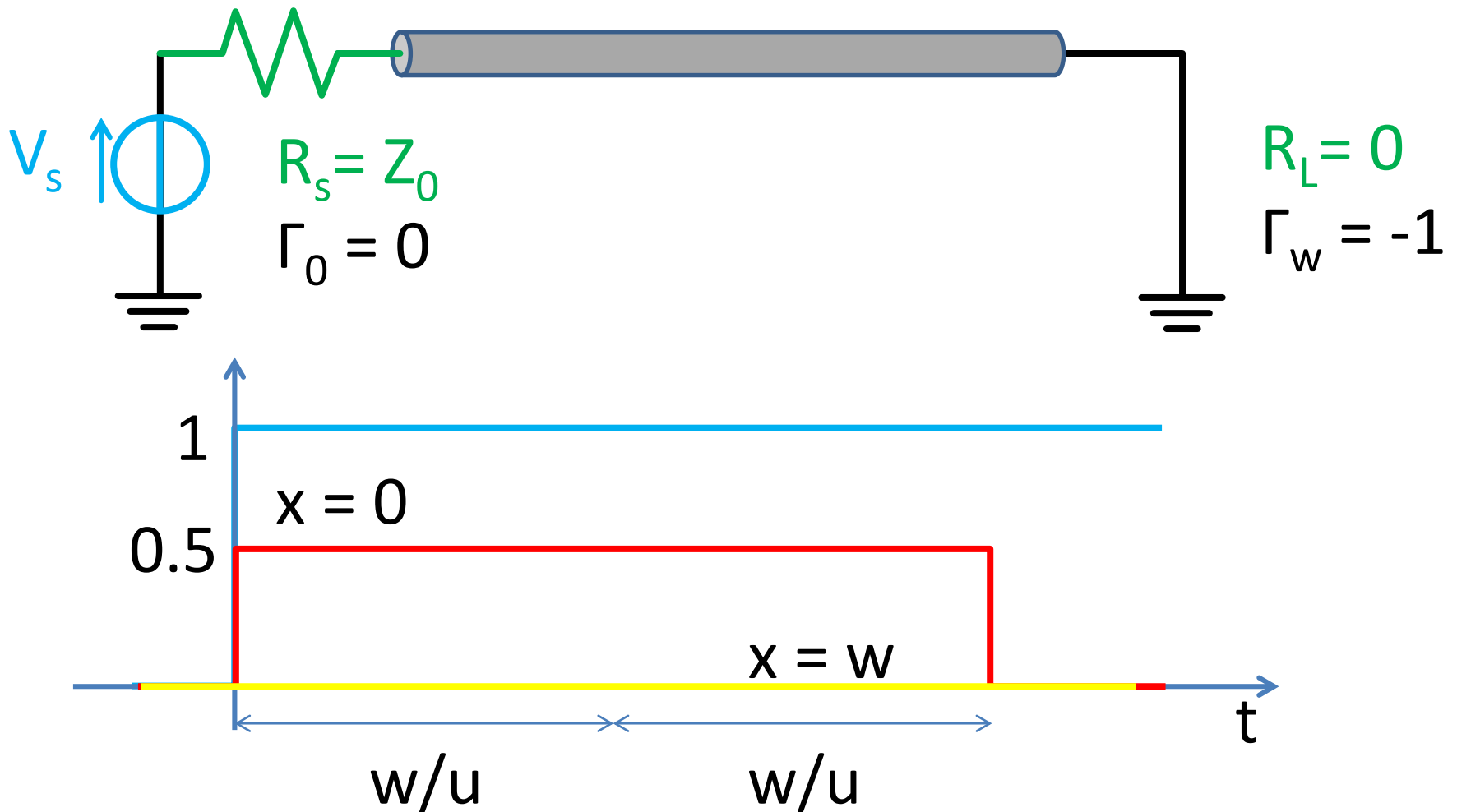


# General case

$$\frac{1 - \Gamma_0}{2} \times \left( \begin{array}{l} 1 \\ + \\ \Gamma_w(1 + \Gamma_0) \\ + \\ \Gamma_0 \Gamma_w^2(1 + \Gamma_0) \\ \vdots \end{array} \right. \begin{array}{l} \rightarrow 1 + \Gamma_w \\ \leftarrow + \\ \rightarrow \Gamma_w \Gamma_0(1 + \Gamma_w) \\ \leftarrow + \\ \rightarrow \vdots \end{array} \right.$$

# Examples (strong mismatch)

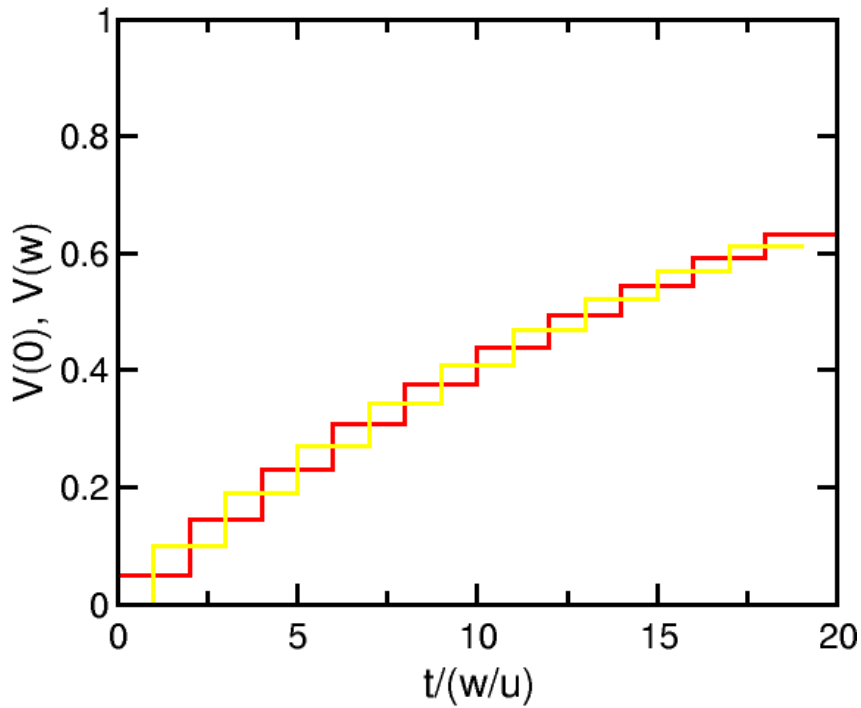

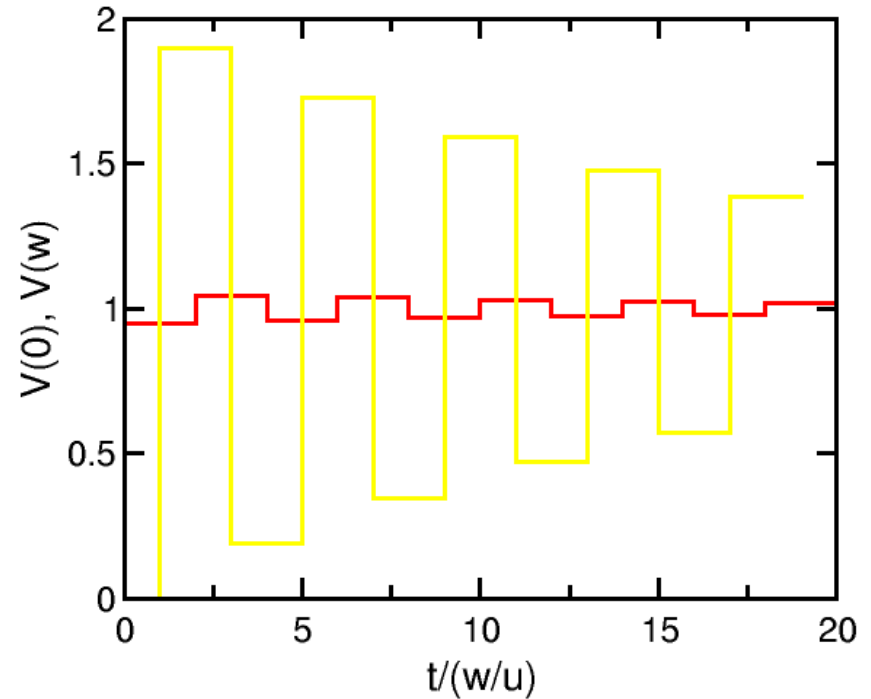
$$\Gamma_0 = 0.9, \Gamma_w = 1$$
$$R_s = 19 Z_0$$




$$\Gamma_0 = -0.9, \Gamma_w = 1$$
$$R_s \approx 0.05 Z_0$$

# Examples (almost matched)

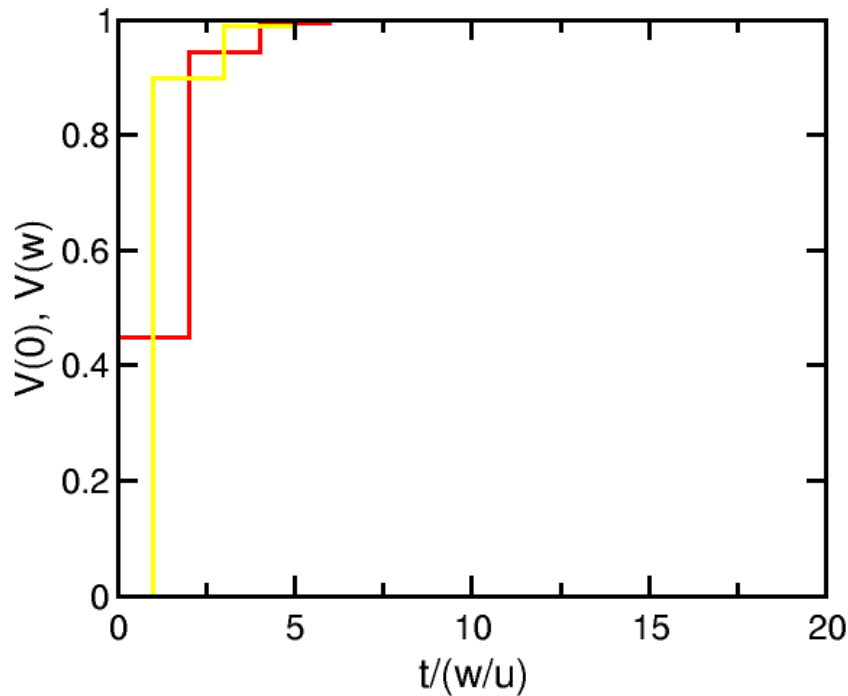
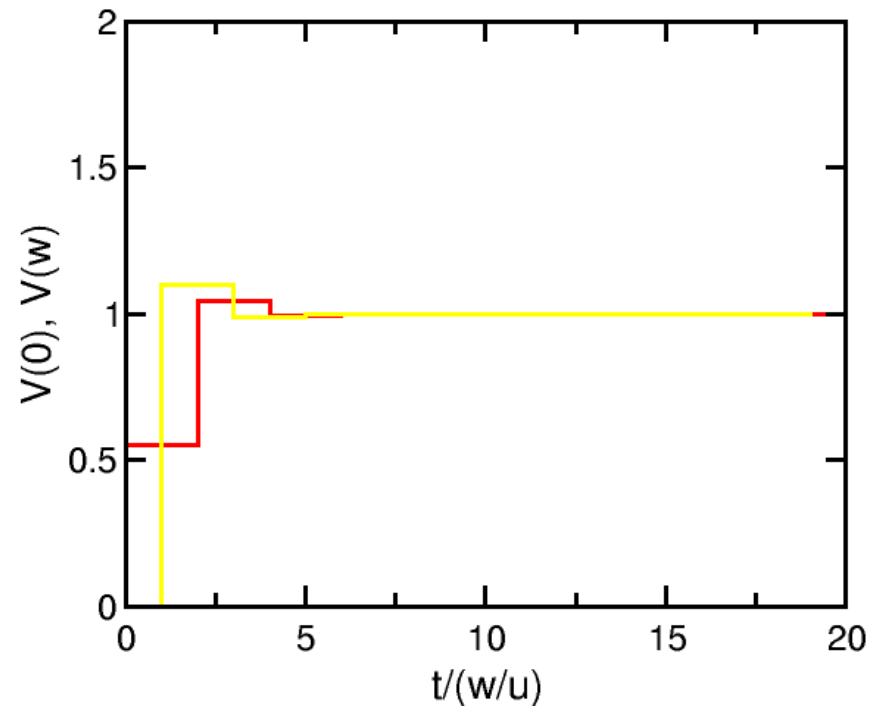
$$\Gamma_0 = 0.1, \Gamma_w = 1$$
$$R_s \approx 1.22 Z_0$$



$$\Gamma_0 = -0.1, \Gamma_w = 1$$
$$R_s \approx 0.82 Z_0$$