



Electronics – 96032



POLITECNICO DI MILANO



Lock-in Amplifiers (LIAs)

Alessandro Spinelli

Phone: (02 2399) 4001

alessandro.spinelli@polimi.it

spinelli.faculty.polimi.it




Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes



Problem: Square wave detection with LIA


5

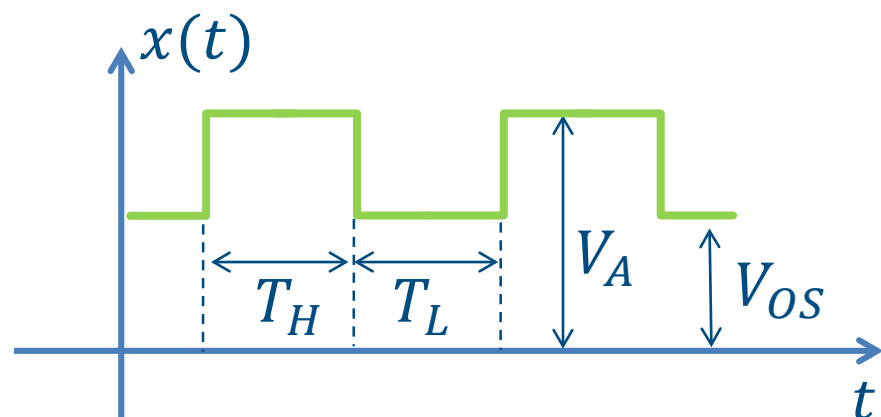

$$f_0 = \frac{1}{T_H + T_L}$$

WN PSD: $S_V = 50\text{nV}/\sqrt{\text{Hz}}$
Flicker noise (unknown)

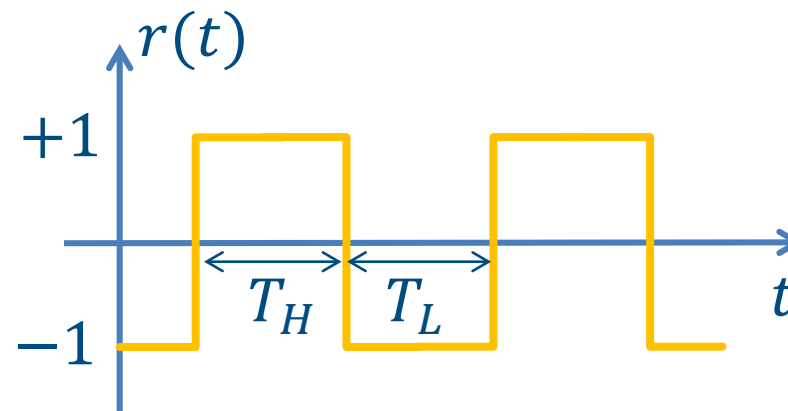
1. Use a LIA to get $S/N = 10$ using as a reference signal $r(t)$





LIA output: signal

6

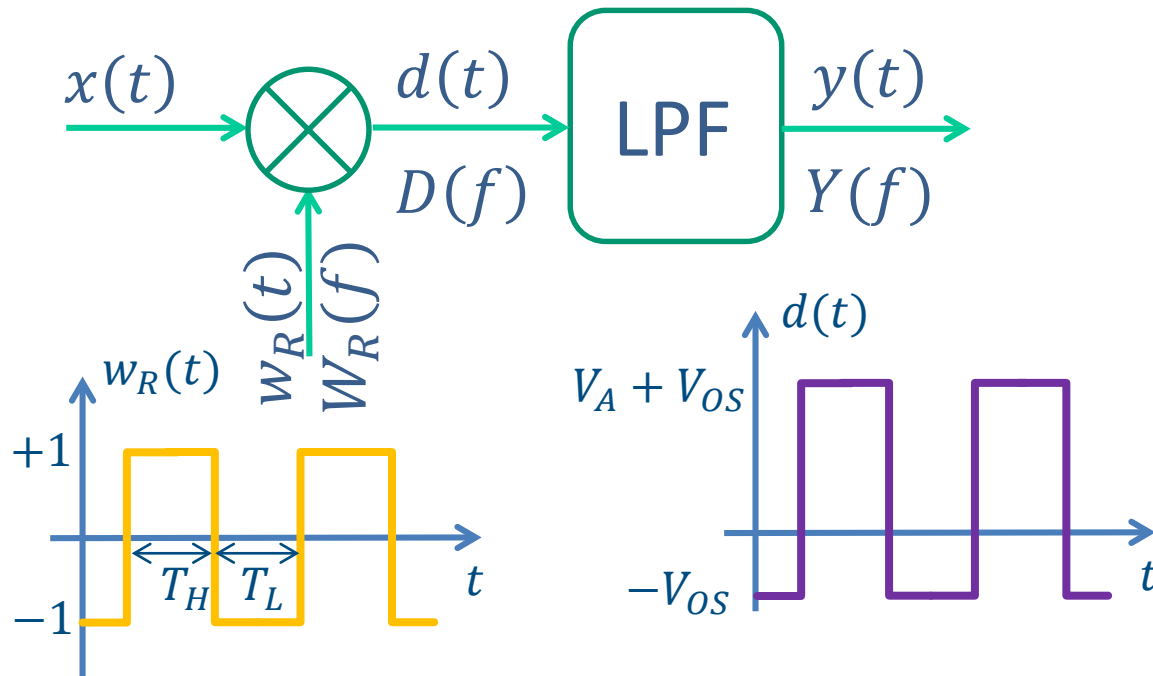

- $x(t)$ is already “modulated” (it is a square wave)
- It is easier to work in the time domain to avoid to deal with sinc (if LPF is a GI)


- $y(t)$ is the output of the LPF, i.e. the DC component of $d(t)$

$$y = \frac{V_A + V_{OS} + (-V_{OS})}{2} = \frac{V_A}{2}$$



LIA output: noise

7

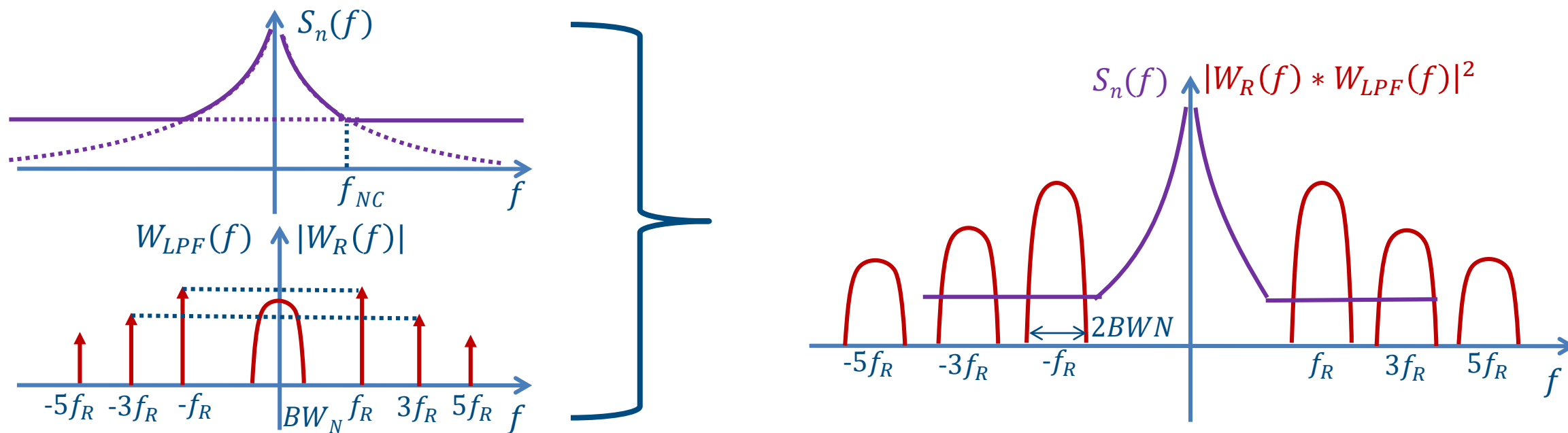

- This is easier in the frequency domain:

$$\overline{n_o^2} = \int S_n(f) |W_R * W_{LPF}|^2 df = 2 \sum_k \left(\frac{2}{\pi} \right)^2 \frac{1}{(2k+1)^2} S_n[(2k+1)f_R] \cdot 2BW_N$$



LIA output: S/N ratio

8

- Choosing $f_R > f_{NC}$ allows to neglect $1/f$ noise: $S_n[(2k + 1)f_R] \simeq \frac{S_n^u}{2}$

$$\overline{n_o^2} = 2 \left(\frac{2}{\pi} \right)^2 \cdot \frac{\pi^2}{8} \cdot \frac{S_n^u}{2} \cdot 2BW_N = S_n^u \cdot BW_N$$



- From S/N expression we derive the LPF bandwidth:

$$\left(\frac{S}{N} \right) = \frac{\frac{V_A}{2}}{\sqrt{S_n^u \cdot BW_{LPF}}} = 10 \rightarrow BW_N = 100\text{Hz}$$



Alternative solution: BPF + demodulation

9

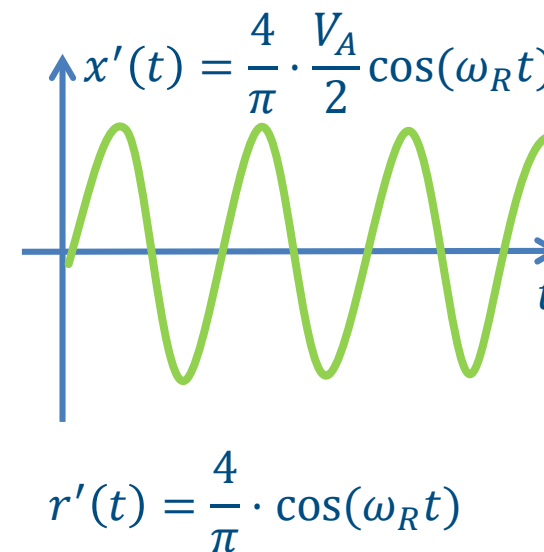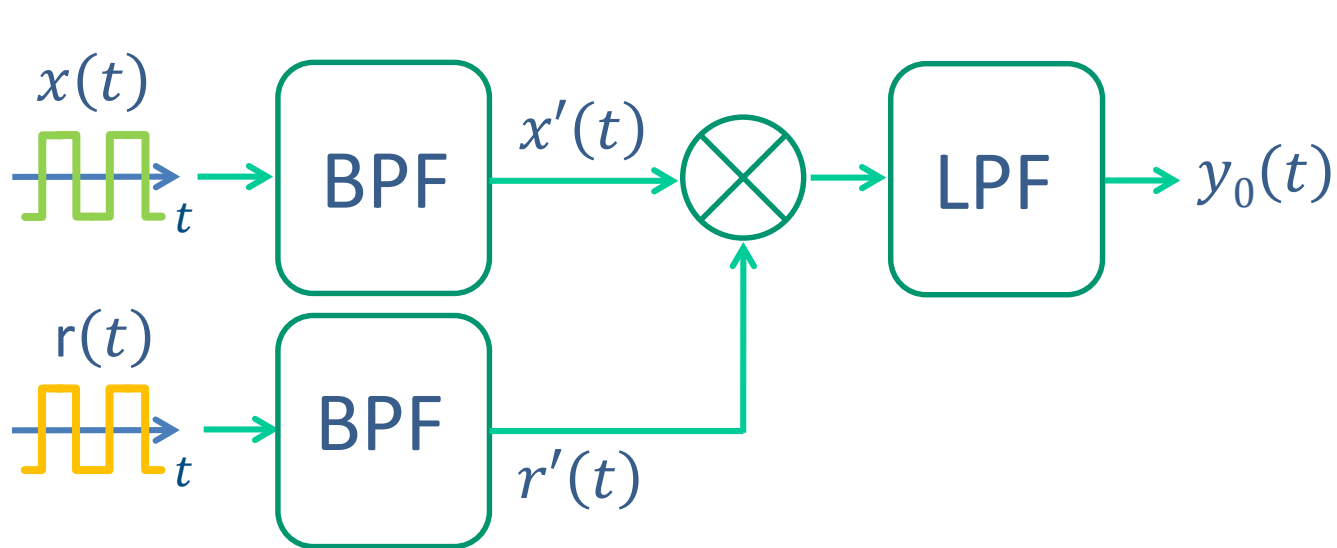


- With two BPFs (for signal and reference) demodulation is done with pure sine waves:

$$\frac{S}{N} = \frac{\left(\frac{4}{\pi}\right)^2 \cdot \frac{V_A}{4}}{\sqrt{\left(\frac{4}{\pi}\right)^2 S_n^u \cdot \frac{BW_{LPF}}{2}}} = 10 \rightarrow BW_{LPF} = 81\text{Hz} = \frac{100}{\pi^2/8} \text{Hz}$$




Problem: sin-square wave modem

10

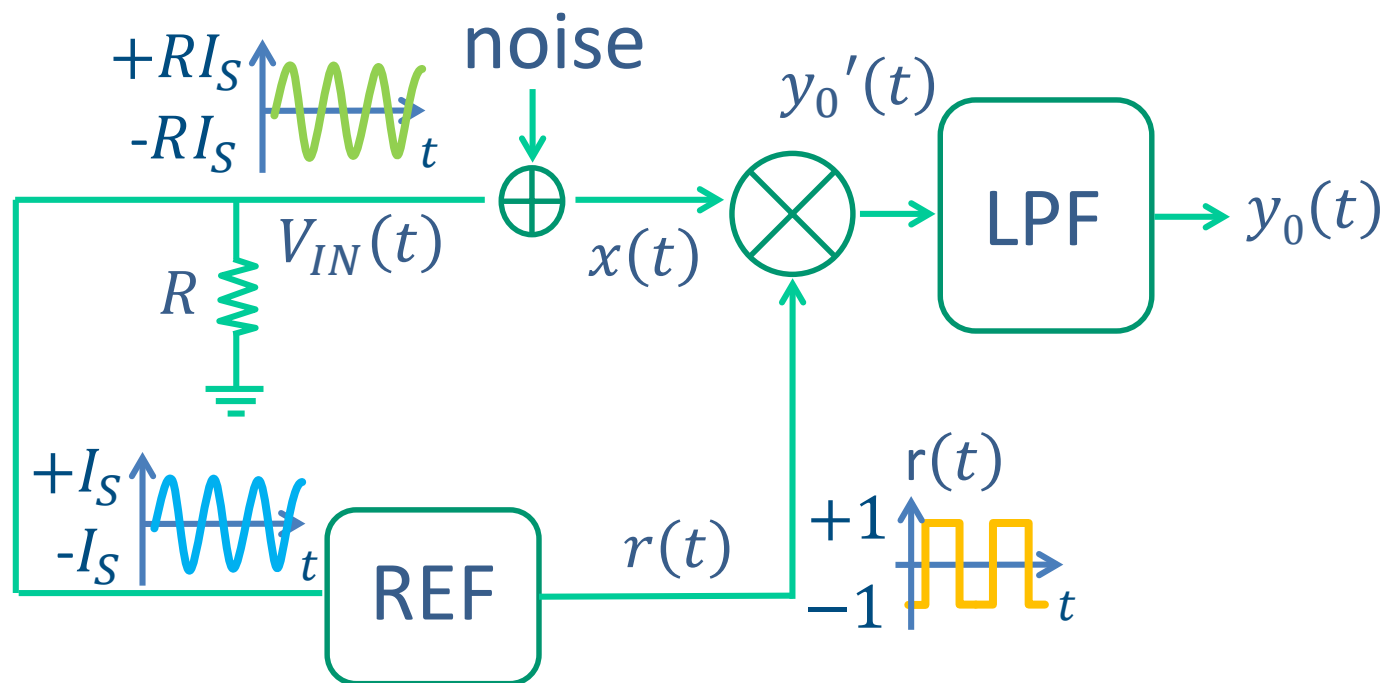


$$\begin{aligned} R &\simeq 1k\Omega \\ BW_R &= 5Hz \\ S_n &= \frac{k_n}{f}, k_n = 6 \cdot 10^{-8} V^2 \\ &\text{(unilateral)} \\ I_S &= 10\mu A \end{aligned}$$

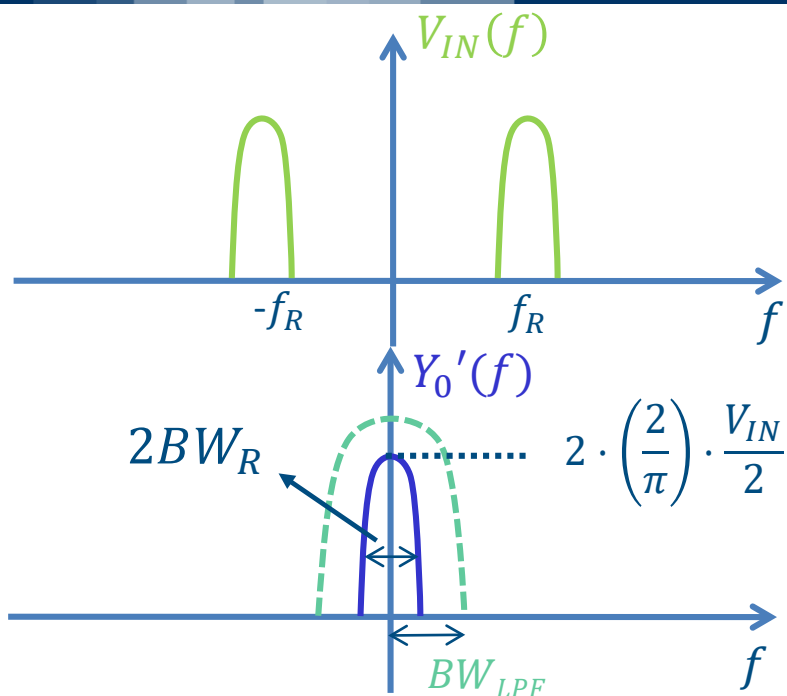1. Size f_R and BW_{LPF} to have $S/N=10$ on the measurement of R
2. Suggest a way to measure a complex impedance (such as $Z = R + 1/SC$)


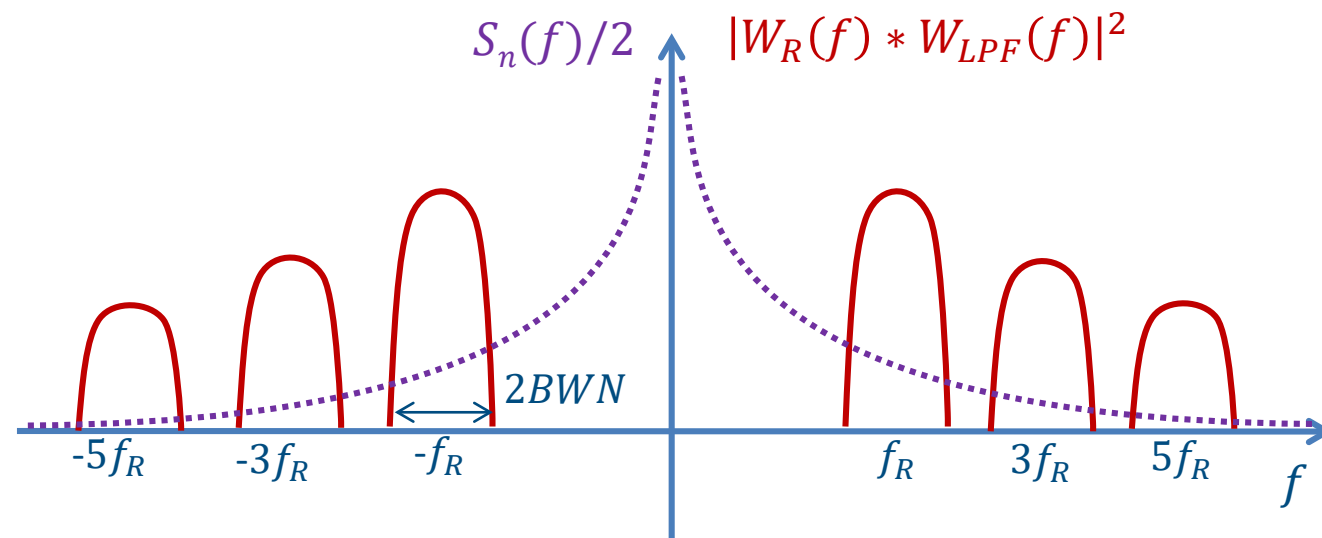
$$\begin{aligned} 2BW_{LPF} &\gg 2BW_R \\ \rightarrow BW_{LPF} &= 10BW_R \\ &= 50\text{Hz} \end{aligned}$$



$$\overline{n_o^2} = \sum_k \left(\frac{2}{\pi}\right)^2 \frac{1}{(2k+1)^2} S_n[(2k+1)f_R] 2BW_N$$

unilateral!



- The difference vs. previous case is that we have no white noise.
We can approximate $S_n[(2k + 1)f_R] = S_n[f_R]$ (worst-case) and also $BW_N = BW_{LPF}$

$$\frac{S}{N} = \frac{\frac{2}{\pi} I_S R}{\sqrt{\left(\frac{2}{\pi}\right)^2 \cdot 2BW_{LPF} \cdot S_n(f_R) \cdot \frac{\pi^2}{8}}} = 10 \rightarrow f_R = \left(\frac{100\pi^2}{8}\right) \text{ kHz}$$



Complex impedance measurement

13

- Measure separately real and imaginary part of Z (phase shift):

$$V_{IN} = I_S \left(R + \frac{1}{sC} \right) = I_S \cos(\omega_R t) + \frac{I_S}{\omega_R C} \cos(\omega_R t + \frac{\pi}{2})$$

