

Electronics – 96032

 POLITECNICO DI MILANO



Closed-loop gain calculation

Alessandro Spinelli

Phone: (02 2399) 4001

alessandro.spinelli@polimi.it

spinelli.faculty.polimi.it




Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes



- Integrator stage
- Differentiator stage
- Phase shifter




Ideal integrator

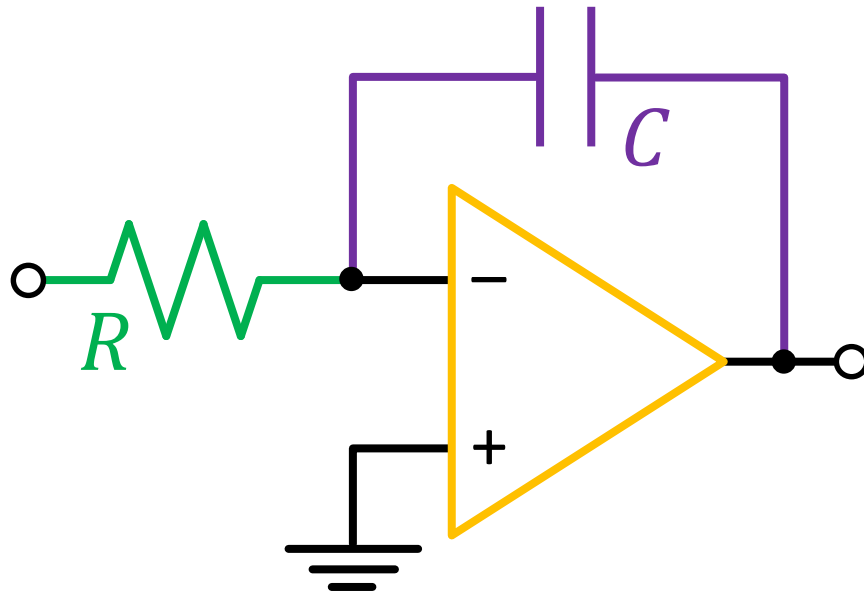


$$\frac{V_o}{V_i} = T(s) = -\frac{1}{sCR}$$
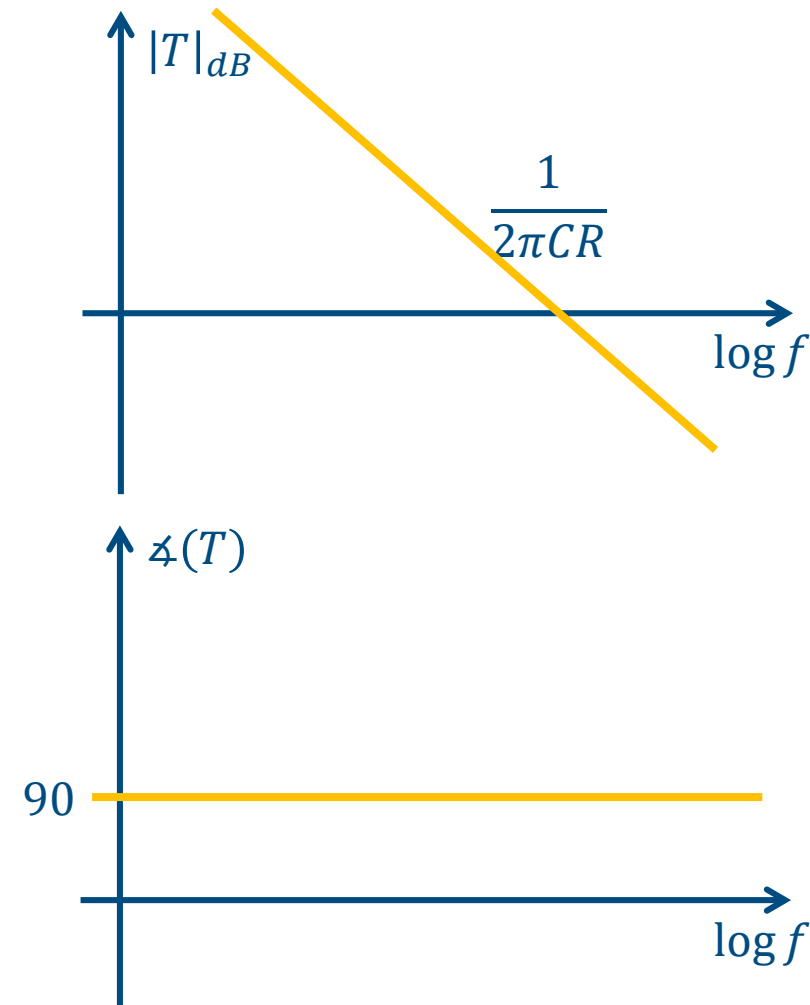
$$T(j\omega) = \frac{j}{\omega CR} = \frac{j}{2\pi f CR}$$





Open-loop gain

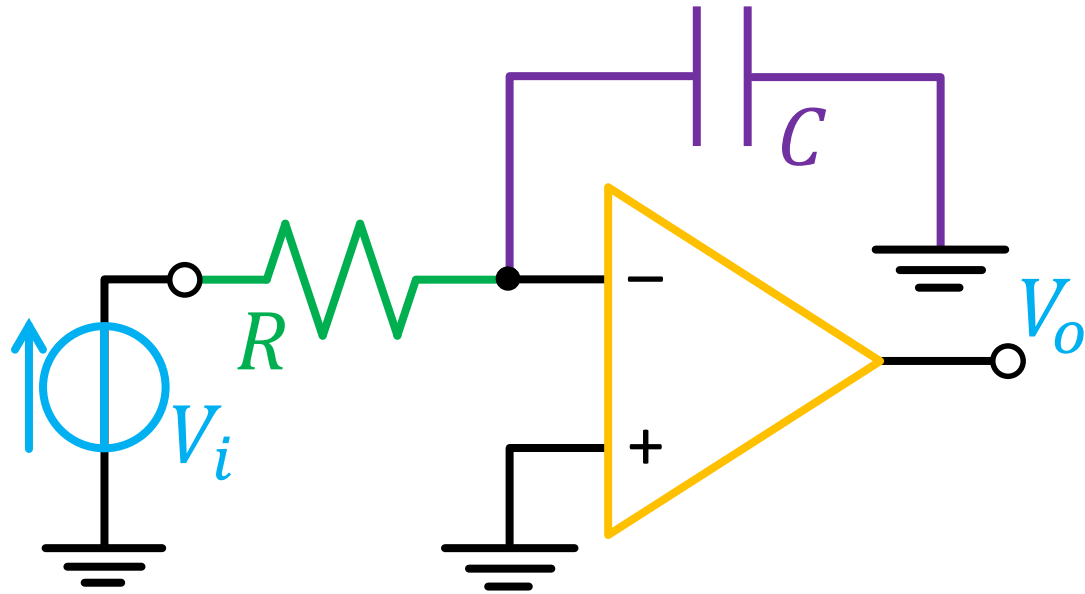


$$G_{id} = \frac{1}{sCR}$$

$$G_{OL} = -\frac{A(s)}{1 + sCR} = -\frac{A_0}{1 + s\tau} \frac{1}{1 + sCR}$$



Closed-loop gain

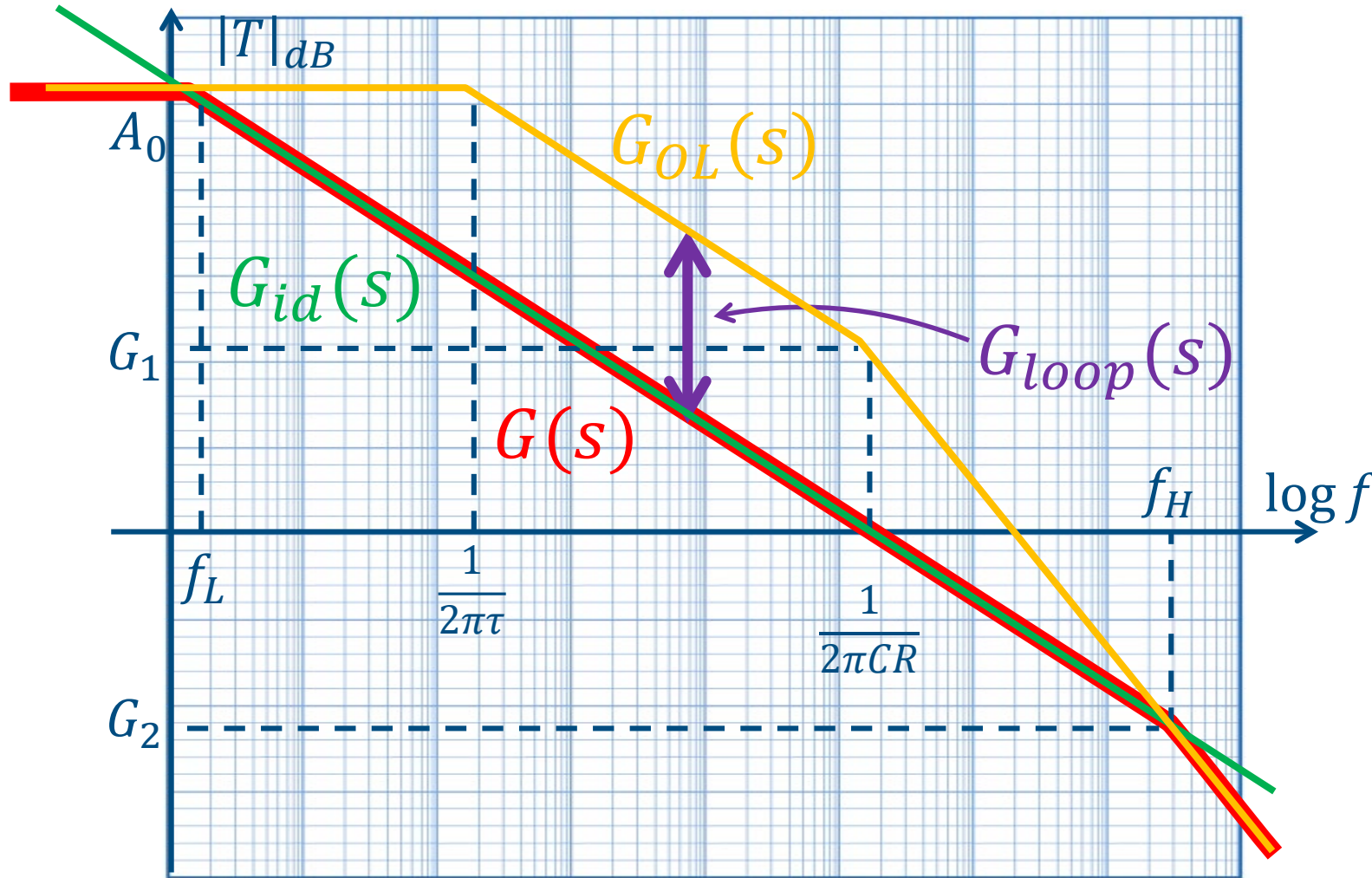

The integration frequency range is $f_L - f_H$



Bode diagram calculations

- Diagram with slope = -1 :

$$|G| = \frac{K}{f} \Rightarrow |G|f = \text{constant}$$

- Diagram with slope = -2 :

$$|G| = \frac{K}{f^2} \Rightarrow |G|f^2 = \text{constant}$$

- Diagram with slope = $+1$:

$$|G| = Kf \Rightarrow \frac{|G|}{f} = \text{constant}$$



- f_L :

$$|G_{id}| = A_0 \Rightarrow \frac{1}{\omega_L CR} = A_0 \Rightarrow f_L = \frac{1}{2\pi CRA_0}$$

- f_H :

$$\text{slope of } -1 \text{ in } G_{OL} \Rightarrow \frac{A_0}{2\pi\tau} = \frac{G_1}{2\pi CR} \Rightarrow G_1 = A_0 \frac{CR}{\tau}$$

$$\left. \begin{array}{l} \text{slope of } -1 \text{ in } G_{id} \Rightarrow A_0 f_L = G_2 f_H \\ \text{slope of } -2 \text{ in } G_{OL} \Rightarrow G_1 \left(\frac{1}{2\pi CR} \right)^2 = G_2 f_H^2 \end{array} \right\} \Rightarrow f_H = \frac{A_0}{2\pi\tau}$$



$$G_{OL} = \frac{A_0}{1 + s\tau} \frac{1}{1 + sCR} \approx \frac{A_0}{s^2\tau CR} \quad (\text{beyond the } 2^{\text{nd}} \text{ pole})$$

$$G_{OL} = G_{id} \Rightarrow \frac{A_0}{s^2\tau CR} = \frac{1}{sCR} \Rightarrow f_H = \frac{A_0}{2\pi\tau}$$

Or via G_{loop} :


$$G_{loop} = -A(s) \frac{R}{R + \frac{1}{sC}} = -A(s) \frac{sCR}{1 + sCR} \left(= -\frac{G_{OL}}{G_{id}} \right)$$


$$|G_{loop}| = 1 \Rightarrow f_L, f_H$$



Bias currents representation
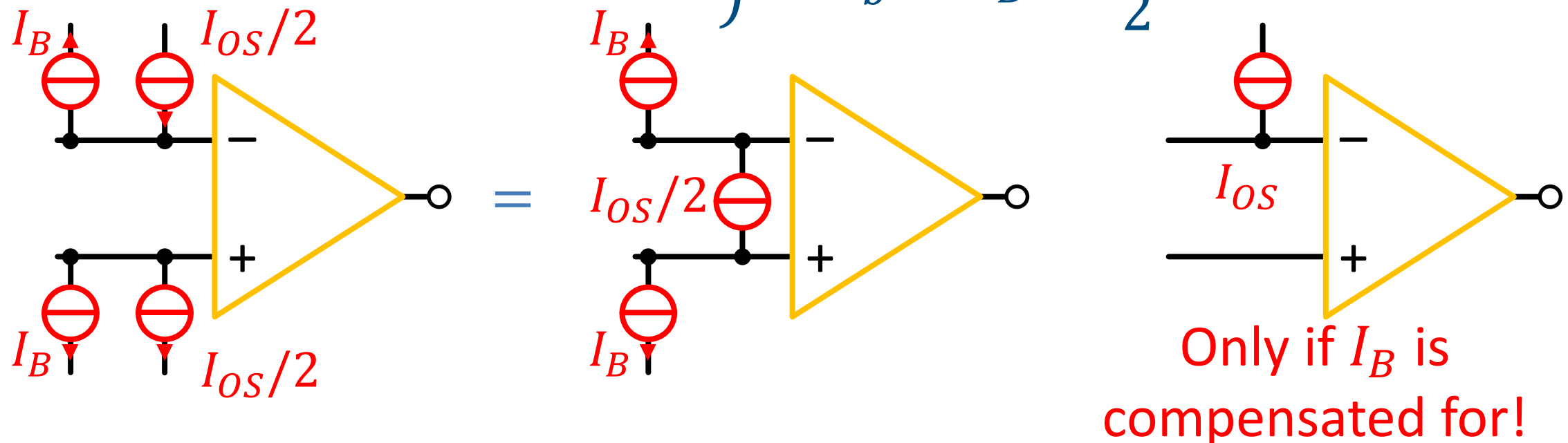
$$\left. \begin{aligned} I_B &= \frac{I_b^+ + I_b^-}{2} \\ I_{OS} &= I_b^+ - I_b^- \end{aligned} \right\} \Rightarrow \begin{aligned} I_b^+ &= I_B + \frac{I_{OS}}{2} \\ I_b^- &= I_B - \frac{I_{OS}}{2} \end{aligned}$$



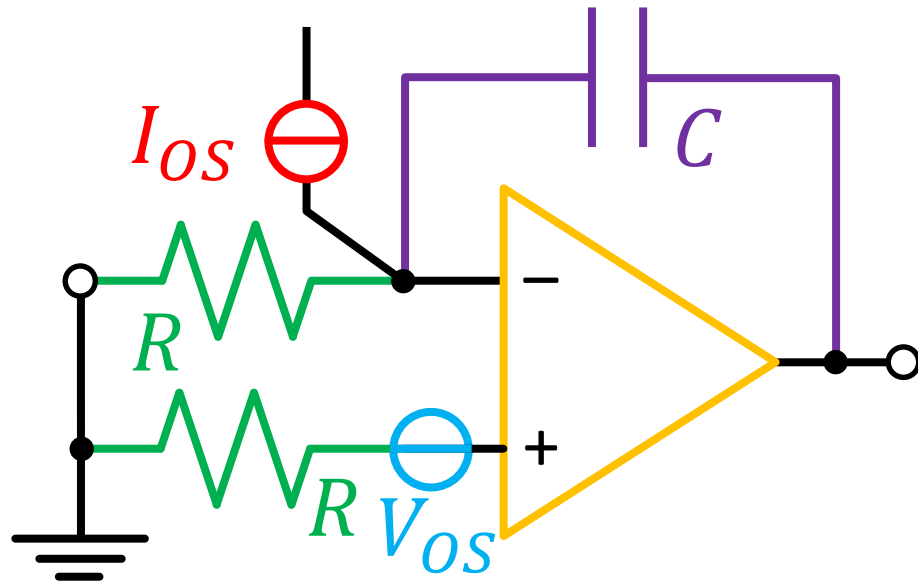


$$V_o = \frac{I_{OS}}{sC} + V_{OS} \left(1 + \frac{1}{sCR} \right)$$

$$v_o(t) = v_{OS} + \frac{1}{C} \int_0^t \left(i_{OS} + \frac{v_{OS}}{R} \right) dt$$


- Nulling resistor can be trimmed for better offset
- Slow drift of the offset will eventually cause saturation of the output \Rightarrow periodic adjustment is needed



Practical integrator

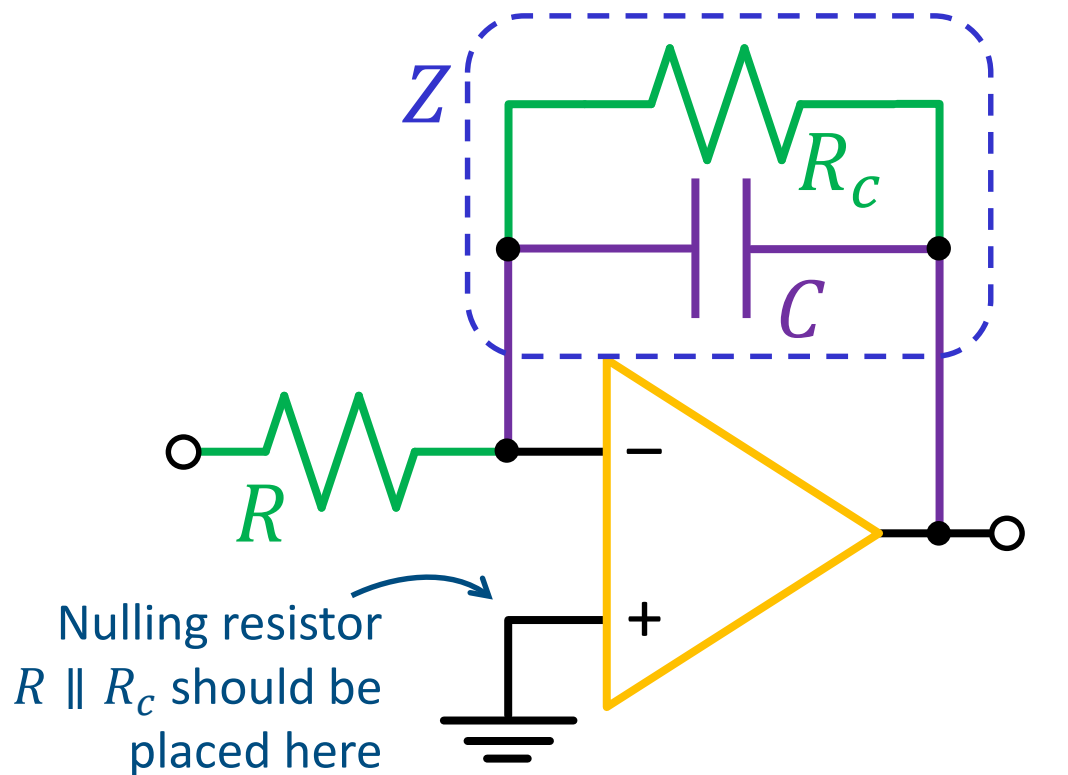
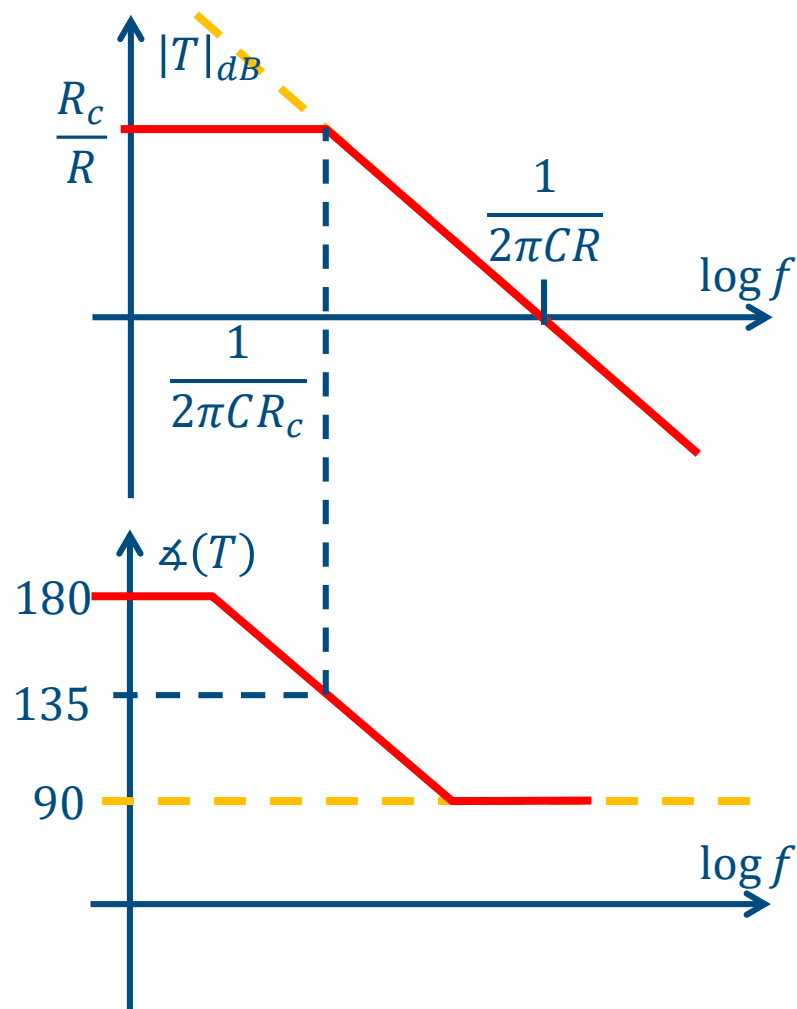
$$\frac{V_o}{V_i} = -\frac{Z}{R} = -\frac{R_c}{R} \frac{1}{1 + sCR_c}$$






Step response

$$\frac{v_o(t)}{V_i} = -\frac{R_c}{R} \left(1 - e^{-\frac{t}{CR_c}} \right)$$
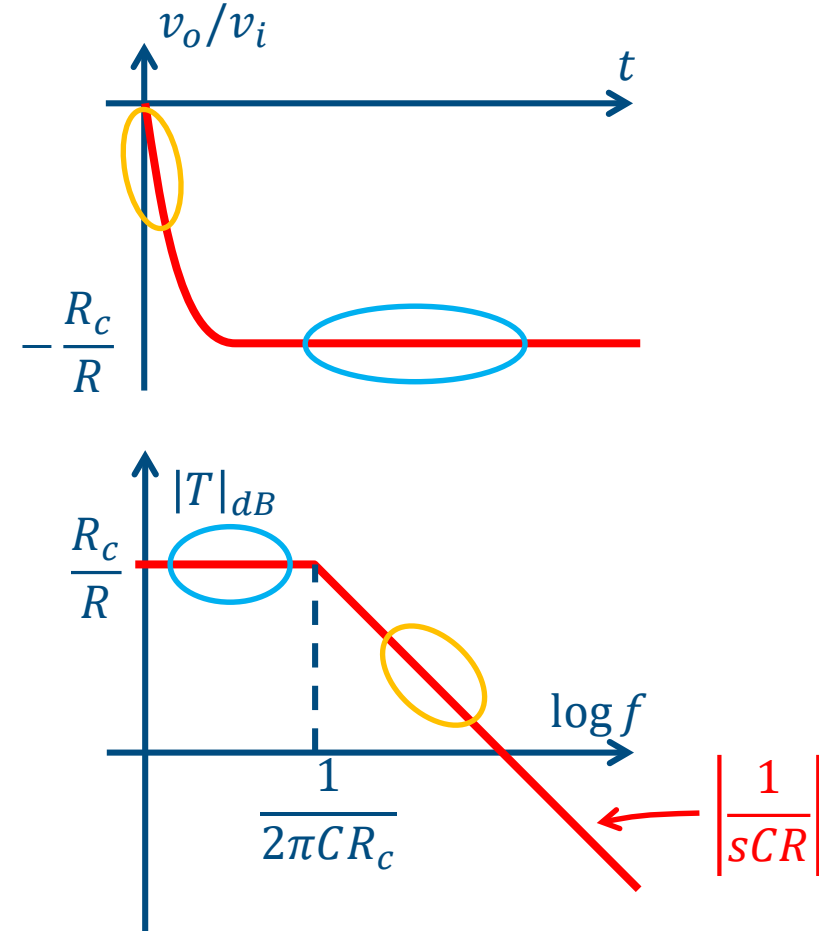
$$\approx \begin{cases} -\frac{R_c}{R} & t \gg CR_c \\ -\frac{R_c}{R} \frac{t}{CR_c} = \frac{-t}{CR} & t \ll CR_c \end{cases}$$







- Integrator stage
- Differentiator stage
- Phase shifter



Ideal differentiator

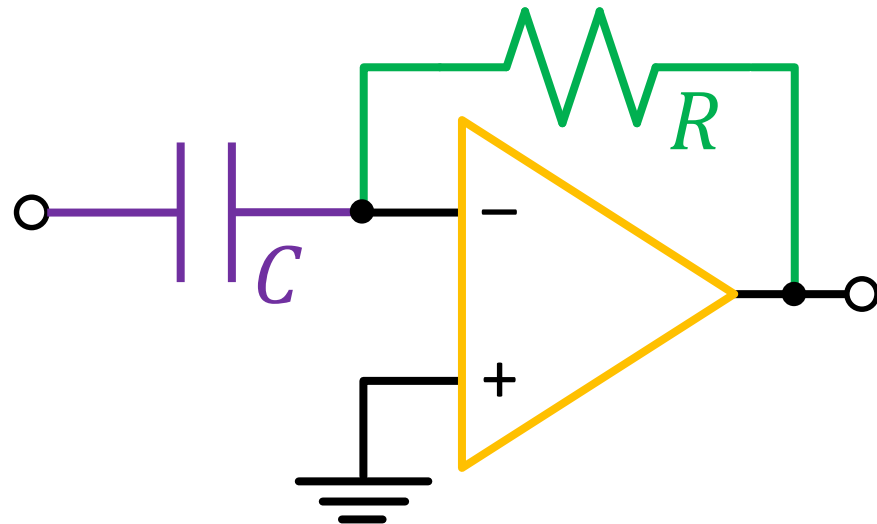

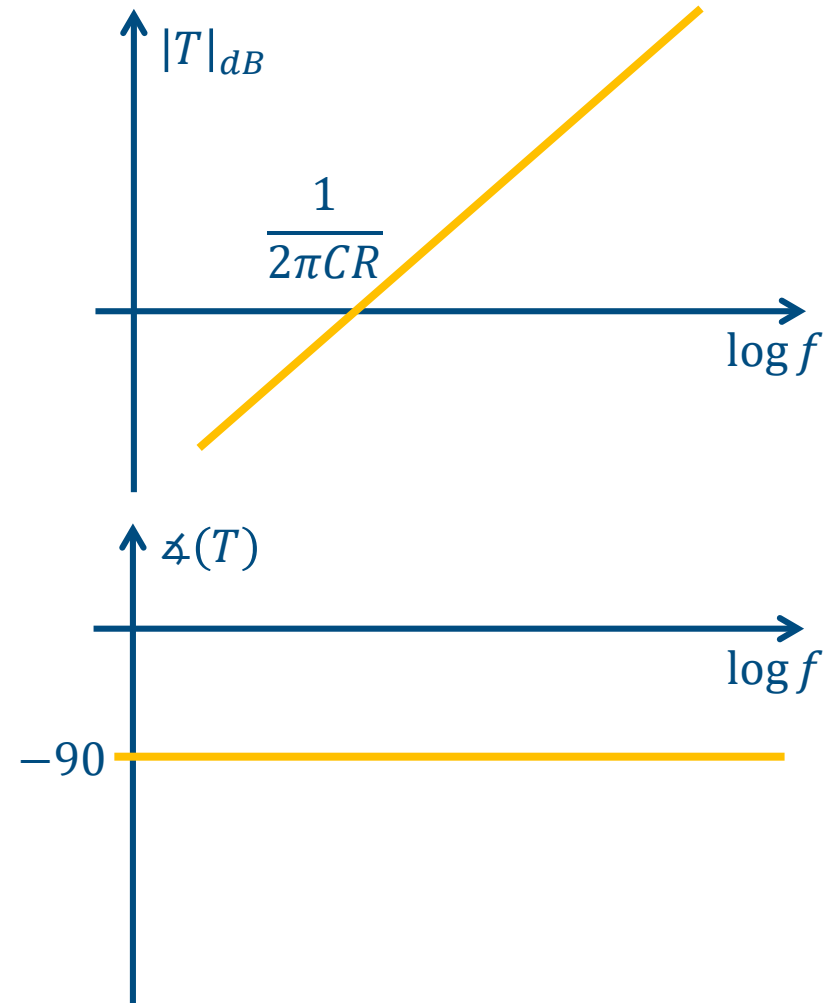
$$\frac{V_o}{V_i} = T(s) = -sCR$$
$$T(j\omega) = -j\omega CR$$






Practical differentiator

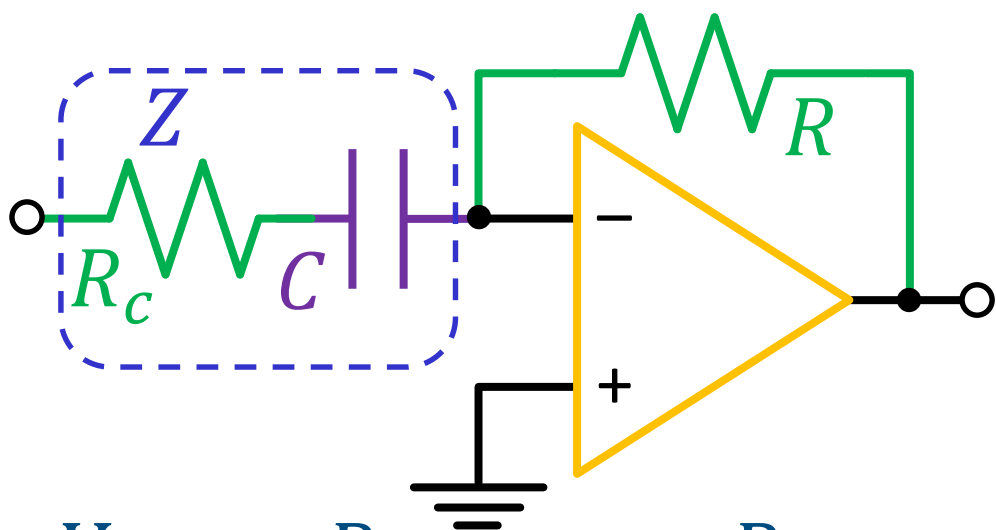
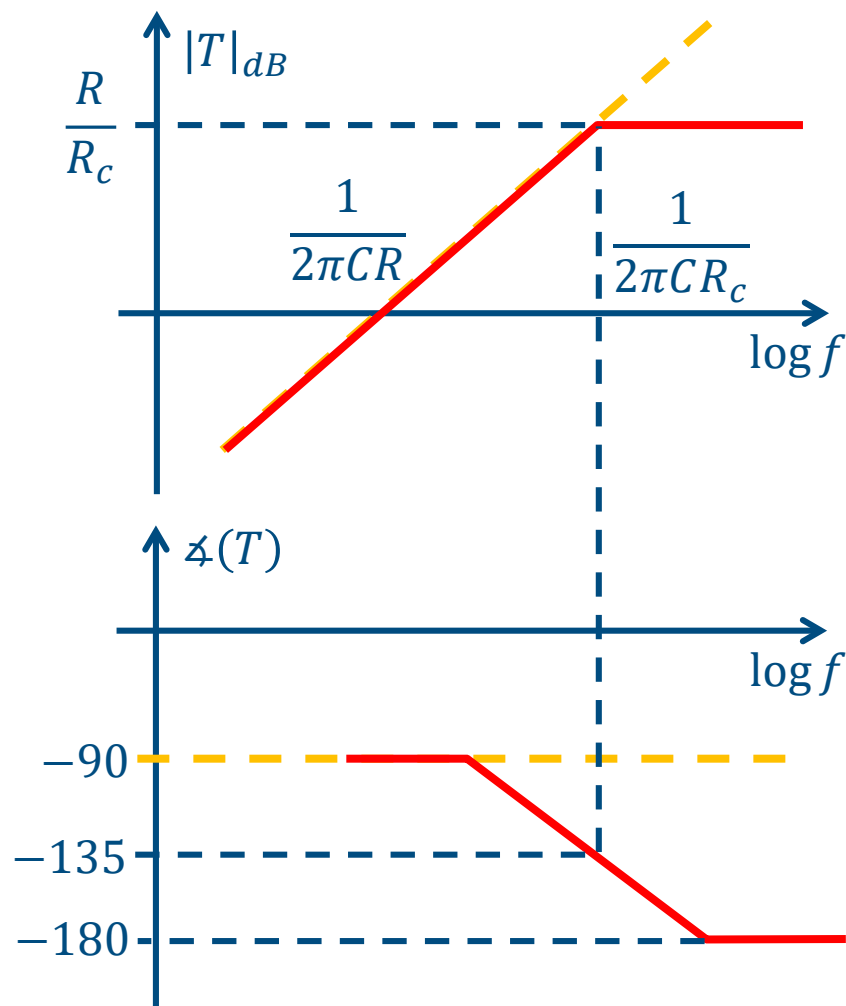
$$\begin{aligned} \frac{V_o}{V_i} &= -\frac{R}{Z} = -\frac{R}{R_c + 1/sC} \\ &= -\frac{sCR}{1 + sCR_c} \end{aligned}$$






Step response


$$\frac{v_o(t)}{V_i} = -\frac{R}{R_c} e^{-\frac{t}{CR_c}}$$
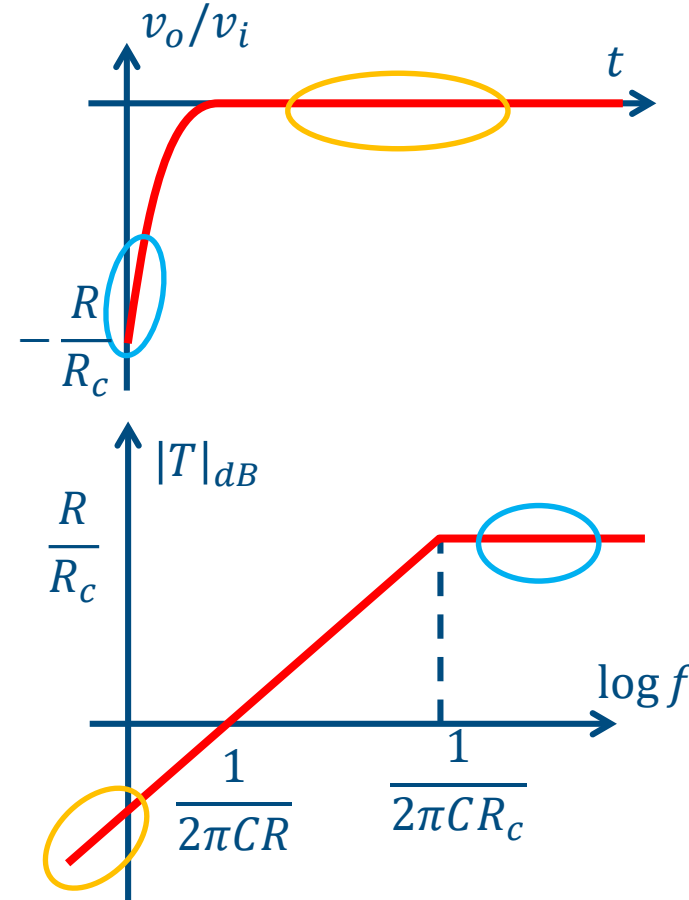
$$\approx \begin{cases} -\frac{R}{R_c} & t \ll CR_c \\ \approx 0 & t \gg CR_c \end{cases}$$





Open-loop gain

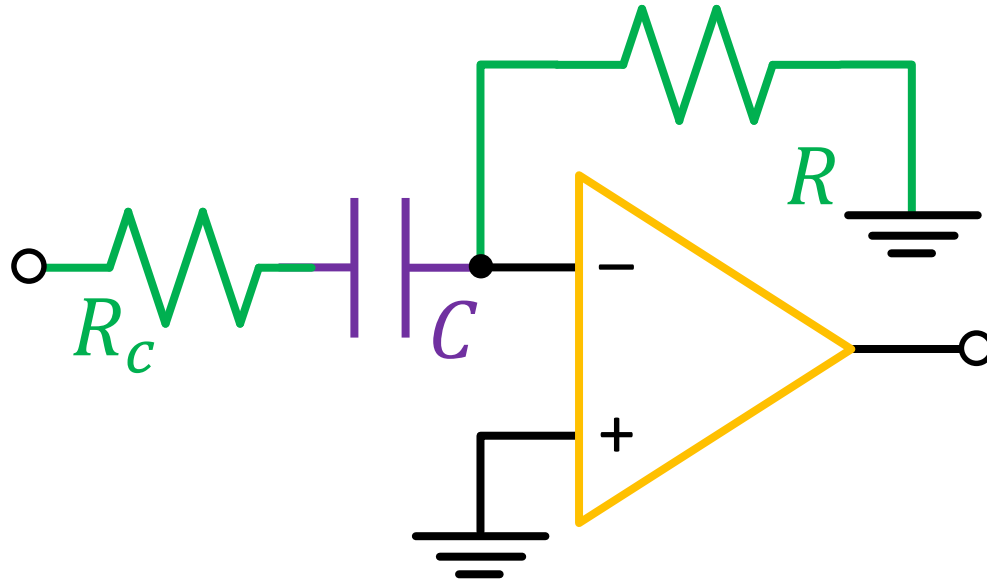

$$C = 100 \text{ nF}$$

$$R = 16 \text{ k}\Omega$$

$$R_c = 450 \Omega$$

$$\tau = 22.5 \text{ ms}$$


$$A_0 = 10^7$$

$$G_{OL} = -A(s) \frac{R}{R + Z} = -\frac{A_0}{1 + s\tau} \frac{sCR}{1 + sC(R + R_c)}$$

$$G_{id} = -\frac{sCR}{1 + sCR_c}$$



Closed-loop gain

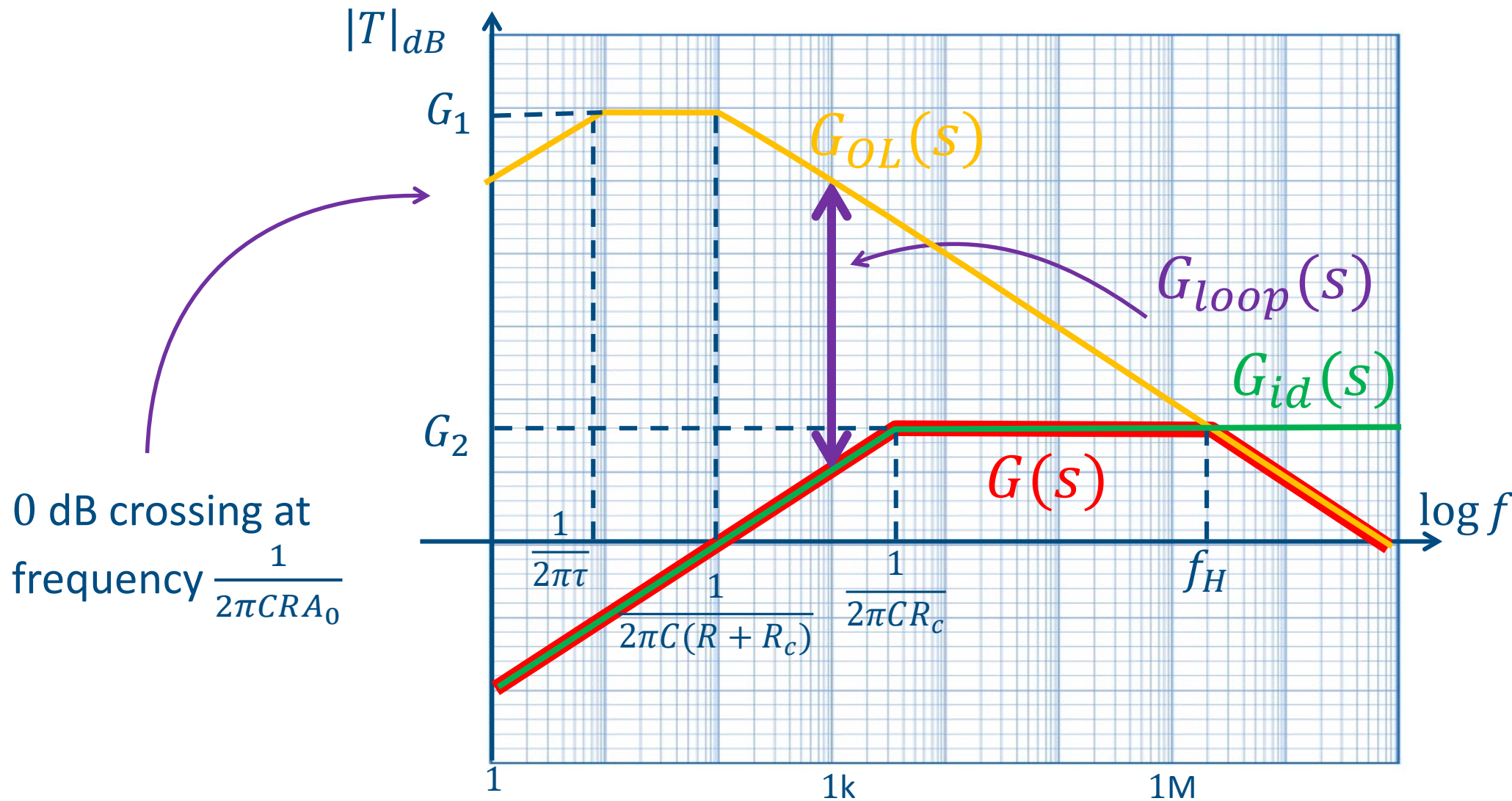



- Poles:

$$\frac{1}{2\pi CR_c} = 3.54 \text{ kHz}; \quad \frac{1}{2\pi C(R + R_c)} = 97 \text{ Hz}; \quad \frac{1}{2\pi\tau} \approx 7 \text{ Hz}$$

- Gains:

$$G_2 = \frac{R}{R_c} = 35.5 = 31 \text{ dB}$$

$$2\pi\tau G_1 = 2\pi CRA_0 \Rightarrow G_1 = \frac{A_0 CR}{\tau} = 7.04 \cdot 10^5 = 117 \text{ dB}$$

- BW:

$$\frac{1}{2\pi C(R + R_c)} G_1 = f_H G_2 \Rightarrow f_H = 97 \frac{G_1}{G_2} = 1.9 \text{ MHz}$$



- Beyond the 2nd pole, G_{OL} can be approximated as (we drop the sign)


$$G_{OL} \approx \frac{A_0}{s\tau} \frac{R}{R + R_c}$$

- Then:

$$G_{OL}(s) = G_{id} = \frac{R}{R_c} \Rightarrow s = \frac{A_0}{\tau} \frac{R_c}{R + R_c} \Rightarrow f_H = \frac{A_0}{2\pi\tau} \frac{R_c}{R + R_c} = 1.9 \text{ MHz}$$



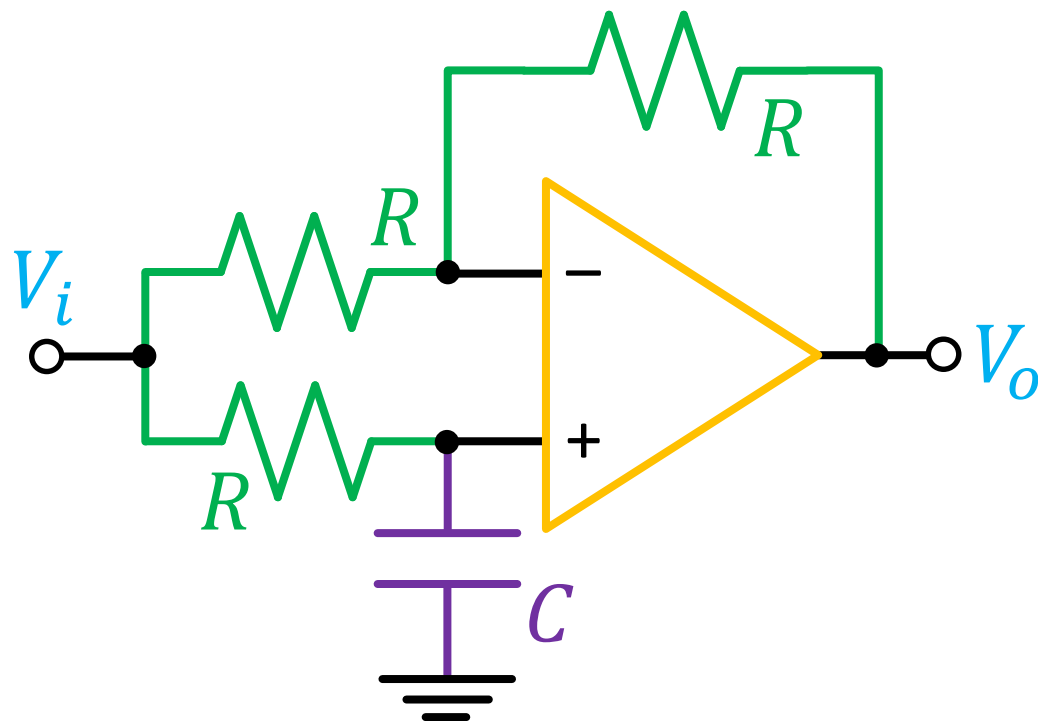- Integrator stage
- Differentiator stage
- Phase shifter



$$C = 10 \text{ nF}$$

$$R = 2 \text{ k}\Omega$$

$$\tau = 16 \text{ ms}$$


$$A_0 = 10^6$$

$$V_0 = -V_i + 2 \frac{V_i}{1 + sCR} = V_i \frac{1 - sCR}{1 + sCR} \Rightarrow G_{id} = \frac{1 - sCR}{1 + sCR}$$

Ideal gain

$$|G_{id}| = \left| \frac{1 - j\omega CR}{1 + j\omega CR} \right| = 1$$
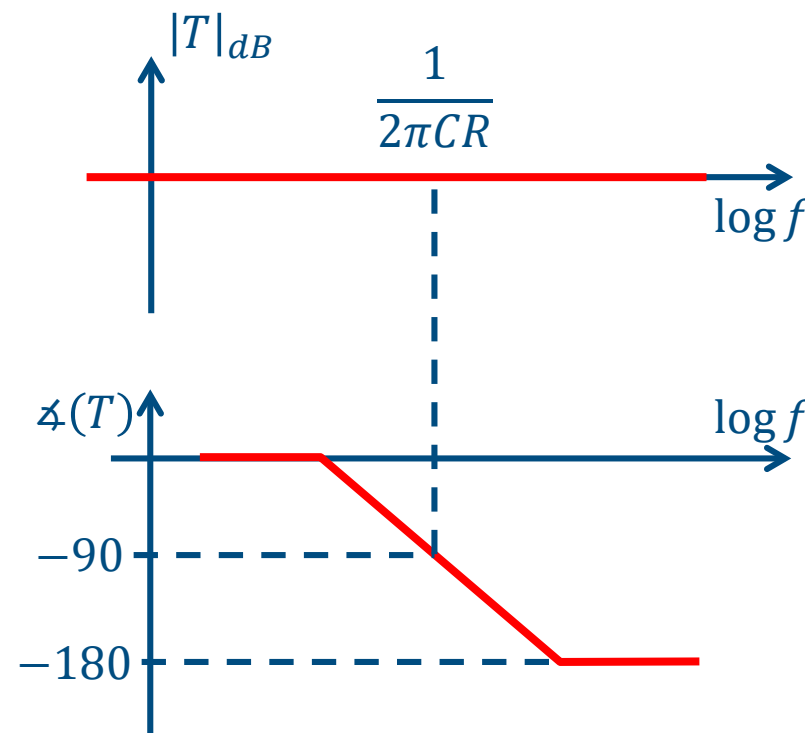
$$\begin{aligned} \angle(G_{id}) &= \\ \arctan(-\omega CR) - \arctan(\omega CR) &= \\ = -2 \arctan(\omega CR) \end{aligned}$$



Step response

$$V_o(s) = \frac{1 - sCR}{1 + sCR} \frac{V_i}{s} = V_i \left(\frac{1}{s} - \frac{2CR}{1 + sCR} \right)$$


$$v_o(t) = V_i(1 - 2e^{-t/CR})$$

Or, alternatively:


$$v_o(0) = \lim_{s \rightarrow \infty} sV_o(s) = -V_i$$

$$v_o(\infty) = \lim_{s \rightarrow 0} sV_o(s) = V_i$$

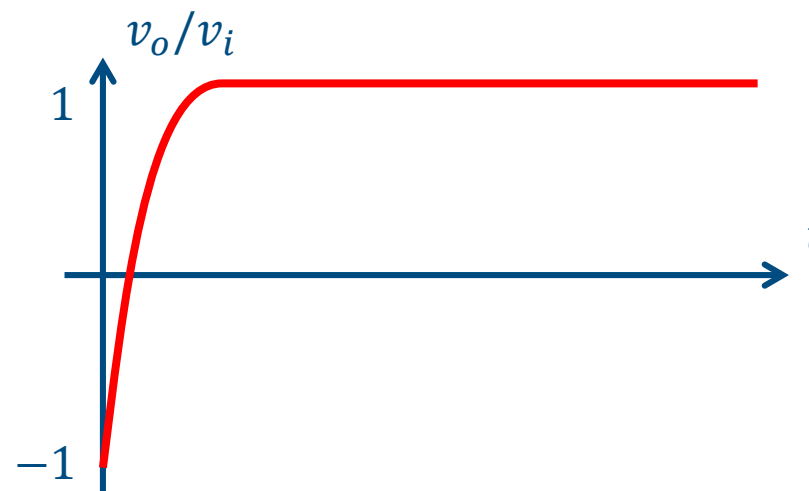Pole time constant = $CR = 20 \mu\text{s}$




Open-loop gain

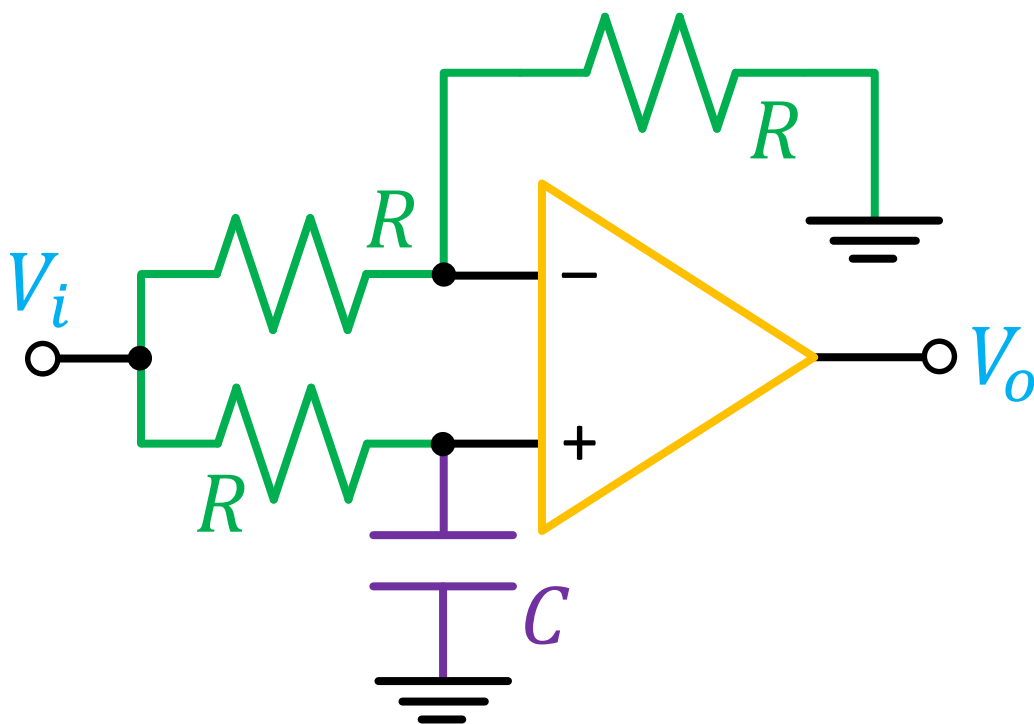

$$\begin{aligned}
 \frac{V_o}{V_i} &= A(s)(V^+ - V^-) \\
 &= A(s) \left(\frac{1}{1 + sCR} - \frac{1}{2} \right) \\
 &= \frac{A(s)}{2} \frac{1 - sCR}{1 + sCR} = G_{OL} \\
 G_{loop} &= -\frac{G_{OL}}{G_{id}} = -\frac{1}{2} A(s)
 \end{aligned}$$



Closed-loop gain

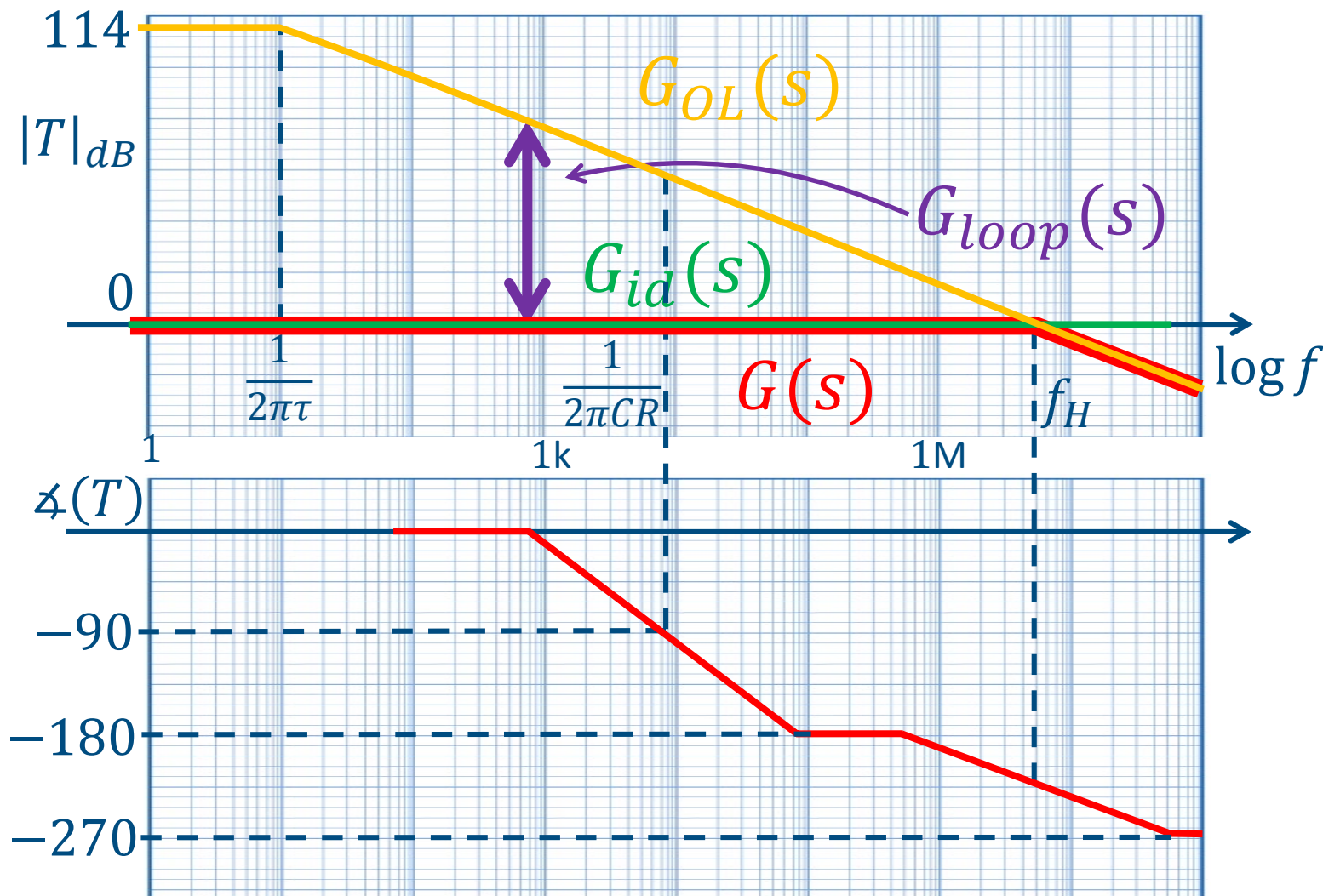



1. Plot the Bode diagram of the closed-loop gain for the scheme in slide #11
2. In the scheme of slide #15, remove resistor R_c and place a capacitor C_c in parallel to R . Compute the gain
3. Compute (approximately) the step response of the phase-shifter circuit accounting for the real gain