



Electronics – 96032

 POLITECNICO DI MILANO



Multiple Feedback Loops

Alessandro Spinelli

Phone: (02 2399) 4001

alessandro.spinelli@polimi.it

spinelli.faculty.polimi.it



Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes



Multiple feedback loops

3

- Stability is easily computed in two cases:
 - There is a node which is common to all loops $\Rightarrow$ break all loops at that position
 - There is a «global» loop which contains «local» ones $\Rightarrow$ check local loops and replace them with their closed-loop transfer functions; check then the global loop
- For the general case, a **sequential loop closure** criterion (not discussed here) was developed by Bode




- HP amplifier
- LP filter
- Current source
- Appendix: relation between G_{id} , G_{OL} , G_{loop} in a multiple-feedback loop



HP Amplifier

5

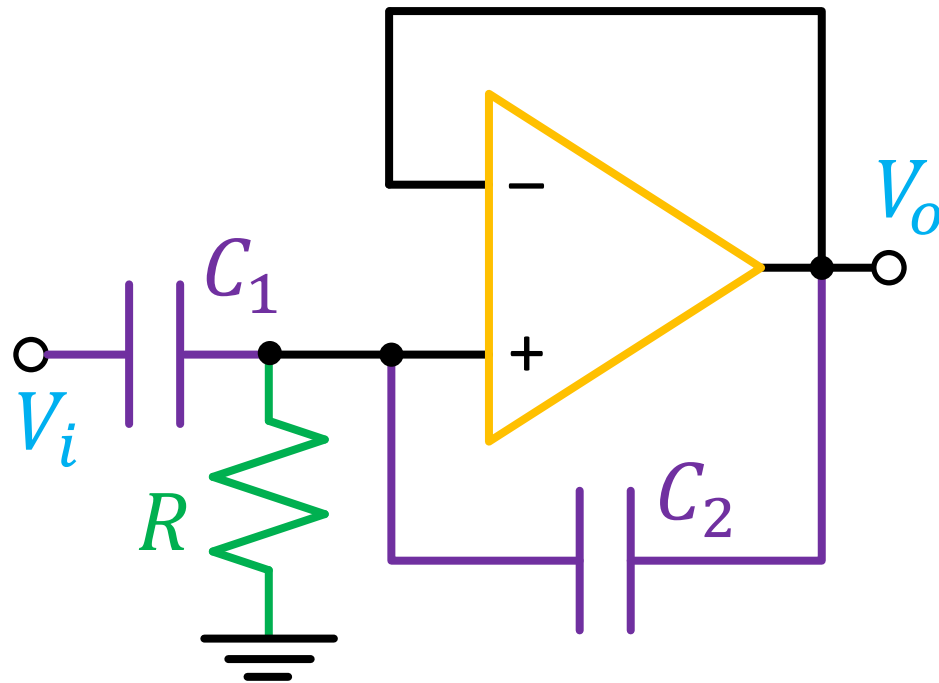

- $R = 8 \text{ k}\Omega$
- $C_1 = 1 \text{ nF}, C_2 = 10 \text{ nF}$
- $GBWP = 10 \text{ MHz}$
- $A_0 = 120 \text{ dB}$

1. Find the TF of the stage
2. Check the stability
3. Compute the closed-loop gain




Gain

6

$$V_o = V^+ \Rightarrow G_{id} = \frac{sC_1R}{1 + sC_1R}$$

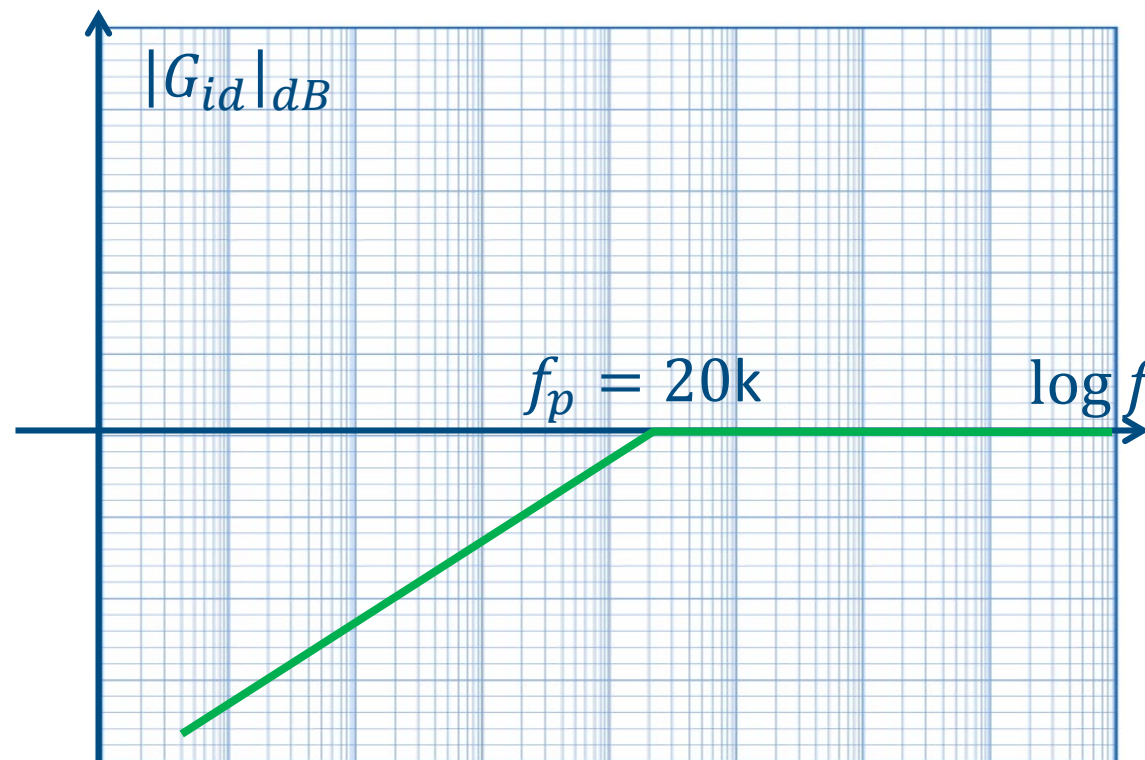
$$f_p = \frac{1}{2\pi C_1R} \approx 20 \text{ kHz}$$





Loop gain

7

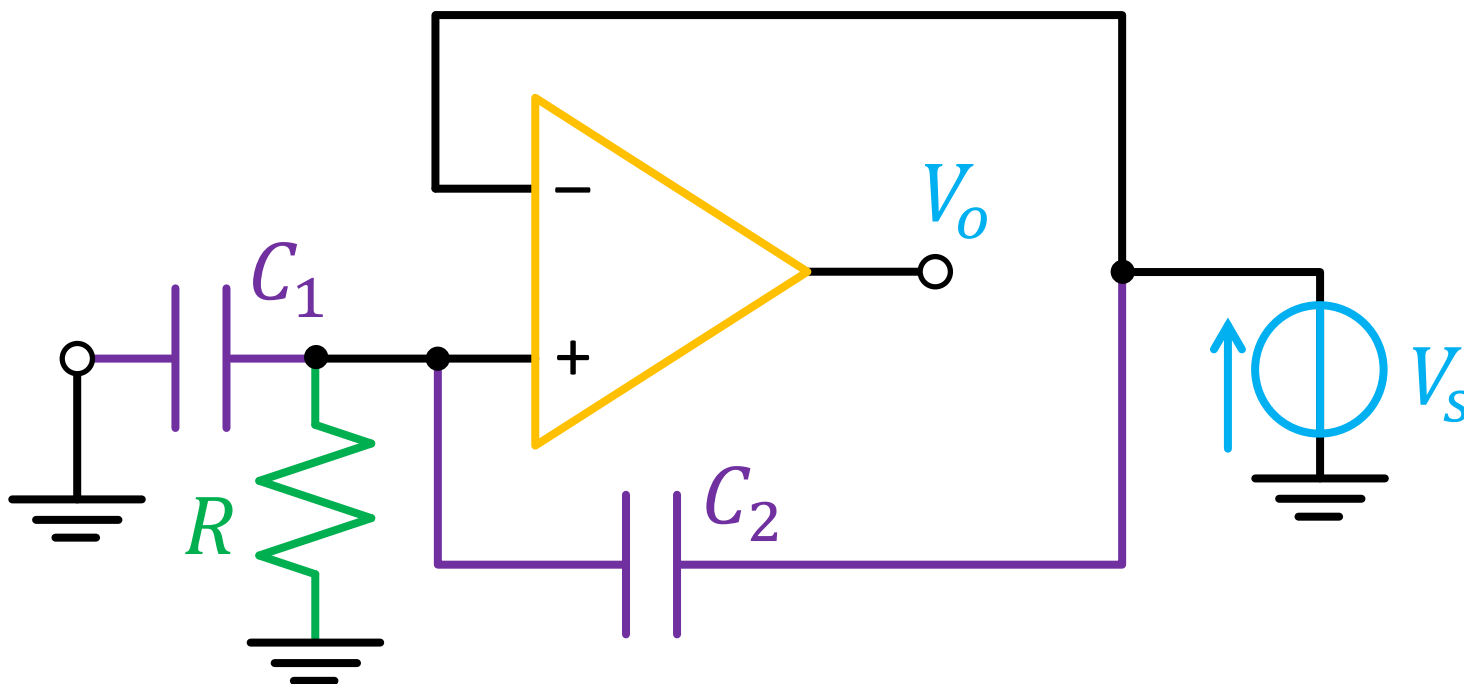



$$\frac{V^+}{V_s} = \frac{R \parallel 1/sC_1}{R \parallel 1/sC_1 + 1/sC_2} = \frac{sC_2R}{1 + s(C_1 + C_2)R}$$
$$G_{loop} = -A(s) \frac{1 + sC_1R}{1 + s(C_1 + C_2)R}$$

Poles and zeros:


$$f_{p0} = \frac{GBWP}{A_0} = 10 \text{ Hz} \quad f_{p1} = \frac{1}{2\pi(C_1 + C_2)R} \approx 1.8 \text{ kHz}$$

$$f_z = \frac{1}{2\pi C_1 R} \approx 20 \text{ kHz}$$



Bode plot

9

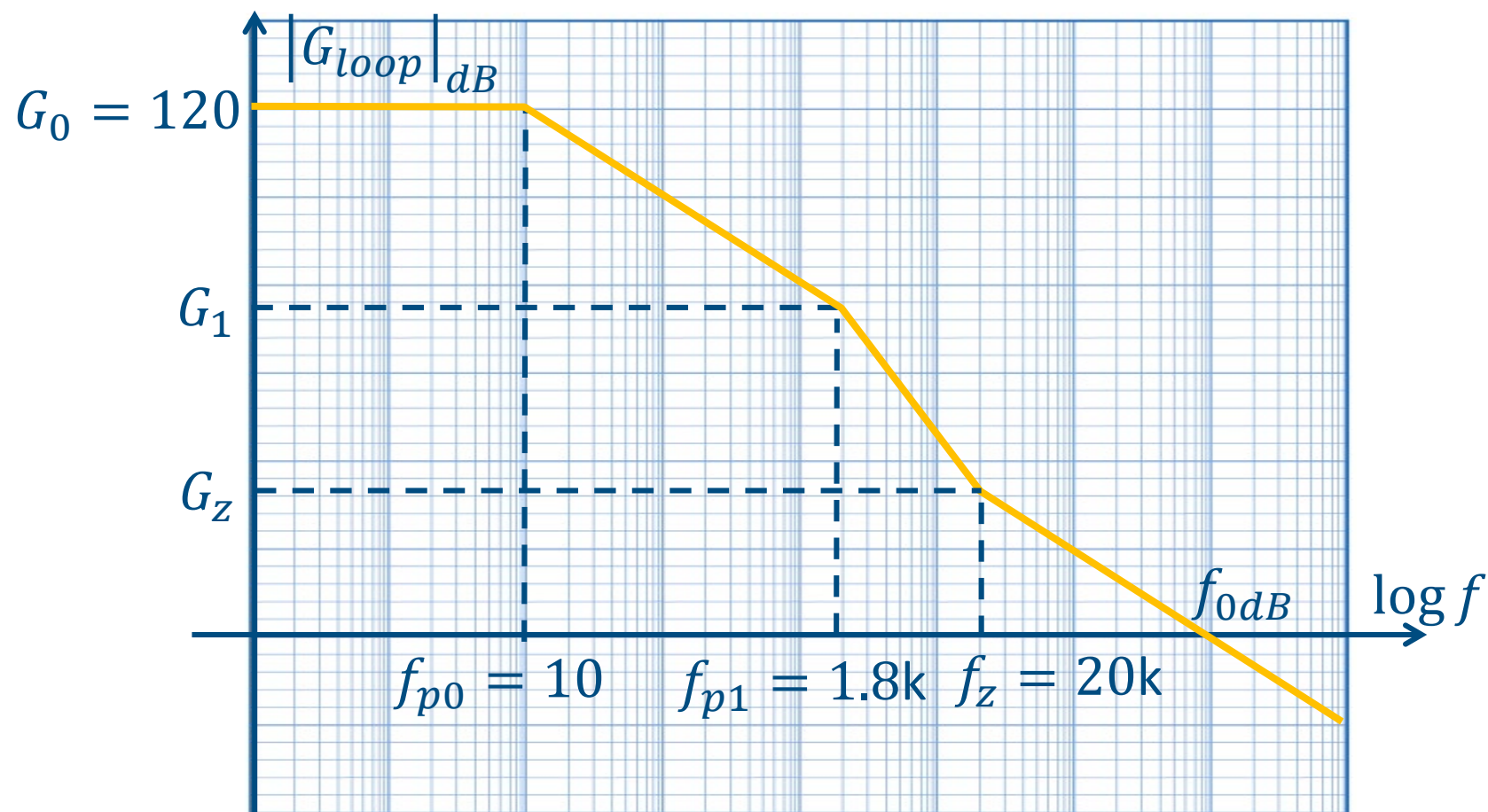



$$G_0 f_{p0} = G_1 f_{p1} \Rightarrow G_1 = 5530 \approx 75 \text{ dB}$$

$$G_1 f_{p1}^2 = G_z f_z^2 \Rightarrow G_z = 45 \approx 33 \text{ dB}$$

$$G_z f_z = f_{0dB} \approx 900 \text{ kHz}$$

The circuit is obviously stable. The phase margin is

$$\phi_m = \arctan \left(\frac{f_{0dB}}{f_z} \right) = 89^\circ$$



At HF, beyond the pole and zero introduced by the capacitors, we have

$$G_{loop} = -A(s) \frac{C_1}{C_1 + C_2}$$


The zero-dB crossing takes place at

$$f_{0dB} = A_0 \frac{C_1}{C_1 + C_2} f_{p0} = GBWP \frac{C_1}{C_1 + C_2} \approx 909 \text{ kHz}$$



Open-loop gain

12

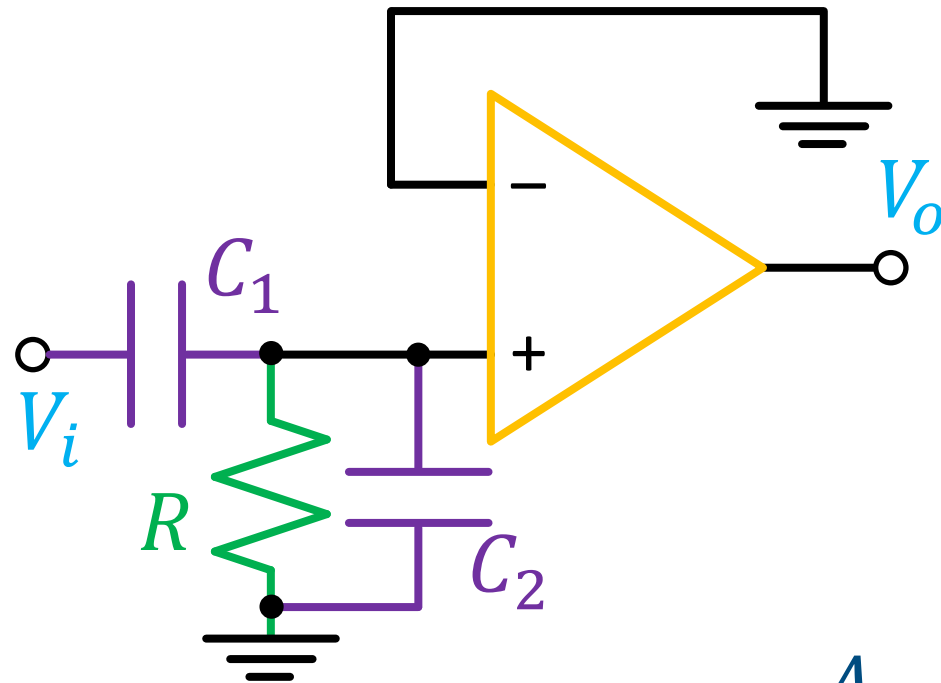


$$G_{OL} = A(s) \frac{R \parallel \frac{1}{sC_2}}{R \parallel \frac{1}{sC_2} + \frac{1}{sC_1}} =$$

$$\frac{A_0}{1 + s\tau} \frac{sC_1 R}{1 + s(C_1 + C_2)R} = -G_{loop} G_{id}$$



Bode plot

13

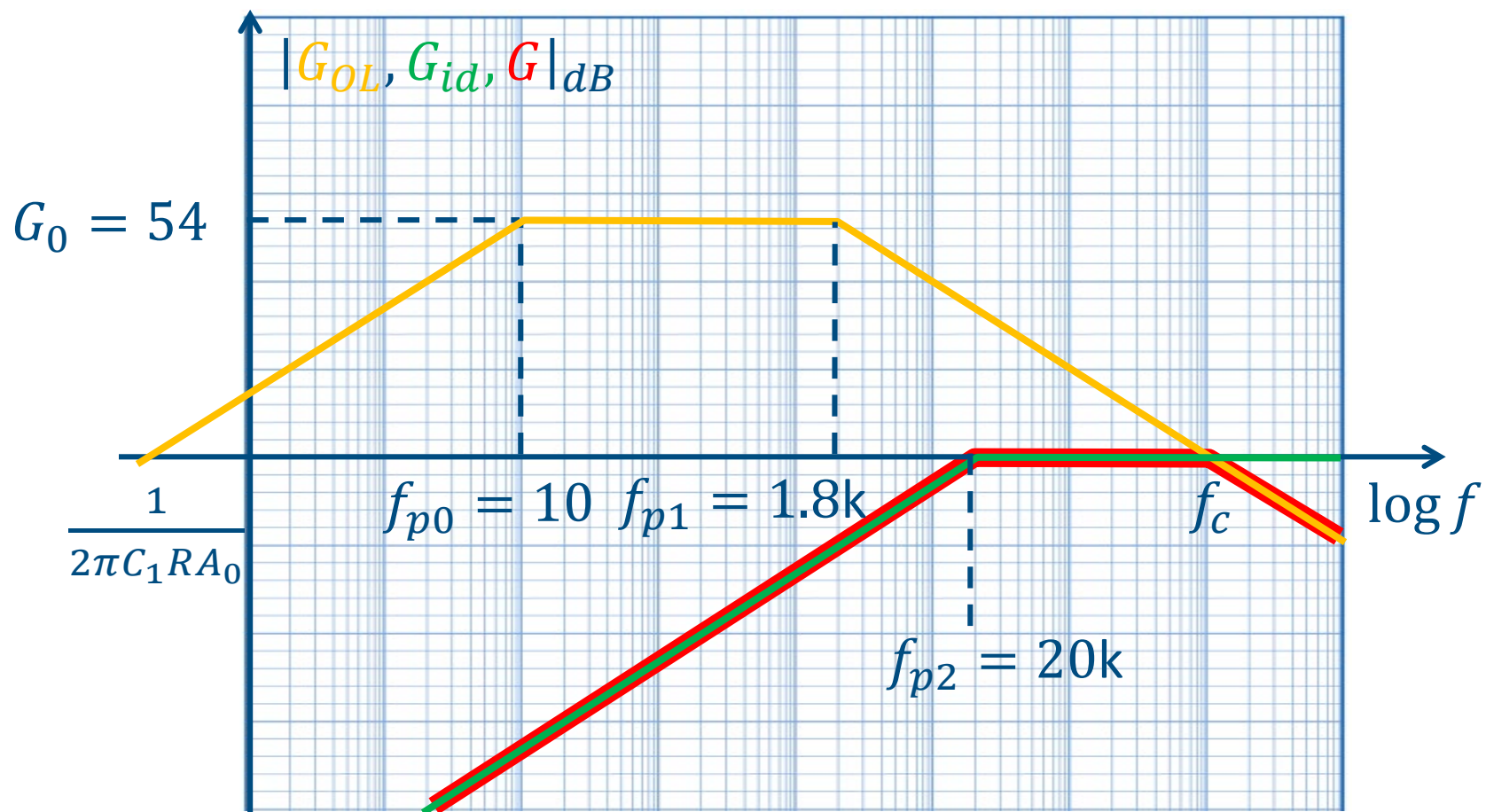



At low frequencies, $G_{OL} \approx sC_1RA_0$

- 0 dB frequency is $f_0 = 1/(2\pi C_1RA_0) \approx 0.02$ Hz

MF gain:

$$\frac{G_0}{f_{p0}} = \frac{1}{f_0} = 2\pi C_1RA_0 \Rightarrow G_0 = 503 = 54 \text{ dB}$$

0 dB frequency:

$$G_0f_{p1} = f_c = 905 \text{ kHz} = f_{0dB}$$

(differences are due to rounding)




- HP amplifier
- LP filter
- Current source
- Appendix: relation between G_{id} , G_{OL} , G_{loop} in a multiple-feedback loop



Sallen-Key LP filter

16

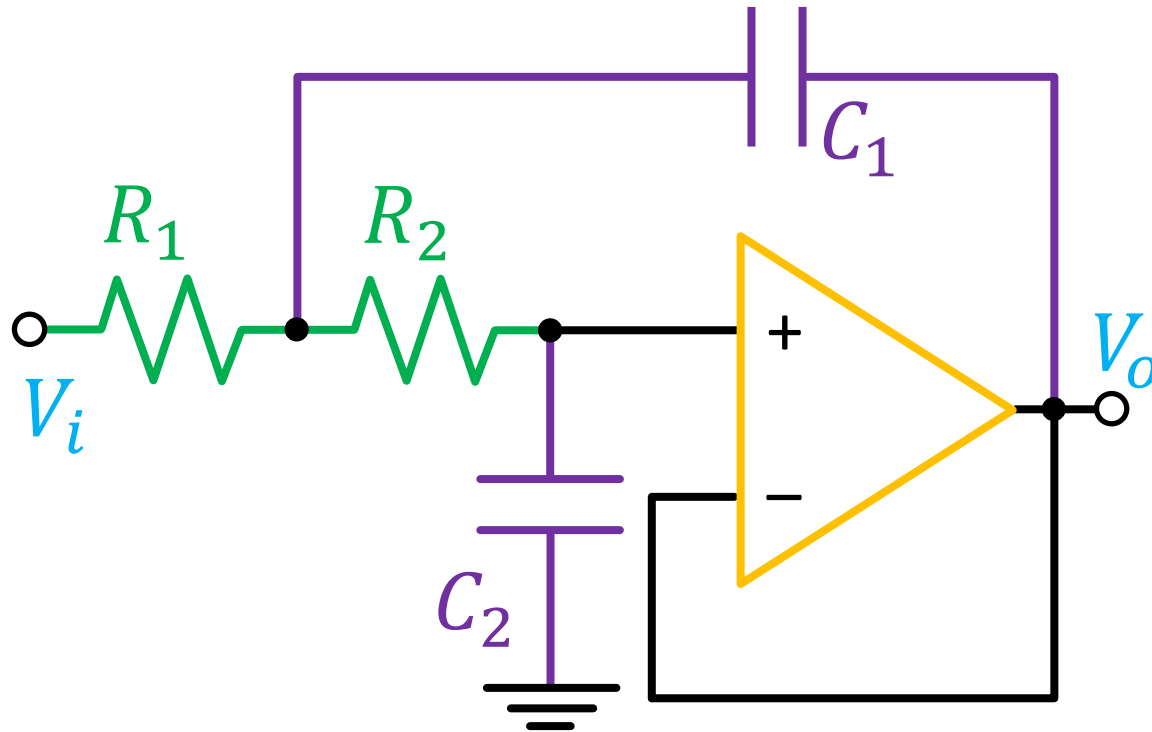

- $R_1 = R_2 = 1 \text{ k}\Omega$
- $C_1 = C_2 = 1 \text{ nF}$
- $GBWP = 10 \text{ MHz}$
- $A_0 = 100 \text{ dB}$

1. Find the TF of the stage
2. Check the stability
3. Compute the closed-loop gain



$$\begin{cases} sC_1(V_o - V_1) + \frac{V_i - V_1}{R_1} = sC_2V_o \\ \frac{V_1}{1 + sC_2 R_2} = V_o \end{cases}$$

$$\begin{aligned} R_1 &= R_2 = R \\ C_1 &= C_2 = C \end{aligned}$$


$$\frac{V_o}{V_i} = \frac{1}{(sRC)^2 + 2sRC + 1} = \frac{1}{(1 + sRC)^2}$$

$$f_p = 159 \text{ kHz}$$



Loop gain

18

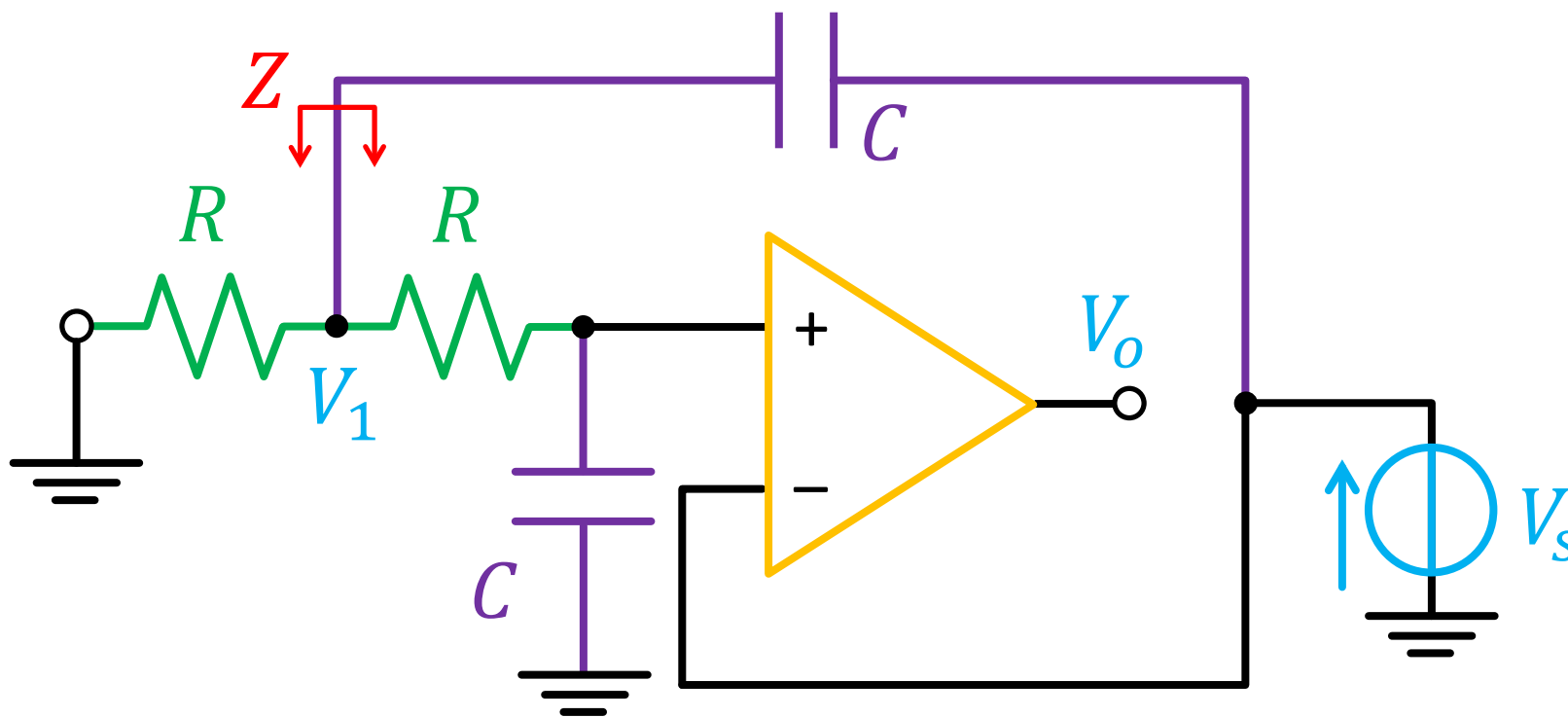



$$Z = R \parallel \left(R + \frac{1}{sC} \right) = R \frac{1 + sCR}{1 + 2sCR}$$

$$V_1 = V_s \frac{Z}{Z + 1/sC} = V_s \frac{sCR(1 + sCR)}{(sCR)^2 + 3sCR + 1}$$

$$V^+ = \frac{V_1}{1 + sCR} \quad V^- = V_s$$

$$G_{loop} = -A(s) \frac{(sCR)^2 + 2sCR + 1}{(sCR)^2 + 3sCR + 1}$$



- Poles and zeros

$$f_{p0} = 100 \text{ Hz}, \quad f_{p1,2} = \frac{-3 \pm \sqrt{5}}{4\pi CR} \approx \begin{matrix} 60.8 \\ 416.7 \end{matrix} \text{ kHz}$$

$$f_{z1,2} = \frac{1}{2\pi CR} = 159 \text{ kHz}$$

- Gains

$$G_0 f_{p0} = G_1 f_{p1} \Rightarrow G_1 = 164 \approx 44 \text{ dB}$$


$$G_1 f_{p1}^2 = G_2 f_z^2 \Rightarrow G_2 = 24 \approx 28 \text{ dB}$$

$$G_2 f_{p2} = f_{0dB} = 10 \text{ MHz}$$



Bode plot


21

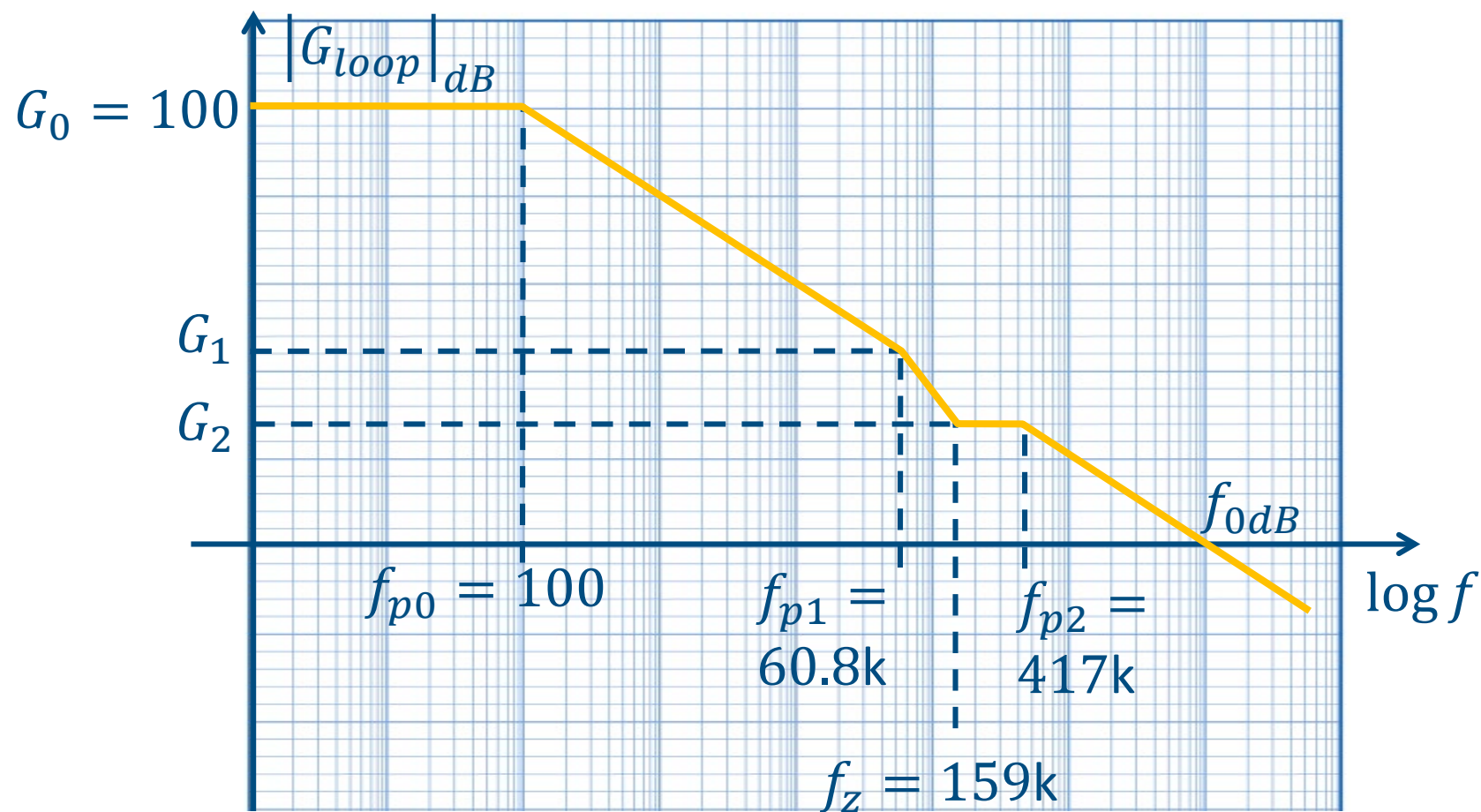



Open-loop gain

22

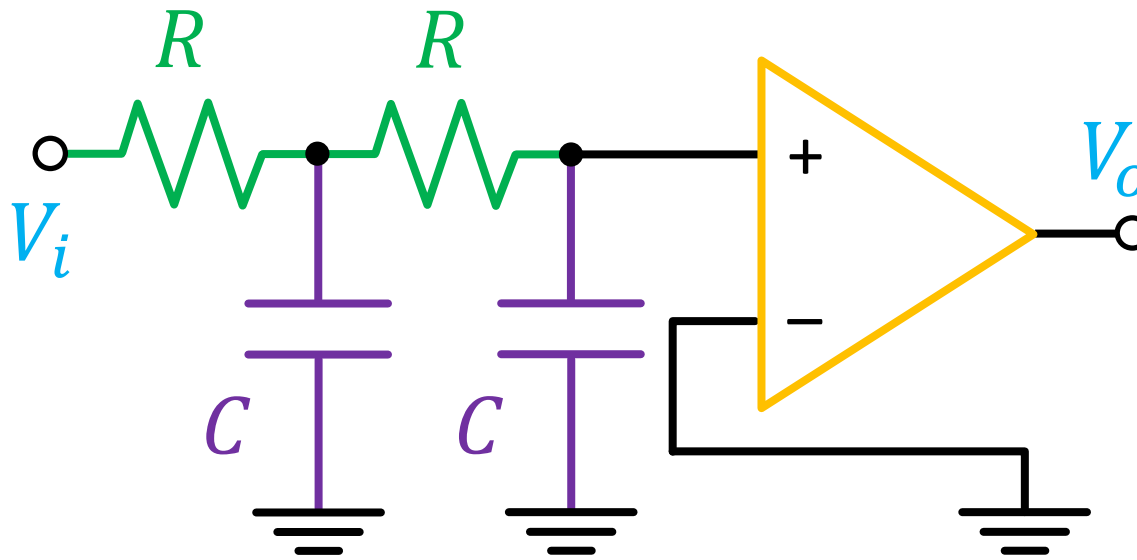

$$G_{OL} = -G_{loop}G_{id} = A(s) \frac{1}{1 + 3sCR + (sCR)^2}$$



$$G_0 f_{p0} = G_1 f_{p1} \Rightarrow G_1 = 164 \approx 44 \text{ dB}$$

$$G_1 f_{p1}^2 = G_2 f_{p2}^2 \Rightarrow G_2 = 3.49 \approx 11 \text{ dB}$$

$$f_{p3}^2 = G_3 f_c^2 \Rightarrow G_3 = 2.5 \times 10^{-4} \approx -72 \text{ dB}$$




or
equivalently

$$G_2 f_{p2}^3 = G_3 f_c^3$$




Bode plot

24

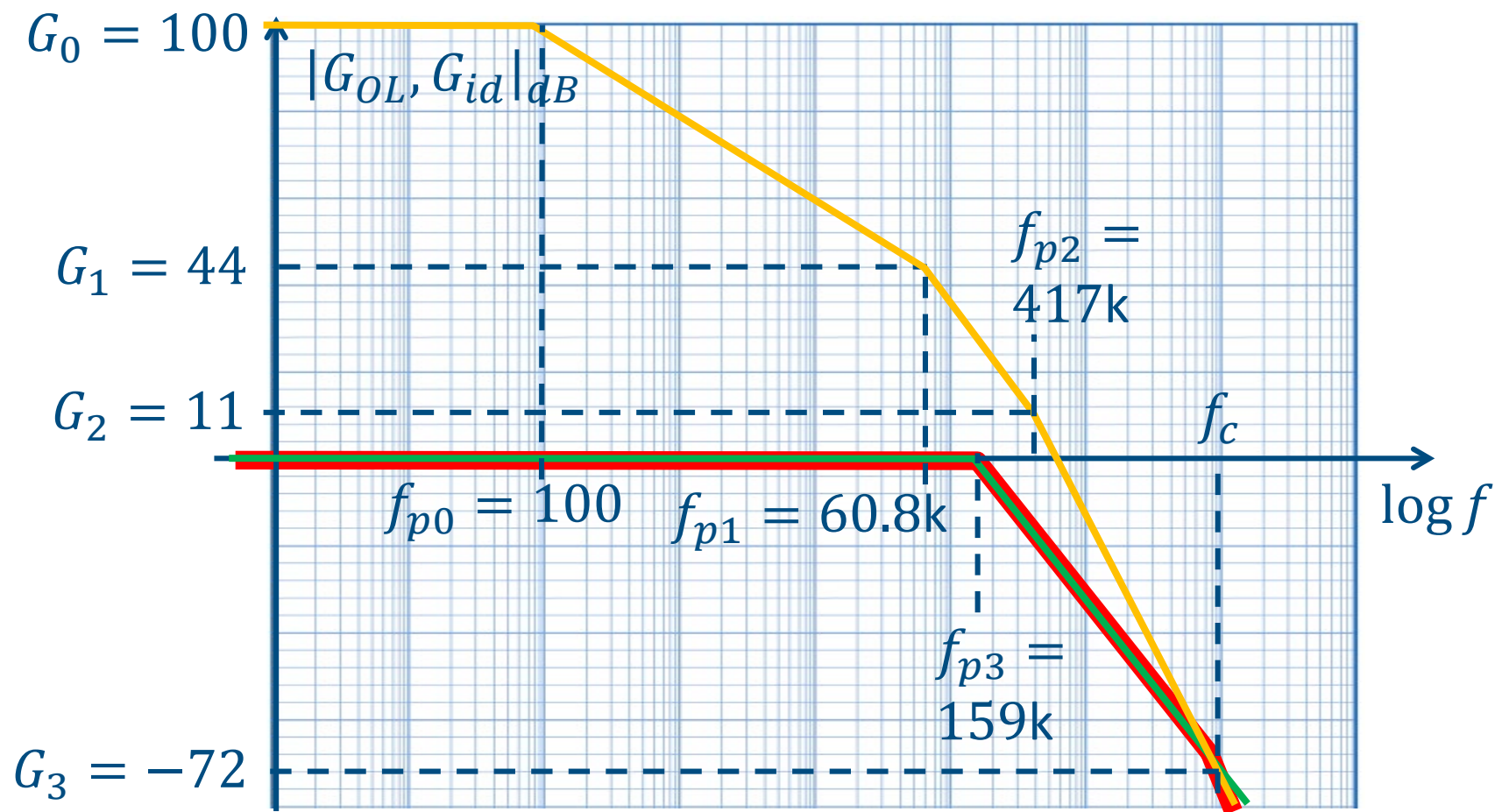



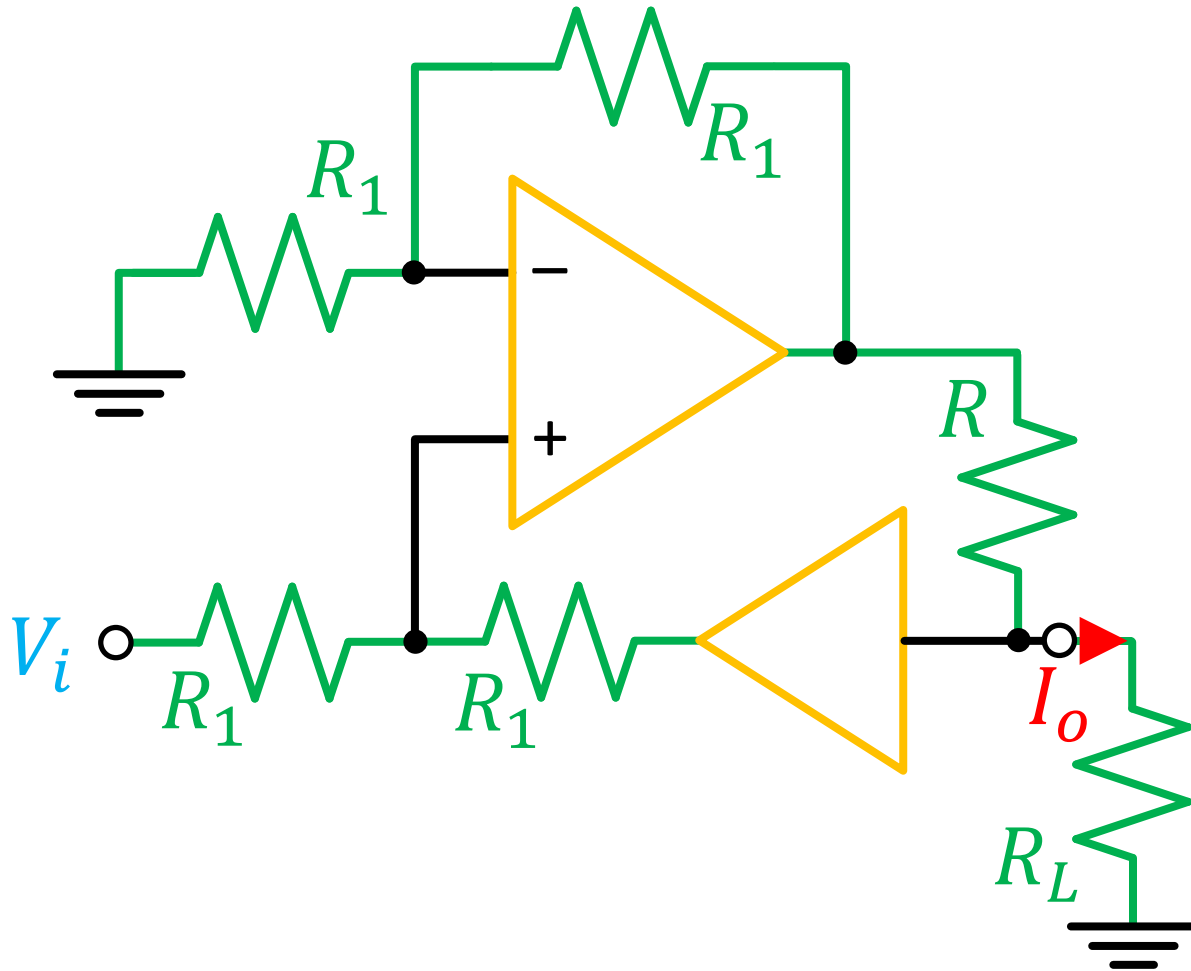- HP amplifier
- LP filter
- Current source
- Appendix: relation between G_{id} , G_{OL} , G_{loop} in a multiple-feedback loop



- $R_1 = 25 \text{ k}\Omega$, $R = 2.5 \text{ k}\Omega$
 - $GBWP = 5 \text{ MHz}$
1. Find the TF of the stage
 2. Check the stability
 3. Compute Z_{out}



$$V^+ = \frac{V_i + V_o}{2} = V^- \Rightarrow V_o^{OA} = 2V^- = V_i + V_o$$


$$I_o = \frac{V_o^{OA} - V_o}{R} = \frac{V_i}{R}$$

The scheme is an ideal current source (note that the output current does not depend on the load)



Loop gain

28

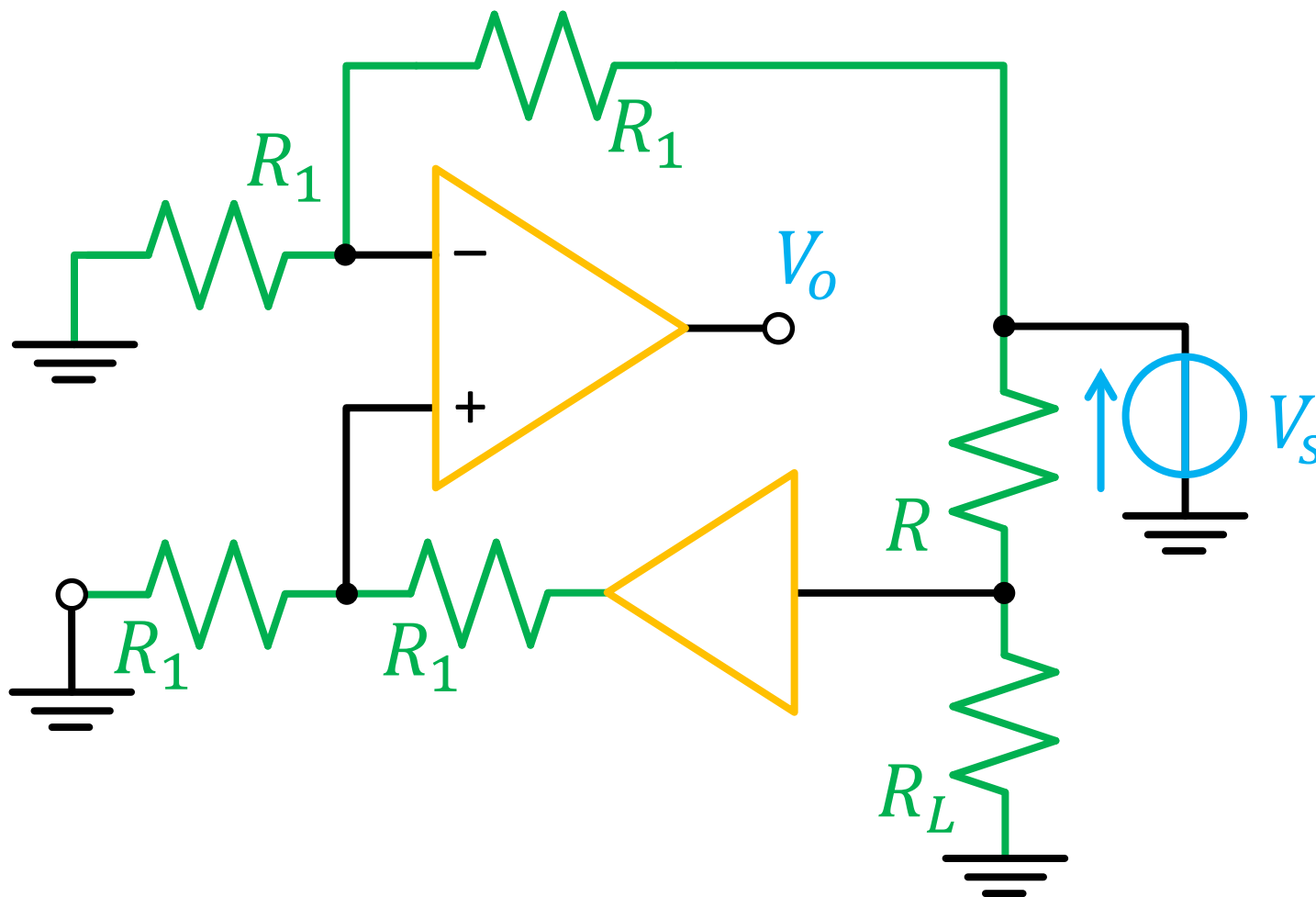




Result

29

$$\frac{V^+}{V_s} = \frac{1}{2} \frac{R_L}{R + R_L} \quad \frac{V^-}{V_s} = \frac{1}{2} \frac{R}{R + R_L}$$

$$G_{loop} = -A(s) \frac{R}{2(R + R_L)}$$

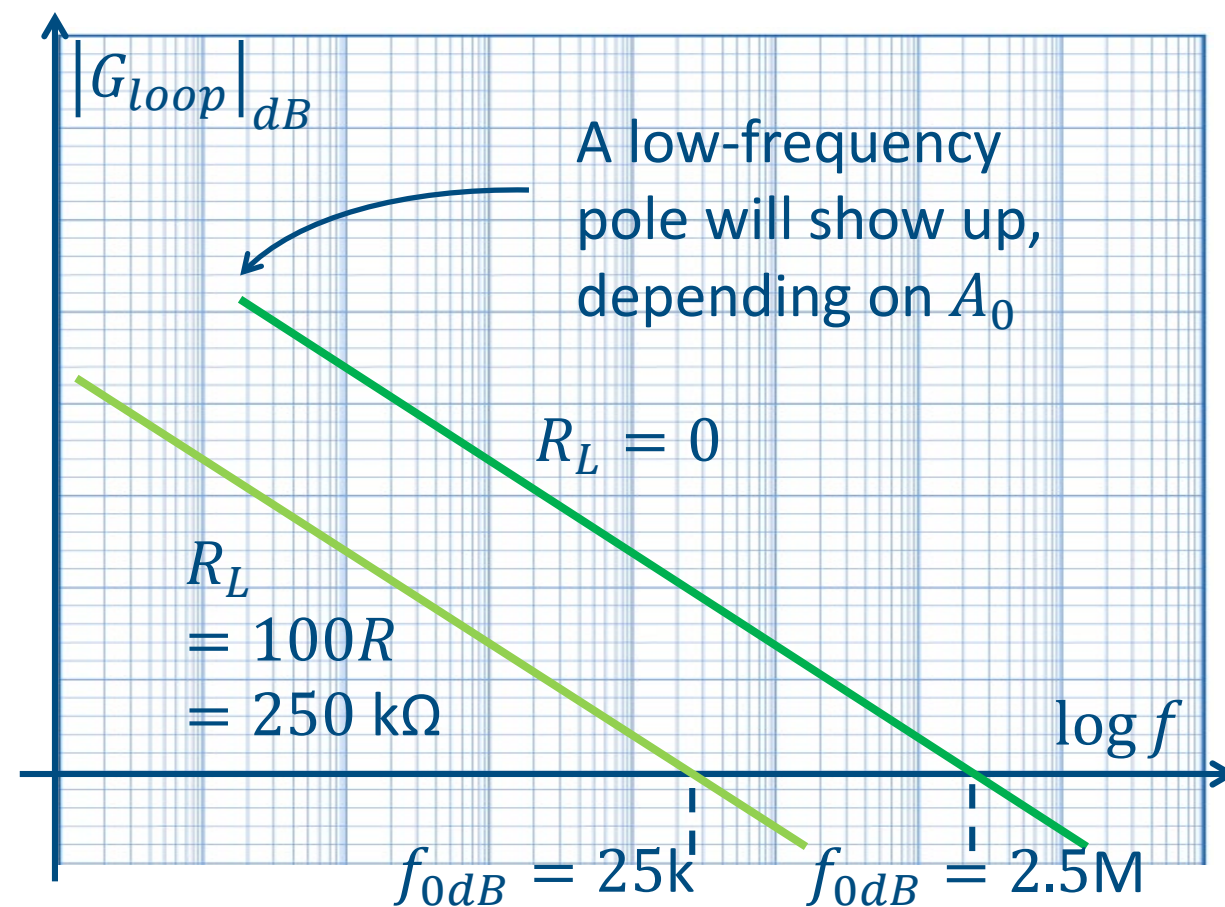
Large values of R_L do not affect stability but reduce precision (related to $1/G_{loop}$)





Open-loop impedance

30

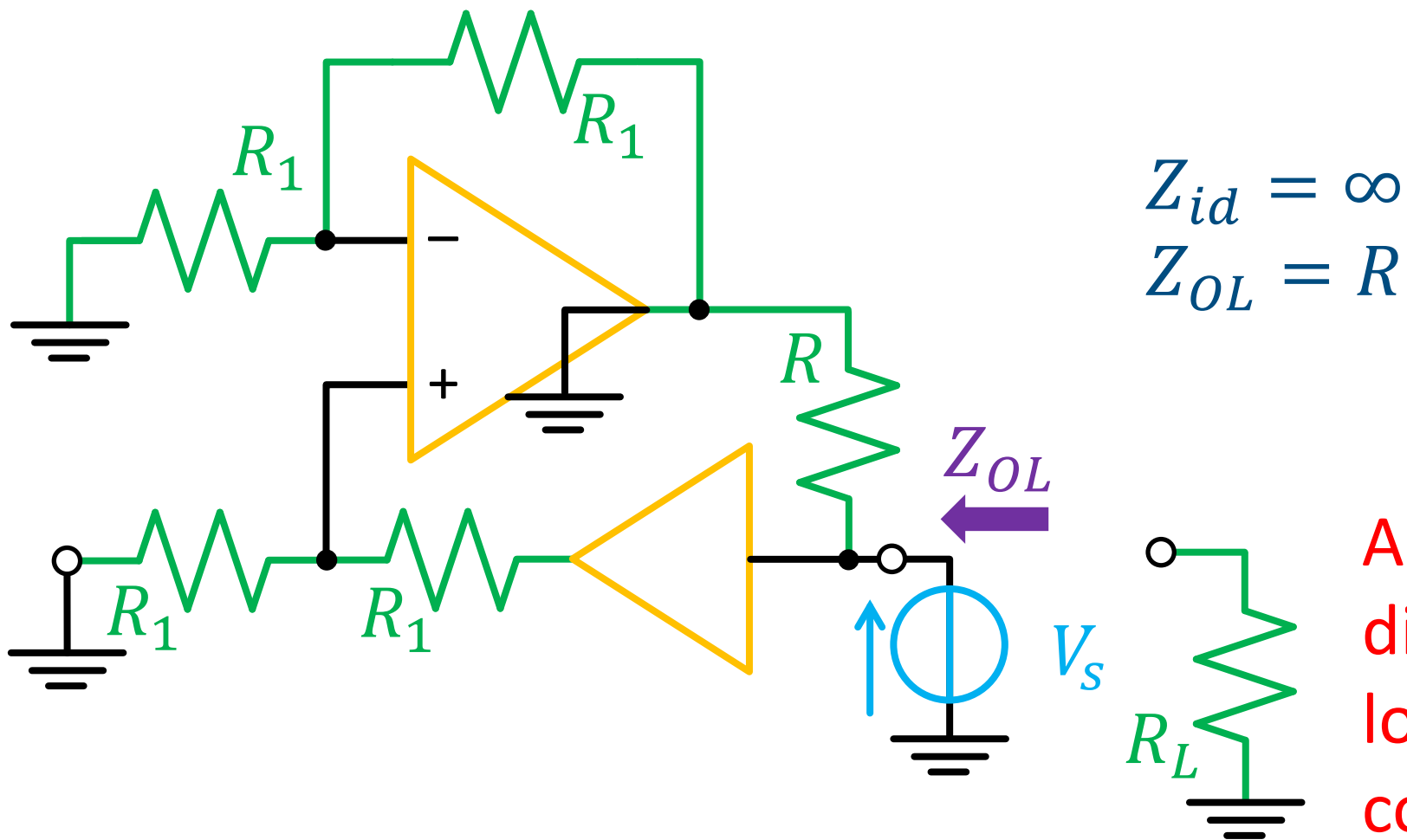


Always
disconnect the
load when
computing Z_{out} !



Loop gain

31

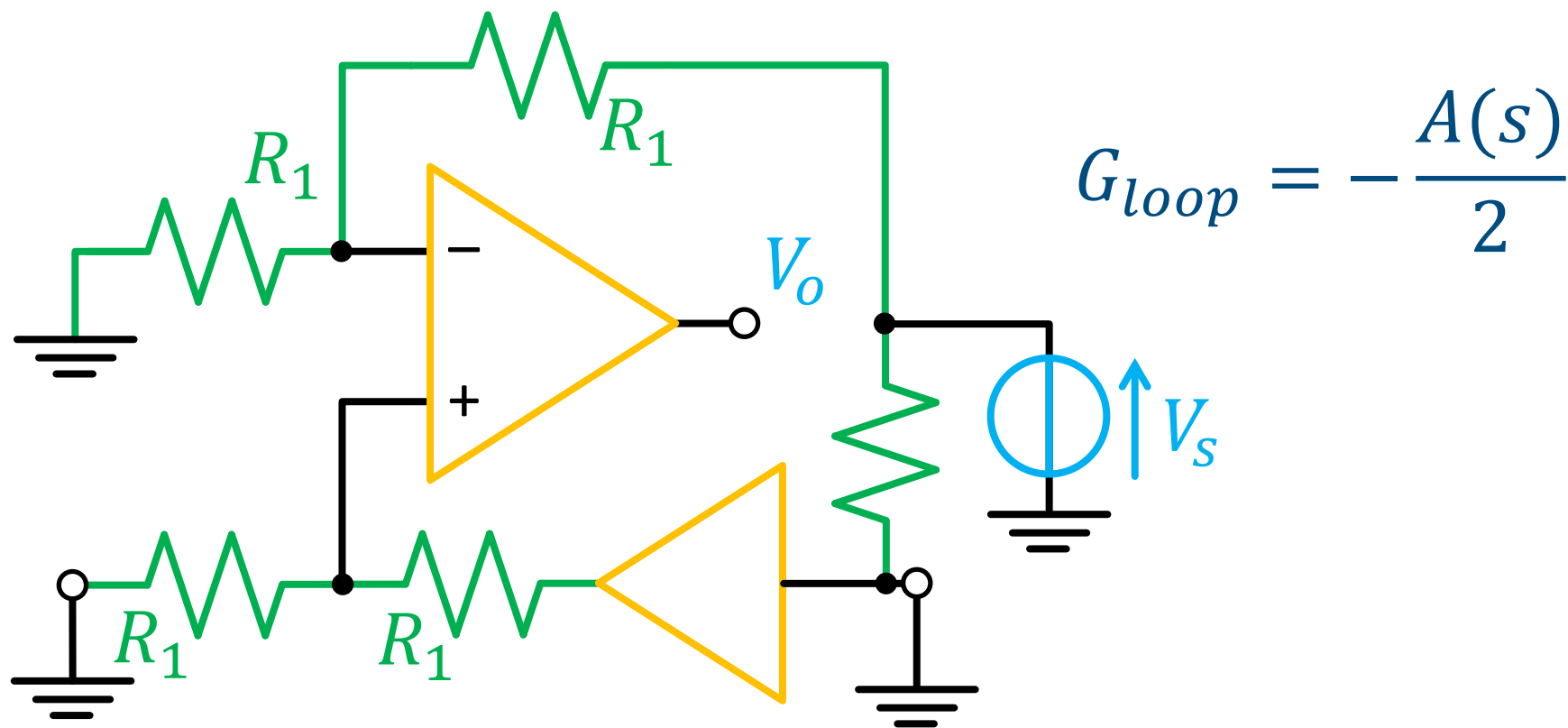


$$Z_{out} = R \left(1 + \frac{A(s)}{2} \right) = 10 \text{ G}\Omega \text{ at LF}$$



Inner loop example

32

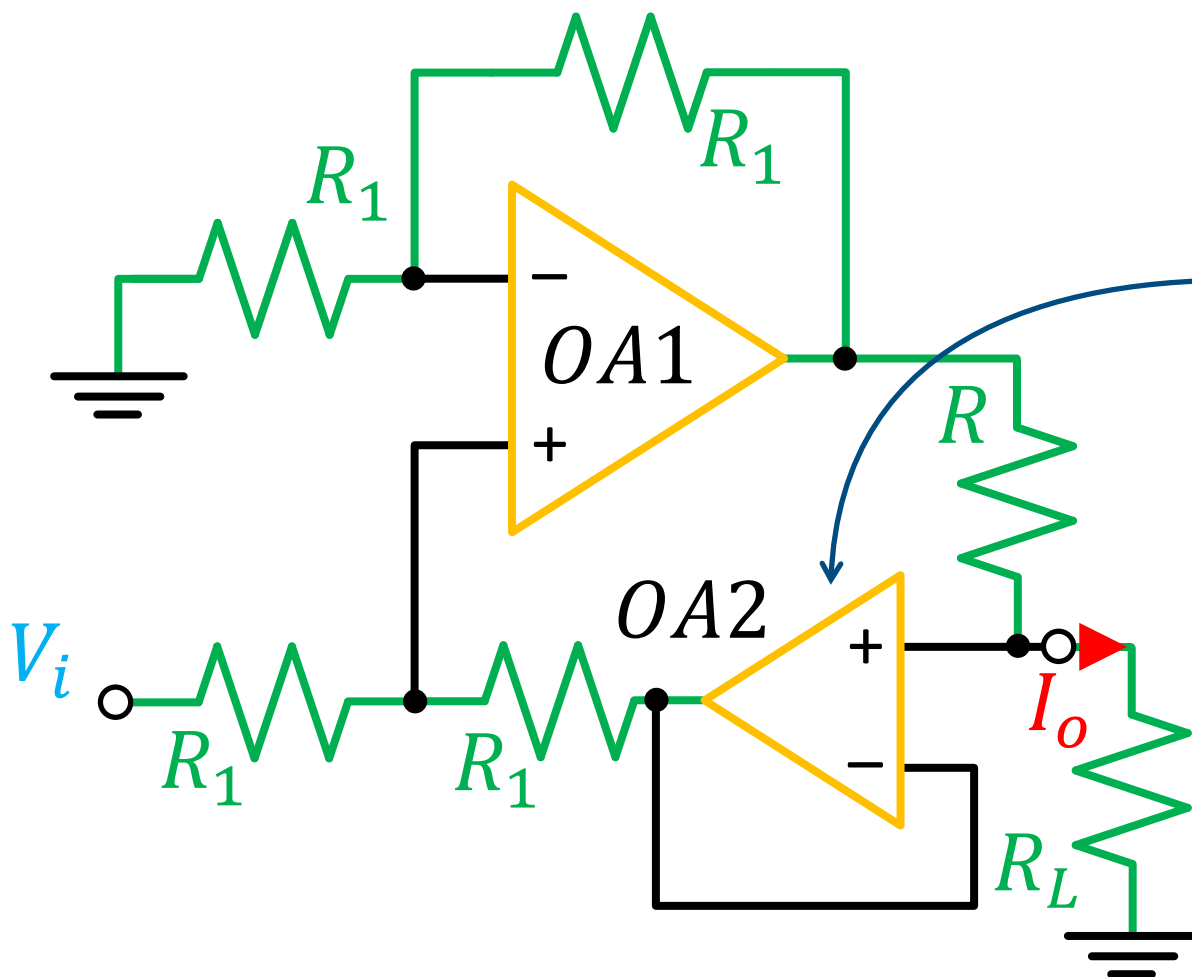

Transfer function becomes $1/(1 + s\tau_c)$, with a pole at $GBWP$



1. Compute the input impedance for the HP amplifier stage in slide #5
2. Compute the output impedance for the scheme in slide #32 when OA1 is ideal and OA2 is not




- HP amplifier
- LP filter
- Current source
- Appendix: relation between G_{id} , G_{OL} , G_{loop} in a multiple-feedback loop



Simplified scheme

35

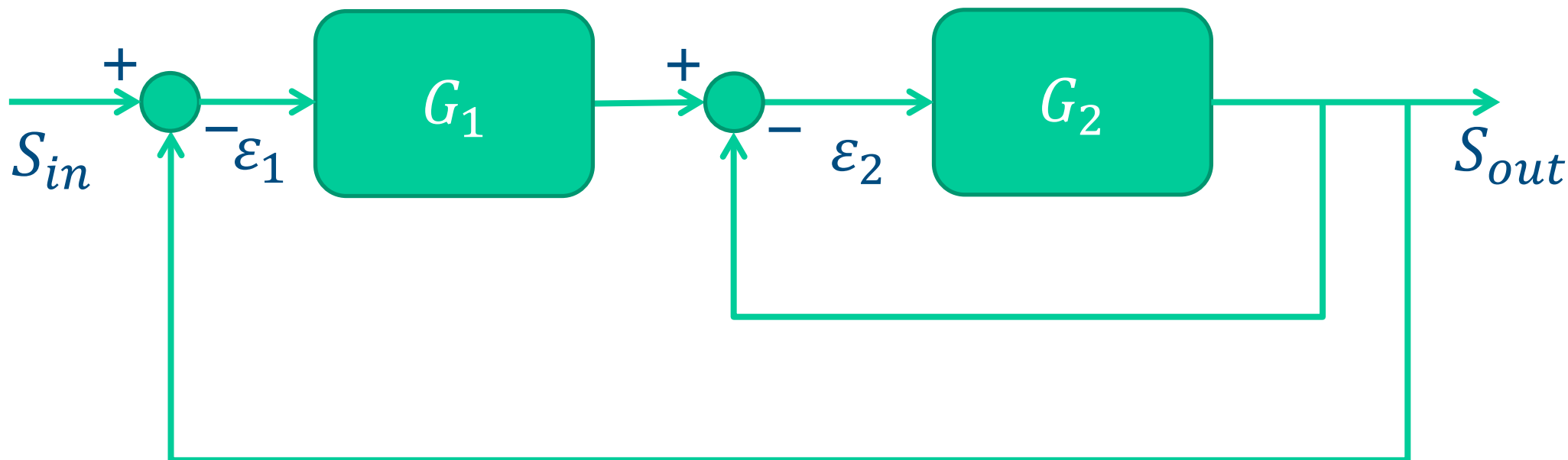


What is the relation between G_{id} , G_{OL} and G_{loop} ?



Approach 1: solving the inner loop

36

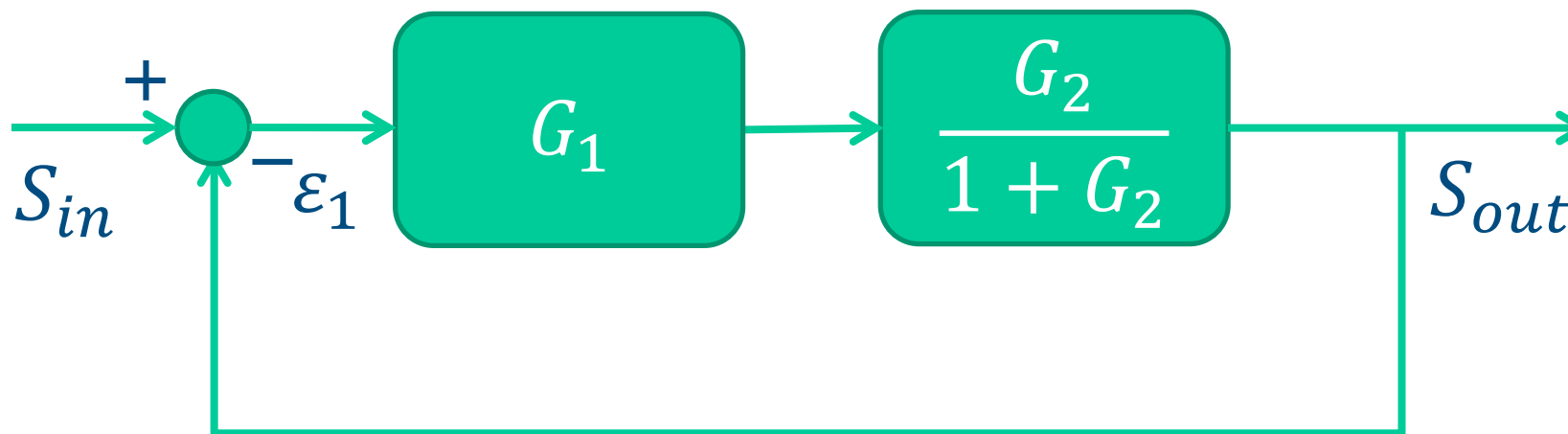


$$G_{loop} = -\frac{G_1 G_2}{1 + G_2} \quad G_{OL} = \frac{G_1 G_2}{1 + G_2} \quad G_{id} = 1$$

$$G = \frac{G_{OL}}{1 - G_{loop}} = \frac{G_1 G_2}{1 + G_2 + G_1 G_2} = \frac{G_{id}}{1 - \frac{1}{G_{loop}}} = \frac{1}{1 + \frac{1 + G_2}{G_1 G_2}}$$



Approach 2: cutting both loops

37

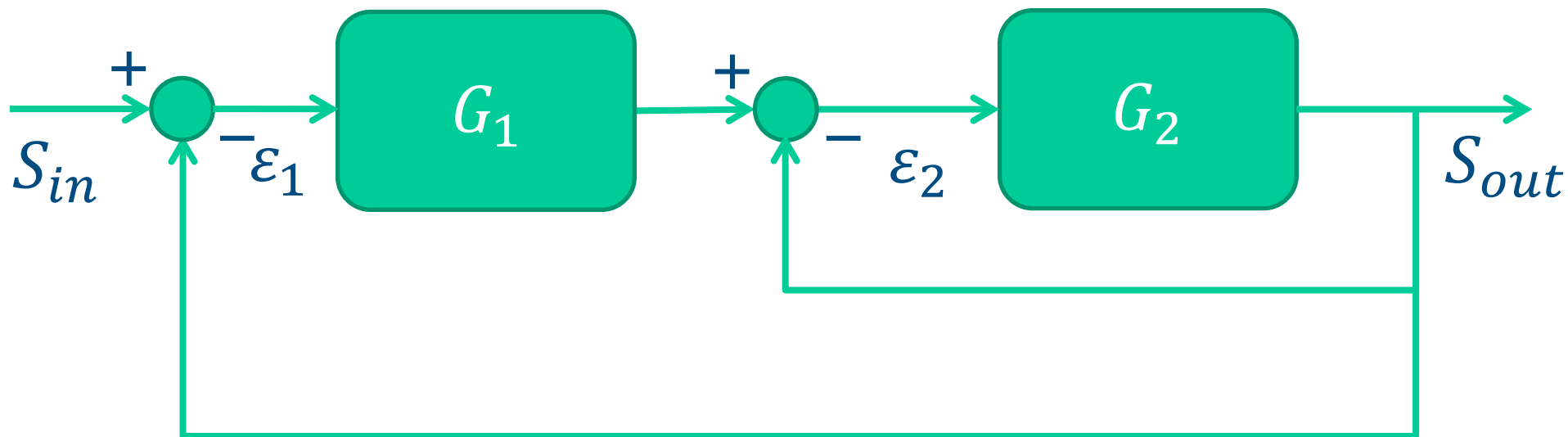

$$G_{loop} = -G_2(1 + G_1) \quad G_{OL} = G_1 G_2 \quad G_{id} = 1$$

$$G = \frac{G_{OL}}{1 - G_{loop}} = \frac{G_1 G_2}{1 + G_2 + G_1 G_2} \neq \frac{G_{id}}{1 - \frac{1}{G_{loop}}} = \frac{1}{1 + \frac{1}{G_2(1 + G_1)}}$$





- From the viewpoint of stability, both approaches return the same condition
- The relation among G_{id} , G_{OL} and G_{loop} is only valid for a single-loop system
- To understand this point, remember that computing G_{id} means assuming $\varepsilon = 0$
 - In the first case, the error signal is ε_1 , which is the error that controls the $S_{out} - S_{in}$ relation
 - When we are cutting both loops, the error signal is different



Loop simplification

39

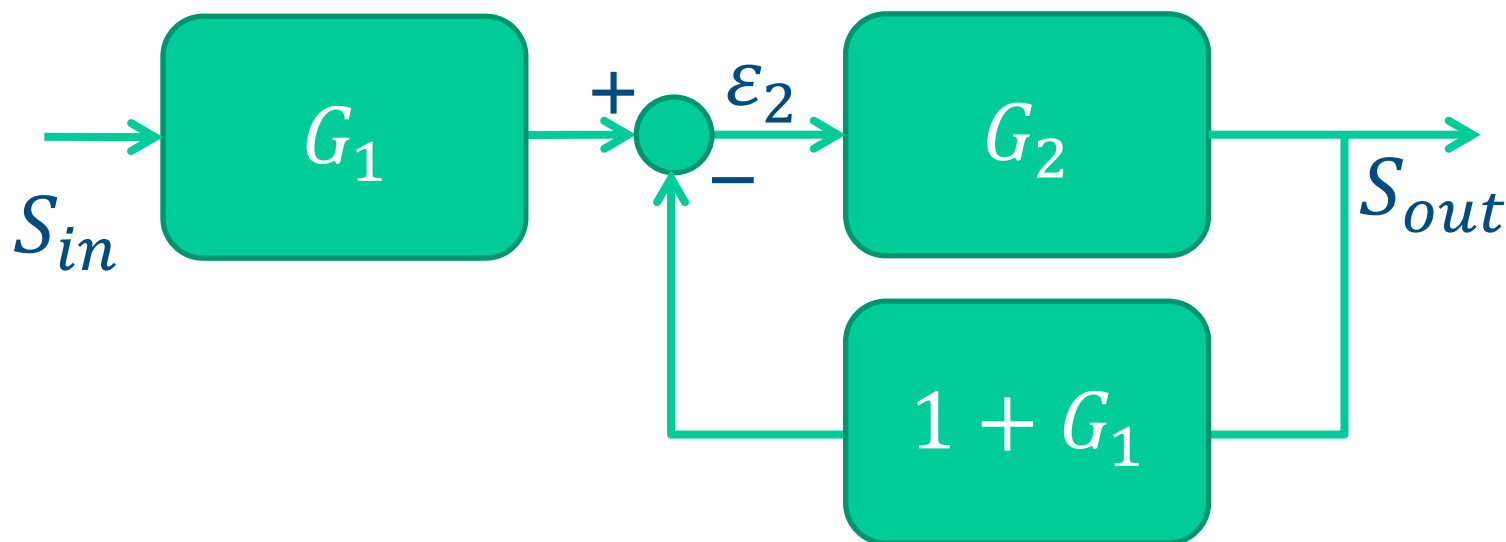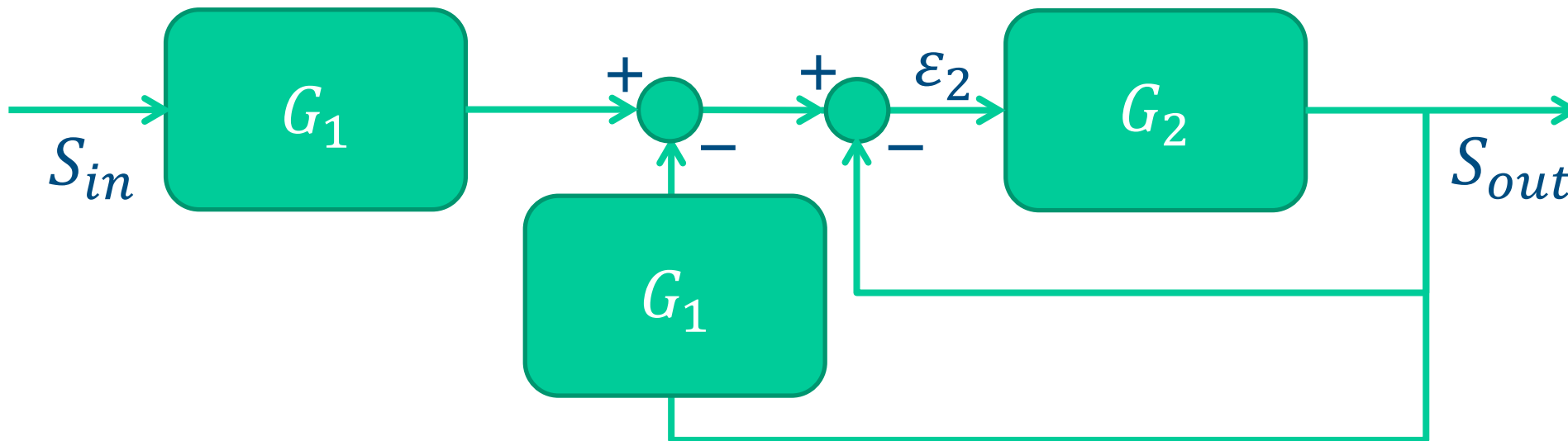

$$\begin{aligned} G_{loop} &= -G_2(1 + G_1) \\ G_{OL} &= G_1 G_2 \\ G_{id} &= \frac{G_1}{1 + G_1} = -\frac{G_{OL}}{G_{loop}} \end{aligned}$$