



Electronics – 96032

 POLITECNICO DI MILANO



Noise Transfer in Circuits

Alessandro Spinelli

Phone: (02 2399) 4001

alessandro.spinelli@polimi.it


spinelli.faculty.polimi.it



Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes



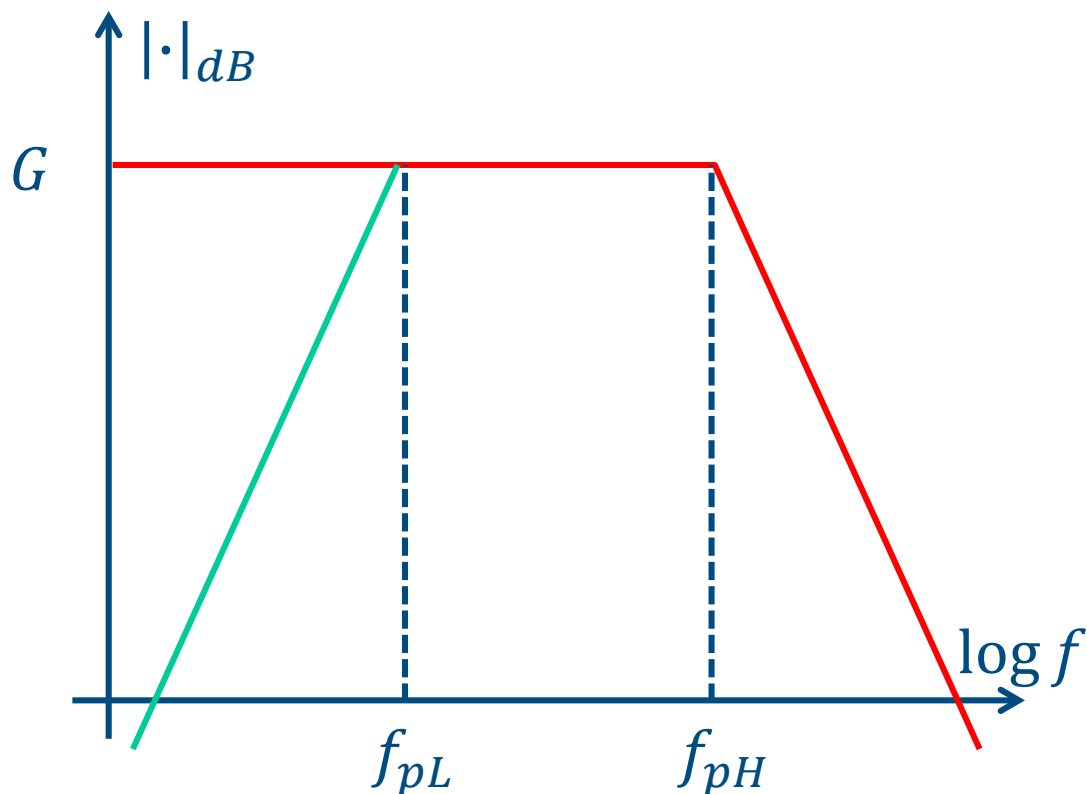- Inverting amplifier
- Integrator
- Differentiator
- Appendix: BP filter and white noise



- LP filter noise transfer:

$$\overline{n^2} = G^2 S_{in} \frac{\pi}{2} f_{pH}$$

- BP filter noise transfer:

$$\overline{n^2} = G^2 S_{in} \frac{\pi}{2} (f_{pH} - f_{pL})$$


$$\approx G^2 S_{in} \frac{\pi}{2} f_{pH}$$

(see Appendix)



Inverting amplifier

5

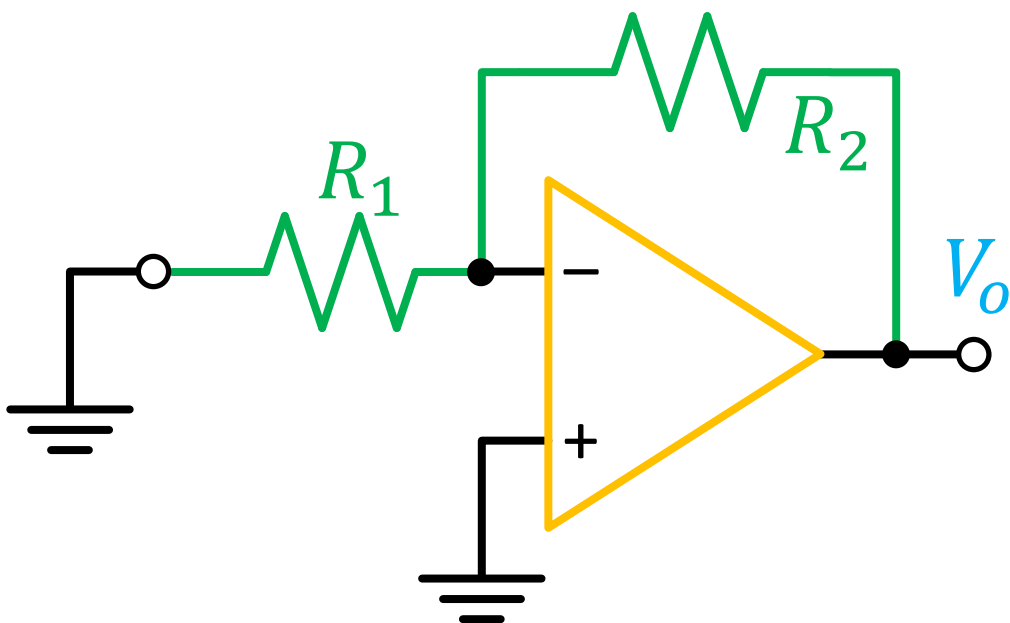


- $R_1 = 1 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$
- $GBWP = 10 \text{ MHz}$
- $\sqrt{S_V} = 10 \text{ nV}/\sqrt{\text{Hz}}$
- $\sqrt{S_I} = 10 \text{ pA}/\sqrt{\text{Hz}}$

1. Find the total output noise



R_1 noise

6

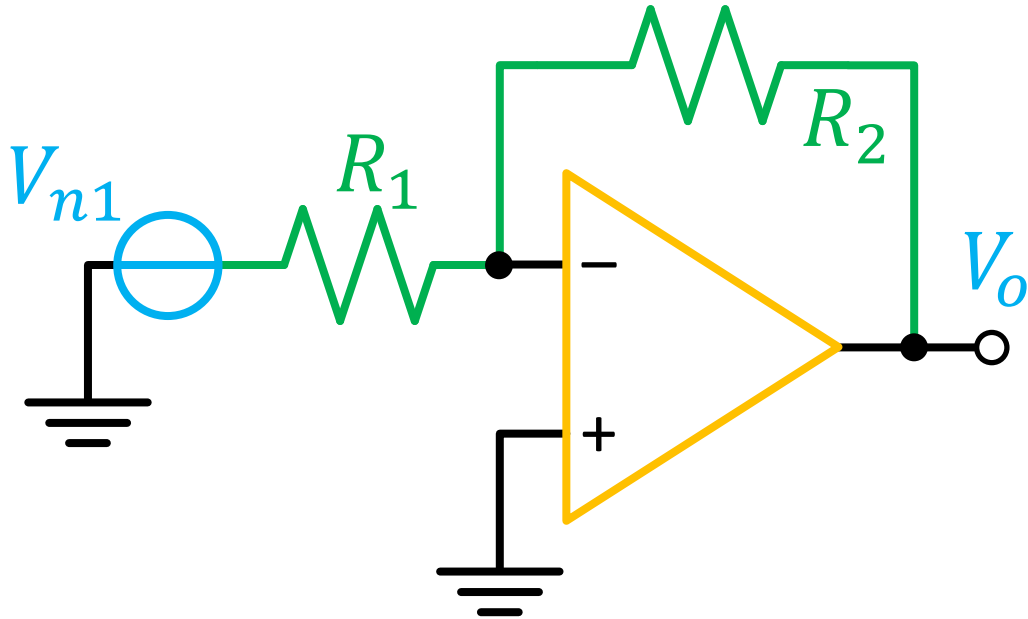

$$V_o = -\frac{R_2}{R_1} V_{n1}$$

$$S_{V_o} = \left(\frac{R_2}{R_1}\right)^2 S_V$$


$$\overline{V_o^2} = \int S_{V_o} df$$

Total output noise diverges $\Rightarrow$ we need to consider the true high-frequency transfer!



Gain

7

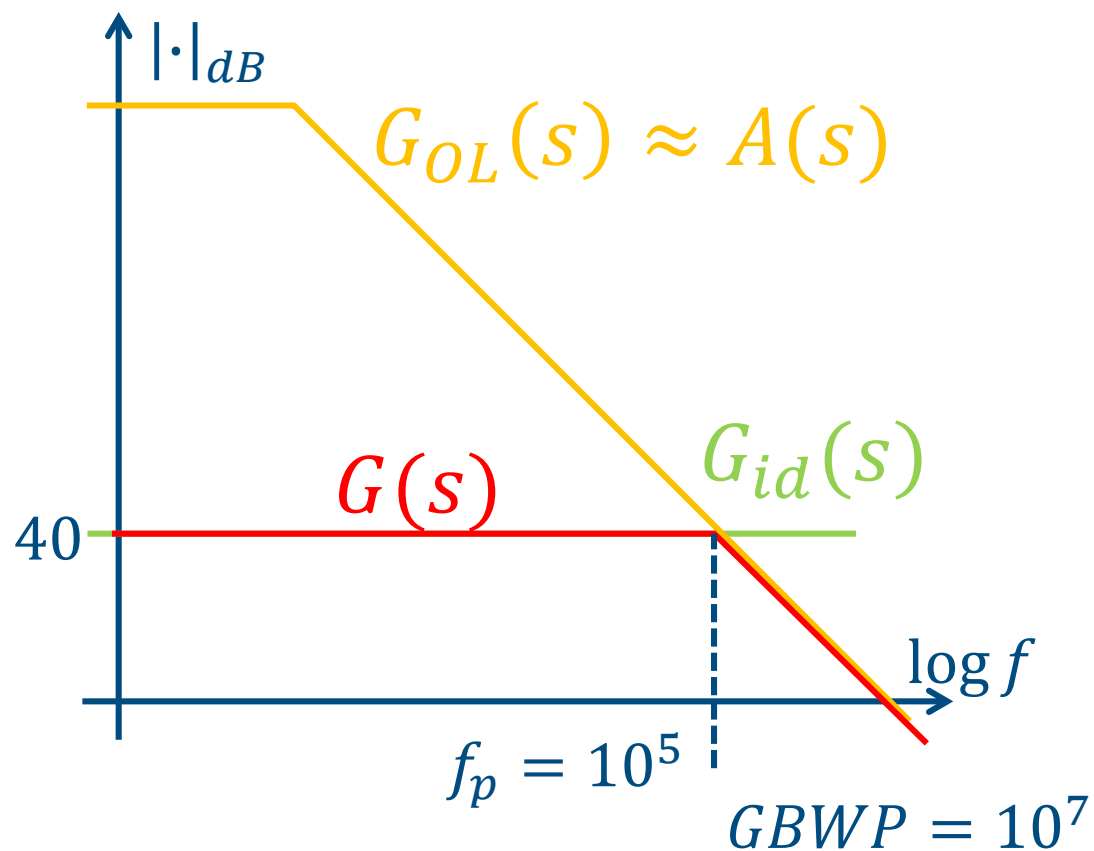

$$G_{OL} = -A(s) \frac{R_2}{R_1 + R_2} \approx -A(s)$$


$$|G| = \frac{R_2/R_1}{1 + s\tau_p} \quad \frac{1}{2\pi\tau_p} = 10^5 \text{ Hz}$$

$$\overline{V_o^2} = 4k_B T R_1 \left(\frac{R_2}{R_1} \right)^2 \frac{\pi}{2} f_p$$
$$\approx 2.59 \times 10^{-8} \text{ V}^2$$




R_2 noise


8

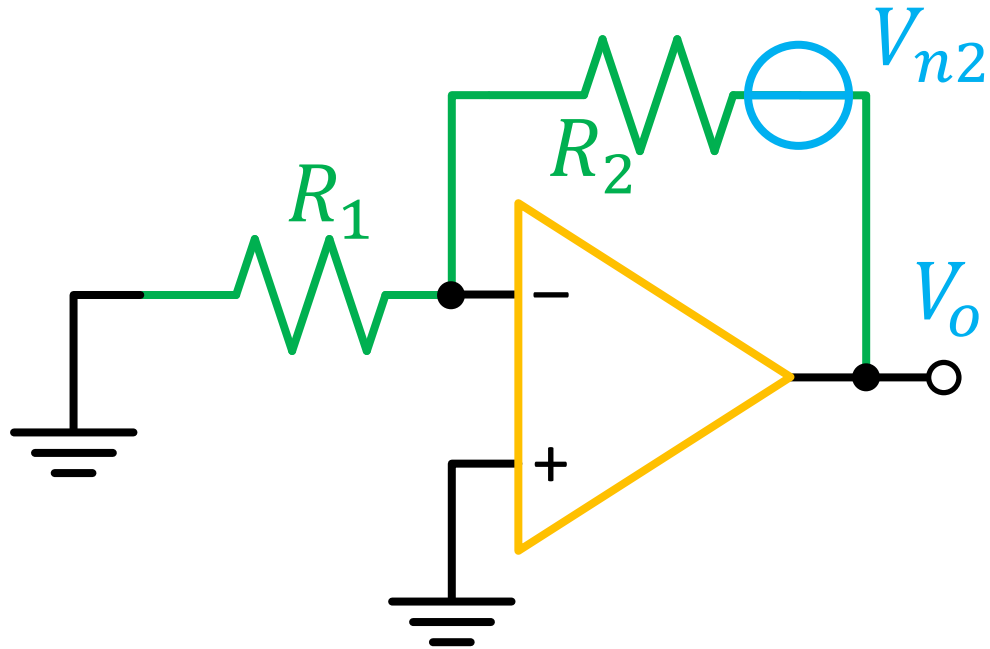
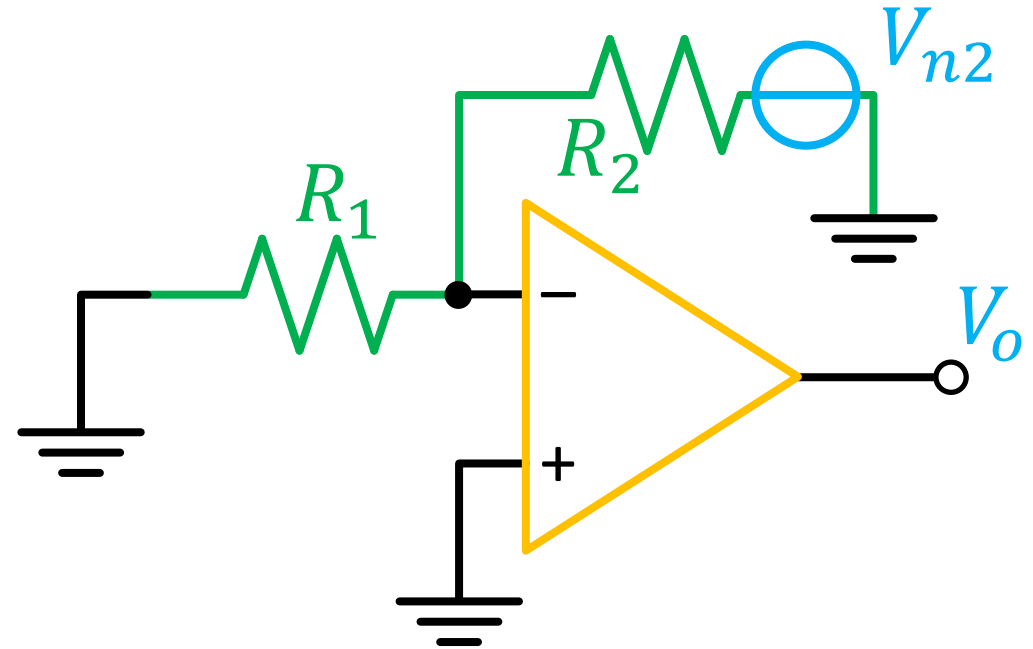
$$V_o = V_{n2} \Rightarrow S_{V_o} = S_V$$



$$G_{OL} = -A(s) \frac{R_1}{R_1 + R_2}$$

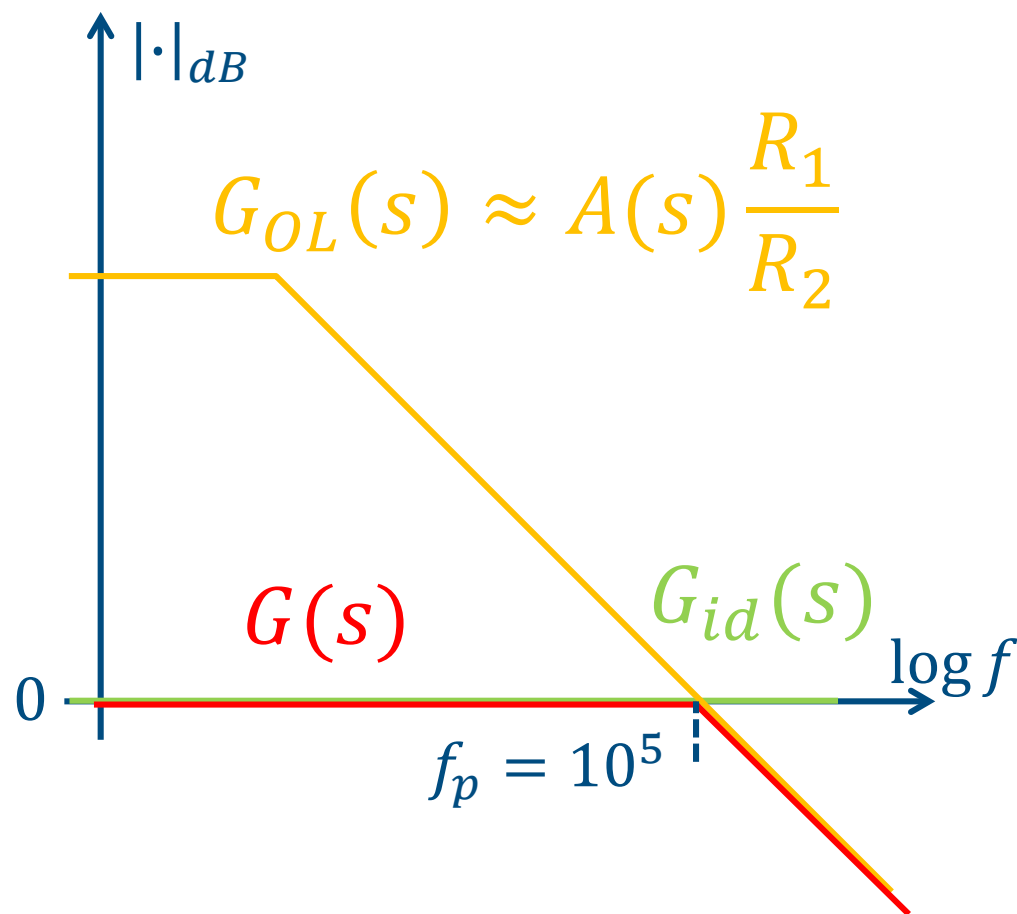

$$G_{OL} \approx -A(s) \frac{R_1}{R_2} \quad |G| = \frac{1}{1 + s\tau_p}$$

$$\frac{1}{2\pi\tau_p} = GBWP \frac{R_1}{R_2} = 10^5 \text{ Hz}$$


$$\overline{V_o^2} = 4k_B T R_2 \frac{\pi}{2} f_p$$
$$\approx 2.59 \times 10^{-10} \text{ V}^2$$

(smaller than R_1 noise)



OpAmp voltage noise


10

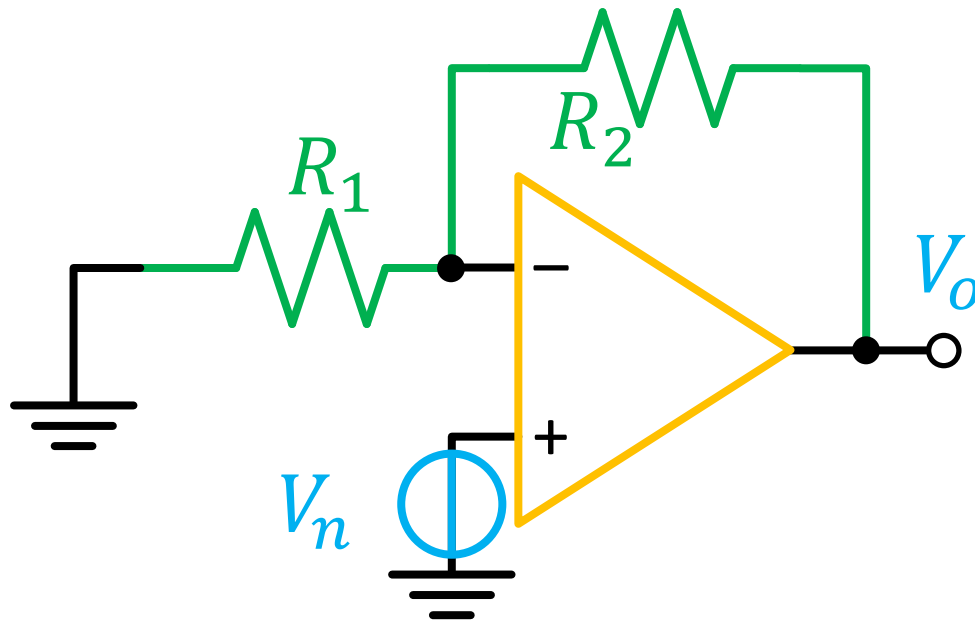

$$V_o = V_n \frac{R_1 + R_2}{R_1}$$

The pole added by the OA is always at $f_p = 100$ kHz (0dB frequency of G_{loop})
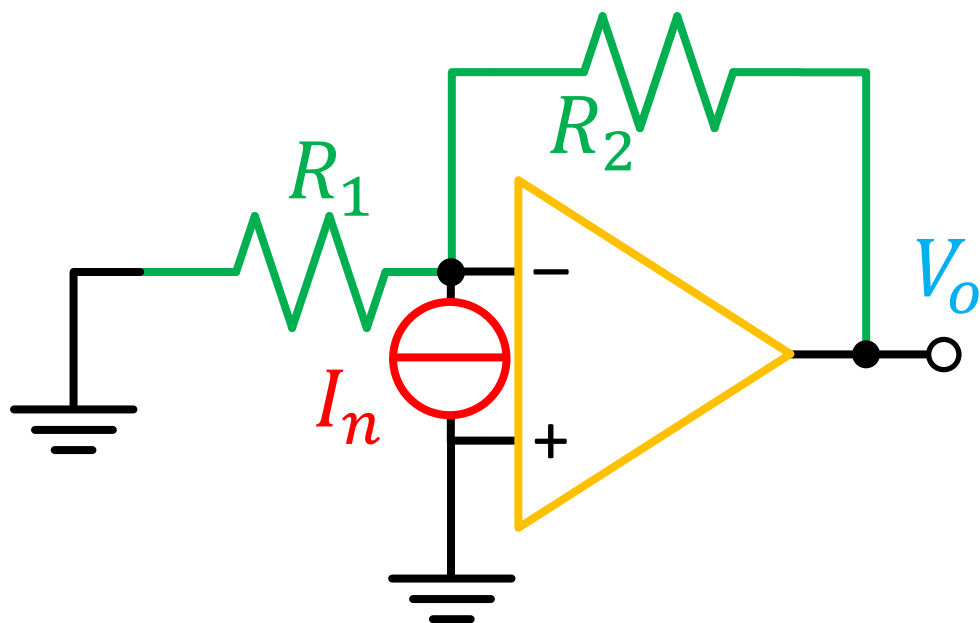
$$\overline{V_o^2} = S_V \left(\frac{R_1 + R_2}{R_1} \right)^2 \frac{\pi}{2} f_p$$
$$\approx 1.59 \times 10^{-7} \text{ V}^2$$



$$V_o = I_n R_2$$

$$\overline{V_o^2} = S_I R_2^2 \frac{\pi}{2} f_p$$
$$\approx 1.57 \times 10^{-7} \text{ V}^2$$

The total output noise is



$$\overline{V_o^2} = 2.59 \times 10^{-8} + 2.59 \times 10^{-10} + 1.59 \times 10^{-7} + 1.57 \times 10^{-7}$$

$$\approx 3.42 \times 10^{-7} \text{ V}^2 \Rightarrow \sqrt{\overline{V_o^2}} = 0.58 \text{ mV}$$



Current source shift theorem



12

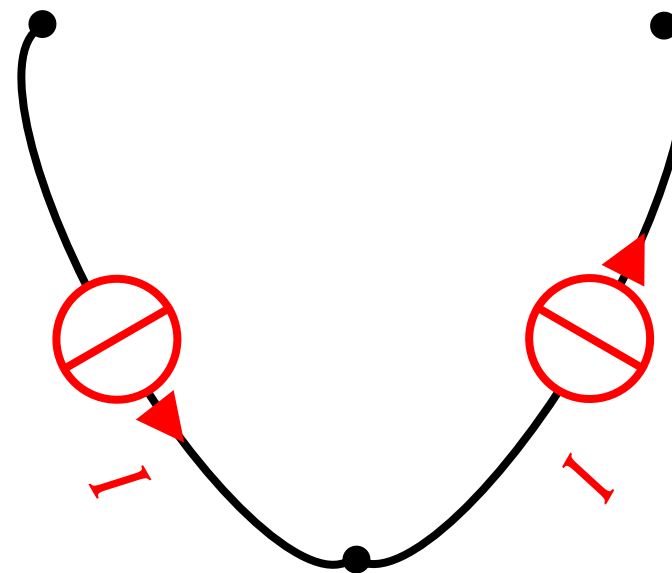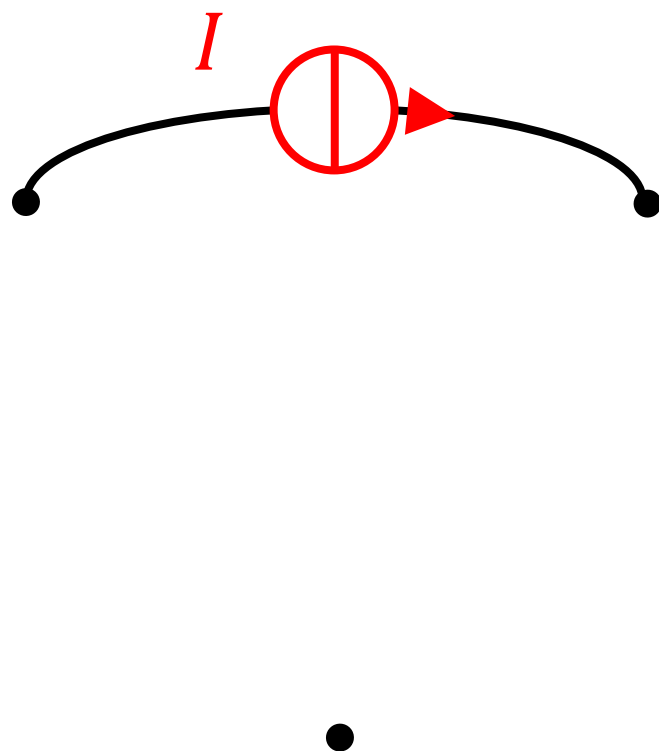



Example: R_2 noise


13

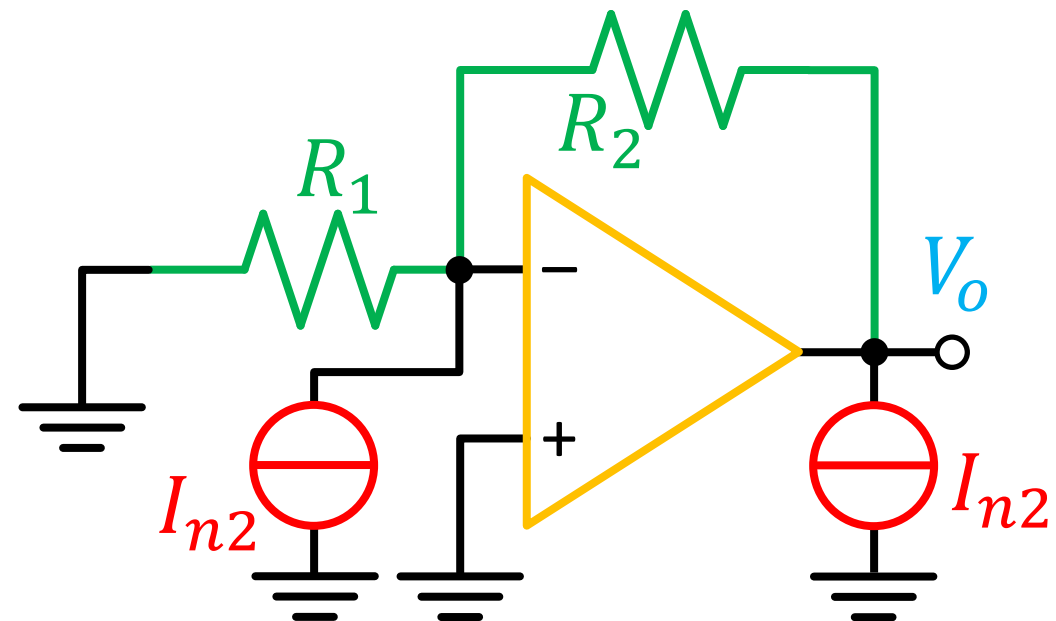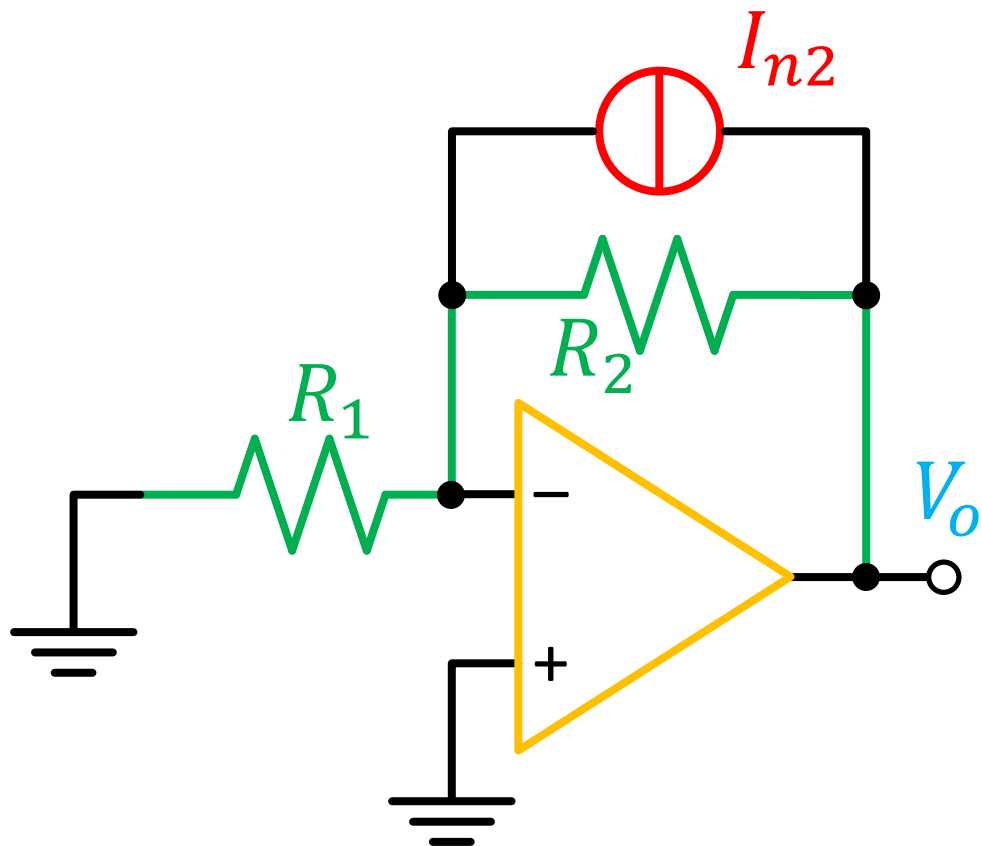



R_1, R_2 , OpAmp current noise

14

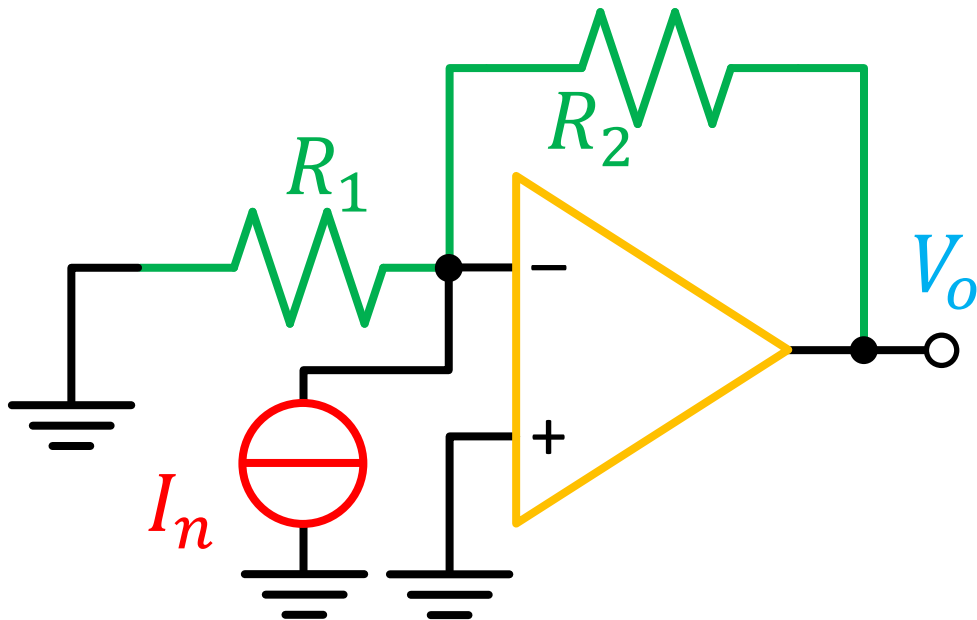


$$S_{I_n} = \frac{4k_B T}{R_1} + \frac{4k_B T}{R_2} + S_I$$
$$\overline{V_o^2} = S_{I_n} R_2^2 \frac{\pi}{2} f_p$$
$$\approx 1.83 \times 10^{-7} \text{ V}^2$$

Many contributions can be grouped into a single noise current source



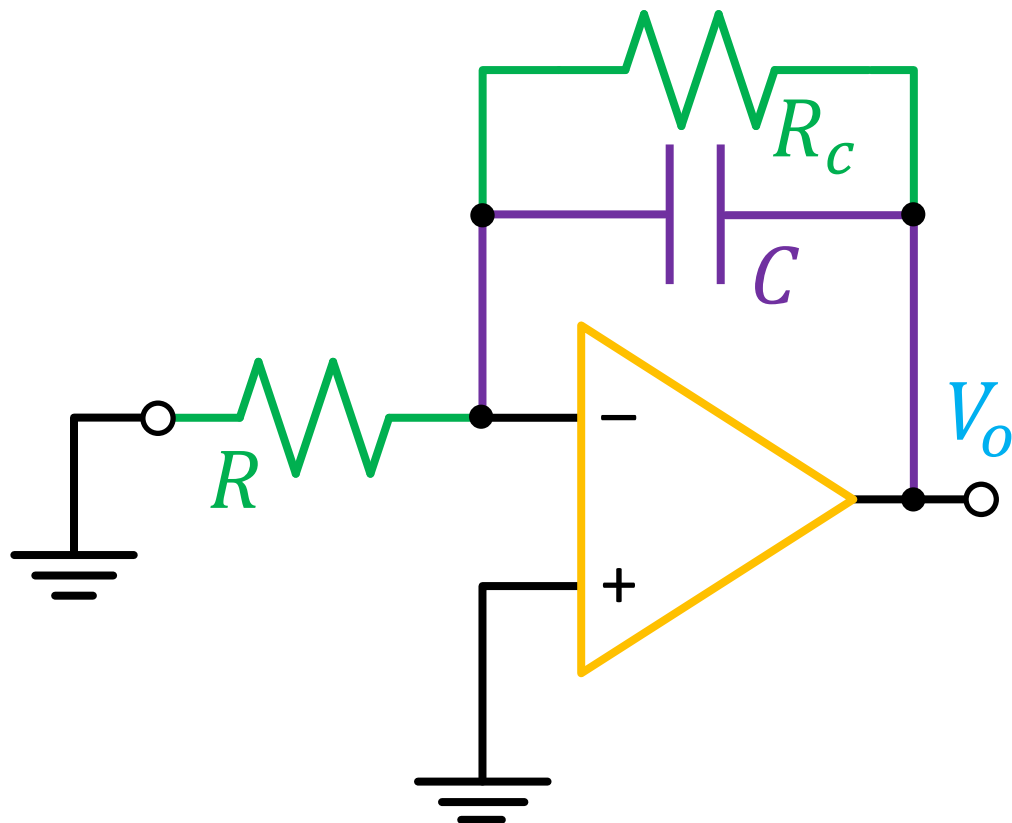- Inverting amplifier
- **Integrator**
- Differentiator
- Appendix: BP filter and white noise




- $R = 1 \text{ k}\Omega$, $R_c = 1 \text{ M}\Omega$
- $C = 160 \text{ nF}$
- $GBWP = 2 \text{ MHz}$
- $\sqrt{S_V} = 10 \text{ nV}/\sqrt{\text{Hz}}$
- $\sqrt{S_I} = 10 \text{ pA}/\sqrt{\text{Hz}}$

1. Find the total output noise



R, R_c , OpAmp current noise

17

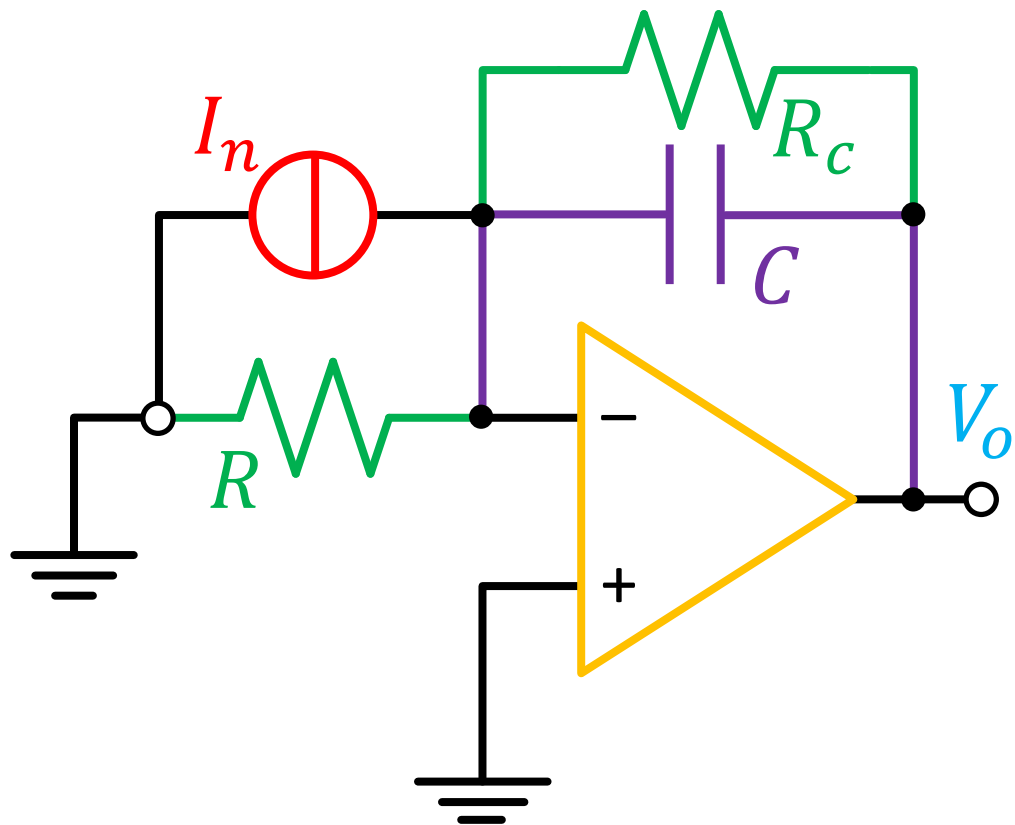

$$S_{I_n} = \frac{4k_B T}{R} + \frac{4k_B T}{R_c} + S_I$$


$$V_o = I_n \frac{R_c}{1 + sCR_c}$$

$$\overline{V_o^2} = S_{I_n} R_c^2 \frac{\pi}{2} \frac{1}{2\pi R_c C}$$
$$\approx 1.82 \times 10^{-10} \text{ V}^2$$



OpAmp voltage noise

18

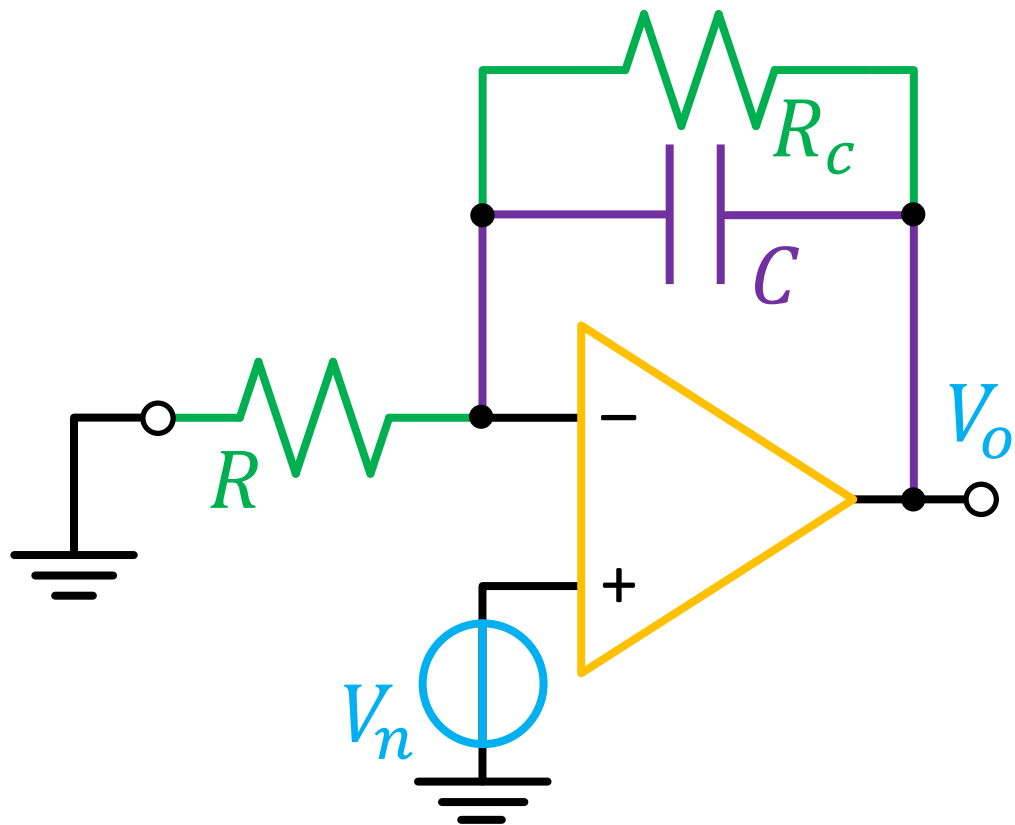


$$V_o = V_n \left(1 + \frac{R_c \parallel 1/sC}{R} \right)$$
$$= V_n \frac{R + R_c}{R} \left(\frac{1 + sC R \parallel R_c}{1 + sC R_c} \right)$$
$$\frac{V_o}{V_n} = G \frac{1 + s\tau_z}{1 + s\tau_{p1}}$$

$$G \approx 1000, f_{p1} = 1 \text{ Hz}, f_z = 1 \text{ kHz}$$



Closed-loop gain

19

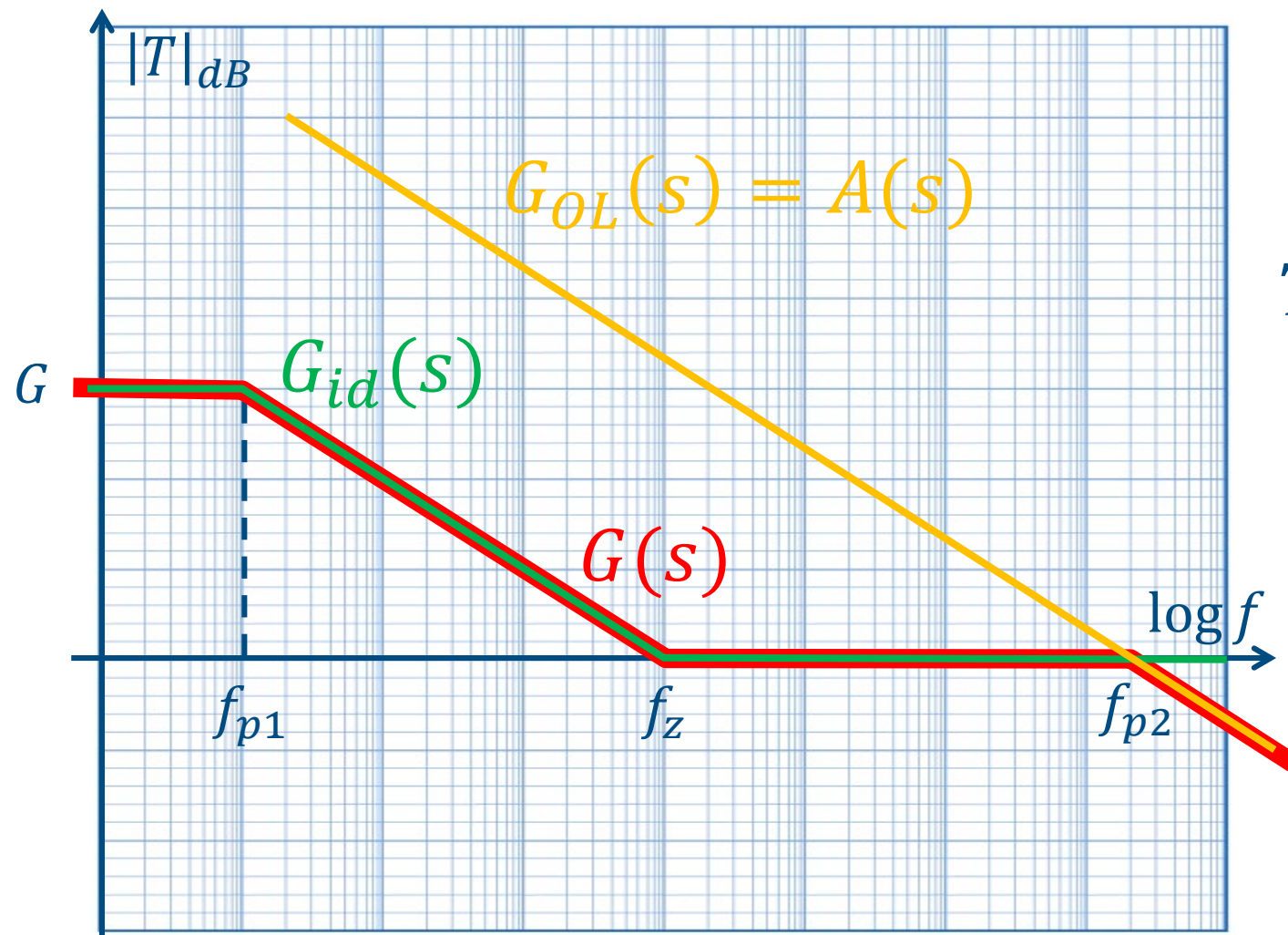

$$T(s) = \frac{G(1 + s\tau_z)}{(1 + s\tau_{p1})(1 + s\tau_{p2})}$$



Output noise – full calculations


20

$$\overline{V_o^2} = \int |T|^2 df = S_V G^2 \int \frac{(1 + \omega^2 \tau_z^2)}{(1 + \omega^2 \tau_{p1}^2)(1 + \omega^2 \tau_{p2}^2)} df$$
$$\int \frac{1 + \omega^2 \tau_z^2}{(1 + \omega^2 \tau_{p1}^2)(1 + \omega^2 \tau_{p2}^2)} df = \int \left(\frac{A}{1 + \omega^2 \tau_{p1}^2} + \frac{B}{1 + \omega^2 \tau_{p2}^2} \right) df$$
$$\begin{cases} A + B = 1 \\ A\tau_{p2}^2 + B\tau_{p1}^2 = \tau_z^2 \end{cases} \Rightarrow \begin{aligned} A &= \frac{\tau_{p1}^2 - \tau_z^2}{\tau_{p1}^2 - \tau_{p2}^2} \approx 1 \\ B &= \frac{\tau_z^2 - \tau_{p2}^2}{\tau_{p1}^2 - \tau_{p2}^2} \approx \left(\frac{\tau_z}{\tau_{p1}} \right)^2 \end{aligned}$$



Piecewise linear approximation

21

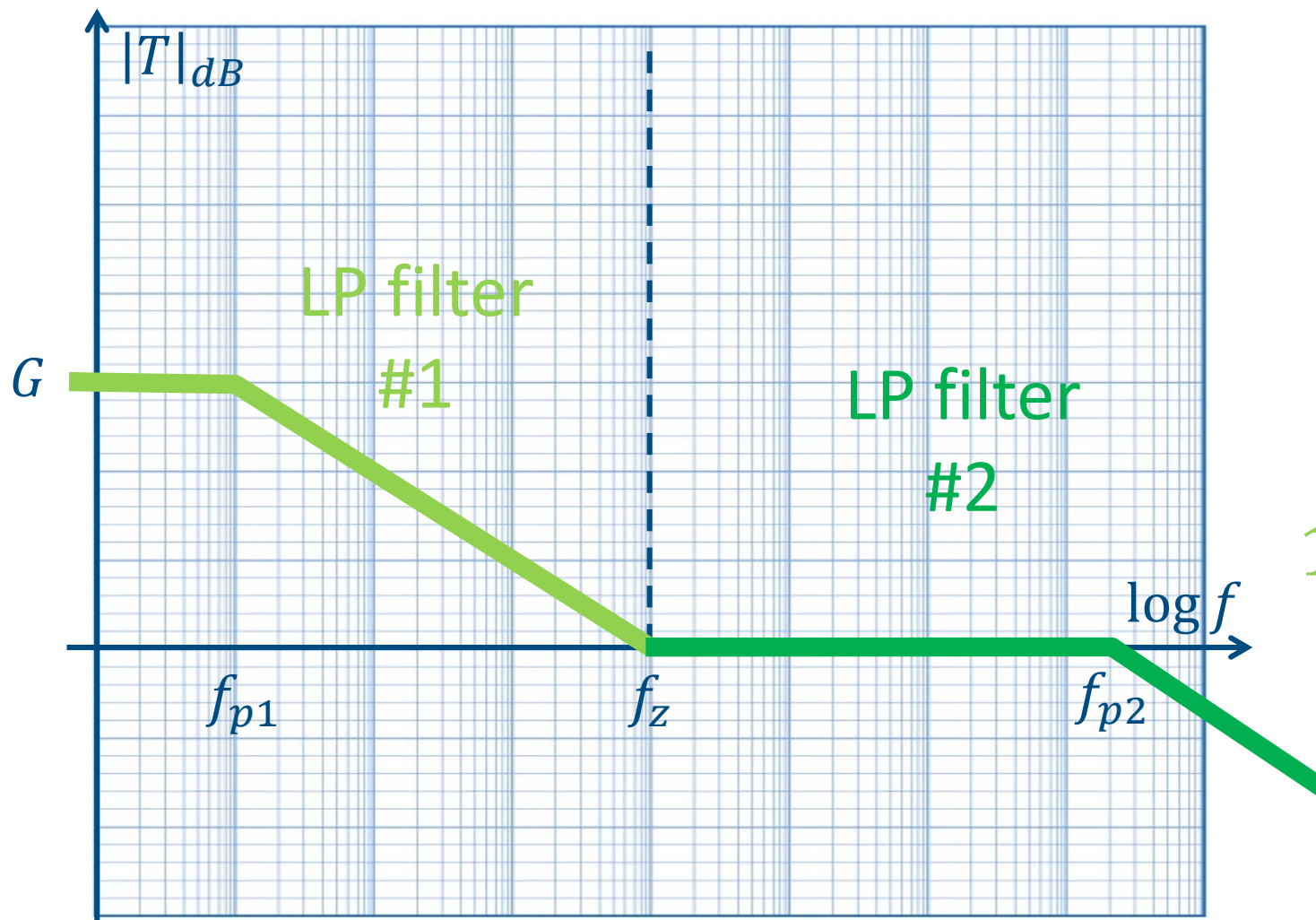

$$\int |T|^2 df \approx$$
$$G^2 \frac{\pi}{2} f_{p1} + \frac{\pi}{2} f_{p2} =$$
$$1.57 \times 10^6 + 3.14 \times 10^6$$



- The OpAmp voltage noise contribution becomes then

$$\overline{V_o^2} = S_V(1.57 + 3.14) \times 10^6 = 4.71 \times 10^{-10} \text{ V}^2$$


- The total noise is then

$$\overline{V_o^2} = 1.82 \times 10^{-10} + 4.71 \times 10^{-10} = 6.53 \times 10^{-10} \text{ V}^2 \Rightarrow$$

$$\sqrt{\overline{V_o^2}} \approx 26 \mu\text{V}$$



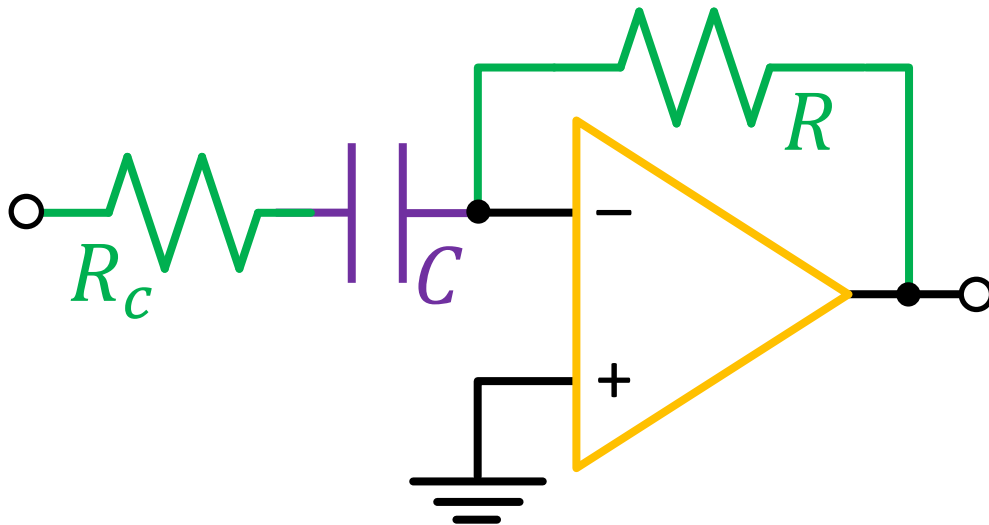- Inverting amplifier
- Integrator
- Differentiator
- Appendix: BP filter and white noise



- $R = 14.4 \text{ k}\Omega$, $R_c = 1.5 \text{ k}\Omega$
- $C = 10 \text{ nF}$
- $GBWP = 10 \text{ MHz}$
- $\sqrt{S_V} = 20 \text{ nV}/\sqrt{\text{Hz}}$
- $\sqrt{S_I} = 1 \text{ pA}/\sqrt{\text{Hz}}$

1. Find the total output noise




$$G_{loop} = -A(s) \frac{R_c + \frac{1}{sC}}{R + R_c + \frac{1}{sC}} = -A(s) \frac{1 + sCR_c}{1 + sC(R + R_c)}$$

$$f_p = 1 \text{ kHz}, f_z = 10.6 \text{ kHz}$$

Beyond the singularities, we have
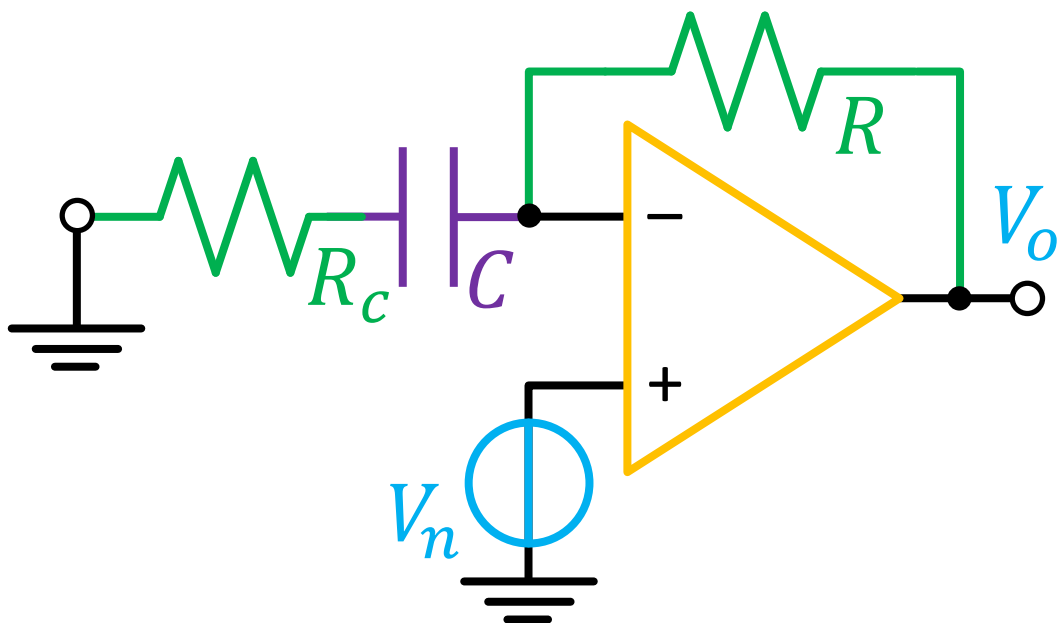
$$G_{loop} \approx -\frac{A_0}{s\tau} \frac{R_c}{R + R_c} \Rightarrow f_{0dB} = GBWP \frac{R_c}{R + R_c} = 0.94 \text{ MHz}$$




$$\begin{aligned} V_o &= V_n \left(1 + \frac{R}{R_c + 1/sC} \right) \\ &= V_n \frac{1 + sC(R + R_c)}{1 + sCR_c} \\ \frac{V_o}{V_n} &= \frac{1 + s\tau_z}{1 + s\tau_{p1}} \end{aligned}$$

$$f_{p1} = 10.6 \text{ kHz}, f_z = 1 \text{ kHz}$$



Closed-loop gain

27

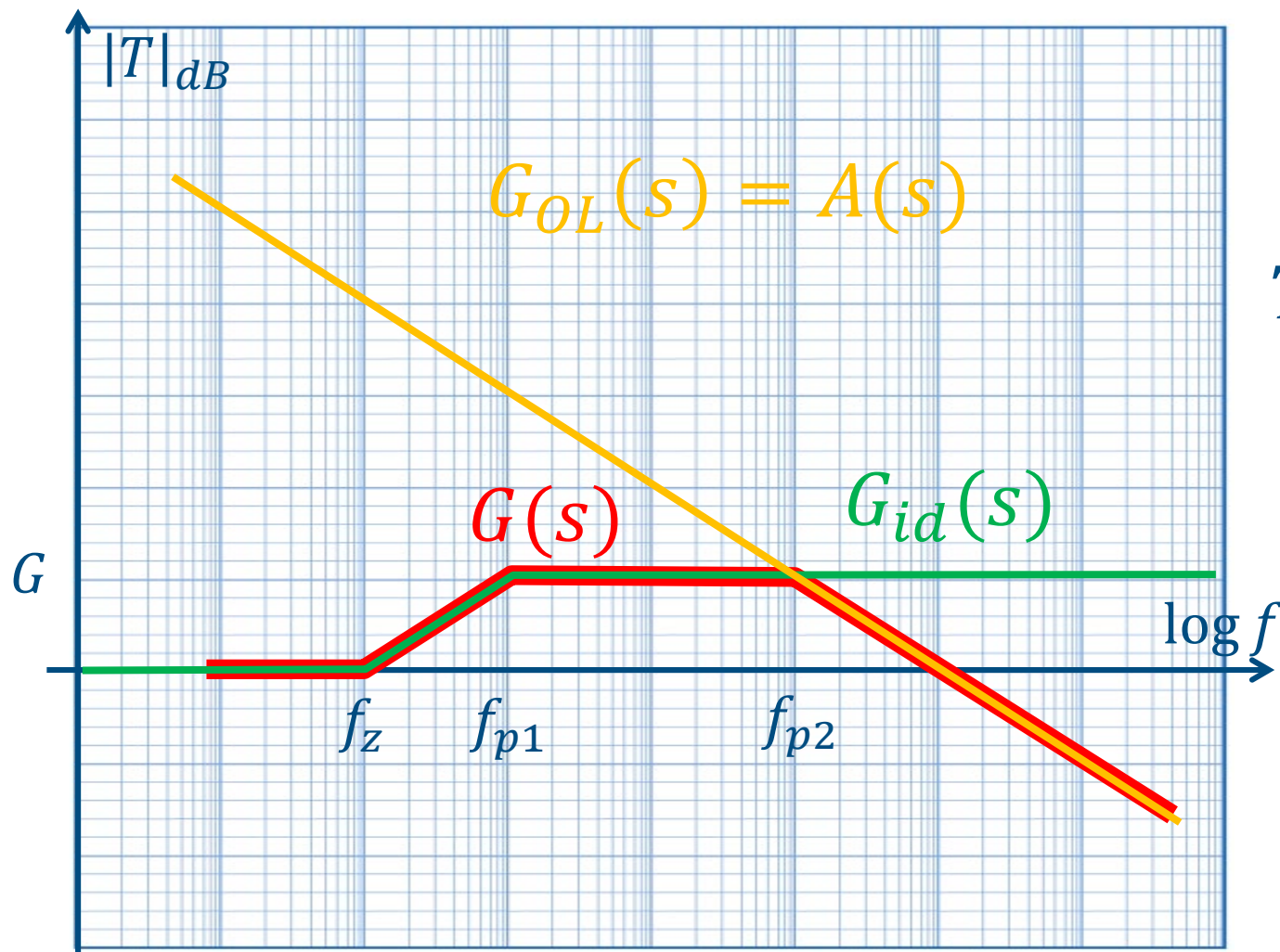

$$T(s) = \frac{1 + s\tau_z}{(1 + s\tau_{p1})(1 + s\tau_{p2})}$$



Output noise – full calculations

28


$$\overline{V_o^2} = \int |T|^2 df = \int \left(\frac{A}{1 + \omega^2 \tau_{p1}^2} + \frac{B}{1 + \omega^2 \tau_{p2}^2} \right) df$$

$$\left\{ \begin{array}{l} A + B = 1 \\ A\tau_{p2}^2 + B\tau_{p1}^2 = \tau_z^2 \end{array} \right. \Rightarrow \begin{array}{l} A = \frac{\tau_{p1}^2 - \tau_z^2}{\tau_{p1}^2 - \tau_{p2}^2} \approx - \left(\frac{\tau_z}{\tau_{p1}} \right)^2 = -G^2 \\ B = \frac{\tau_z^2 - \tau_{p2}^2}{\tau_{p1}^2 - \tau_{p2}^2} \approx \left(\frac{\tau_z}{\tau_{p1}} \right)^2 = G^2 \end{array}$$



Piecewise linear approximation

29

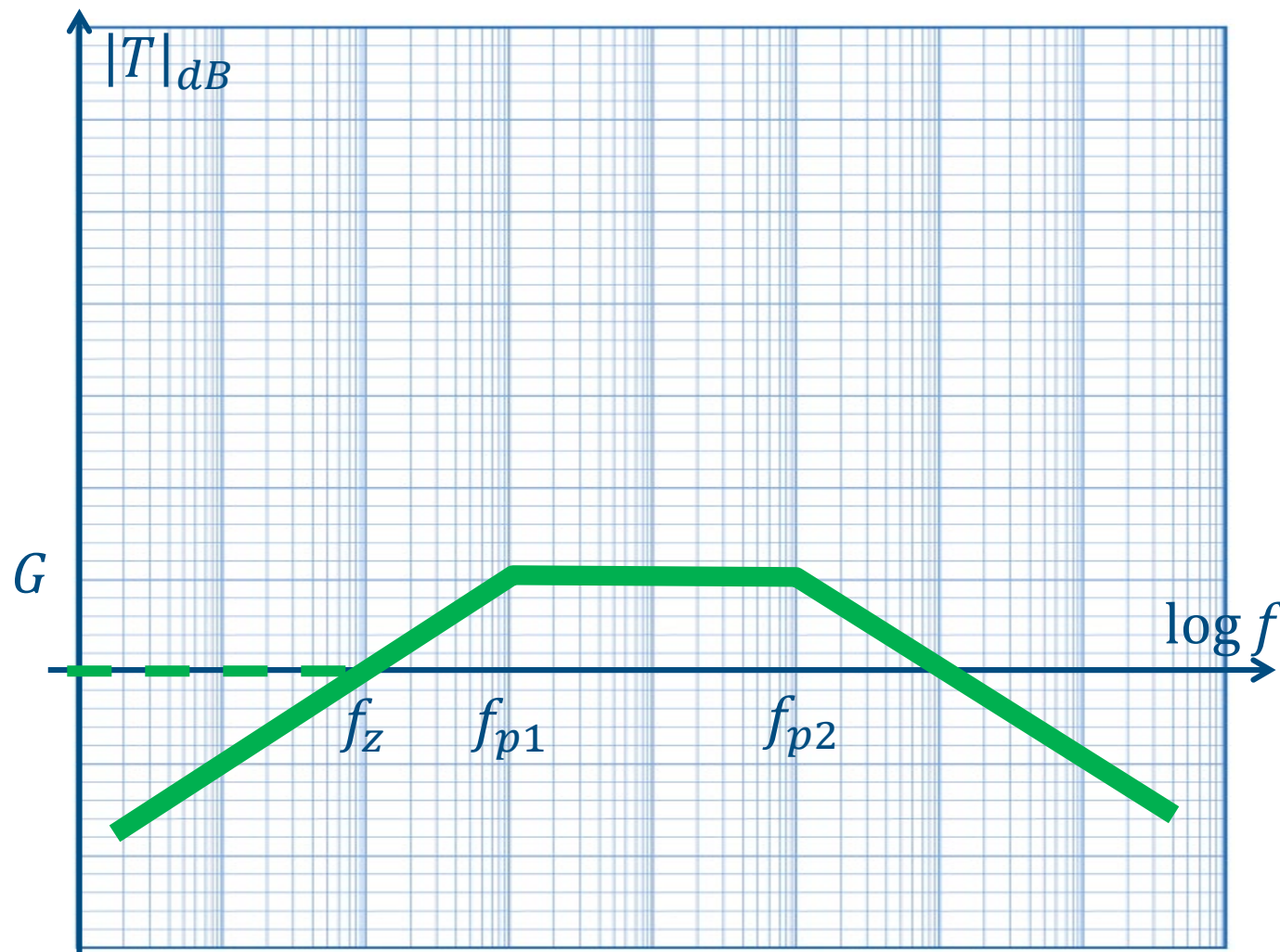

$$\int |T|^2 df \approx$$


$$G^2 \frac{\pi}{2} (f_{p2} - f_{p1}) = 1.64 \times 10^8$$

$$\overline{V_o^2} = 1.64 \times 10^8 S_V \\ = 6.56 \times 10^{-8} \text{ V}^2$$



OpAmp + R current noise

30

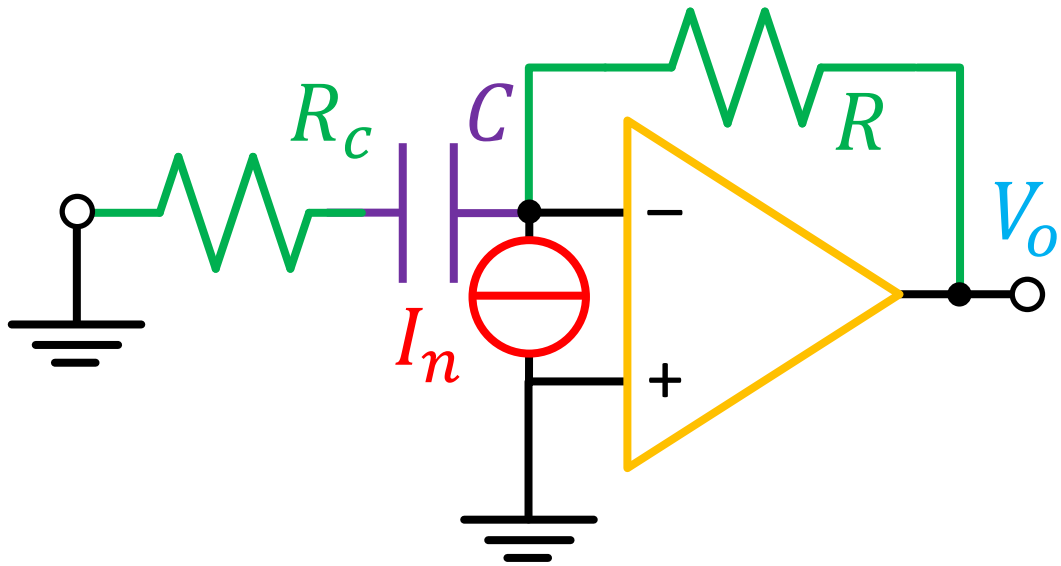

$$S_{I_n} = S_I + \frac{4k_B T}{R}$$
$$V_o = I_n R$$
$$\overline{V_o^2} = S_{I_n} R^2 \frac{\pi}{2} f_{0dB}$$
$$= 3.06 \times 10^{-10} \text{ V}^2$$



Transfer function is the same as the input

$$V_o = V_n \frac{sCR}{1 + sCR_c}$$

With the addition of the pole at f_{0dB} we have a BP filter with mid-band gain equal to $R/R_c = 9.6$

$$\overline{V_o^2} = S_{R_c} \left(\frac{R}{R_c} \right)^2 \frac{\pi}{2} (f_{0dB} - f_{p1}) = 2.14 \times 10^{-9} \text{ V}^2$$



The total noise is then

$$\begin{aligned}\overline{V_o^2} &= 6.56 \times 10^{-8} + 3.06 \times 10^{-10} + 2.14 \times 10^{-9} \\ &= 6.61 \times 10^{-8} \text{ V}^2 \Rightarrow \sqrt{\overline{V_o^2}} \approx 261 \mu\text{V}\end{aligned}$$



- Inverting amplifier
- Integrator
- Differentiator
- Appendix: BP filter and white noise



$$\begin{aligned} H(s) &= \frac{s\tau_L}{(1 + s\tau_L)(1 + s\tau_H)} \\ \overline{V_o^2} &= S_V \int_0^\infty \frac{(\omega\tau_L)^2}{(1 + \omega^2\tau_L^2)(1 + \omega^2\tau_H^2)} \frac{d\omega}{2\pi} \\ &= \frac{S_V}{2\pi} \frac{\tau_L^2}{\tau_H^2 - \tau_L^2} \int_0^\infty \left(\frac{1}{1 + \omega^2\tau_L^2} - \frac{1}{1 + \omega^2\tau_H^2} \right) d\omega = \frac{S_V}{2\pi} \frac{\tau_L^2}{\tau_H^2 - \tau_L^2} \left(\frac{\pi}{2\tau_L} - \frac{\pi}{2\tau_H} \right) \\ &= \frac{S_V}{4} \frac{\tau_L}{\tau_H(\tau_L + \tau_H)} = \frac{S_V}{4} \frac{1}{\tau_H(1 + \tau_H/\tau_L)} \approx \frac{S_V}{4} \frac{1}{\tau_H} \left(1 - \frac{\tau_H}{\tau_L} \right) = \frac{S_V}{4} \left(\frac{1}{\tau_H} - \frac{1}{\tau_L} \right) \\ &= S_V \frac{\pi}{2} (f_H - f_L) \end{aligned}$$



-3dB bandwidth and noise

36

- The maximum of $|H(j\omega)| = \frac{\omega\tau_L}{|1 - \omega^2\tau_L\tau_H + j\omega(\tau_L + \tau_H)|}$ is at

$$\omega_p = \frac{1}{\sqrt{\tau_L\tau_H}} \quad |H(j\omega_p)| = \frac{\tau_L}{\tau_L + \tau_H}$$

- The -3dB BW is given by

$$\frac{\omega\tau_L}{|1 - \omega^2\tau_L\tau_H + j\omega(\tau_L + \tau_H)|} = \frac{1}{\sqrt{2}} \frac{\tau_L}{\tau_L + \tau_H}$$

$$(1 - \omega^2\tau_L\tau_H)^2 + \omega^2(\tau_L + \tau_H)^2 = 2\omega^2(\tau_L + \tau_H)^2 \Rightarrow 1 - \omega^2\tau_L\tau_H = \pm\omega(\tau_L + \tau_H) \Rightarrow \omega^2 \pm \omega \frac{\tau_L + \tau_H}{\tau_L\tau_H} - \frac{1}{\tau_L\tau_H} = 0$$

- We pick only the positive solutions:

$$\omega_L = -\frac{\tau_L + \tau_H}{2\tau_L\tau_H} + \sqrt{\left(\frac{\tau_L + \tau_H}{2\tau_L\tau_H}\right)^2 + \frac{1}{\tau_L\tau_H}} \quad \omega_H = \frac{\tau_L + \tau_H}{2\tau_L\tau_H} + \sqrt{\left(\frac{\tau_L + \tau_H}{2\tau_L\tau_H}\right)^2 + \frac{1}{\tau_L\tau_H}}$$

$$BW = \frac{\omega_H - \omega_L}{2\pi} = \frac{1}{2\pi} \frac{\tau_L + \tau_H}{\tau_L\tau_H} \quad \overline{V_o^2} = S_V |H(f_p)|^2 \frac{\pi}{2} BW = S_V \left(\frac{\tau_L}{\tau_L + \tau_H}\right)^2 \frac{\tau_L + \tau_H}{4\tau_L\tau_H} = \frac{S_V}{4} \frac{\tau_L}{\tau_H(\tau_L + \tau_H)}$$



General case: the quality factor

37

- The second-order polynomials describing two poles (or zeros) can be written as

$$H(s) = 1 + \frac{s}{\omega_p Q} + \frac{s^2}{\omega_p^2}$$

- Q is the **quality factor** of the poles:
 - $0 < Q < 0.5 \Rightarrow$ real and separated poles
 - $Q = 0.5 \Rightarrow$ real and coincident poles at ω_p
 - $Q > 0.5 \Rightarrow$ complex conjugated poles at ω_p



- Consider a BP filter

$$H(s) = \frac{s/\omega_p}{1 + \frac{s}{\omega_p Q} + \frac{s^2}{\omega_p^2}}$$

- The maximum of $|H(j\omega)|$ is at $\omega = \omega_p$, where $|H(j\omega_p)| = Q$
- The -3dB bandwidth (for both real and complex poles) is

$$BW = \frac{f_p}{Q}$$

- The output noise is

$$\overline{V_o^2} = S_V \frac{\pi}{2} BW |H(j\omega_p)|^2 = S_V \frac{\pi}{2} BW Q^2 = S_V \frac{\pi}{2} Q f_p$$