



Electronics – 96032

 POLITECNICO DI MILANO



Signals and Noise in LTI Systems and OpAmps

Alessandro Spinelli

Phone: (02 2399) 4001

alessandro.spinelli@polimi.it

spinelli.faculty.polimi.it



Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes



Purpose of the lesson

3

- Up to now we have seen Amplifiers and Sensors and we know how to deal with the problems **from the viewpoint of the signal**
- In reality, **noise** is always present and can affect the precision or even overshadow the signal
- In the final part of the class, we will discuss techniques for noise reduction. Before doing this, however, we need to learn:
 - how to mathematically describe noise (lesson before the previous);
 - what are the origins of noise (previous lesson);
 - **how circuits respond to noise (this lesson);**



- LTI systems response to signal and noise
- Noise in OAs
- Feedback and noise



- Linearity

- If input $x_i(t)$ produces output $y_i(t)$, then

$$\sum_k c_k x_k(t) \Rightarrow \sum_k c_k y_k(t)$$

$$\int c(\tau) x(t, \tau) d\tau \Rightarrow \int c(\tau) y(t, \tau) d\tau$$


- Time invariance

$$x(t + T) \Rightarrow y(t + T)$$



Impulse response

6

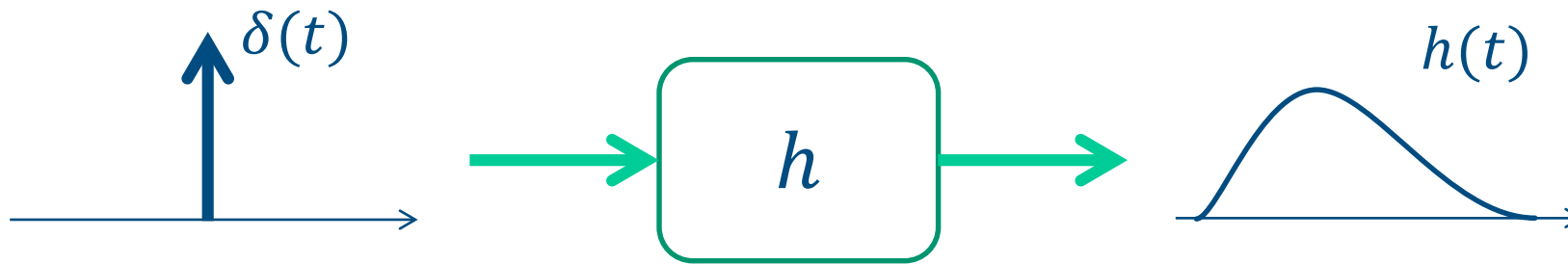

LTI systems are wholly characterized by their impulse response,
 $h(t)$



The “sifting” principle



7

- We consider an approximated δ function (with unit area), δ_Δ
- We approximate a generic signal $x(t)$ as

$$x_\Delta(t) = \sum_k x(k\Delta) \delta_\Delta(t - k\Delta)\Delta$$

- For $\Delta \rightarrow 0$ we have
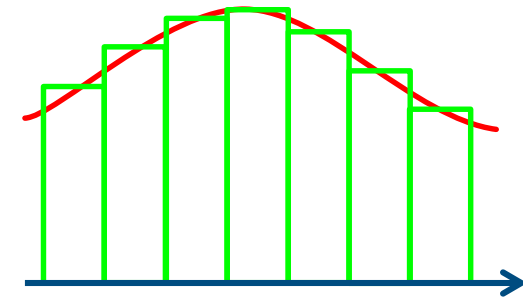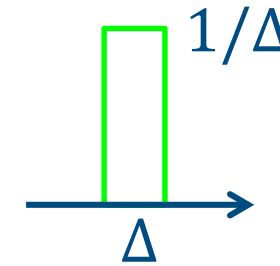
$$\lim_{\Delta \rightarrow 0} x_\Delta(t) = \int x(\tau) \delta(t - \tau) d\tau = x(t)$$





- The LTI output to x_Δ is the superposition of the responses to $\delta_\Delta(t - k\Delta)$, $h_\Delta(t - k\Delta)$

$$y_\Delta(t) = \sum_k x(k\Delta) h_\Delta(t - k\Delta) \Delta$$

- For $\Delta \rightarrow 0$ we have


$$y(t) = \lim_{\Delta \rightarrow 0} y_\Delta(t) = \int x(\tau) h(t - \tau) d\tau = x(t) * h(t)$$

Weighting function
of the filter



Weighting function

9

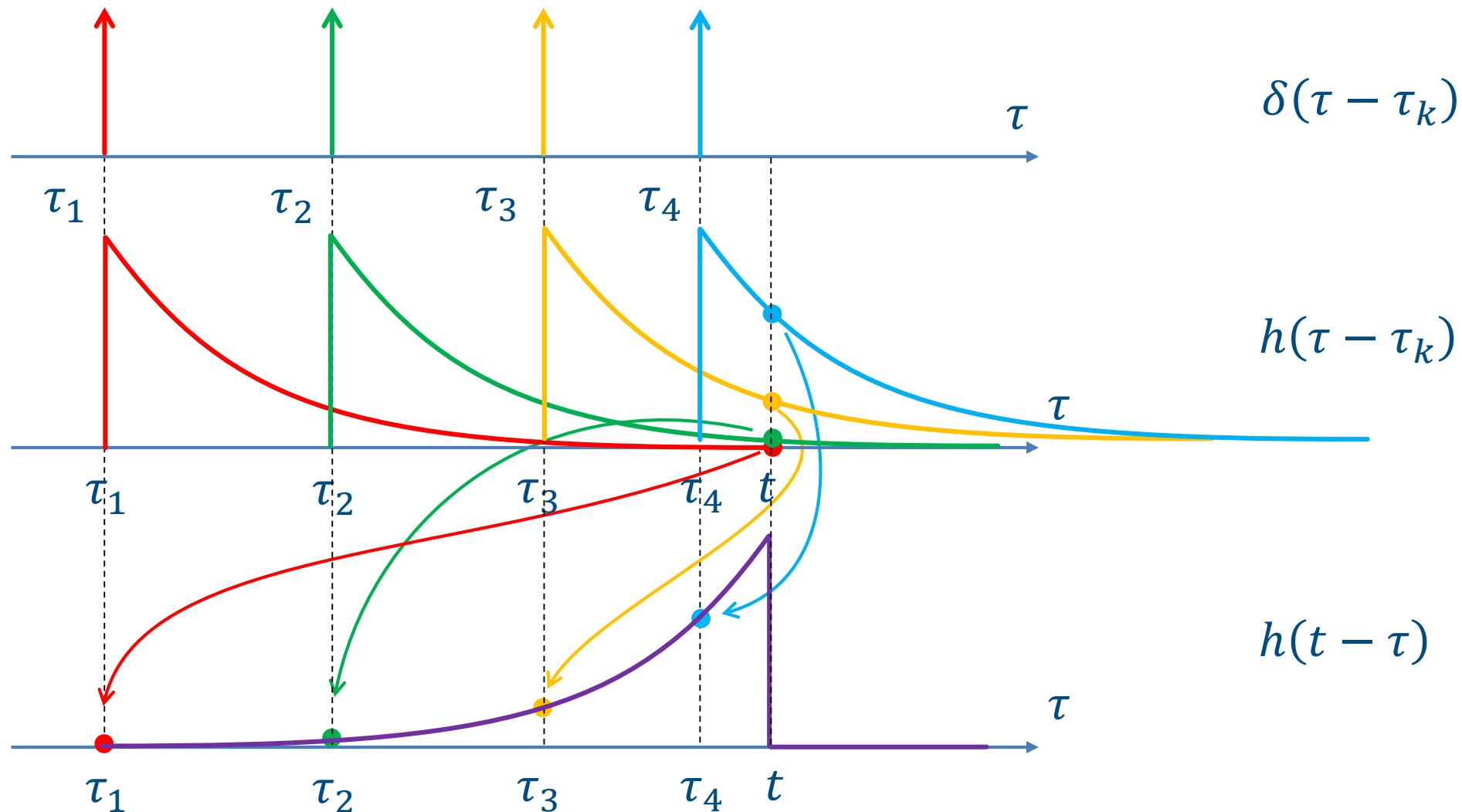



$$\begin{aligned} R_{yy}(t_1, t_2) &= \overline{y(t_1)y(t_2)} = \overline{\iint x(\alpha)h(t_1 - \alpha) x(\beta)h(t_2 - \beta) d\alpha d\beta} \\ &= \iint R_{xx}(\alpha, \beta)h(t_1 - \alpha)h(t_2 - \beta)d\alpha d\beta \\ &= \int h(t_2 - \beta)d\beta \int R_{xx}(\alpha, \beta)h(t_1 - \alpha)d\alpha = \int h(t_2 - \beta)R_{xx}(t_1, \beta) * h(t_1)d\beta \\ &= \int R_{xx}(t_1, \beta)h(t_2 - \beta)d\beta * h(t_1) = R_{xx}(t_1, t_2) * h(t_2) * h(t_1) \end{aligned}$$



$$R_{yy}(\tau) = \overline{y(t)y(t+\tau)} = \iint R_{xx}(\beta - \alpha)h(t - \alpha)h(t + \tau - \beta)d\alpha d\beta$$

$$= \iint R_{xx}(\gamma)h(t - \alpha)h(t + \tau - \gamma - \alpha)d\alpha d\gamma$$

$$= \int R_{xx}(\gamma)d\gamma \int h(t - \alpha)h(t - \alpha + \tau - \gamma)d\alpha = \int R_{xx}(\gamma)d\gamma \int h(z)h(z + \tau - \gamma)dz$$

$$= \int R_{xx}(\gamma)k_{hh}(\tau - \gamma)d\gamma = R_{xx}(\tau) * k_{hh}(\tau)$$



- For stationary input noise

$$\overline{n_y^2} = R_{yy}(0) = \int R_{xx}(\gamma) k_{hh}(\gamma) d\gamma$$

- If the input noise is non-stationary, so is the output, and there is no simple expression for it

$$\overline{n_y^2(t)} = \iint R_{xx}(\alpha, \beta) h(t - \alpha) h(t - \beta) d\alpha d\beta$$



- For the signal we have

$$Y(f) = X(f)H(f)$$

- For the (stationary) noise:

$$S_y(f) = S_x(f)|H(f)|^2$$

$$\overline{n_y^2} = \int S_x(f)|H(f)|^2 df$$

Also from the expression
in the time domain via
Parseval theorem



The case of white stationary noise

14

- Time domain: $R_{xx}(\tau) = \lambda\delta(\tau)$

$$R_{yy}(\tau) = R_{xx}(\tau) * k_{hh}(\tau) = \lambda k_{hh}(\tau)$$

$$\overline{n_y^2} = R_{yy}(0) = \lambda k_{hh}(0) = \lambda \int h^2(t) dt$$


- Frequency domain: $S_x(f) = \lambda$

$$S_y(f) = S_x(f)|H(f)|^2 = \lambda|H(f)|^2$$


$$\overline{n_y^2} = \int S_x(f) df = \lambda \int |H(f)|^2 df$$



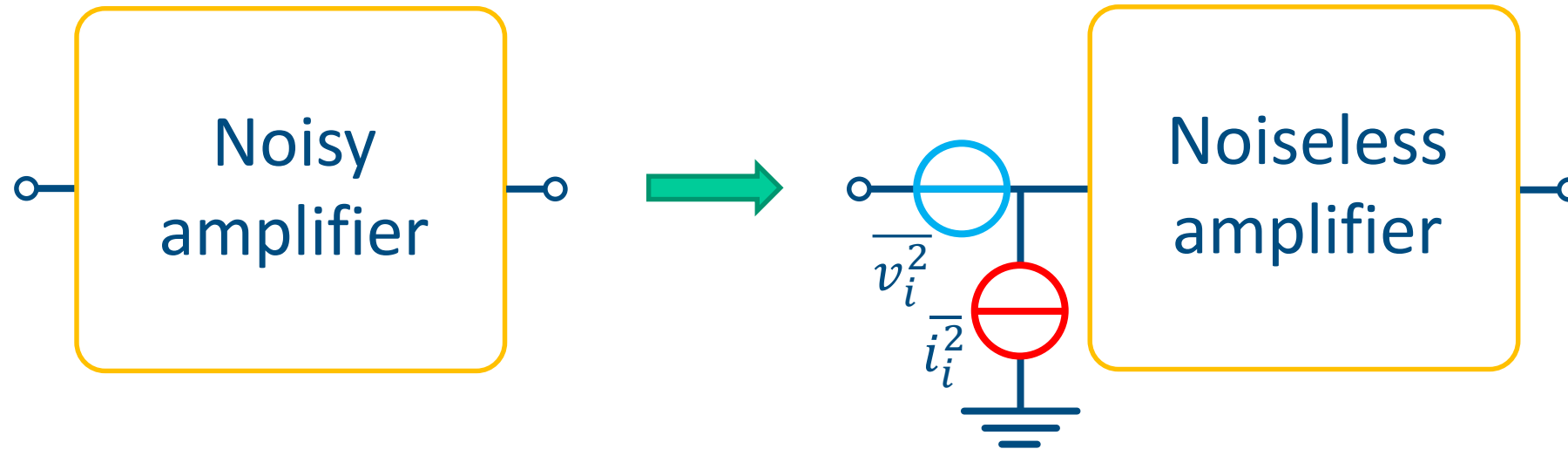- LTI system response to signal and noise
- Noise in OAs
- Feedback and noise



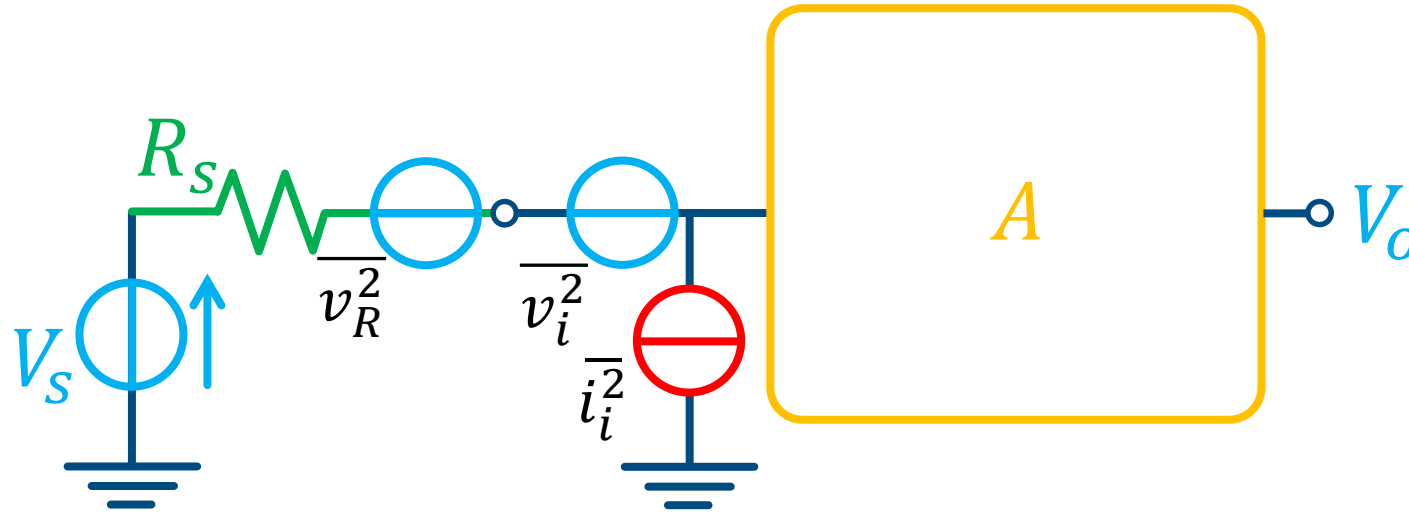- Equivalent input noise voltage and current are used to get non-zero output noise for every input condition
- Correlation between the sources is neglected



We consider a sinusoidal signal and a frequency interval Δf :

$$V_o = AV_s \cos \omega t$$

$$\overline{V_o^2} = S_{V_o} \Delta f = (S_{V_R} + S_V + S_I R_s^2) A^2 \Delta f$$




S/N ratio


18

$$\left(\frac{S}{N}\right)_{out} = \frac{\text{signal amplitude}}{\text{noise rms amplitude}} = \frac{V_o}{\sqrt{V_o^2}}$$


$S/N = 0.1$

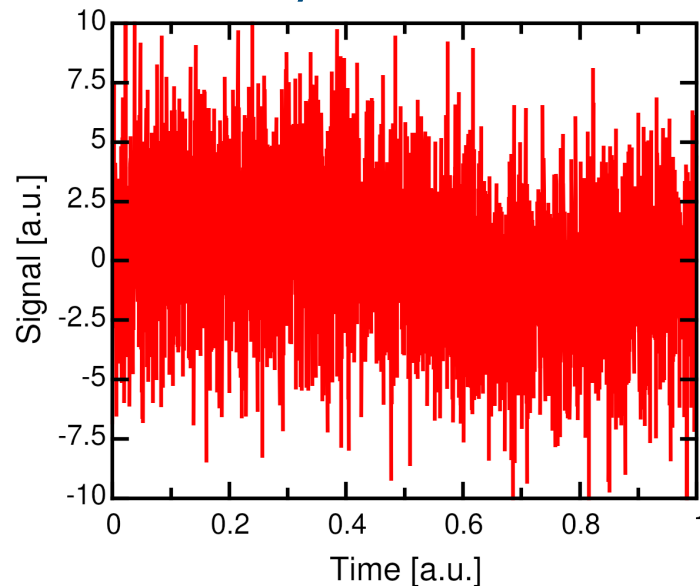

$S/N = 1$

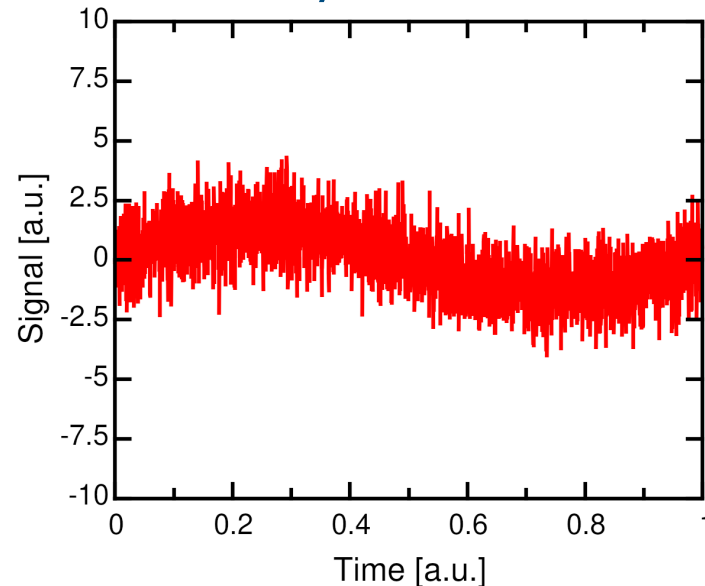

$S/N = 10$

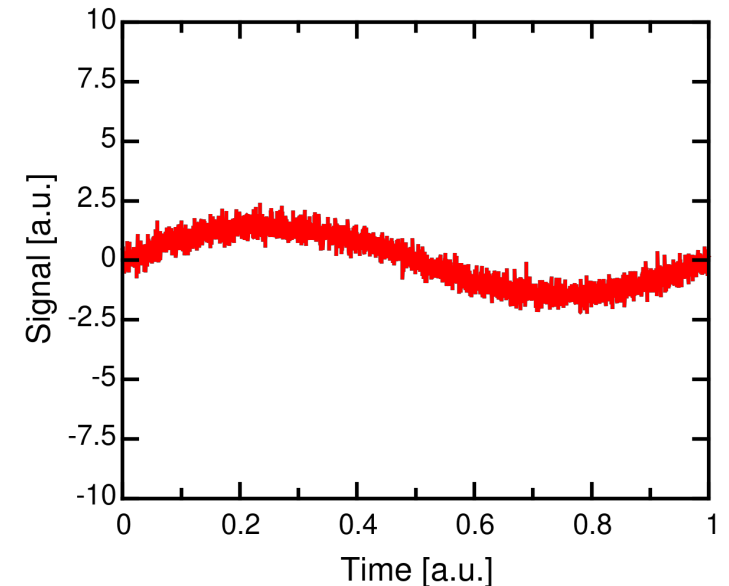



$$\left(\frac{S}{N}\right)_{out}^2 = \frac{V_S^2}{(S_{V_R} + S_V + S_I R_S^2) \Delta f}$$
$$\left(\frac{S}{N}\right)_{in}^2 = \frac{V_S^2}{S_{V_R} \Delta f}$$

S/N is lower at the amplifier output, because of the noise of the amplifier itself



Noise factor $F = \frac{\left(\frac{S}{N}\right)_{in}^2}{\left(\frac{S}{N}\right)_{out}^2} = 1 + \frac{S_V(f) + S_I(f)R_S^2}{S_{V_R}}$

Amplifier noise



Source noise $(4k_BTR_S)$

- F is minimum for $R_{S,opt}^2 = \frac{S_V(f)}{S_I(f)}$

- The noise figure is commonly used:

$$NF = 10 \log_{10} F$$

(very useful in RF applications)

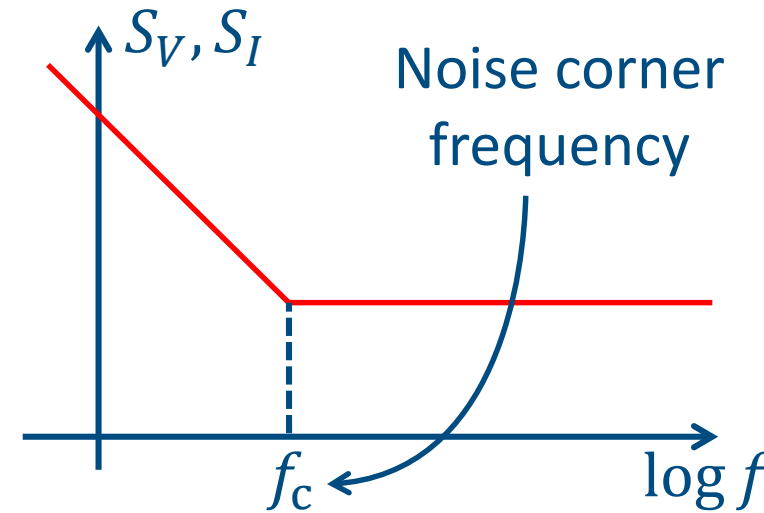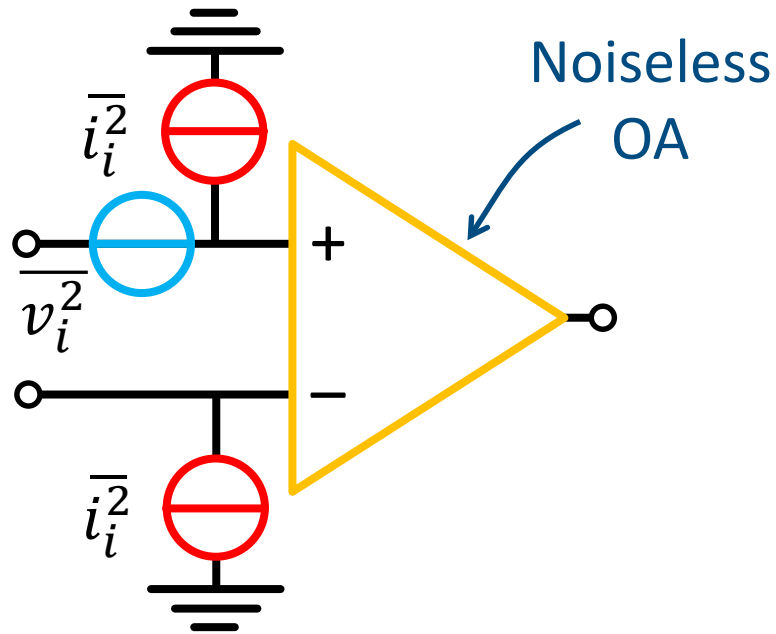

- Noise is referred to the input via the **equivalent input noise voltage and currents**
- All contain white and flicker components




- Voltage noise (white component)
 - BJT: 1 to 10 – 20 nV/ $\sqrt{\text{Hz}}$
 - JFET/MOS: usually higher, 20 – 30 nV/ $\sqrt{\text{Hz}}$
- Current noise (white component)
 - BJT: a few pA/ $\sqrt{\text{Hz}}$
 - JFET: a few fA/ $\sqrt{\text{Hz}}$; can be even less for CMOS
- Noise corner frequency
 - BJT/JFET: 1 – 100 Hz
 - MOS: a few kHz or even much higher, but improving (can find some in the 50 Hz range)




Input noise voltage PSD


23

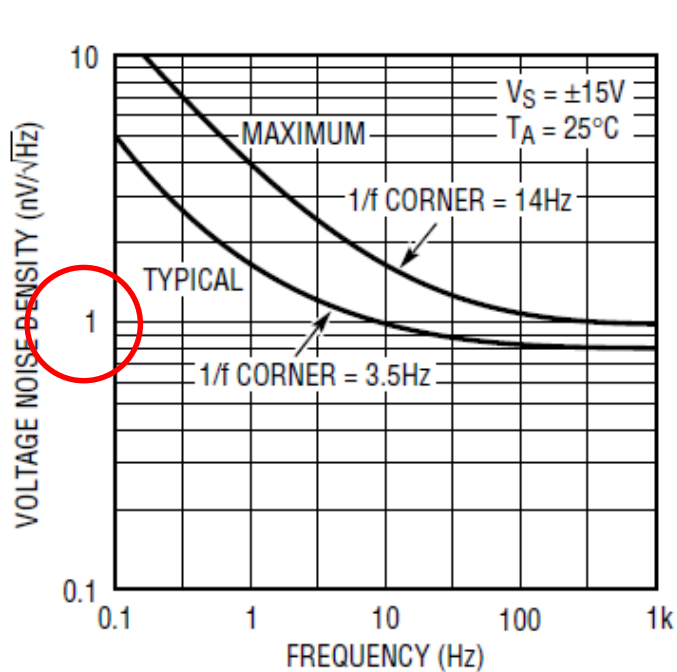

BJT

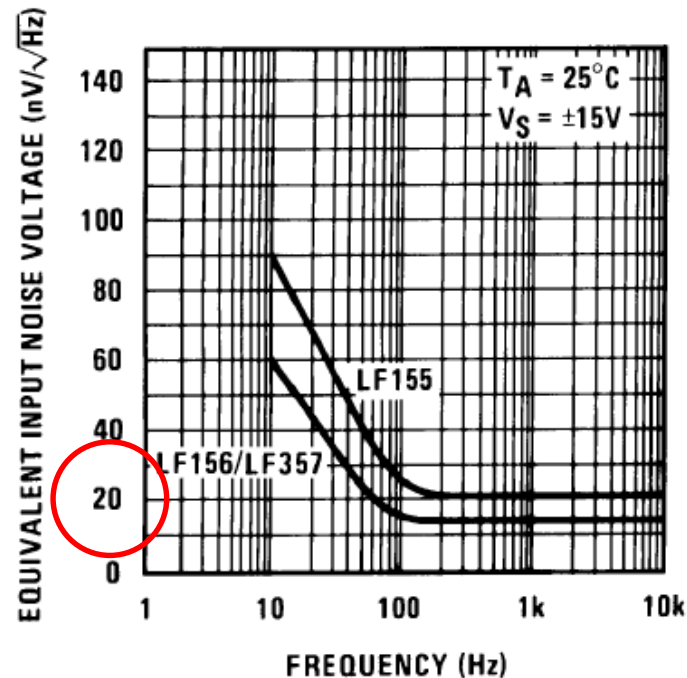

JFET

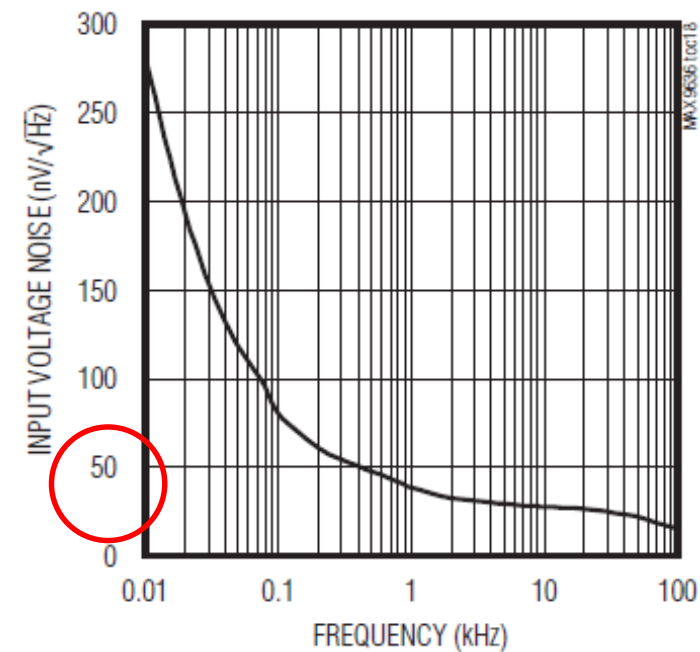


CMOS




Input noise current PSD


24

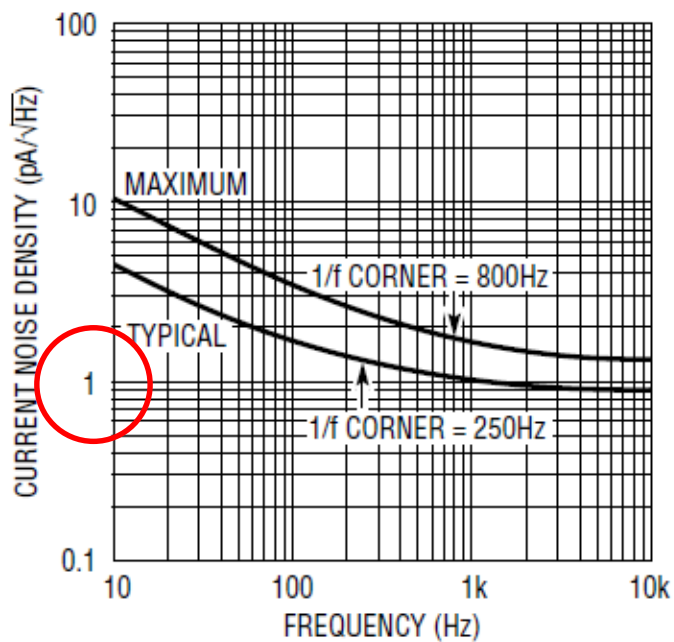

BJT

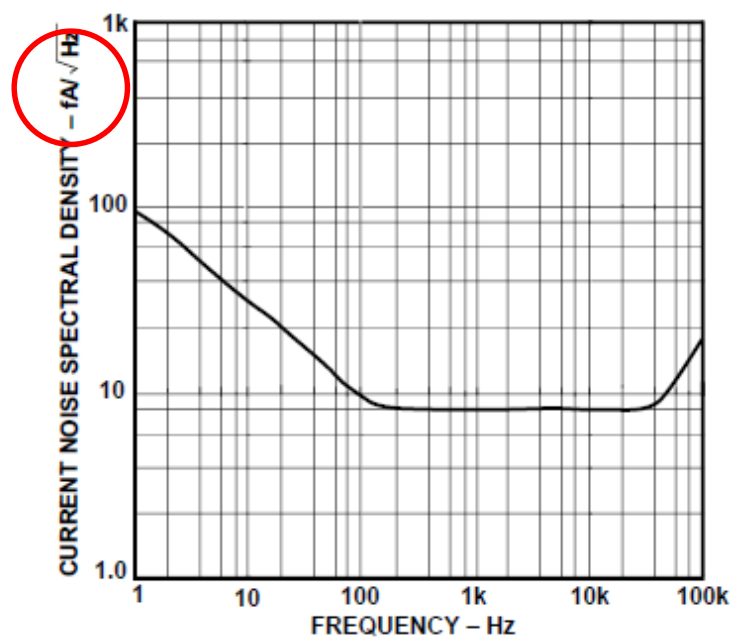

JFET

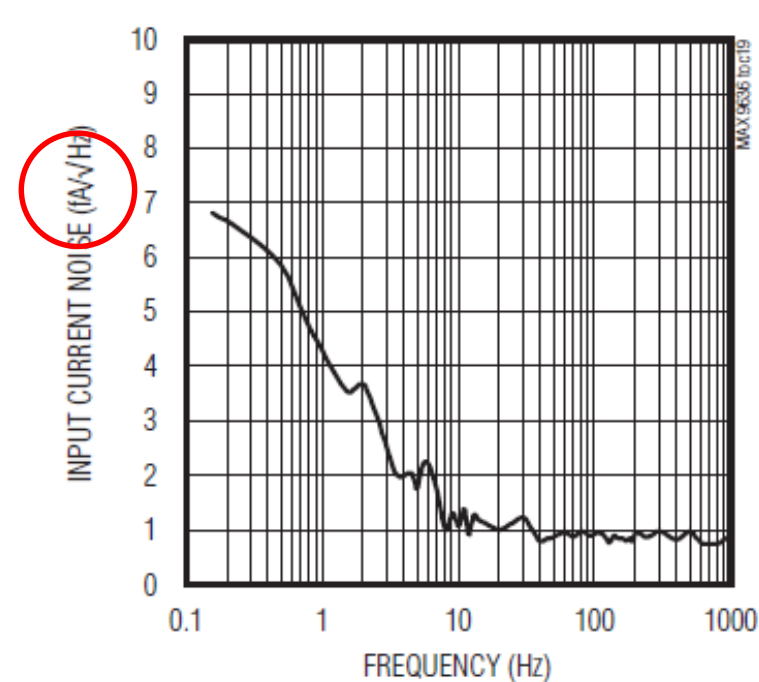


CMOS



OA comparison

25

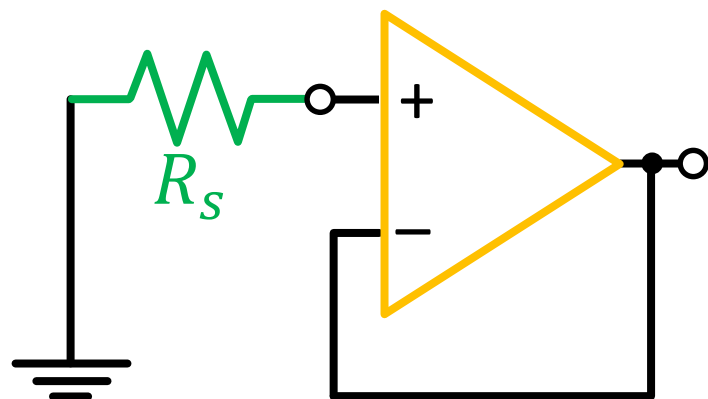

$$S_{V_o} = S_V + S_I R_S^2 + 4k_B T R_S$$

From [1]



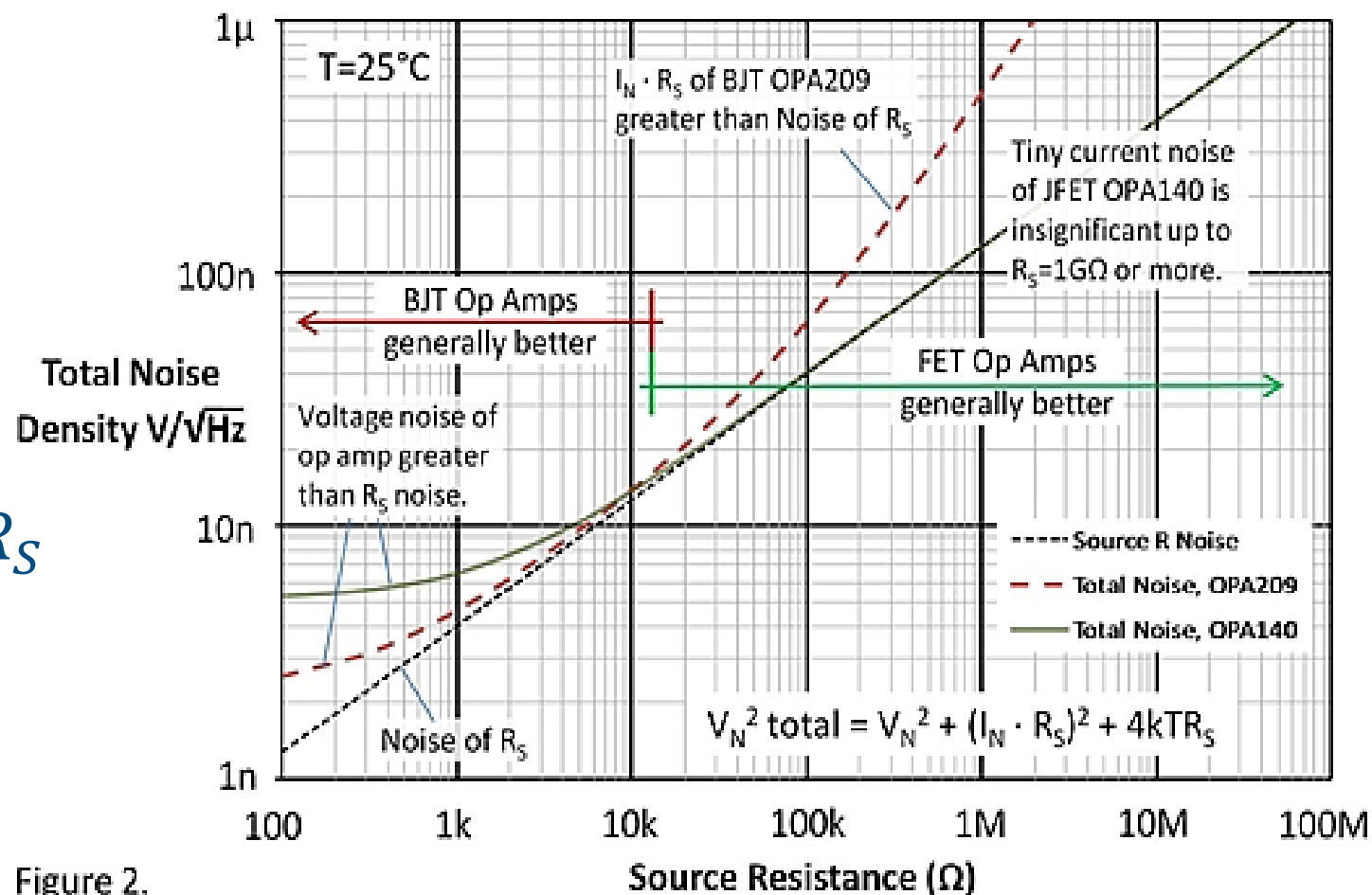


Figure 2.

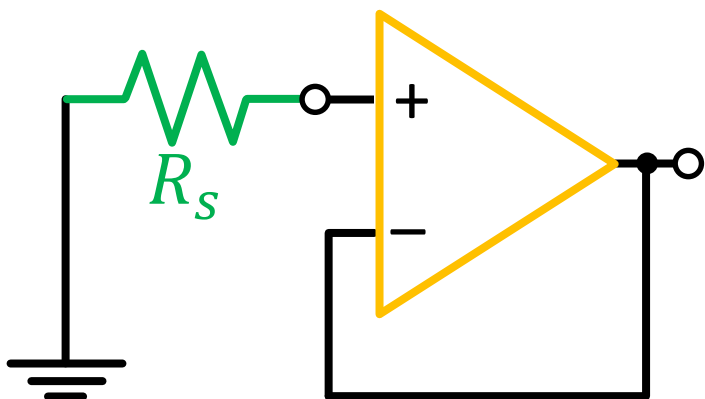

$$S_{V_o} = S_V + S_I R_S^2 + 4k_B T R_S$$

From [2]

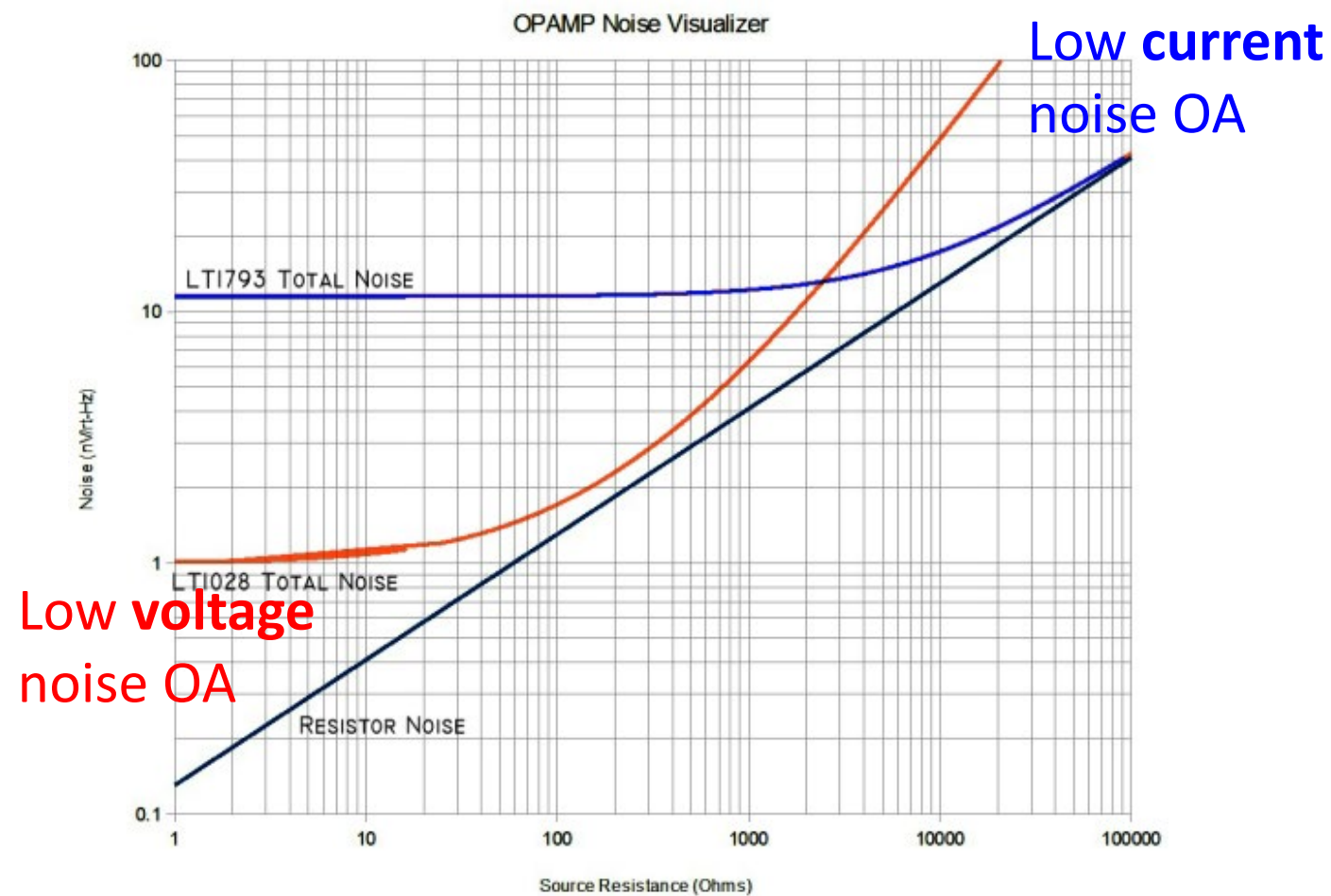




- LTI system response to signal and noise
- Noise in OAs
- Feedback and noise



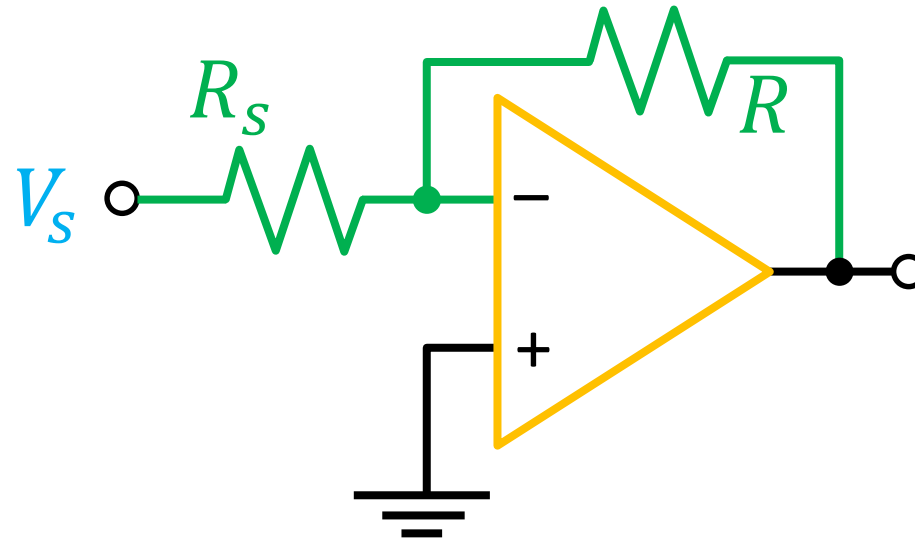
- We want to assess the effect of negative feedback on the noise performance, measured via F or S/N
- We consider a simple inverting amplifier example:





F – open-loop case

29

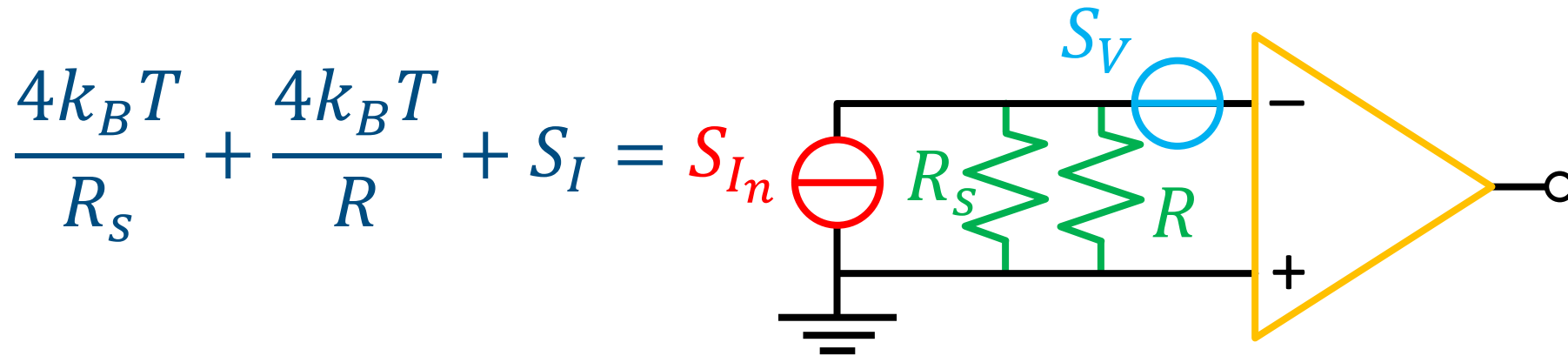


$$S_{V_o} = (S_{I_n} (R_s \parallel R)^2 + S_V) |A(s)|^2 \quad S_{V_o}^{source} = \frac{4k_B T}{R_s} (R_s \parallel R)^2 |A(s)|^2$$

$$F^{OL} = 1 + \left(\frac{4k_B T}{R} + S_I + \frac{S_V}{(R_s \parallel R)^2} \right) \frac{R_s}{4k_B T}$$



F – closed-loop case

30

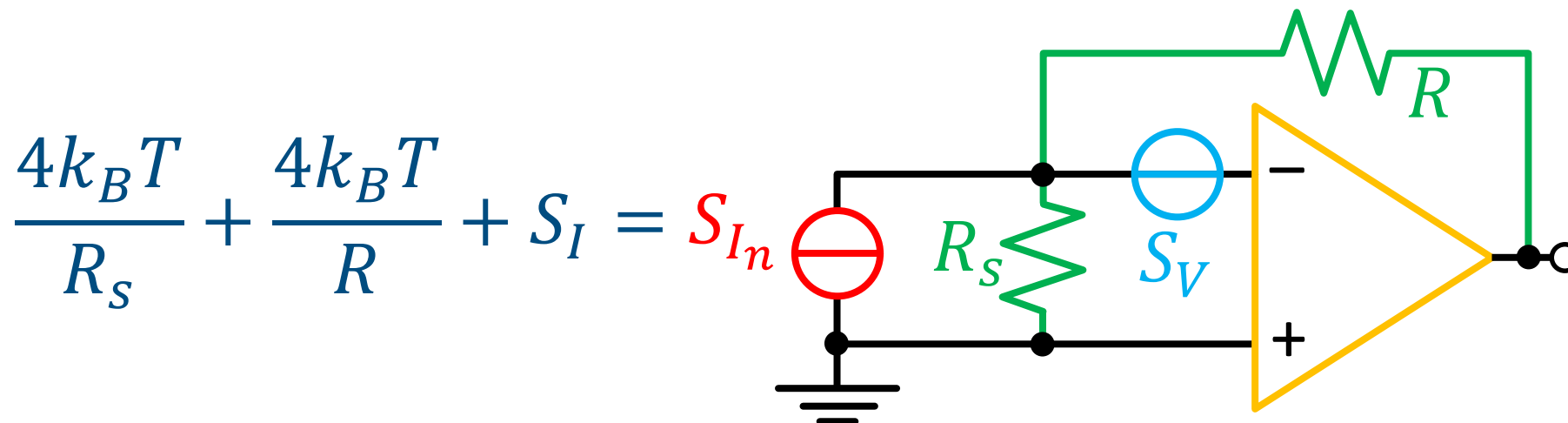

$$\frac{4k_B T}{R_s} + \frac{4k_B T}{R} + S_I = S_{I_n}$$

$$S_{V_o} = \frac{(\text{open-loop PSD})}{|1 - G_{loop}|^2}$$


$$S_{V_o}^{source} = \frac{(\text{open-loop PSD})}{|1 - G_{loop}|^2}$$

$$F^{CL} = F^{OL}$$




S/N – open-loop case

31

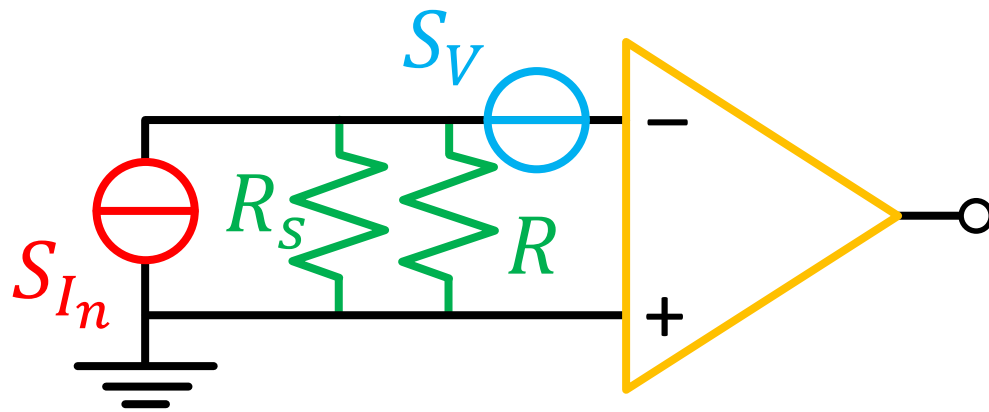

$$V_o = A_0 \frac{R}{R + R_s} V_s \quad (\text{step voltage input, steady-state value})$$



$$\begin{aligned} \overline{V_o^2} &= \int_0^\infty S_{V_o}(f) df = (S_{I_n} (R_s \parallel R)^2 + S_V) \int_0^\infty |A(f)|^2 df \\ &= (S_{I_n} (R_s \parallel R)^2 + S_V) A_0^2 BW_n^{OL} \end{aligned}$$

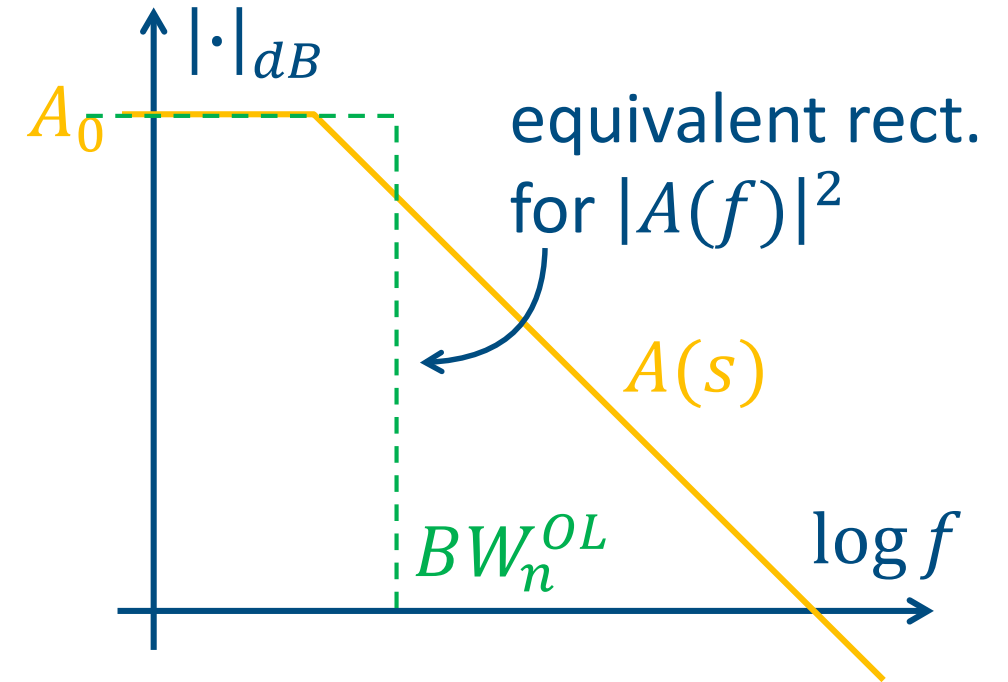



S/N – closed-loop case

32

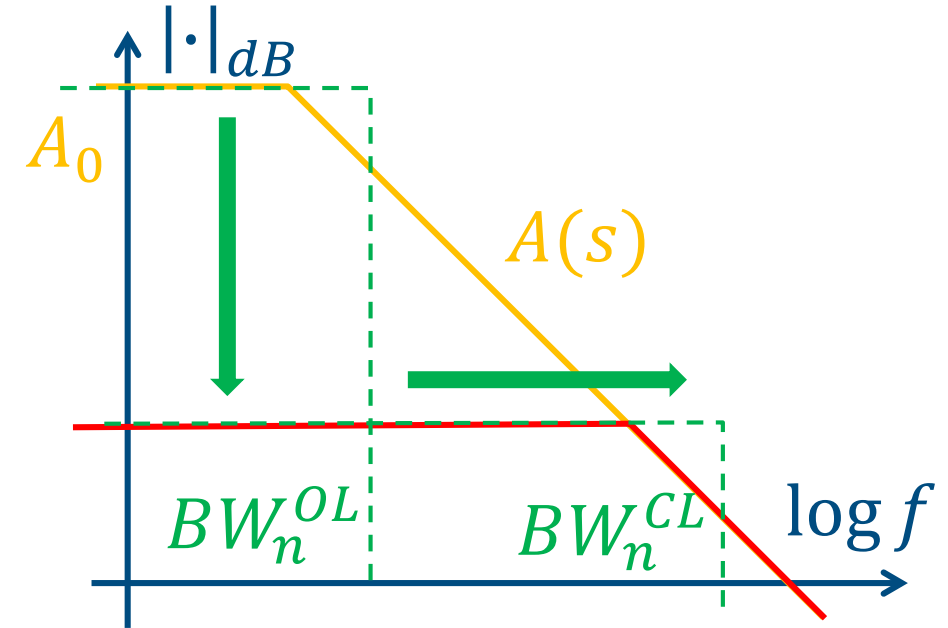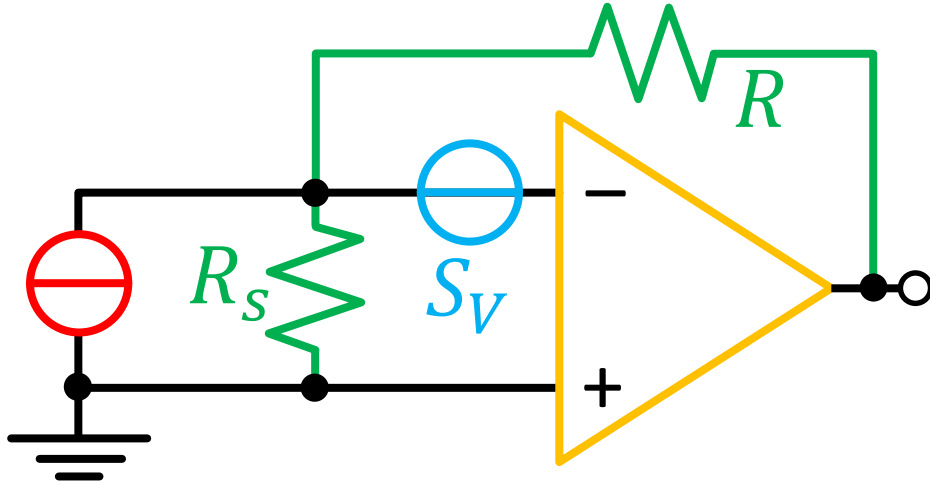

$$V_o = (\text{open-loop transfer}) / (1 - G_{loop}(0))$$

$$\overline{V_o^2} = \int_0^\infty \frac{\text{open-loop PSD}}{|1 - G_{loop}(f)|^2} df = (S_{I_n}(R_s \parallel R)^2 + S_V) \int_0^\infty \left| \frac{A(f)}{1 - G_{loop}(f)} \right|^2 df$$

$$= (S_{I_n}(R_s \parallel R)^2 + S_V) \frac{A_0^2}{(1 - G_{loop}(0))^2} BW_n^{CL}$$



S/N – summary

33

$$\left(\frac{S}{N}\right)^{OL} = \frac{V_s \frac{R}{R + R_s}}{\sqrt{S_{I_n} (R_s \parallel R)^2 + S_V}} \frac{1}{\sqrt{BW_n^{OL}}}$$

this term is
 $\frac{1}{1 - G_{loop}(0)} \ll 1$

$$\left(\frac{S}{N}\right)^{CL} = \frac{V_s \frac{R}{R + R_s}}{\sqrt{S_{I_n} (R_s \parallel R)^2 + S_V}} \frac{1}{\sqrt{BW_n^{CL}}} = \left(\frac{S}{N}\right)^{OL} \sqrt{\frac{BW_n^{OL}}{BW_n^{CL}}}$$



- Negative feedback modifies all open-loop transfers by the same factor $\Rightarrow F$ is unaffected
- Negative feedback widens the bandwidth, collecting more noise $\Rightarrow S/N$ is degraded
- For this reason, you should never use extra BW beyond what is needed by the signal
- If BW is independently set by the requirements, **negative feedback does not modify the noise performance**



1. <http://www.edn.com/electronics-blogs/the-signal/4404375/Op-Amp-Noise-the-non-inverting-amplifier>
2. <http://www.edn.com/electronics-blogs/the-practicing-instrumentation-engineer/4410043/Visualize-op-amp-noise>