

#### Electronics – 96032





Alessandro Spinelli Phone: (02 2399) 4001 alessandro.spinelli@polimi.it

spinelli.faculty.polimi.it



Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes

## **Purpose of the lesson**

• To briefly show how the previous approaches to LF noise filtering have been implemented in OA design



- They are a class of OAs employing the techniques just discussed for reducing LF noise (incl. offset)
- We have seen two techniques
  - Sampling (BLR/CDS) ⇒ auto-zero amplifiers
  - Modulation/demodulation ⇒ chopper amplifiers







- Output noise contains a peak at the chopping frequency
- BW limited by the chopping frequency



### **Chopper-stabilized OAs**



- AC-coupled amplifier plus a DC chopper amplifier (see [1])
- Only inverting operation allowed

#### **Offset cancellation idea**





- Several trade-offs were to be made in CSAa
- Modern approach is to employ a nulling amplifier to compensate for the offset and LF noise (see [2,3])
  - As the approach is different, such amplifiers are also known as auto-zero
  - As usual, terminology changes a bit from one manufacturer to the other...

# **Auto-zero OAs**

- During phase 1, A<sub>N</sub> cancels its own offset
- During phase 2,  $A_N$  cancels  $A_M$ 's offset



From [3]

9





$$V_{O}^{1} = A_{1}V_{OS}^{1} - B_{1}V_{O}^{1}$$
$$V_{O}^{1} = V_{OS}^{1}\frac{A_{1}}{1 + B_{1}} = V_{C_{1}}$$

- The value is stored on capacitor C<sub>1</sub>
- When the switches commute, we

$$= store on C_2 the value V_0^1 = A_1 V_i + A_1 V_{0S}^1 - B_1 V_{C_1} = A_1 V_i + V_{0S}^1 A_1 \left( 1 - \frac{1}{1} \right)$$

 $=A_1\left(V_i + \frac{V_{OS}^{-1}}{1+B_1}\right)$ 



# The output is now $V_0^2 = A_2 V_i + A_2 V_{0S}^2 + B_2 V_{C_2}$ • $C_2$ is connected to $V_0^1$ , leading to $V_O^2 = A_2 V_i + A_2 V_{OS}^2 + B_2 A_1 \left( V_i + \frac{V_{OS}^1}{1 + B_1} \right)$ $= V_i(A_2 + B_2A_1) + A_2V_{OS}^2 + V_{OS}^1A_1 \left(\frac{B_2}{1 + R}\right)$ $\approx ABV_i + A\left(V_{OS}^1 + V_{OS}^2\right) = AB\left(V_i + \frac{V_{OS}^1 + V_{OS}^2}{B}\right)$



- Auto-zero OAs have very high gain and reduce the offset down to the  $\mu V$  range
- Note that the signal is NOT modulated ⇒ AZ technique is more similar to a BLR or CDS approach
- A comparison can be found in [4]

# **Typical parameters**

- GBWP  $\approx 1 3$  MHz
- Chopping frequency: 100 Hz kHz
- Offset voltage drift  $\approx nV/^{\circ}C$
- Flat noise spectrum (no 1/f noise), but higher WN level



- 1. <u>https://www.eeweb.com/chopper-stabilized-operational-amplifiers/</u>
- 2. <u>https://www.analog.com/media/en/training-</u> <u>seminars/tutorials/MT-055.pdf</u>
- 3. <u>https://www.ti.com/lit/an/slyt204/slyt204.pdf</u>
- 4. <u>https://www.analog.com/en/technical-articles/to-chop-or-auto-</u> zero-that-is-the-question.html