



Electronics – 96032

 POLITECNICO DI MILANO



Linear Applications of OpAmps

Alessandro Spinelli

Phone: (02 2399) 4001

alessandro.spinelli@polimi.it

spinelli.faculty.polimi.it




Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes



Acquisition chain

3

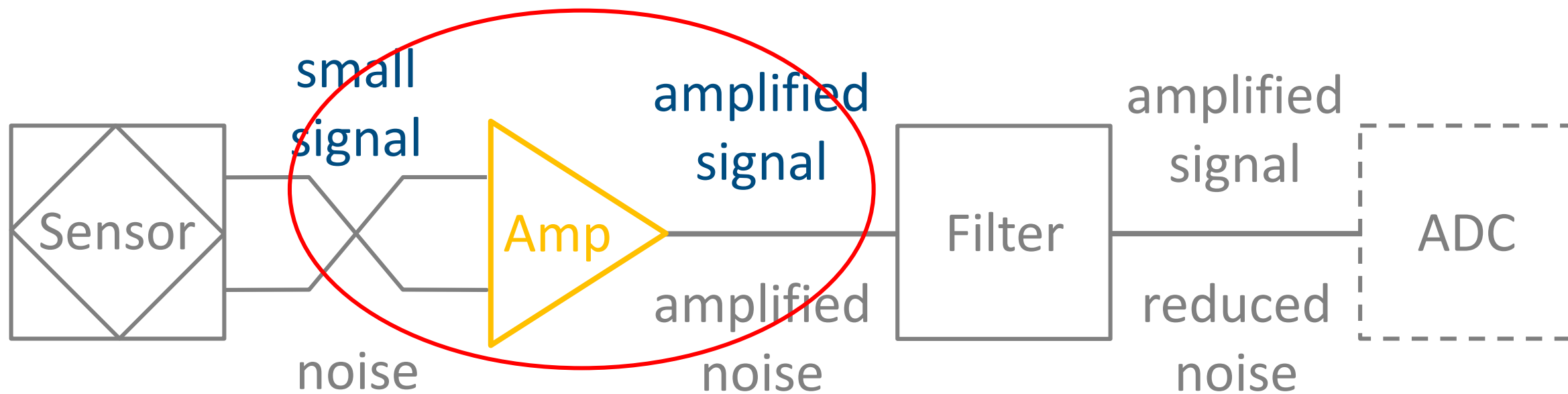

next lessons



Purpose of the lesson

4

- We begin our study with the analysis and design of simple amplifiers
- Next lessons will deal with
 - Basic amplifier principles and the feedback amplifier concept
 - Linear applications of OpAmps (this lesson)
 - Feedback amplifier properties
 - Stability of feedback amplifiers
 - Instrumentation amplifiers and OpAmp parameters




- Non-inverting amplifier
- Inverting amplifier and applications
- Other linear circuits



Calculation of G_{id}

6

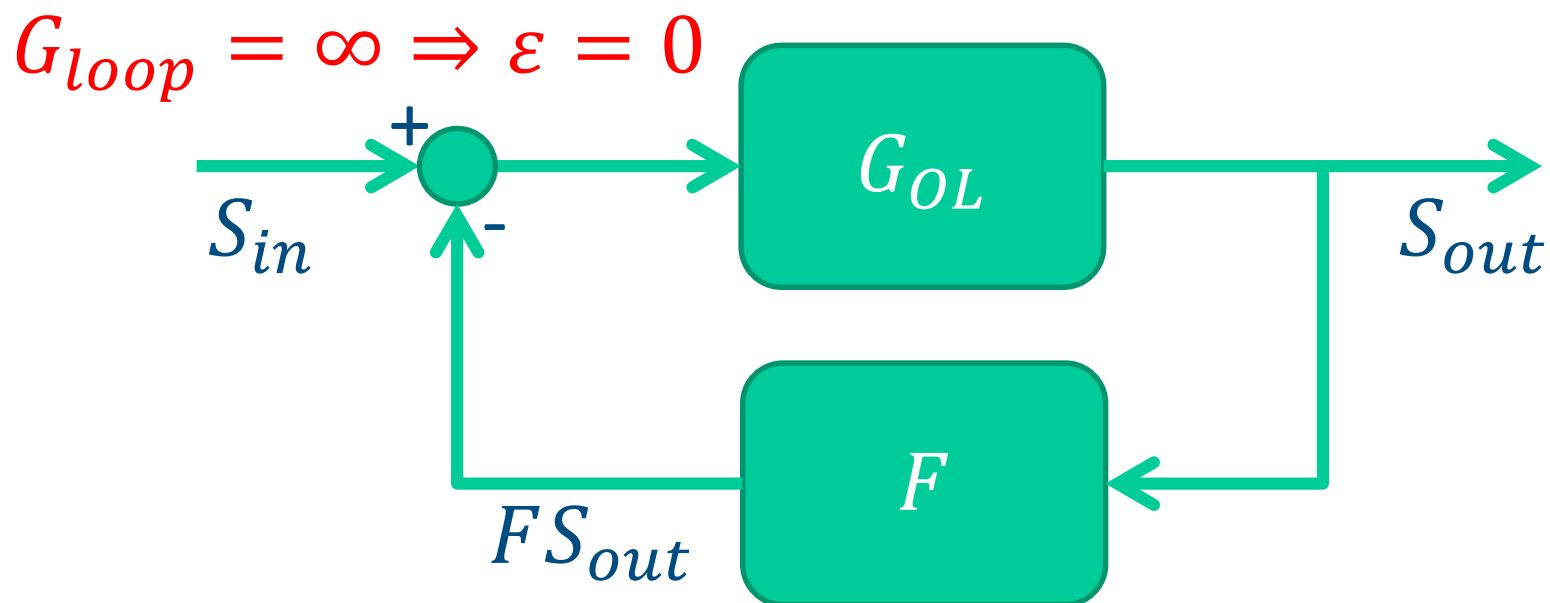


$$G_{loop} = \infty \Rightarrow \varepsilon = \frac{S_{out}}{G_{OL}} = 0 \Rightarrow S_{in} - F S_{out} = 0 \Rightarrow \frac{S_{out}}{S_{in}} = \frac{1}{F} = G_{id}$$



Non-inverting amplifier

7

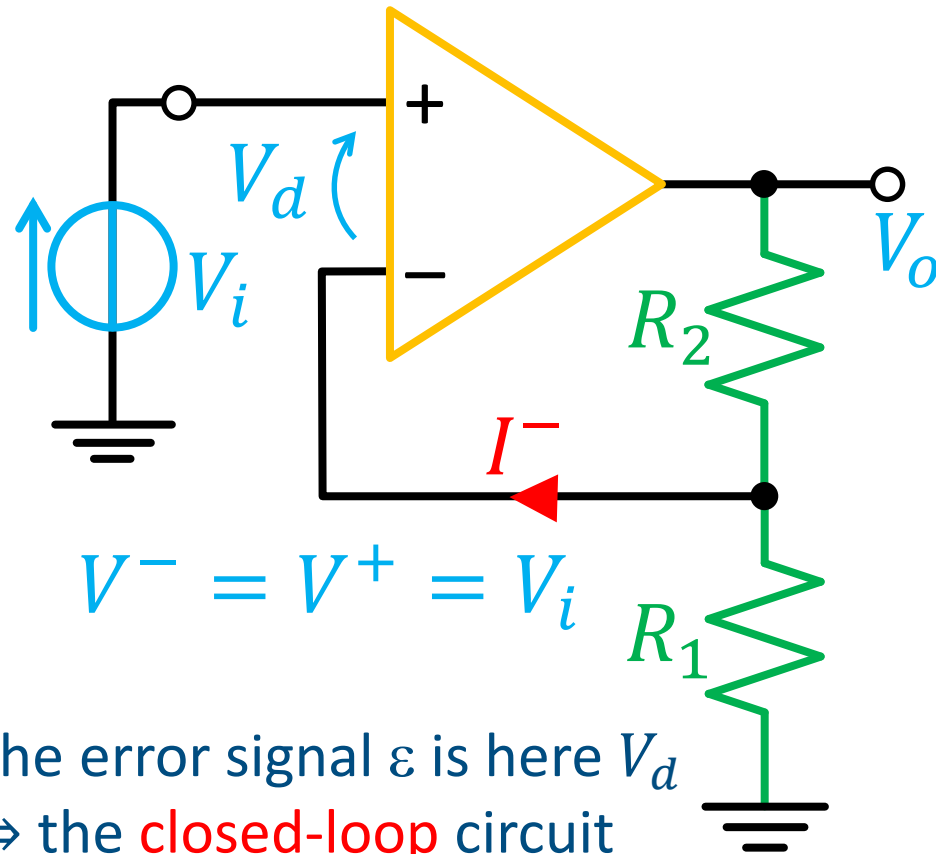

$$V^- = V^+ = V_i$$

The error signal ε is here V_d
 $\Rightarrow$ the **closed-loop** circuit
keeps the same voltage at
the $-$ and $+$ inputs

Since $I^- = 0$, we have

$$V^- = V_o \frac{R_1}{R_1 + R_2}$$


$$V_d = V^+ - V^- = \frac{V_o}{A} = 0$$
$$\Rightarrow V^- = V^+ = V_i$$

$$G_{id} = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_1} \geq 1$$



Input and output impedances


8

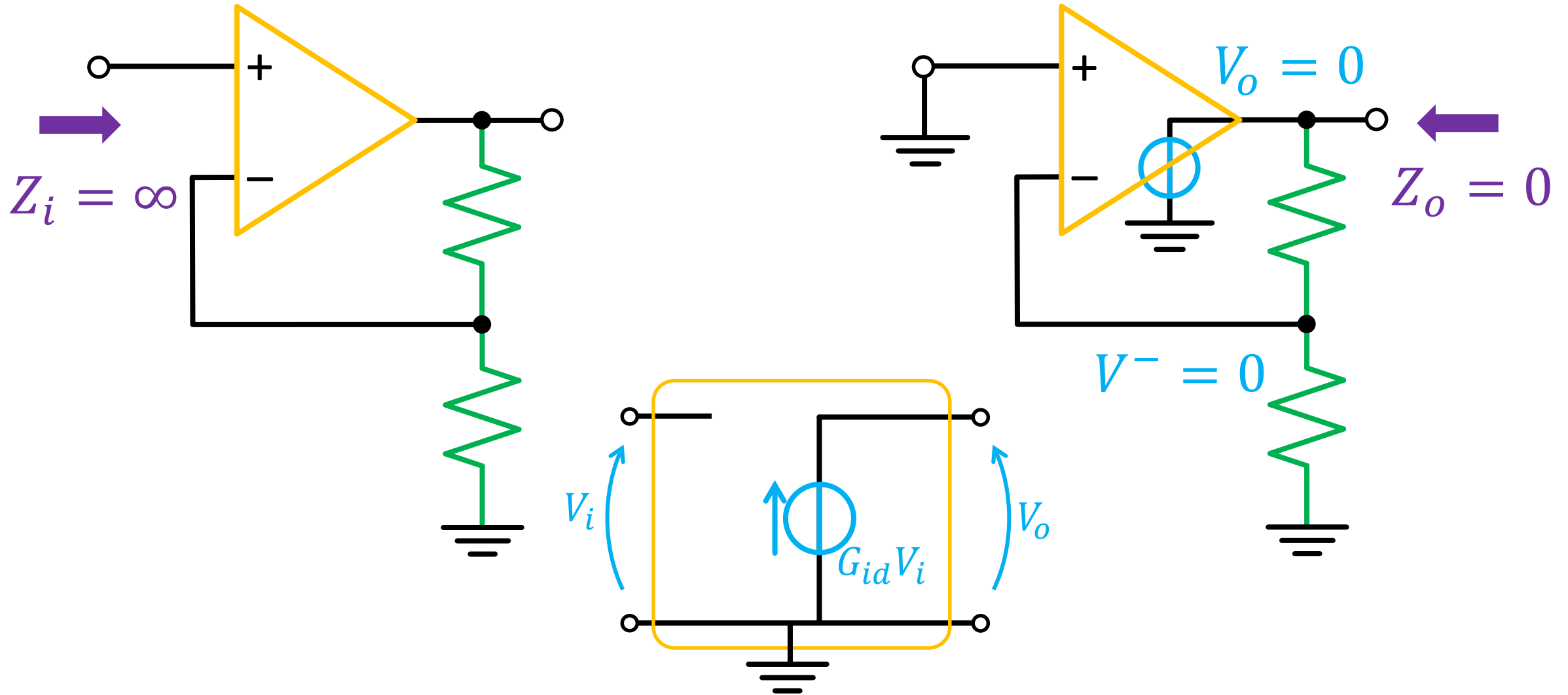



Voltage follower

9

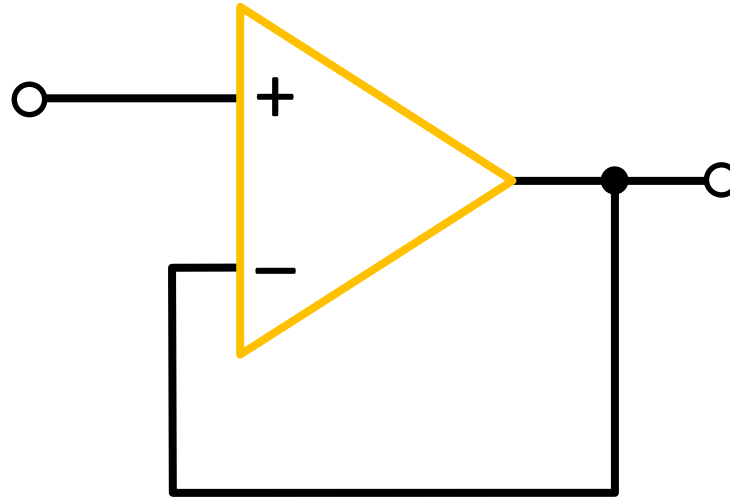


- A non-inverting amplifier having $R_1 = \infty$ (and $R_2 = 0$) $\Rightarrow G_{id} = 1$
- Used as buffer stage




Buffer stage

10

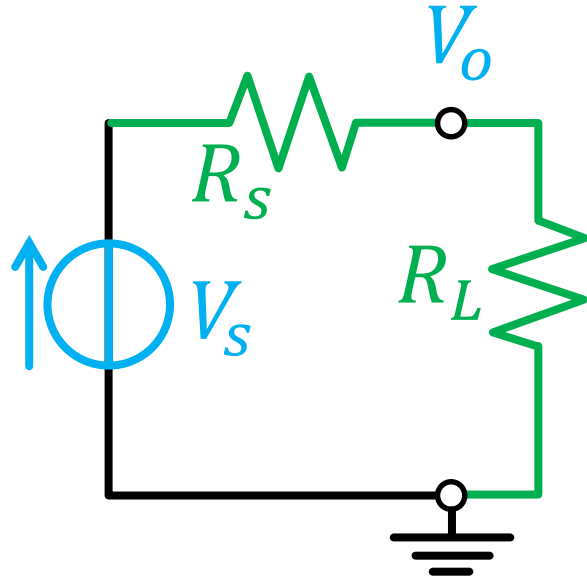

$$V_o = V_s \frac{R_L}{R_L + R_s}$$

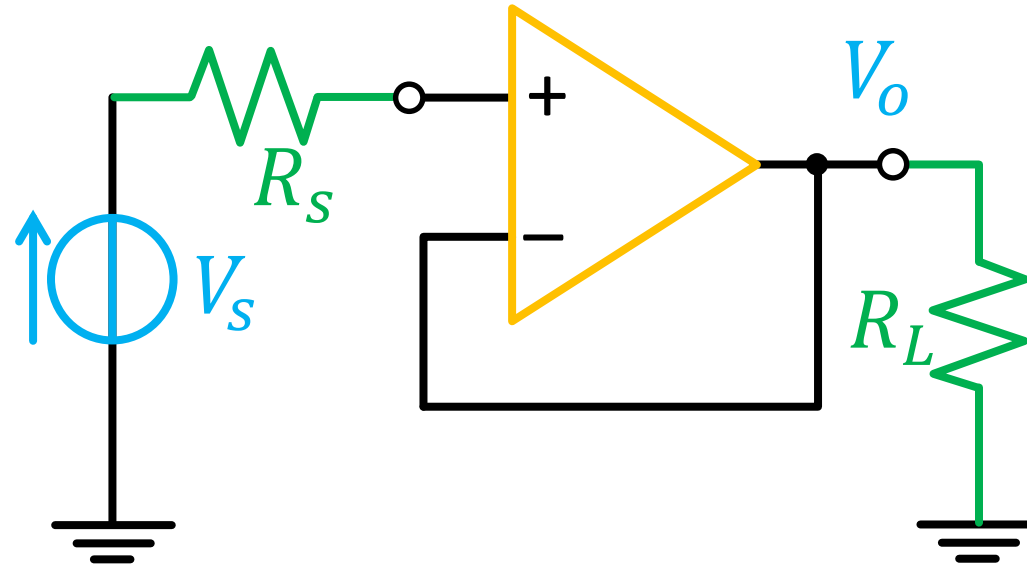

$$V_o = V_s$$




- Non-inverting amplifier
- Inverting amplifier and applications
- Other linear circuits



Inverting amplifier

12

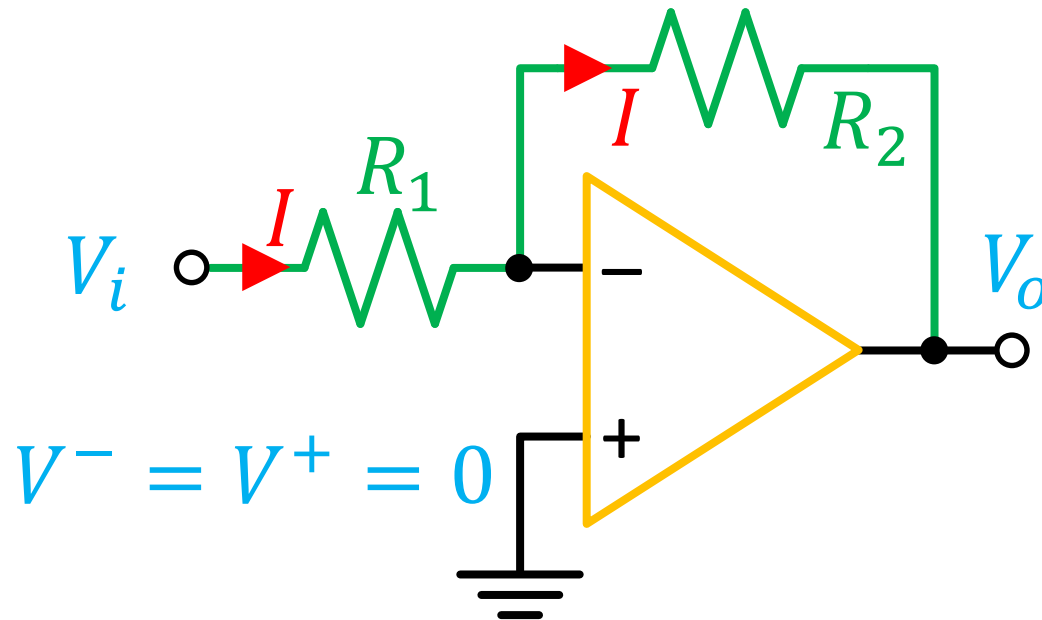

$$I = \frac{V_i - V^-}{R_1} = \frac{V_i}{R_1}$$

$$V_o = -IR_2 = -V_i \frac{R_2}{R_1}$$


the inverting input is a **virtual ground** (the feedback keeps it at ground potential even if not physically connected to it)

$$G_{id} = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$




Input and output impedances

13

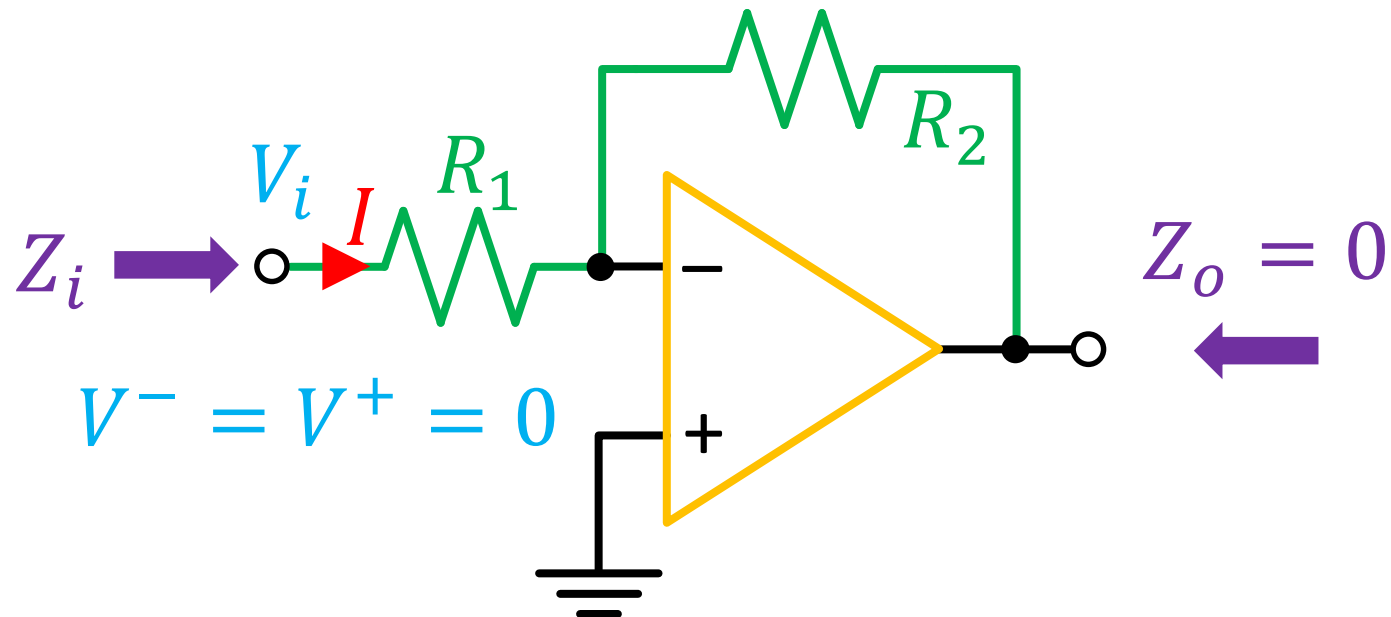

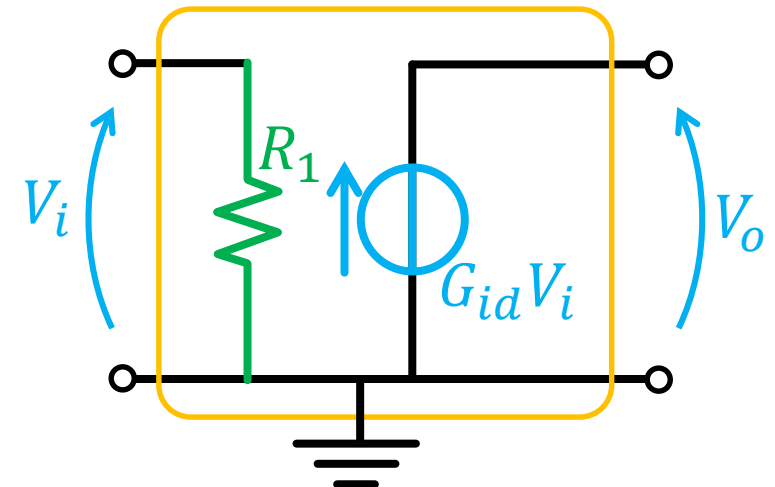
$$I = \frac{V_i}{R_1} \Rightarrow Z_i = \frac{V_i}{I} = R_1$$





Another look at the gain

14

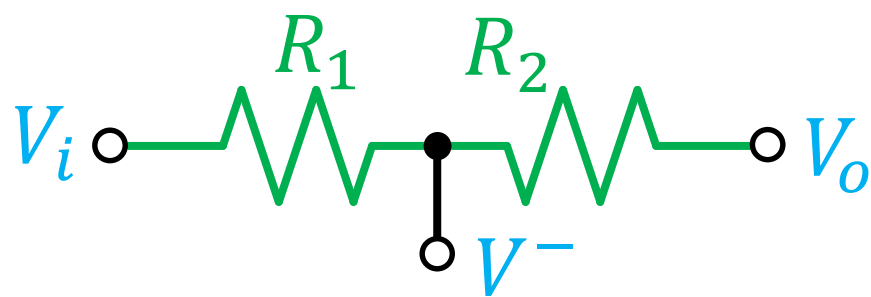

$$V^- = V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2}$$





The OA settles to the value of V_o that brings $V^- = V^+ = 0$

$$V^- = 0 \Rightarrow \frac{V_o}{V_i} = -\frac{R_2}{R_1} = G_{id}$$



The lever analog


15

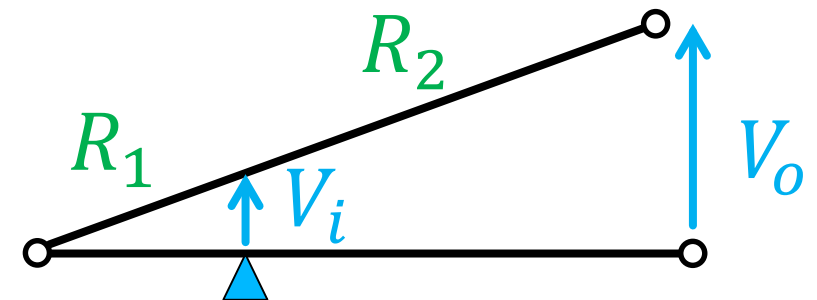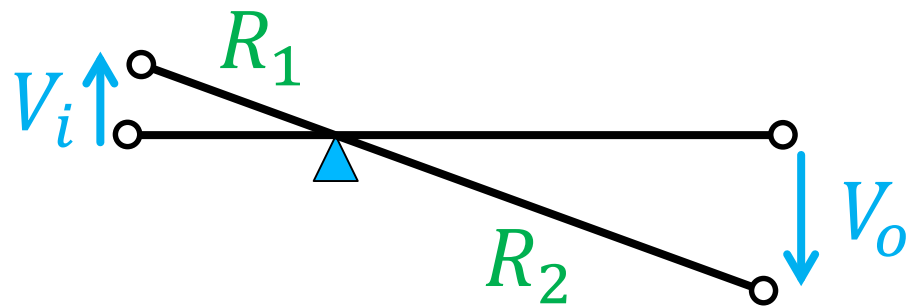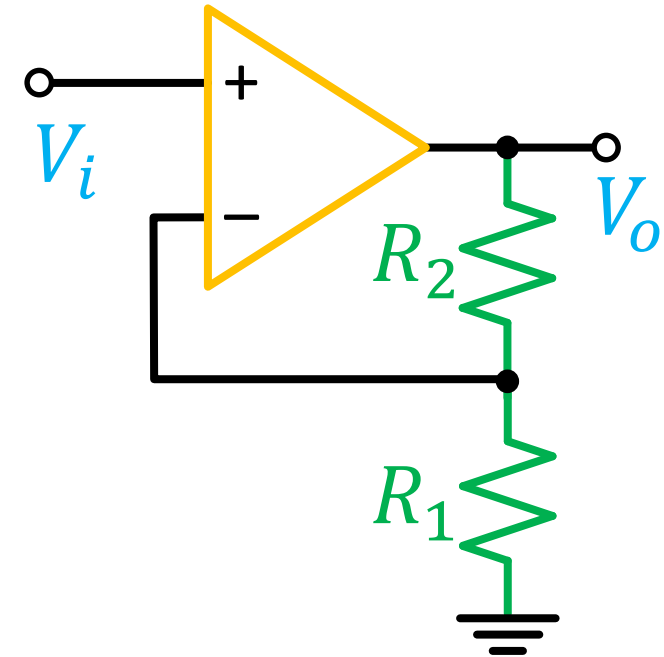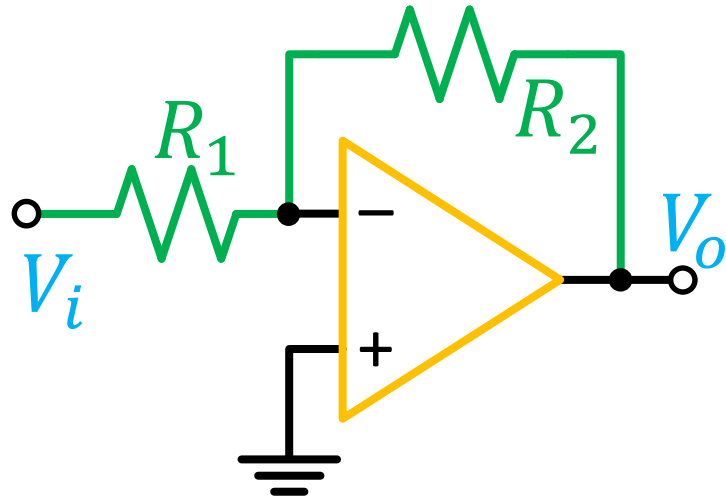



Adder circuit


16

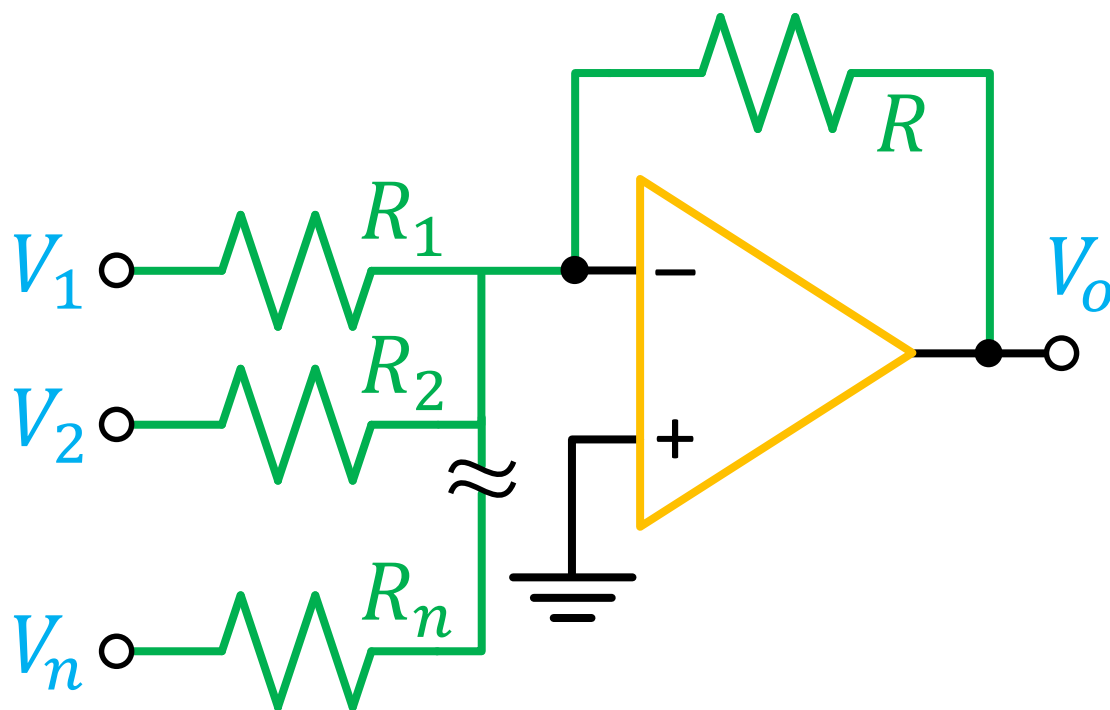



Superposition principle

17

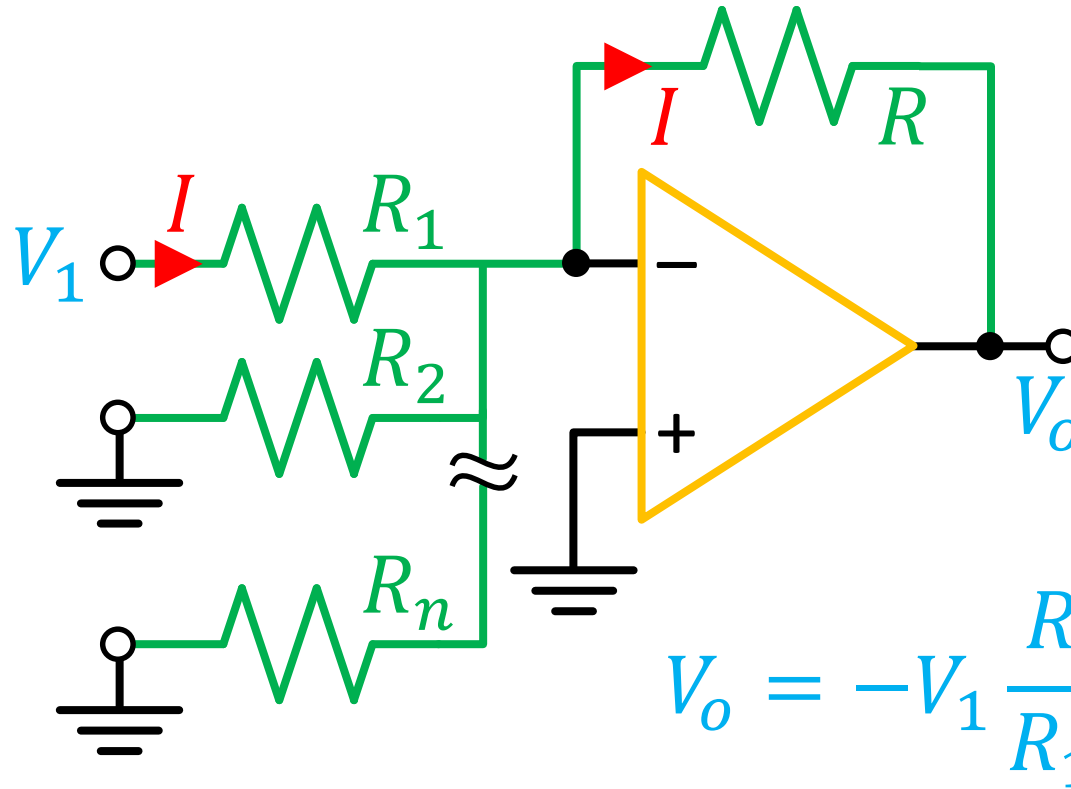

No current flowing in resistors $R_2, \dots, R_n$:

$$V_{o1} = -V_1 \frac{R}{R_1}$$


$$V_o = -V_1 \frac{R}{R_1} - V_2 \frac{R}{R_2} - \dots - V_n \frac{R}{R_n}$$

$$\text{If } R_1 = R_2 = \dots = R_n: V_o = -\frac{R}{R_1} (V_1 + V_2 + \dots + V_n)$$



Subtractor circuit


18

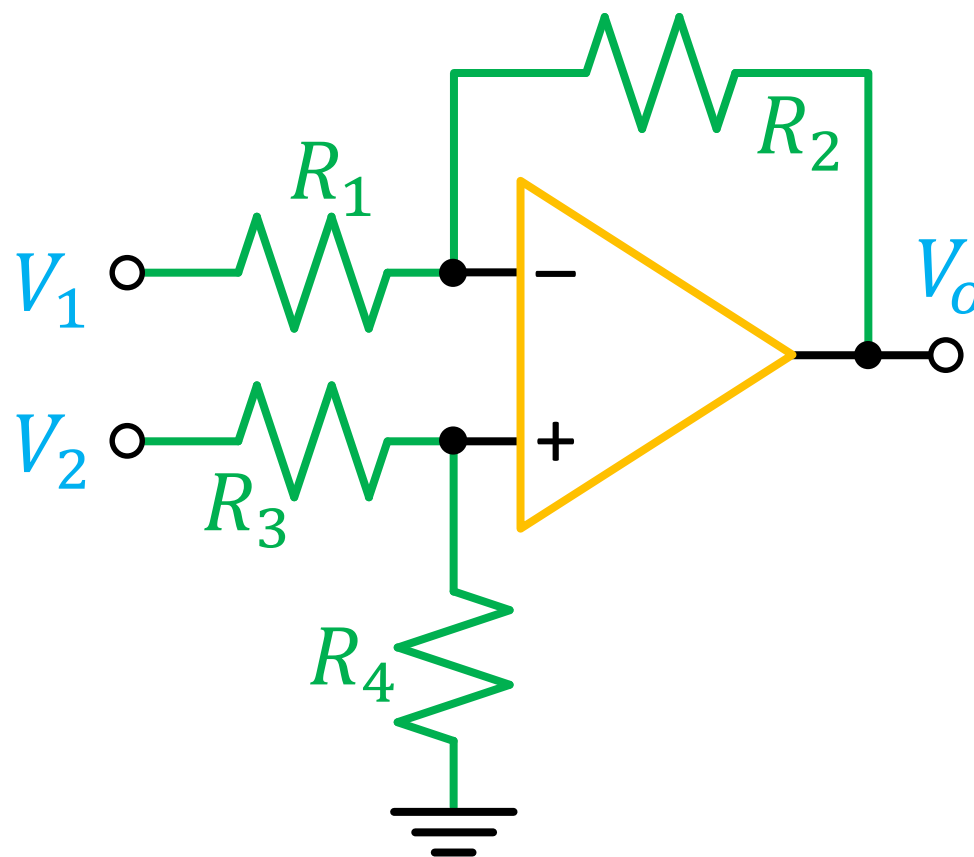



Superposition principle – 1

19

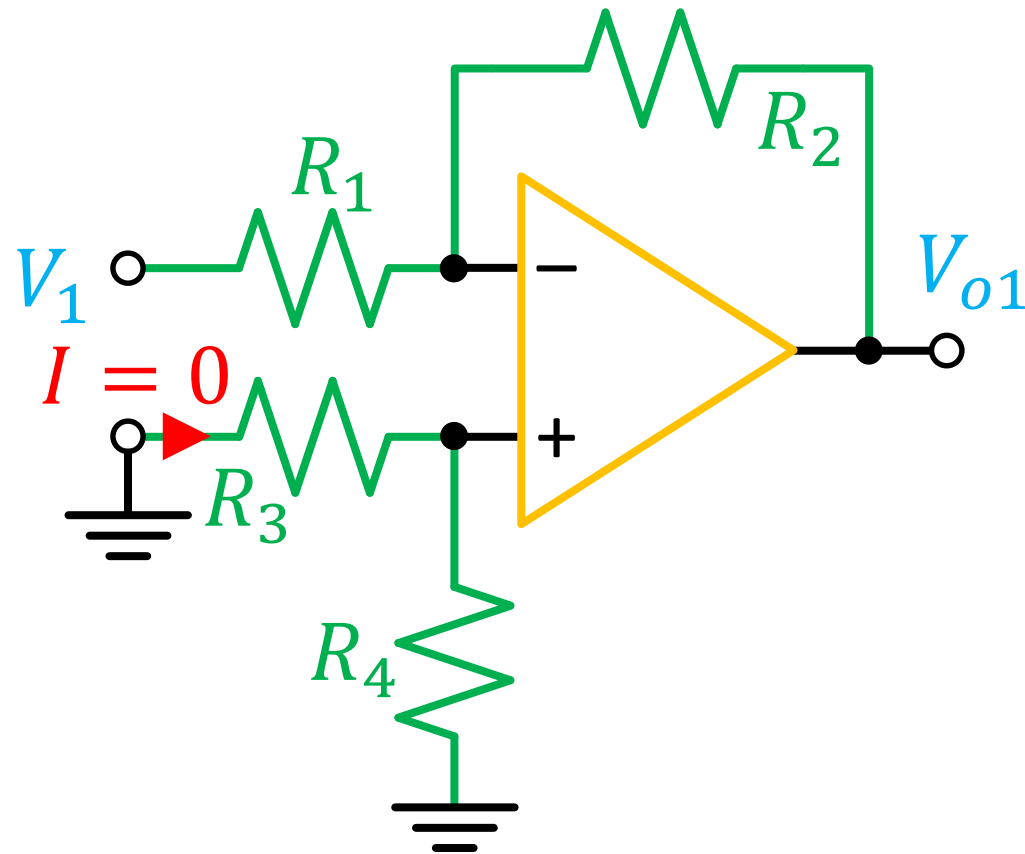


The circuit becomes an inverting amplifier:

$$V_{o1} = -\frac{R_2}{R_1} V_1$$



Superposition principle – 2

20

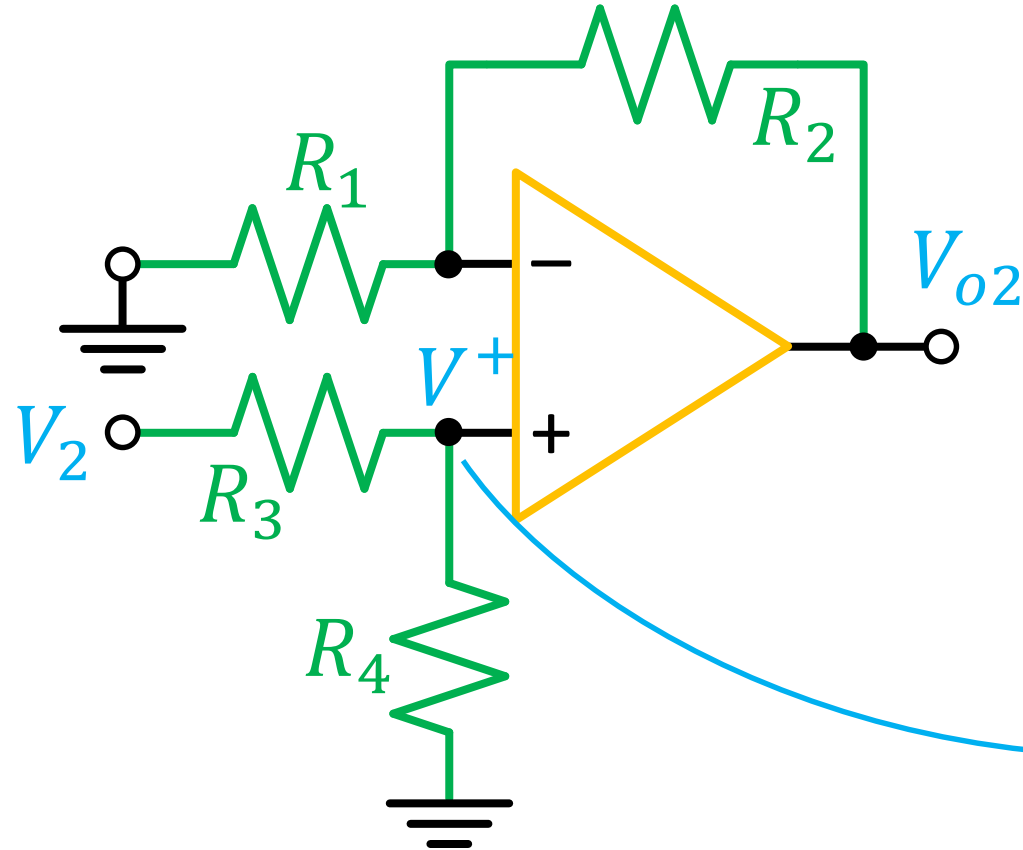

The circuit is now a non-inverting amplifier

$$V_{o2} = V_2 \frac{R_4}{R_3 + R_4} \frac{R_1 + R_2}{R_1}$$



$$\begin{aligned} V_o = V_{o1} + V_{o2} &= -\frac{R_2}{R_1} V_1 + \frac{R_4}{R_3 + R_4} \frac{R_1 + R_2}{R_1} V_2 \\ &= \frac{R_2}{R_1} \left(-V_1 + \frac{1 + R_1/R_2}{1 + R_3/R_4} V_2 \right) \end{aligned}$$

If we pick $\frac{R_1}{R_2} = \frac{R_3}{R_4}$, we get

$$V_o = \frac{R_2}{R_1} (-V_1 + V_2)$$



- Closed-loop gain often depends on resistor ratio, not absolute values
- Low-value resistors draw more current but have better frequency response
- High-value resistors are more noisy and enhance any leakage current
- Typical values are in the range 10 – 100 k Ω




- Non-inverting amplifier
- Inverting amplifier and applications
- Other linear circuits




I-V converter (TR amp)

24

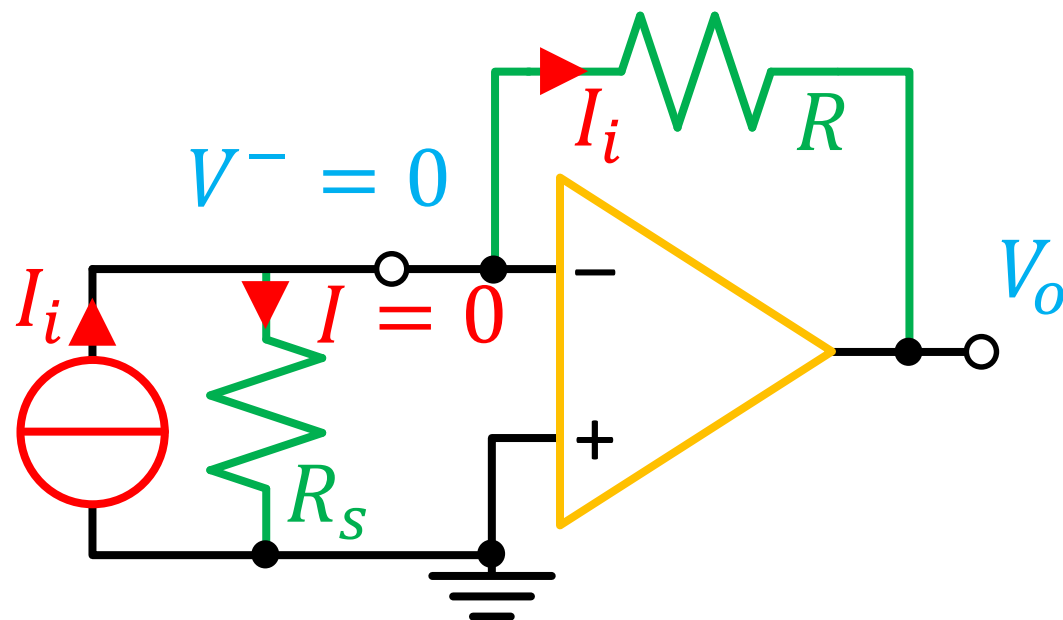


$$V_o = -RI_i$$
$$Z_i = 0; Z_o = 0$$

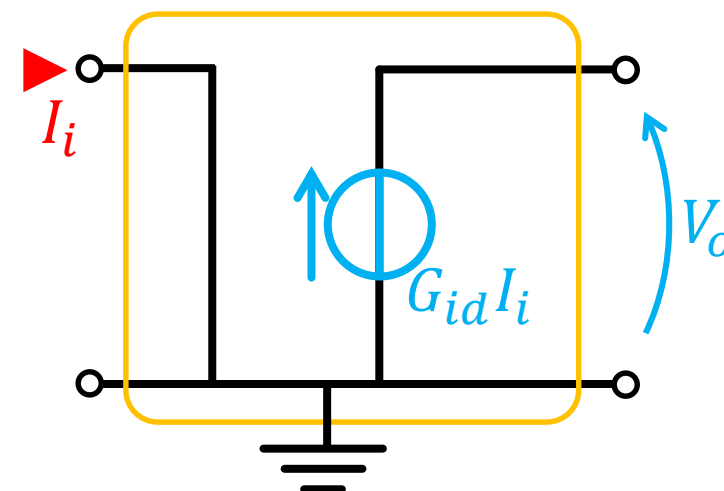



V-I converter (TC amp)

25

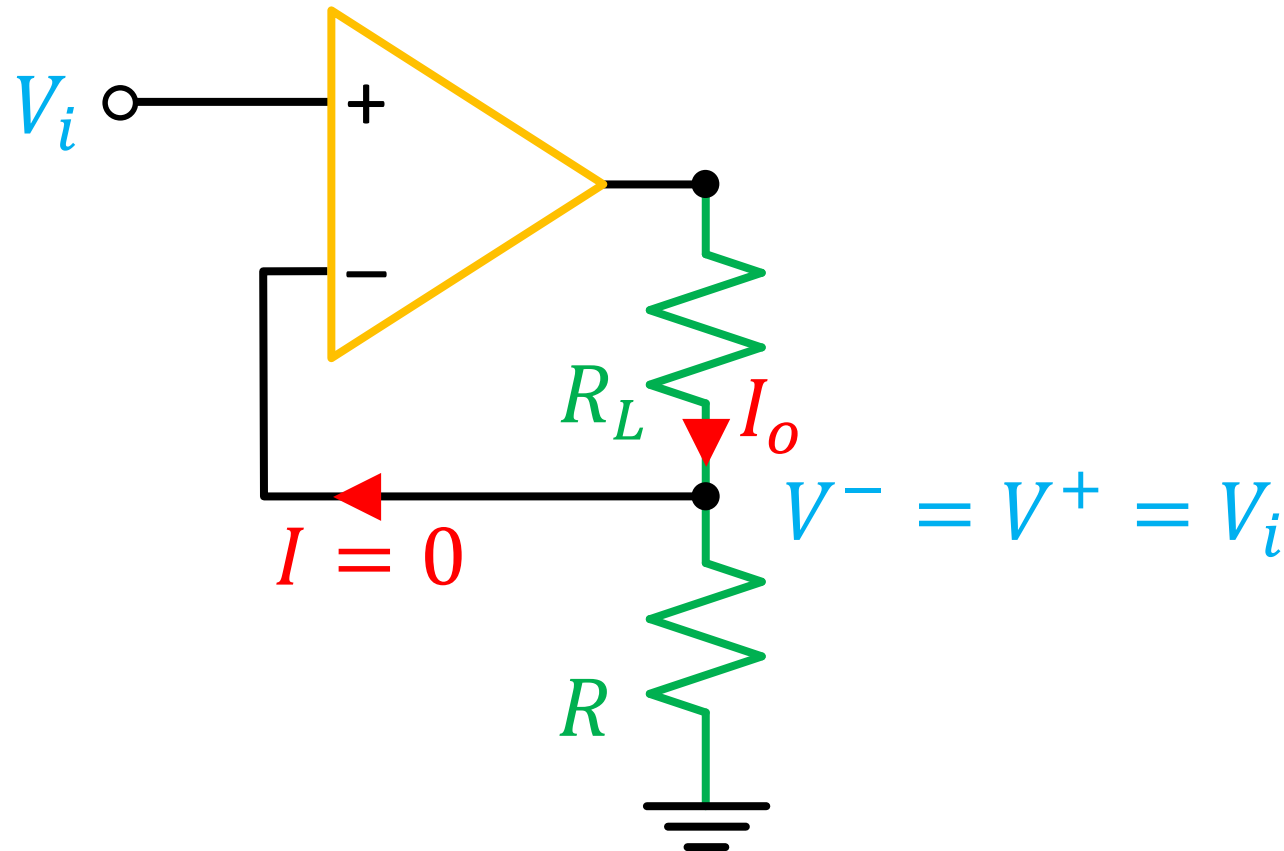


$$I_o = \frac{V_i}{R}$$
$$Z_i = \infty; Z_o = ?$$



Integrator

26

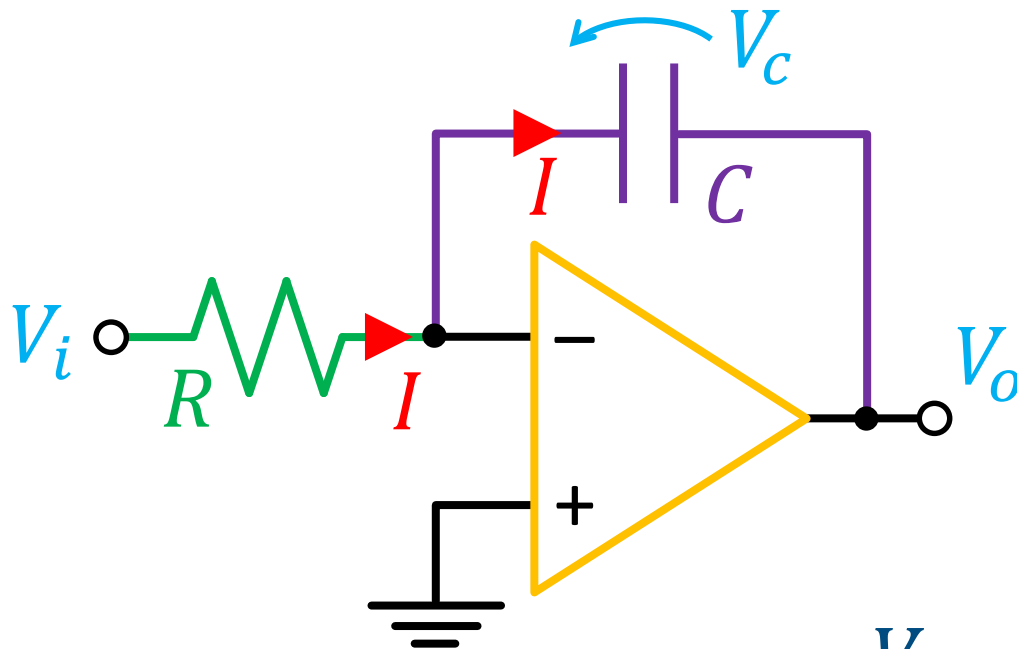


$$I = C \frac{dV_c}{dt} \Rightarrow V_c = \frac{1}{C} \int I dt$$

$$V_o = -V_c = -\frac{1}{C} \int I dt = -\frac{1}{RC} \int V_i dt$$



Differentiator

27

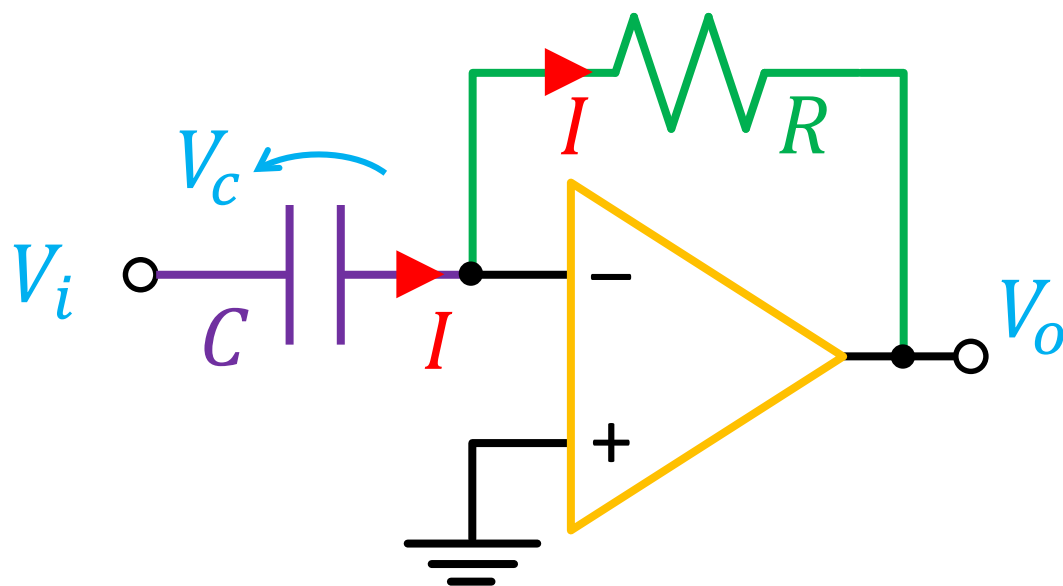

$$I = C \frac{dV_c}{dt}$$

$$V_o = -RI = -RC \frac{dV_c}{dt} = -RC \frac{dV_i}{dt}$$