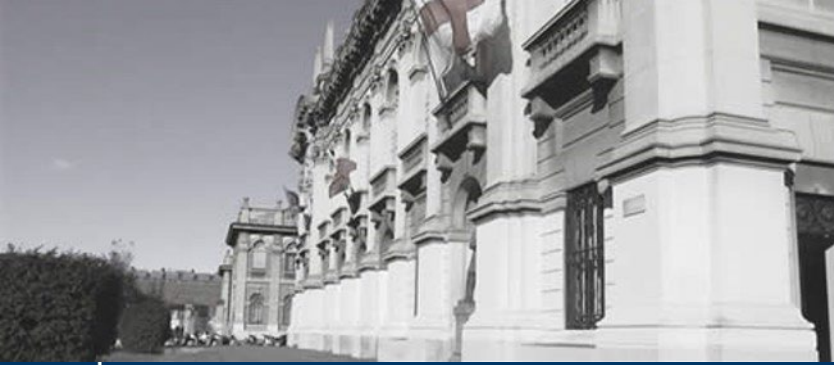




Electronics – 96032



POLITECNICO DI MILANO



Closed-loop Gain and Impedances

Alessandro Spinelli

Phone: (02 2399) 4001

alessandro.spinelli@polimi.it

spinelli.faculty.polimi.it




Slides are supplementary material and are NOT a replacement for textbooks and/or lecture notes



Acquisition chain

3

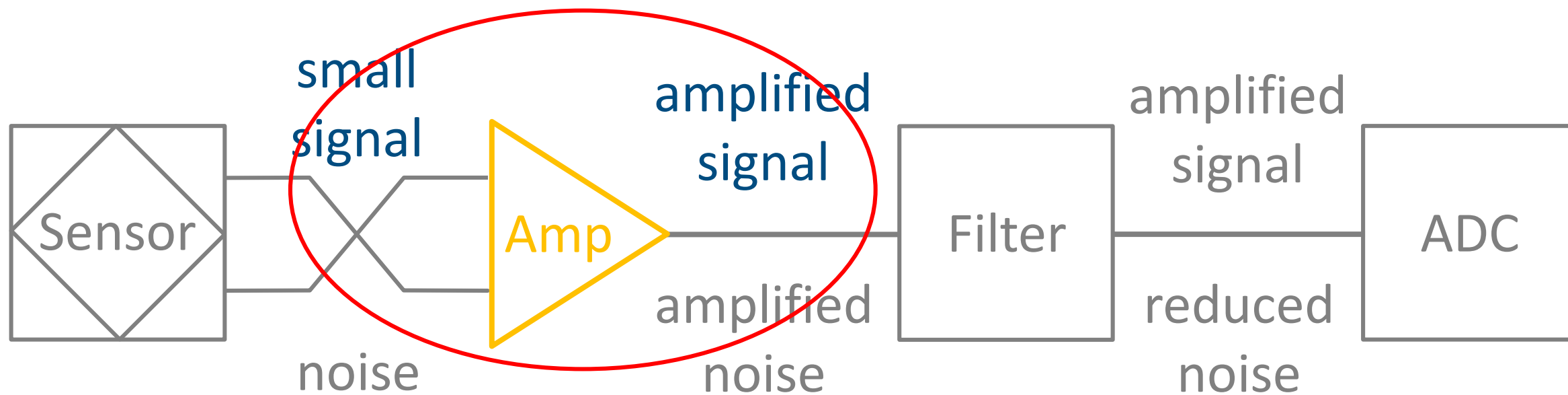

next lessons



Purpose of the lesson

4

- We begin our study with the analysis and design of simple amplifiers
- Next lessons will deal with
 - Basic amplifier principles and the feedback amplifier concept
 - Linear applications of OpAmps
 - Feedback amplifier properties (this lesson)
 - Stability of feedback amplifiers
 - Instrumentation amplifiers and OpAmp parameters




- Loop gain and closed-loop gain calculation
- Input/output impedances



OA parameter: large-signal voltage gain

6

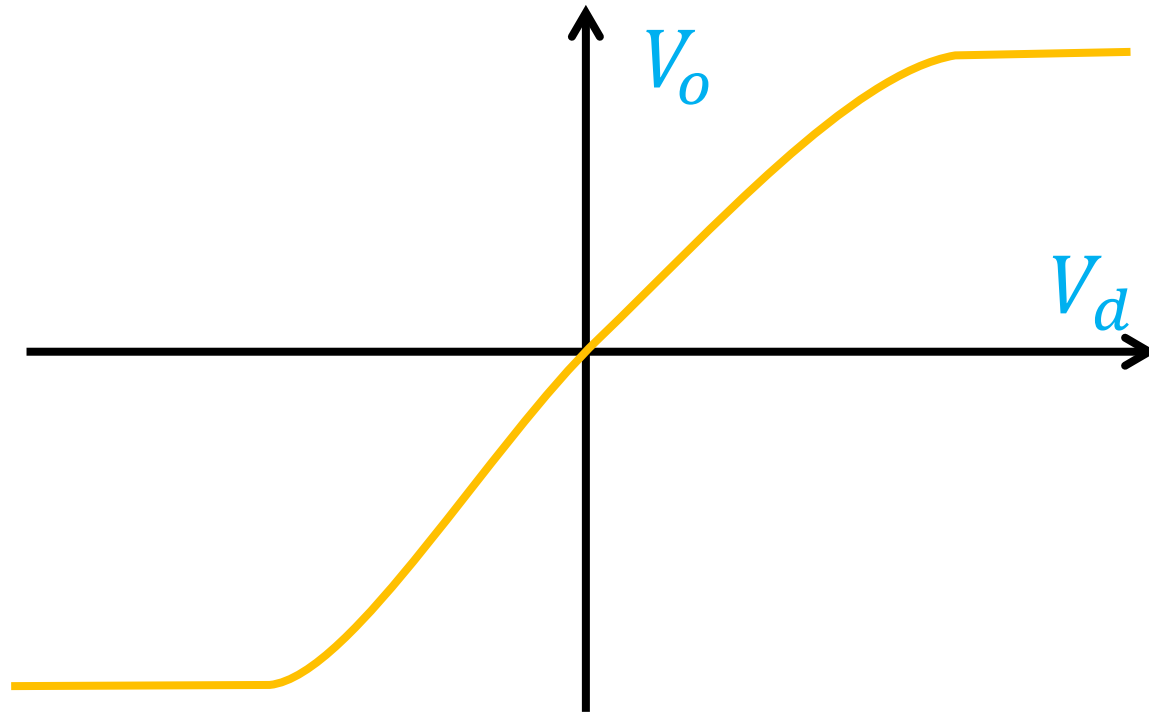


- I/O characteristic is non-linear
 $\Rightarrow$ gain A_V is the slope of the linear interpolation
- Typical values are 80 – 120 dB (sometimes expressed in V/mV), but dependent on V_{CC} , R_L , T ,...




Actual values from datasheets

7

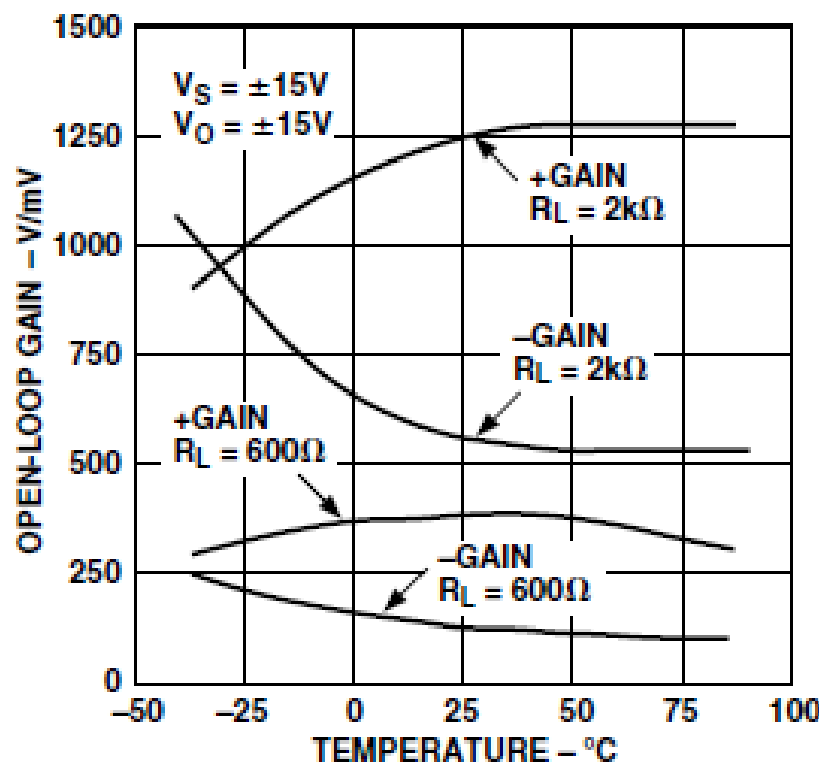

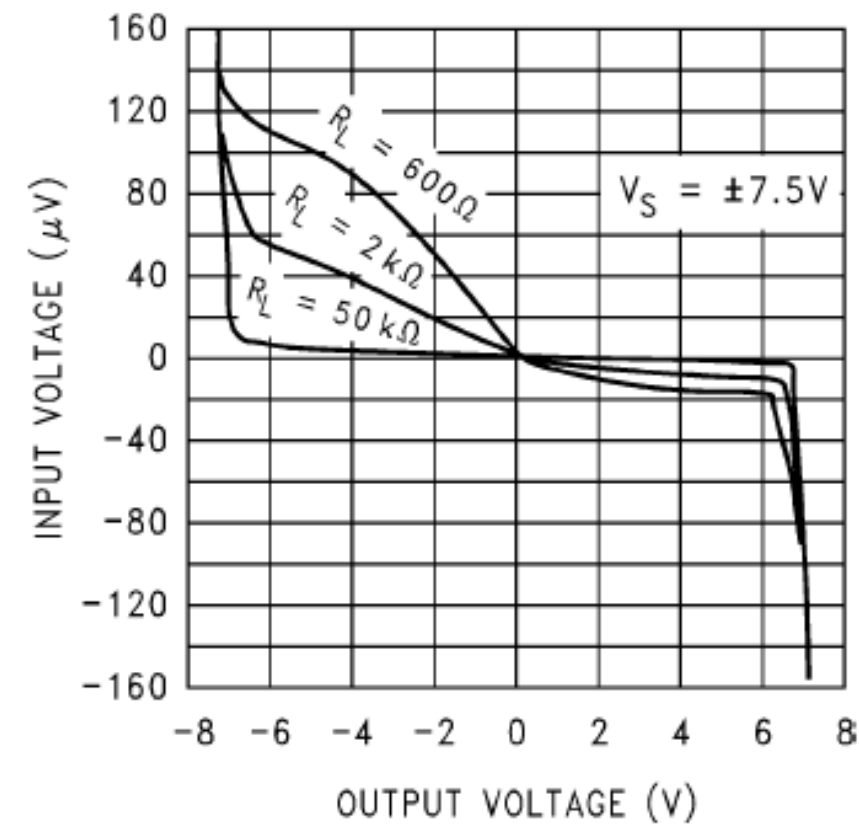Dependence on T and R_L (note the asymmetry of the gain)




(low-power CMOS OA)



Loop gain calculation (concept)



8

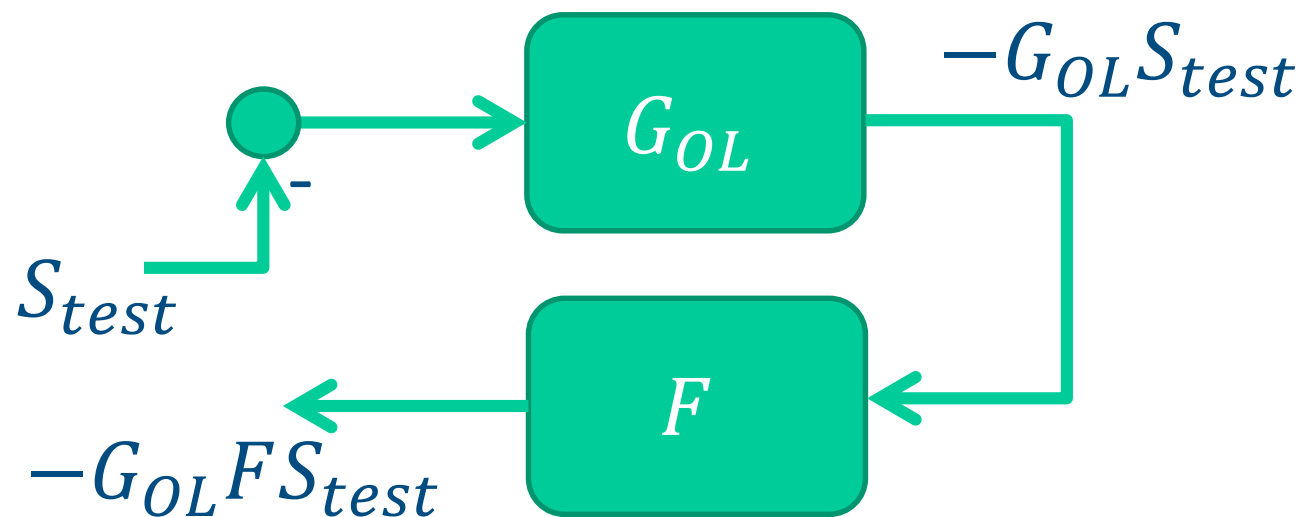



Loop gain calculation

9

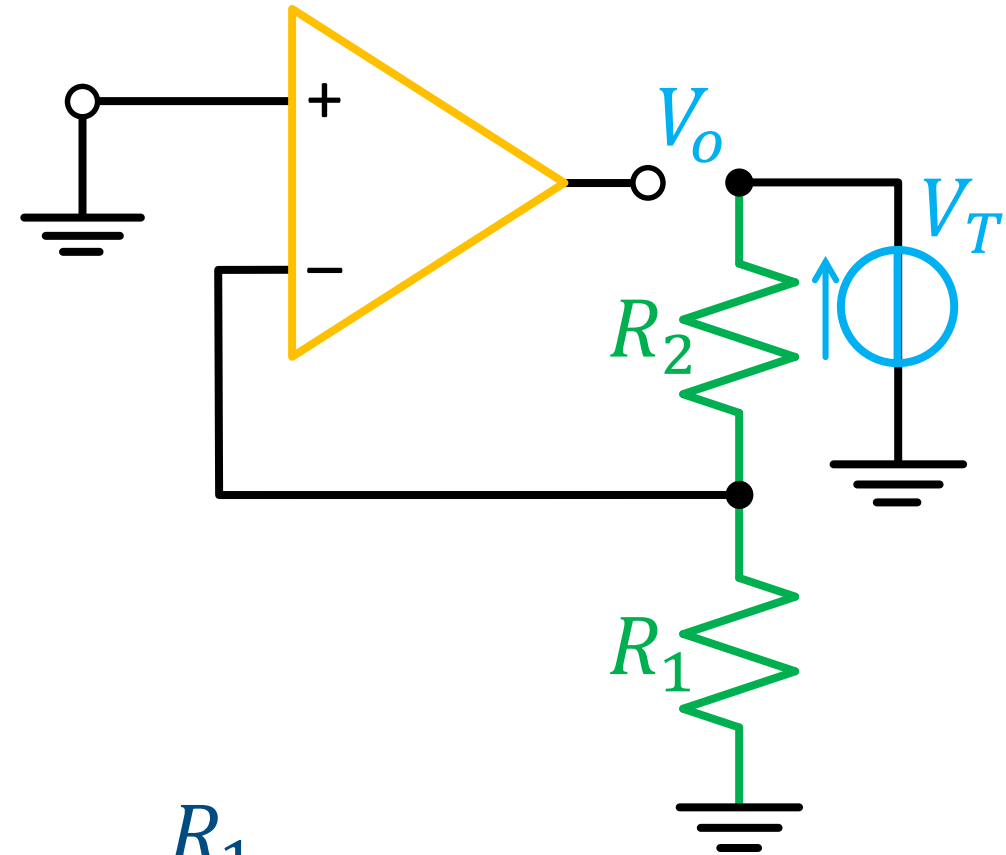
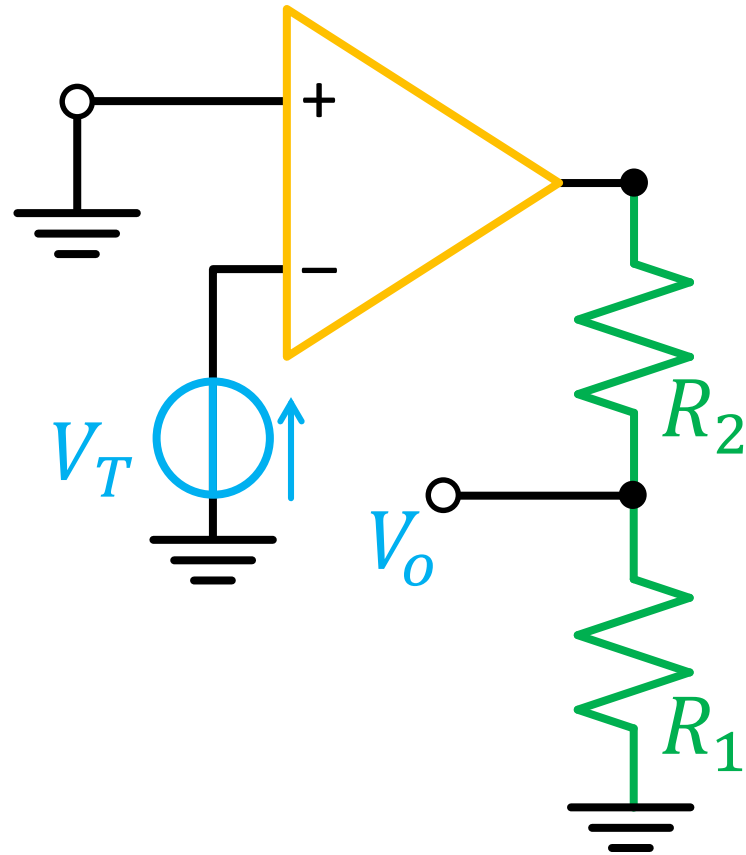


$$G_{loop} = -A \frac{R_1}{R_1 + R_2}$$



Impedance reconstruction


10

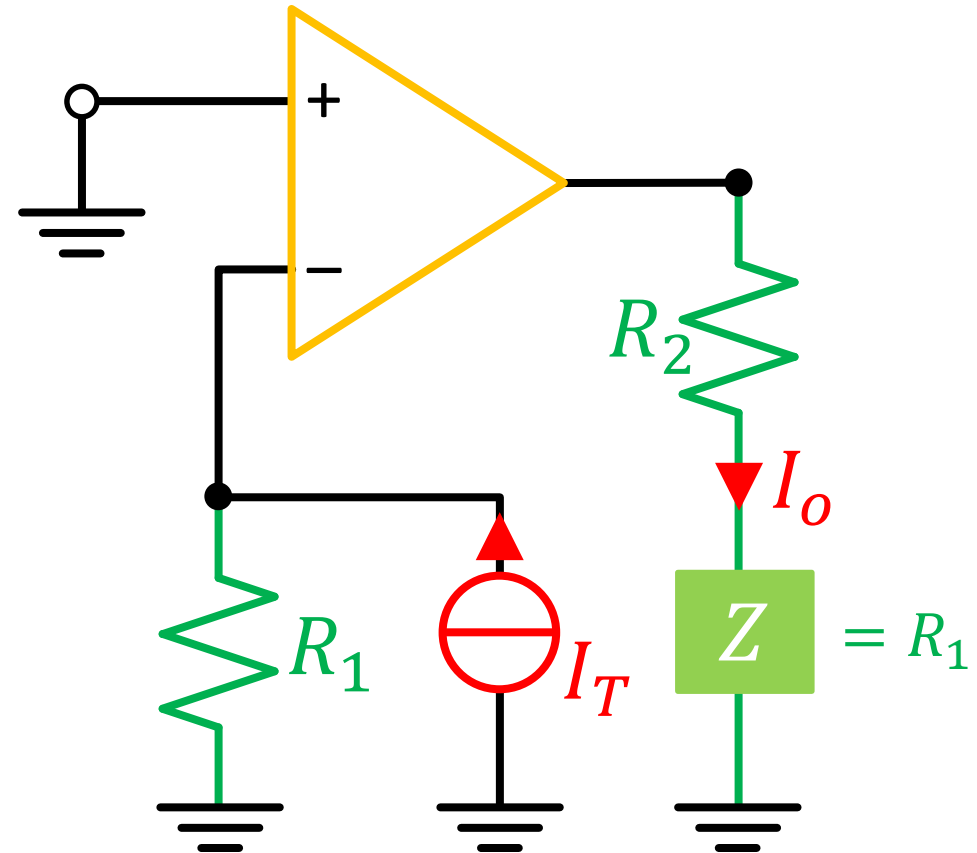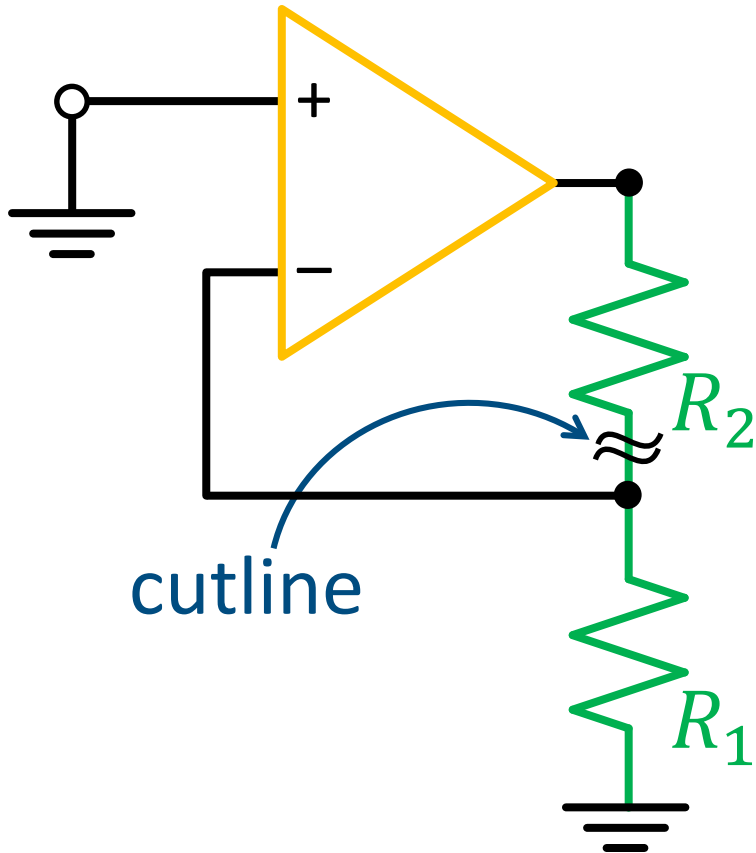



Smart cutpoints

11

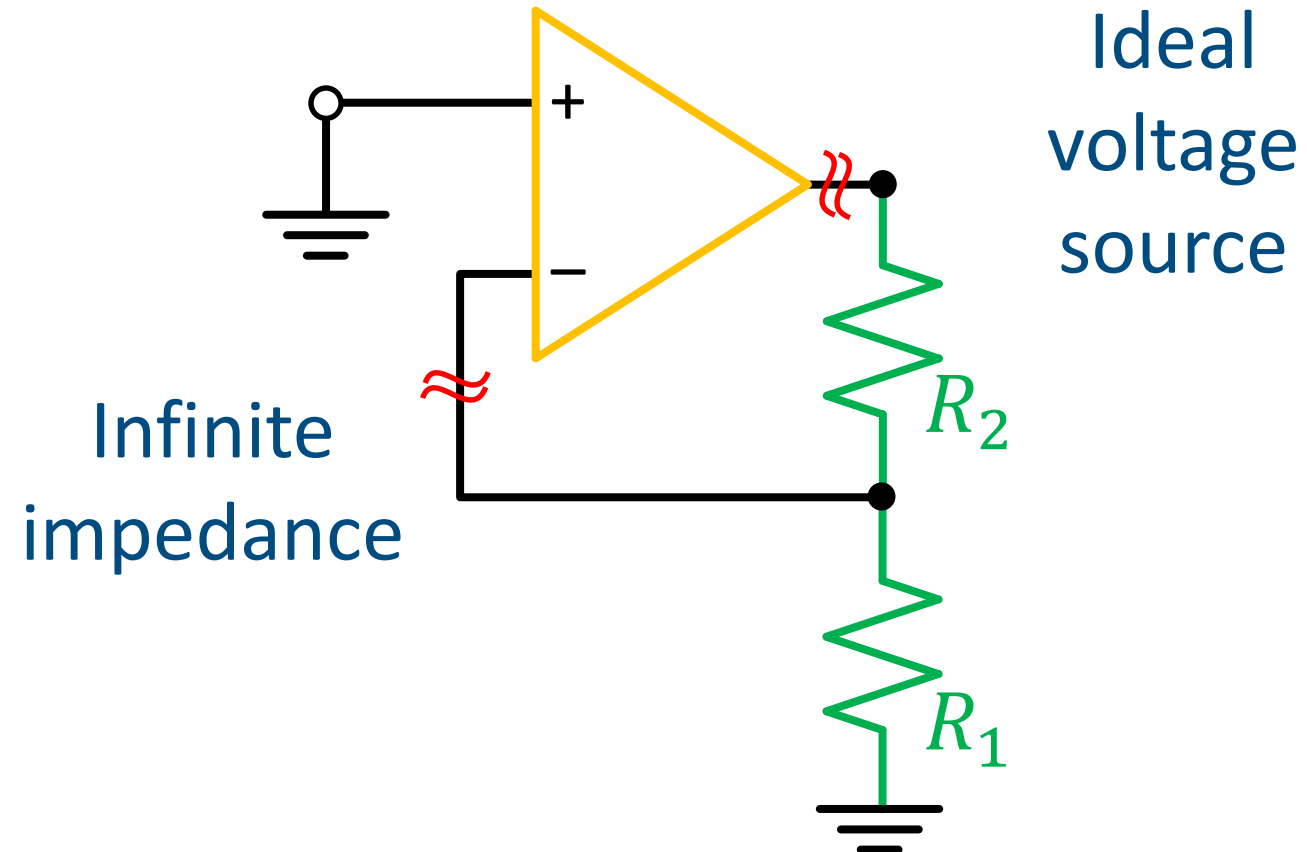



Closed-loop gain


12

$$G = \frac{V_o}{V_i} = \frac{G_{id}}{1 - \frac{1}{G_{loop}}} = \frac{\frac{R_1 + R_2}{R_1}}{1 + \frac{R_1 + R_2}{AR_1}} = \frac{A}{1 + \frac{AR_1}{R_1 + R_2}} = \frac{G_{OL}}{1 - G_{loop}}$$



Open-loop gain calculation (concept)



13

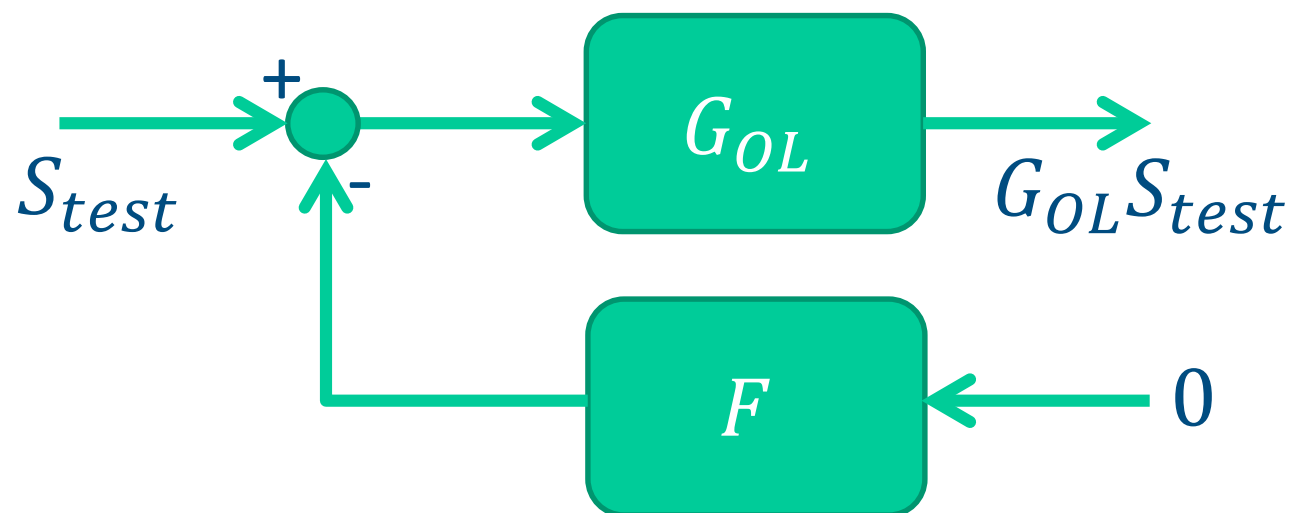



Open-loop gain calculation


14

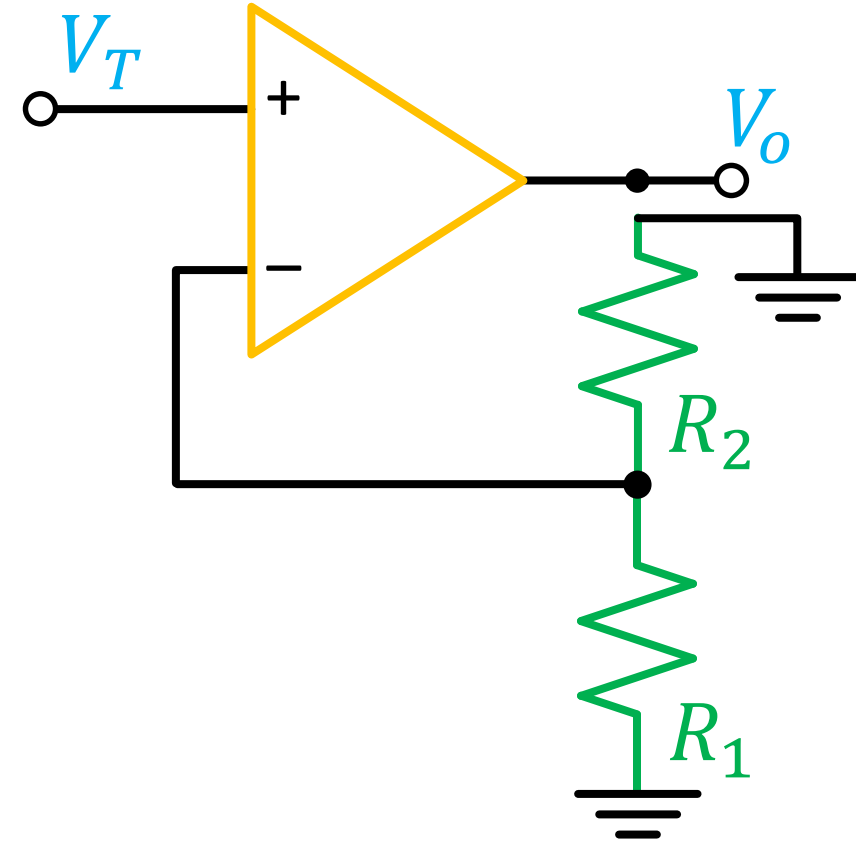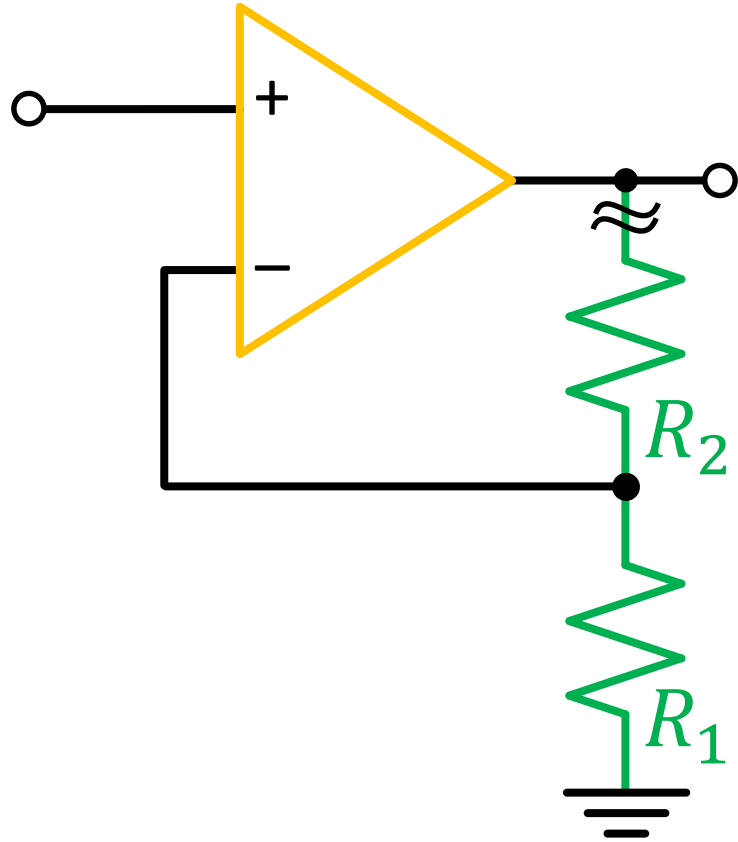

$$G_{OL} = A$$



Direct calculation (no feedback theory)

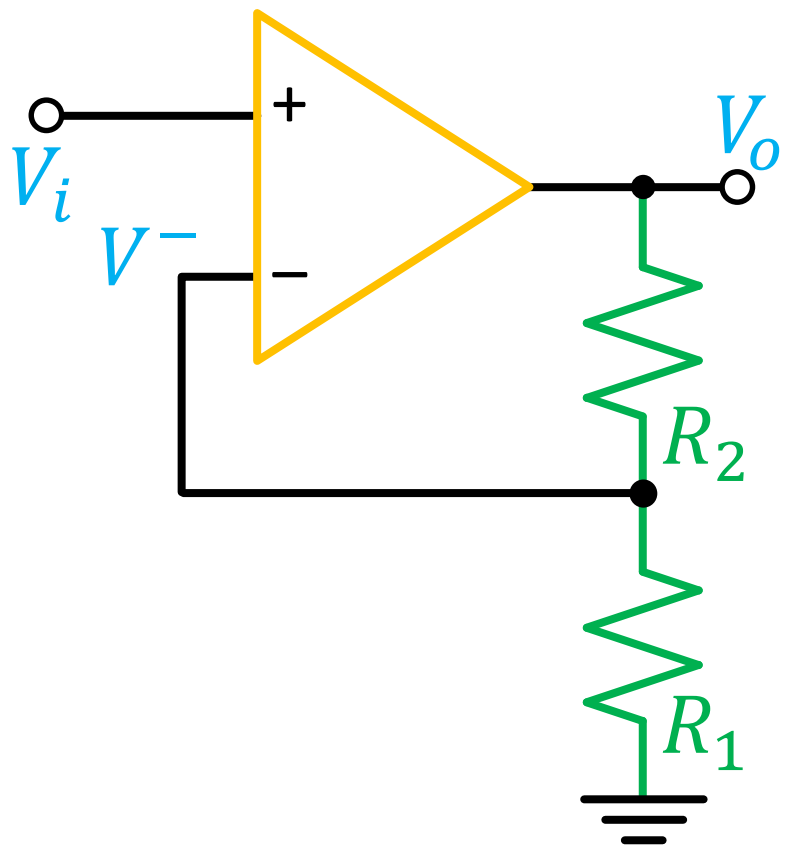

$$V^- = V_o \frac{R_1}{R_1 + R_2}$$


$$V_o = A(V^+ - V^-) = A(V_i - V^-)$$

$$\frac{V_o}{V_i} = \frac{A}{1 + \frac{AR_1}{R_1 + R_2}}$$




Impedance reconstruction

16

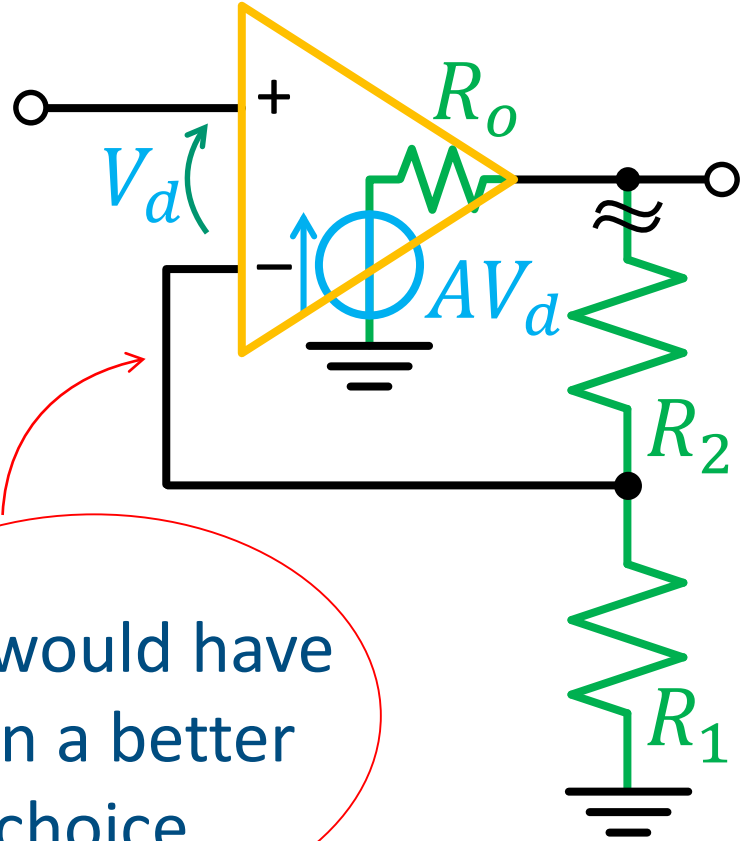

This would have been a better choice


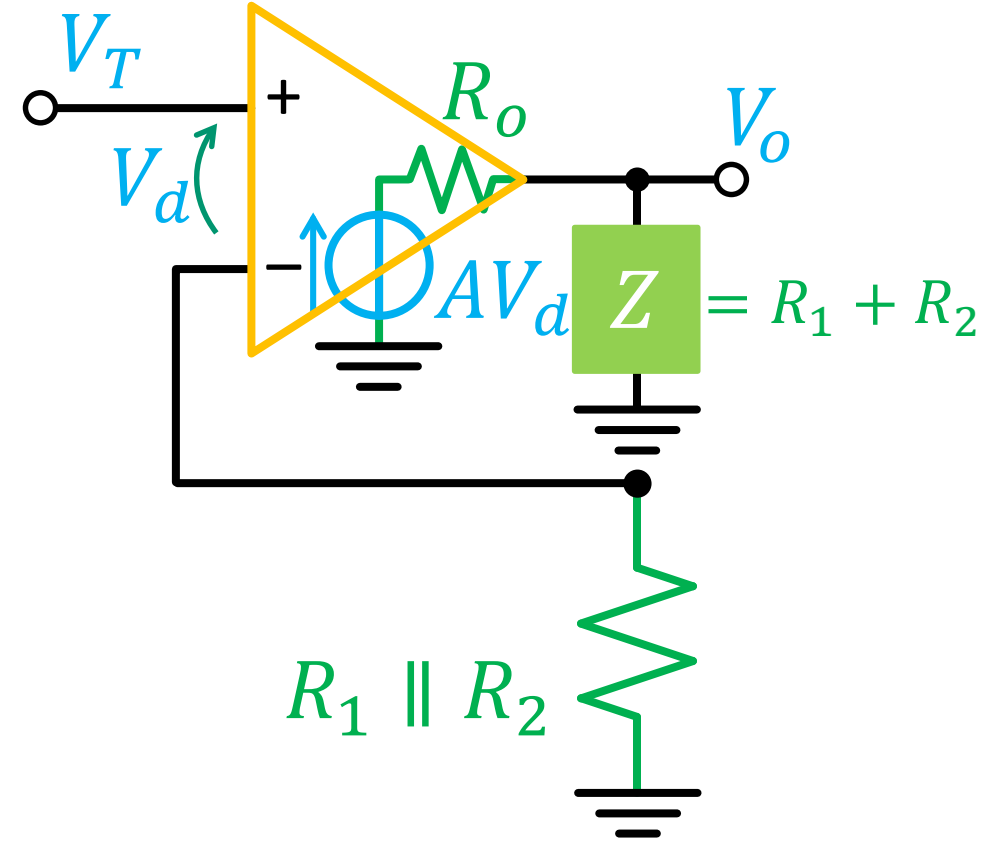


$$G_{OL} = A \frac{R_1 + R_2}{R_1 + R_2 + R_o} \quad G_{loop} = ?$$



Inverting amplifier case

17

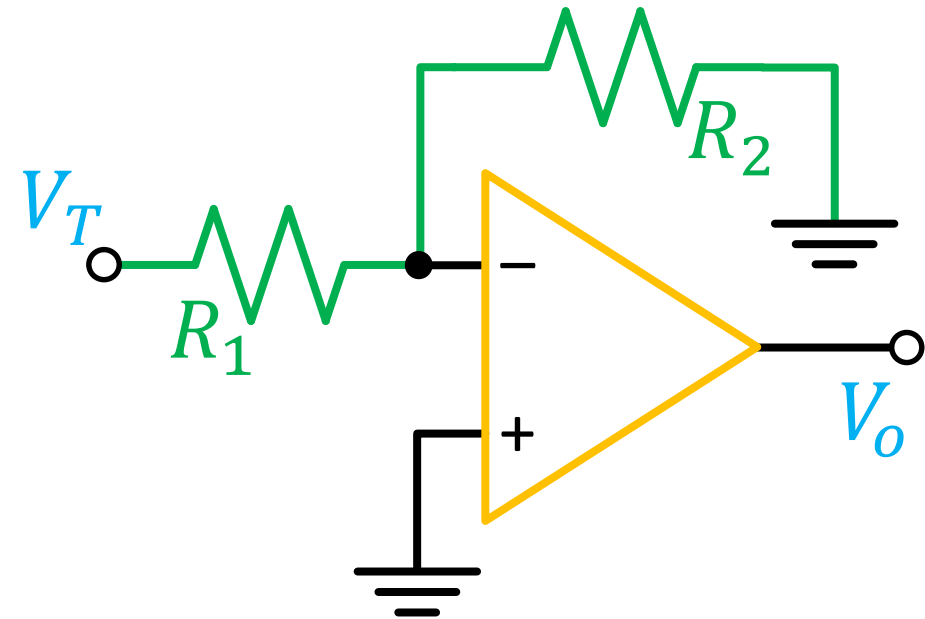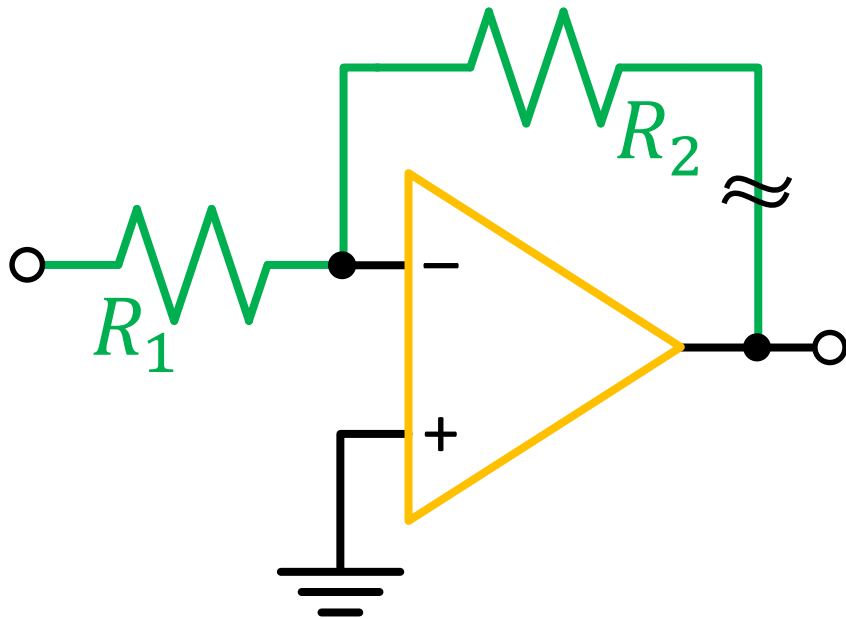

$$G_{OL} = -A \frac{R_2}{R_1 + R_2}$$



Closed-loop gain

18

$$G = \frac{V_o}{V_i} = \frac{G_{id}}{1 - \frac{1}{G_{loop}}} = \frac{-\frac{R_2}{R_1}}{1 + \frac{R_1 + R_2}{AR_1}} = \frac{-A \frac{R_2}{R_1 + R_2}}{1 + \frac{AR_1}{R_1 + R_2}} = \frac{G_{OL}}{1 - G_{loop}}$$




- Always remember to reconstruct the impedance in non-ideal cases
- In any case, G_{OL} can always be calculated as

$$G_{OL} = -G_{loop}G_{id}$$

- The closed-loop gain may contain an additional term (called *direct gain* or *feedthrough gain*) due to direct transfer through the feedback network. This term is usually (but not always) small and neglected

Direct gain calculation (concept)

20


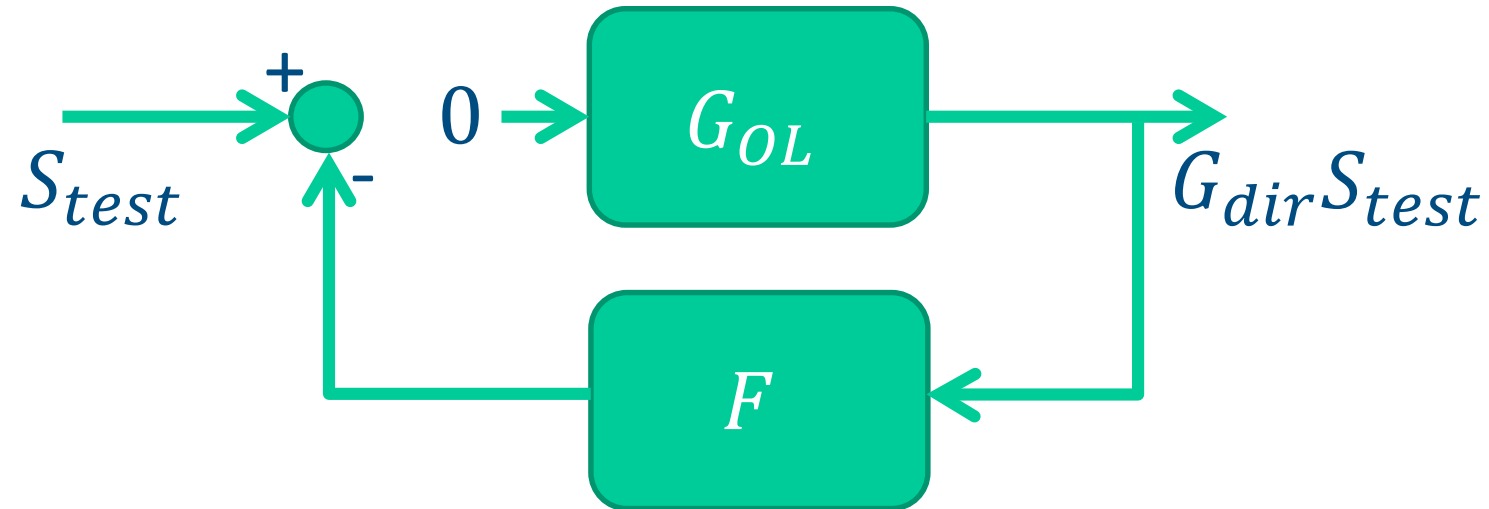


$G_{dir} = 0$ is expected



Direct gain calculation (simple cases)

21

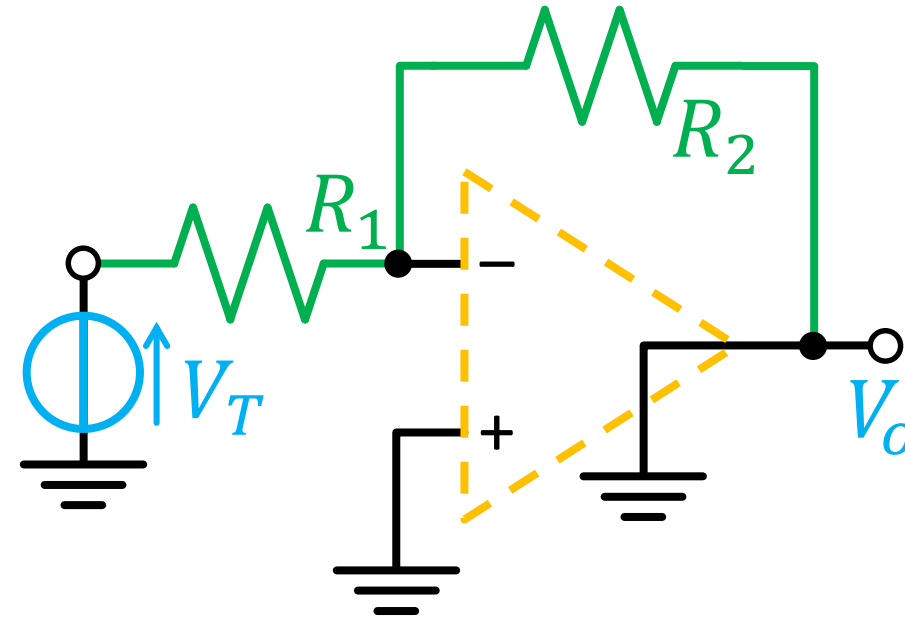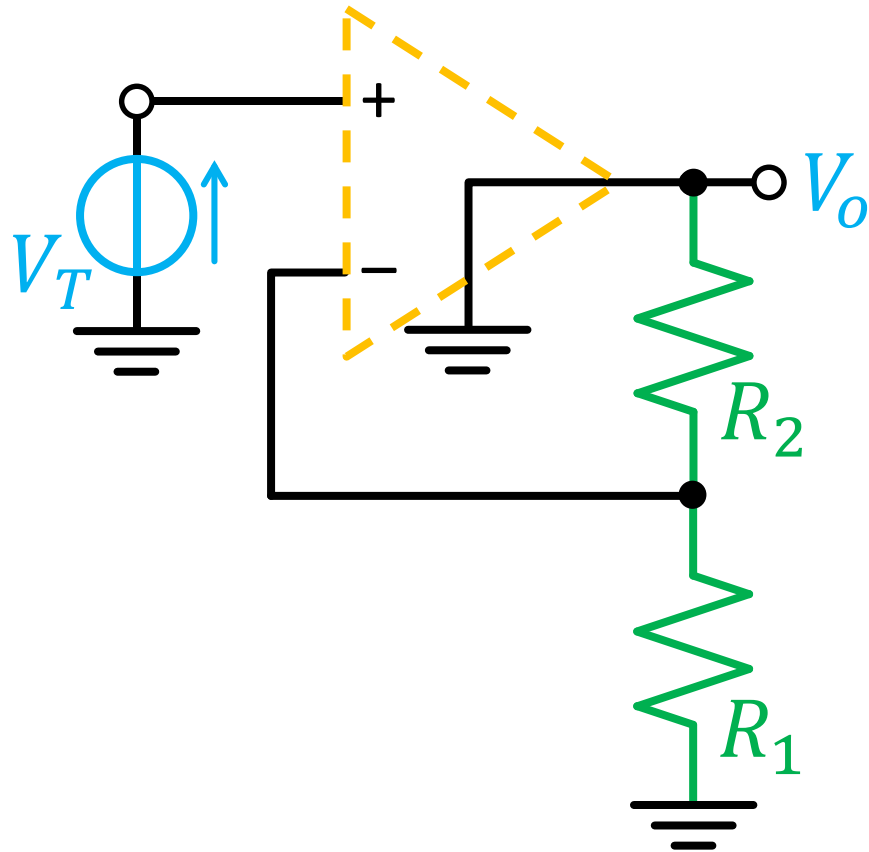


$G_{dir} = 0$ is obtained



Direct gain calculation (with R_o)

22

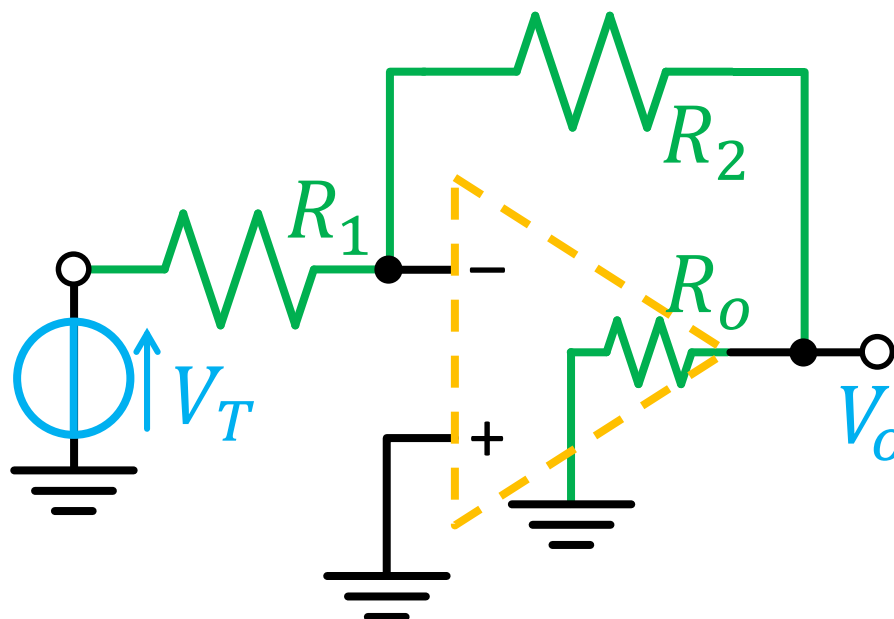


$$G_{dir} = \frac{R_o}{R_o + R_1 + R_2}$$



Block scheme

23

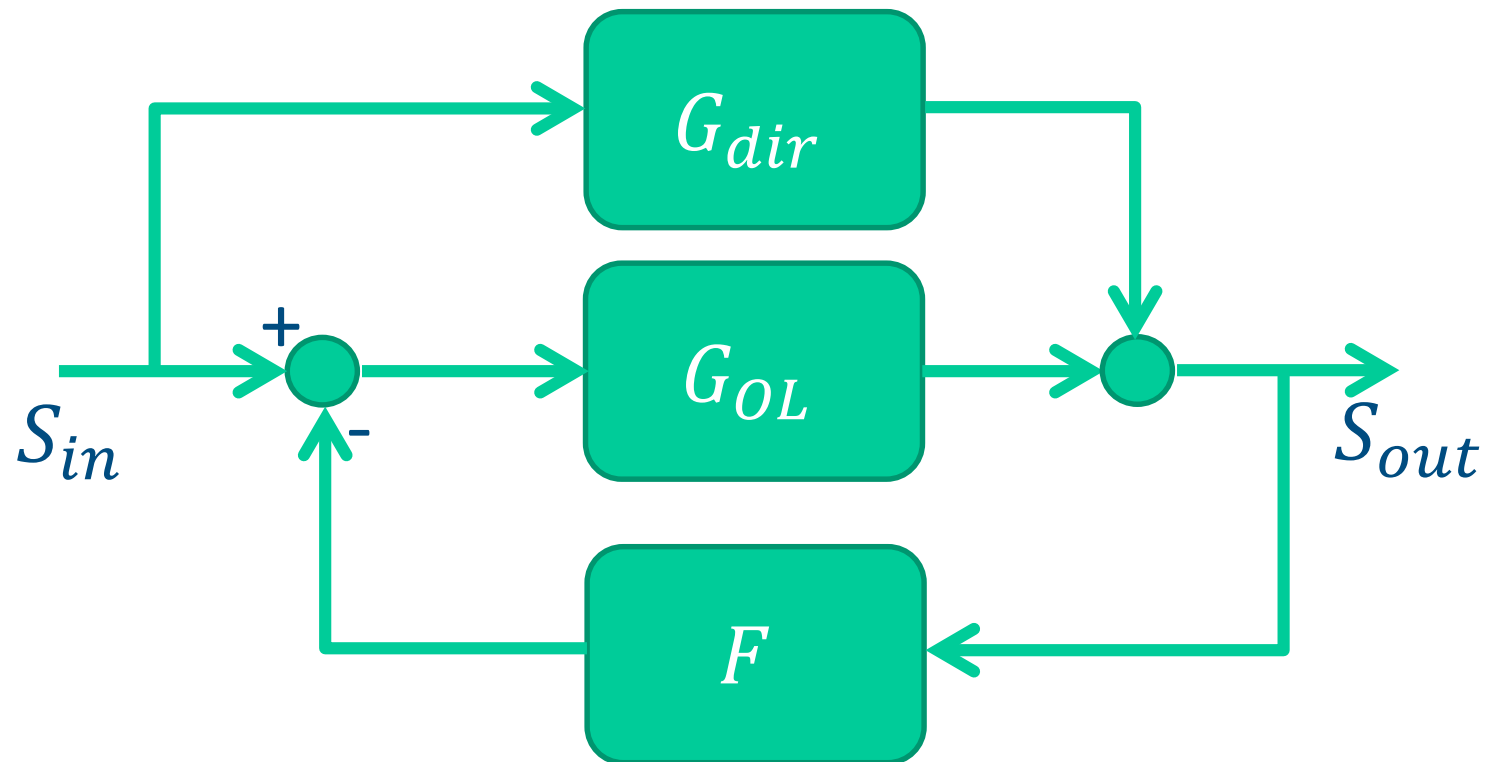

$$G = \frac{G_{OL} + G_{dir}}{1 - G_{loop}}$$




- Loop gain and closed-loop gain calculation
- Input/output impedances



OA parameter: input resistance

25

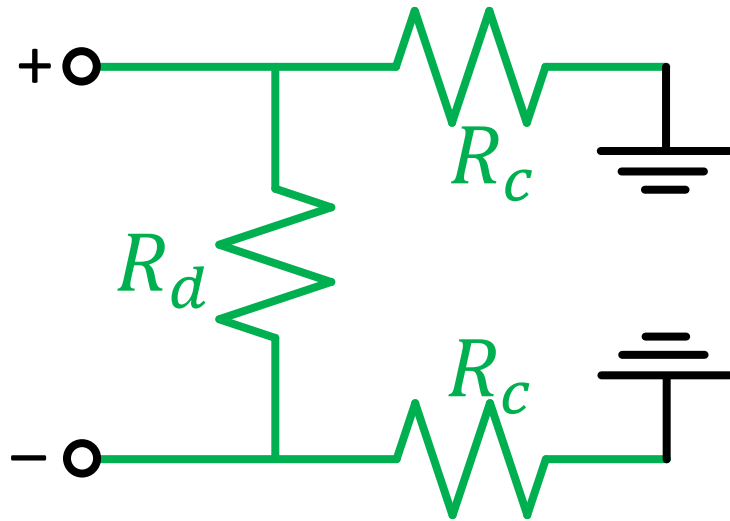


- Usually $R_c \gg R_d$
- An input capacitance of a few pF must also be considered at high frequencies

- Typ. BJT OA: $10^5 - 10^8 \Omega$
- Typ. JFET OA: $10^9 - 10^{10} \Omega$
- Typ. CMOS OA: $10^{12} \Omega$



OA parameter: output resistance

26


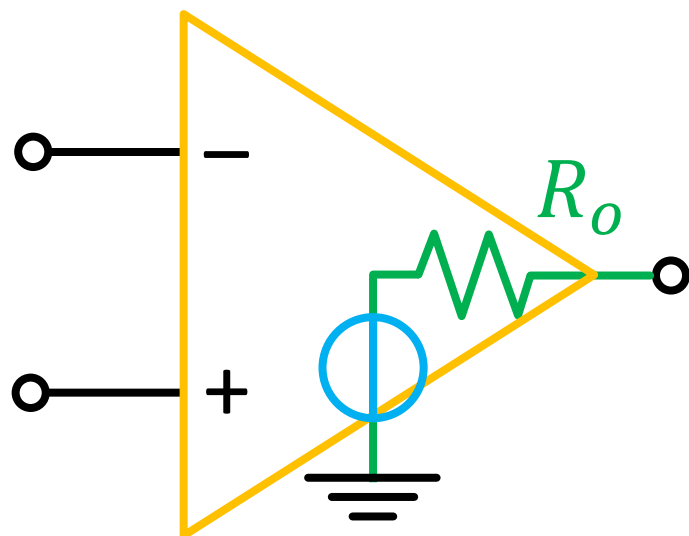


- Typically smaller than $100\ \Omega$
- A bit higher in CMOS OA



Actual values from datasheets

27

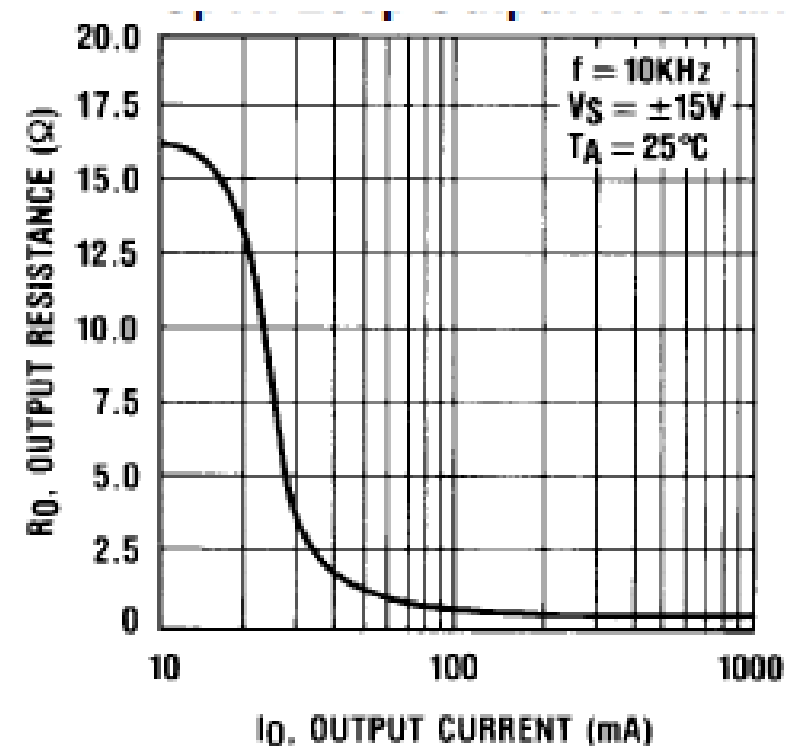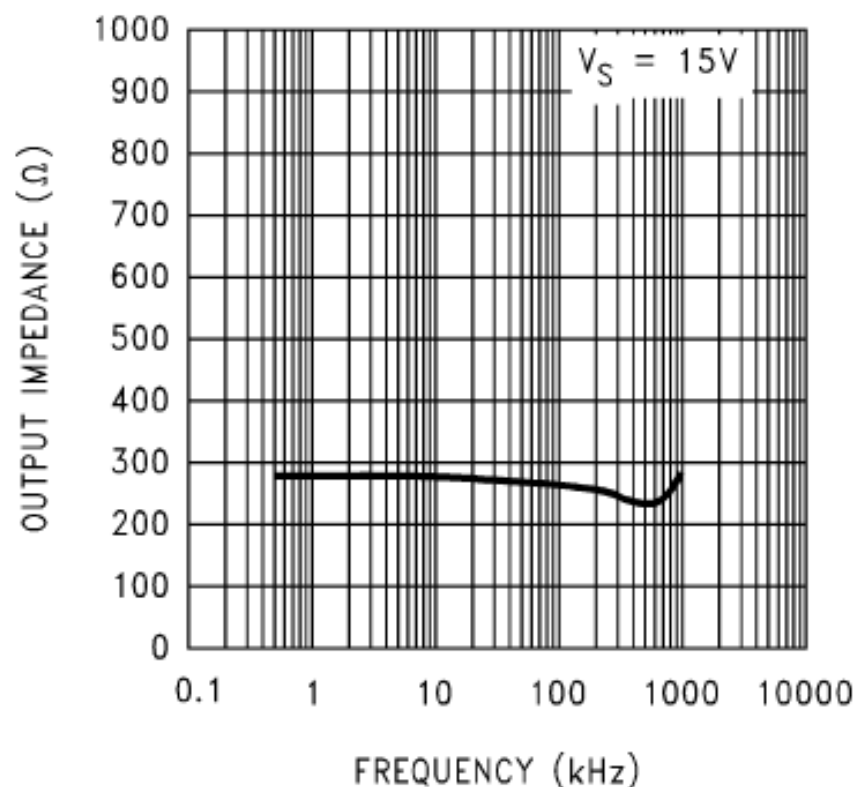


Power OA



Input impedance ($R_d \gg R_1 \parallel R_2$)

28

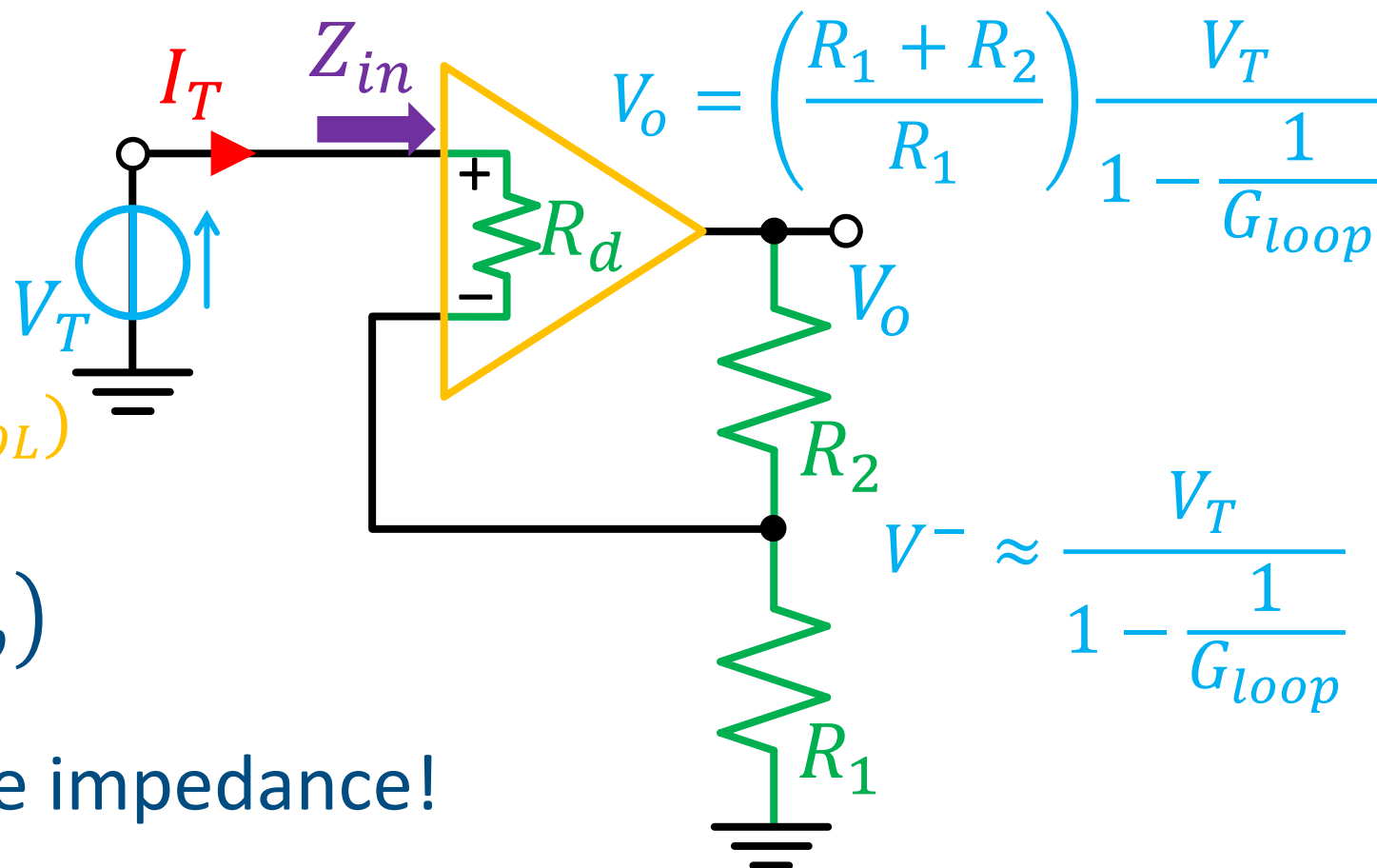

Impedance for $G_{loop} = 0$ (Z_{OL})

$$Z_{in} = \frac{V_T}{I_T} \approx R_d (1 - G_{loop})$$

Feedback has changed the impedance!

For $|G_{loop}| = \infty$ (ideal case), we get $Z_{in} = \infty$



Output impedance ($R_o \ll R_1 + R_2$)

29


$$-AV^- = -A \frac{R_1}{R_1 + R_2} V_T \approx G_{loop} V_T$$

Impedance for $G_{loop} = 0$ (Z_{OL})

$$Z_{out} = \frac{V_T}{I_T} \approx \frac{R_o}{1 - G_{loop}}$$

Feedback has changed the impedance!

For $|G_{loop}| = \infty$ (ideal case), we get $Z_{out} = 0$

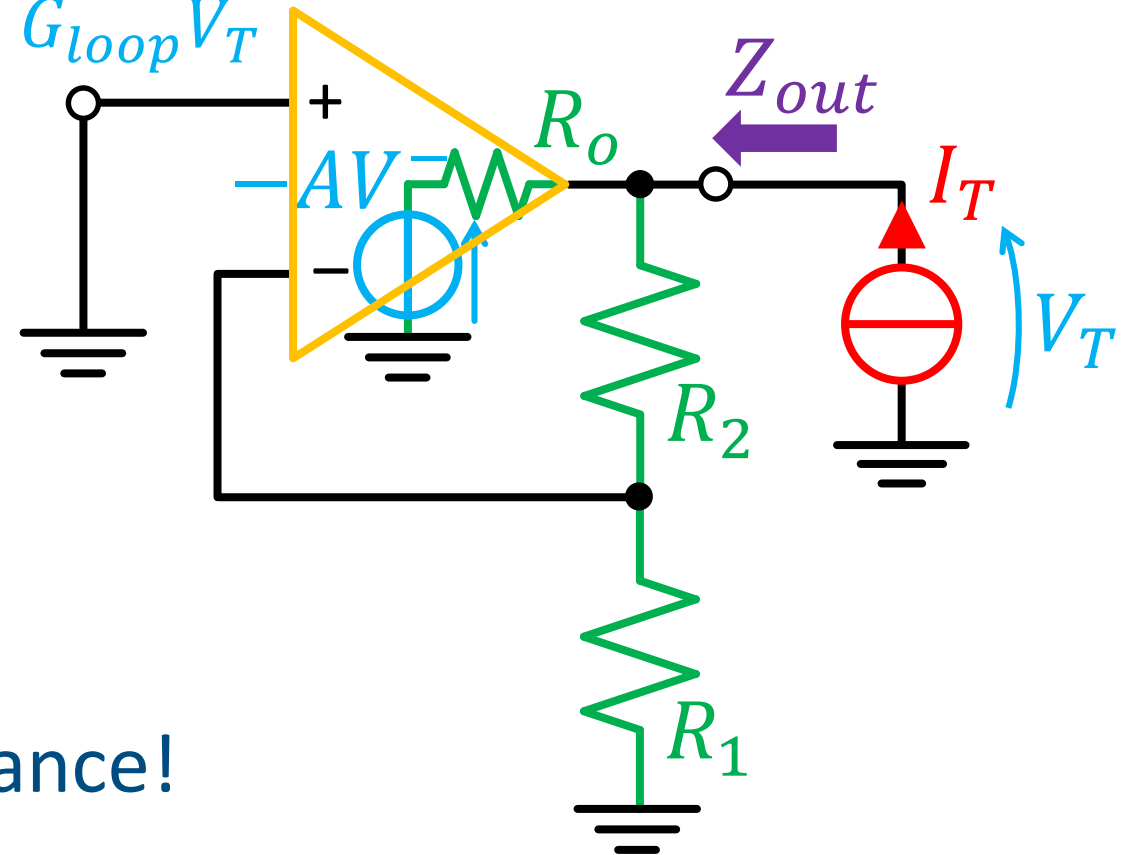





1. Compute $Z_{in/out}$ in the ideal case
2. If $Z_{ideal} = \infty \Rightarrow Z = Z_{OL}(1 - G_{loop})$
If $Z_{ideal} = 0 \Rightarrow Z = Z_{OL}/(1 - G_{loop})$
3. Compute terms



Z_{OL} calculation

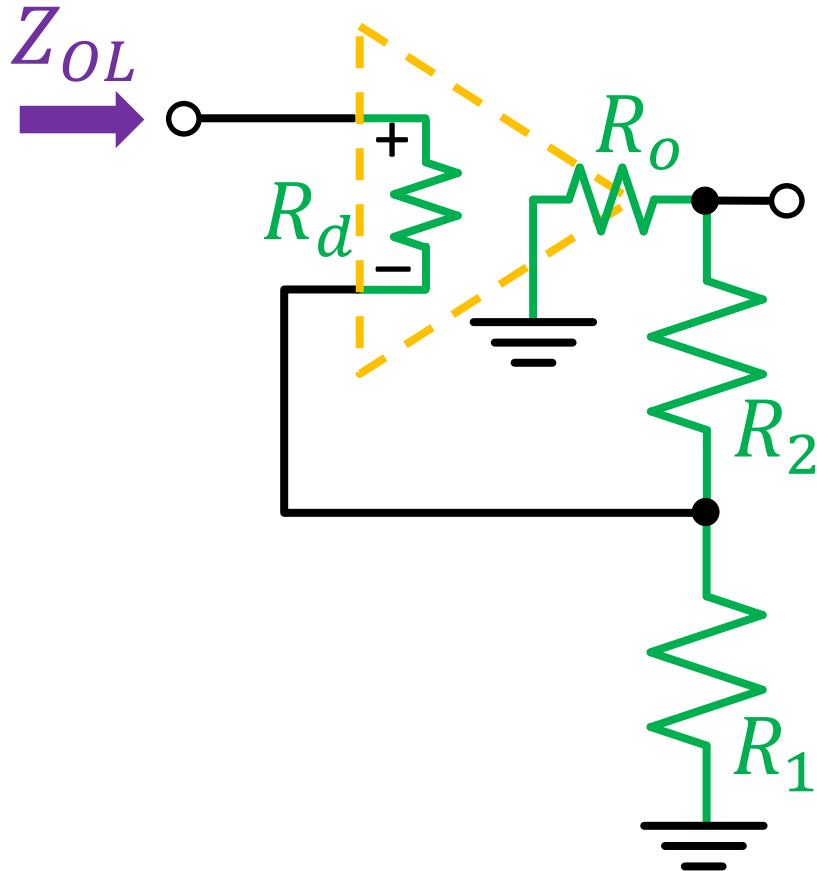
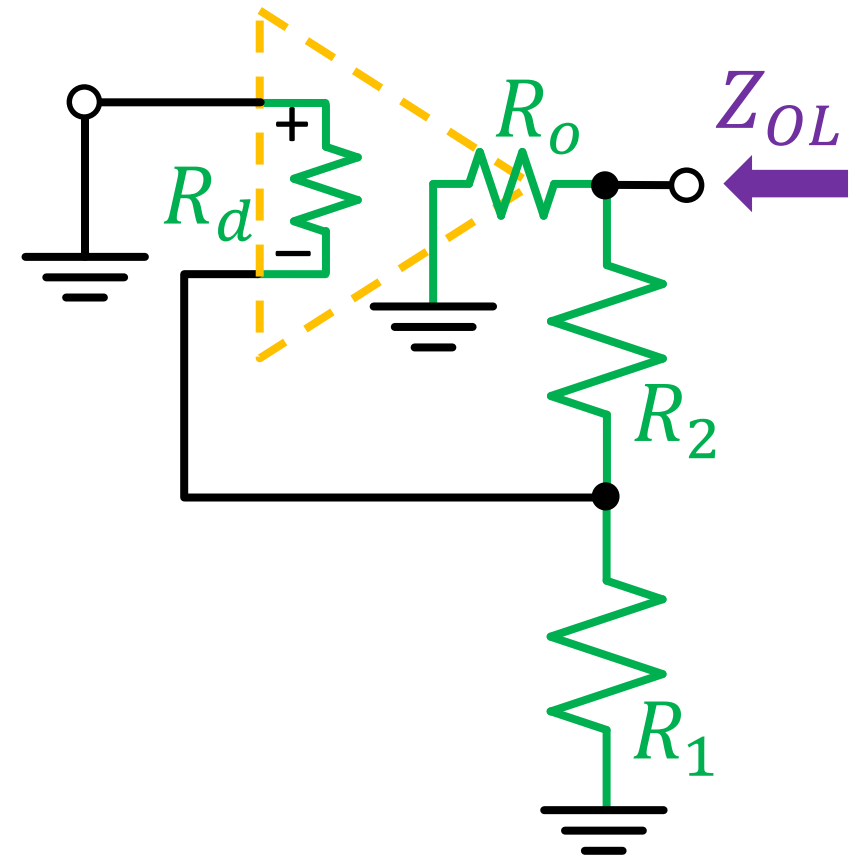
$$Z_{OL} = R_d + R_1 \parallel (R_2 + R_o)$$




$$Z_{OL} = R_o \parallel (R_2 + R_1 \parallel R_d)$$



The inverting case

32

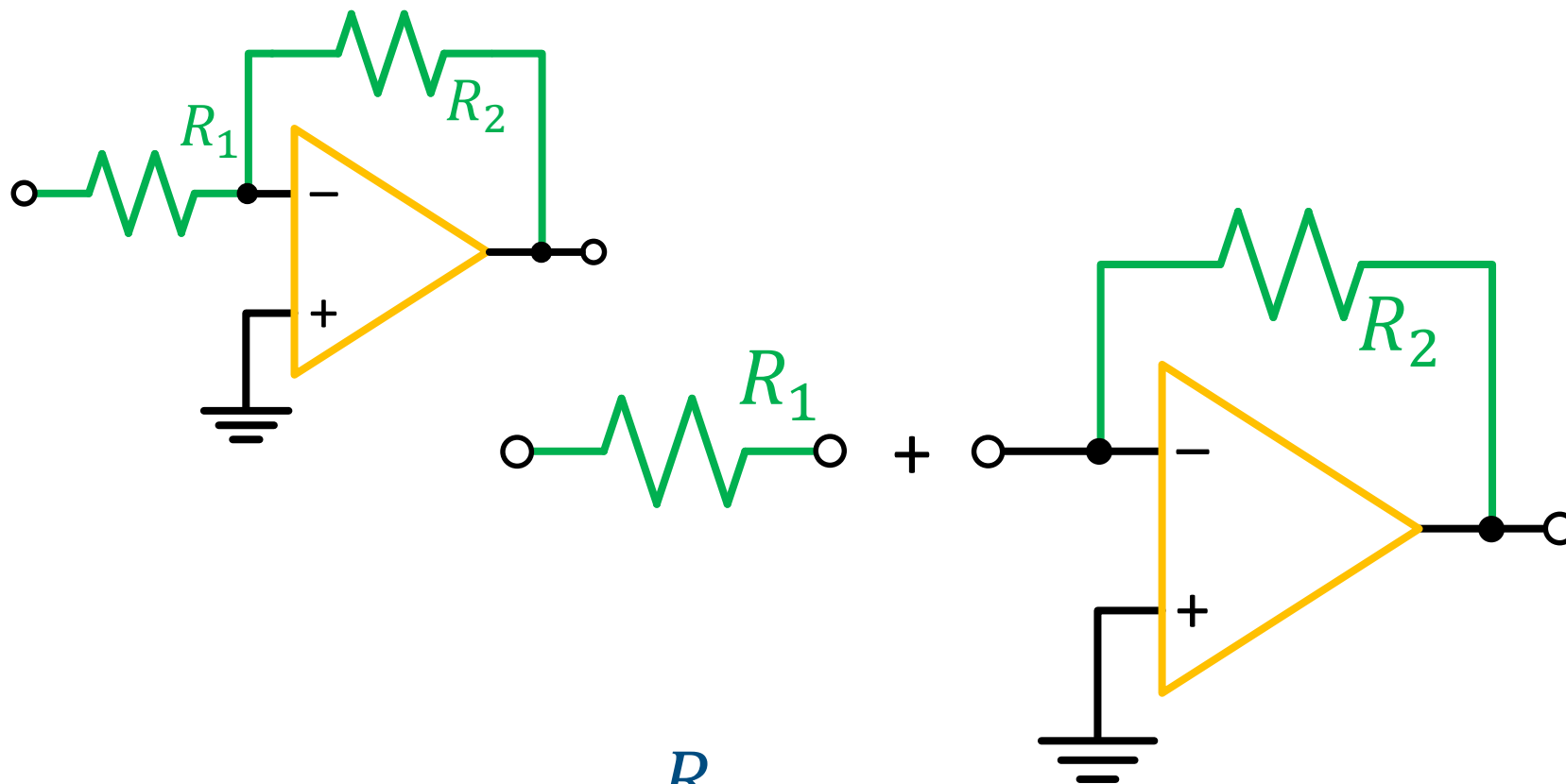

$$Z_{in} = R_1 + \frac{R_2}{1 + A}$$



Closed-loop output impedance

33

